

AUG. 1980  
\$1.60\* NZ\$1.75

# eti

## ELECTRONICS TODAY INTERNATIONAL

# TURNTABLE TECHNOLOGY

Inside the modern turntable

## LED Tacho

Super car project

## DIGITAL CLOCK PROJECT

Has 60mm high display

## Digital

## Frequency Meters

How to choose,  
how to use

**Hi-Fi: FM's booming - new Rotel receiver reviewed  
plus - Dick Smith mini speakers, how good?**



# A new dynamic generation of Maxell tapes.

When Maxell announces an improvement in the quality of its tape, you can bet the improvement has to be pretty dynamic. In fact, we think our new generation has even gone beyond our own standards of superior sound reproduction.

Take our high level (CrO<sub>2</sub>) position tape — the UD-XL II. Maxell engineers have succeeded in expanding its dynamic range in the middle-low frequency range by 1 dB, while also pushing its sensitivity by 1 dB in the high frequency range. Then look at our normal position UD-XL I, UD and LN tapes — our engineers expanded the dynamic range at all frequency points, while also boosting output in the high frequency range. The new dynamic range, of course, allows for better music reproduction even for LN-type tapes.

On the UD-XL I and II, we also added an exclusive shell stabilizer for significantly improved tape running and track positioning.

One thing hasn't changed on all Maxell tapes — our functional features like 4-function leader tape, replaceable index labels for UD-XL series tapes and Maxell's through-production system — your guarantee of quality and superior sound reproduction.

Tape selector position UD-XL I, UD, LN: Normal position (Normal bias/120  $\mu$ sec. EQ)  
UD-XL II: High level position (High level bias/70  $\mu$ sec. EQ)



For details on all Maxell Recording Tape write to Maxell Advisory Service, P.O. Box 307, North Ryde, N.S.W. 2113

Available time length UD-XL I: 60, 90 min./UD-XL II: 60, 90 min.  
UD: 60, 90, 120 min./LN: 60, 90, 120 min.

Distributed by...  
**HAGEMEYER**

**maxell**®  
simply excellent





# ELECTRONICS TODAY INTERNATIONAL

Registered for posting as a publication —  
Category B

## QUICK INDEX

### FEATURES:

- 13 Digital Counter/Timers
- 21 Toys for a Bored Consumer Society
- 119 Modern Turntable Technology

### SOUND SECTION:

- 111 Sound News
- 144 Rotel RX1000 AM/FM Receiver Review
- 156 Dick Smith Mini Speakers Review
- 141 Reel-to-Reel Tape Offer

### PROJECT SECTION:

- 27 564: Digital Clock
- 35 324: LED Tachometer
- 42 262: Simple House Alarm
- 51 Lab Notes
- 59 Short Circuits (plus pages 61, 63 & 65)
- 69 Ideas for Experimenters
- 77 Shoparound

THE CHICAGO Consumer Electronics Show, held each year in June, is the biggest of its kind in the world, attracting 50 000 people from all over the world. Every year a more fantastic array of products is presented — want a pair of \$20 000 loudspeakers, a \$10 000 satellite TV receiver system, a voice controlled TV, a solar powered radio? It's all there. Dennis Lingane, who reports in this issue on the 1980 show, has a few caustic observations to make on the crazier aspects of the industry. Some products — like power saving devices — obviously do play a useful role, but others seem to be produced solely to extract money from "... bored people who want new toys, and want to keep ahead of the Joneses." Is the demand for high-priced, high technology toys a real or created one? I fear it's the latter.

The craziness of this phenomenon was thrown into sharp relief for me by a local news story about a University of NSW research team whose research into breast cancer detection has come to a standstill for lack of funds. They don't need huge sums of money — just \$15 000 or so to buy an essential X-ray camera. Meanwhile, \$300 000 worth of other equipment lies idle as Dr Veronica James, of the University's School of Physics, struggles to build the camera herself (acting as her own mechanic and electronics technician!). It seems that grants for this sort of research tend to be the absolute minimum — any less and the research can't go ahead at all.

So there's lot of money for 'toys' but none for health research. Where are our priorities?



Roger Harrison  
Editor




## advertisers

Acoustic Electronic Developments	94
Adcola	92
Advanced Electronic Systems	76
Agfa-Gevaert	118
All Electronic Components	70
Andrews Communications	64
Applied Technology	58
A.P. Products	126
Audax	142
Audio Engineers	152
Audio Kits	150
Auditec Aust. P/L	38
Aust General Electric	20
Aust Govt Transport	48
Aust Guarantee Corp.	32, 33
AWA	143
Barratt Lighting	159
Belle Lumiere P/L	152
Bell Instruments	40
Bose Aust	140
Cema	80
Chadwick Audio	151
Christie Rand	64
Cletrronics	98
Daneva Control	68
David East Components	74
Defence Recruiting Board	66
Delound P/L	152
Dicker Data Projects P/L	17
Dick Smith. 24,25,26,82,83,96,97,98,102,139	
Diggerman Electronics	40
DSA Concert Systems	163
Electrocraft P/L	105
Electronic Agencies	54
Electronic Calculator Discounts	103
Ellistronics	56, 57
Elmeasco Instruments	41
Emac Industries	150
Emona Enterprises	142
Energy Control	98
Freedman Electronics	146
Gregory's Directories	68
Hagemeyer Aust	2, 171
Hanimex	88
Hewlett Packard	65
H.F. Coates	74
Hitachi Sales	116, 117
Holden Wasp International	150
Home Computer Show	78
Insound	163
Jaycar P/L	147
John F. Rose Computer Services	12
JS&A	72
Logic Shop	18
Looky Video	98
Magraths P/L	6
Maruni Corp	11
McGills Newsagency	155
Micro Pro Designs	55
Microtrix	64
Micro 80	93
Modern Boating & Seacraft	48
National Panasonic	172
Northpoint Hi Fi	160
Overlander	165
Parameters	136
Philips	50, 106, 133
Phodis P/L	154
Plessey Components	105
Pre Pak Electronics	67
Radio Despatch Service	105
Radio Parts	76
Rank Australia	153
Rod Irving Electronics	34, 62
Sansui Electric Co P/L	127, 129, 131
Scope Laboratories	10
Sevlen Lighting P/L	146
Sigma International	103
SM Electronics	60
Small Business Computer Co.	59
Sony	114
Soundair Hi Fi	163
Speedy Communications	162
Stanton Magnetics	158
Stuart Alexander	between 50-51, 134, 135
Sydney City Monthly	between 50-51
Superscope Aust P/L	113
Systems Automation	74, 75
Tasman Electronics	78
The Electronic Circuit	90
Vicom International	100
Warburton Frankl.	49




**ELECTRONICS  
TODAY  
INTERNATIONAL**

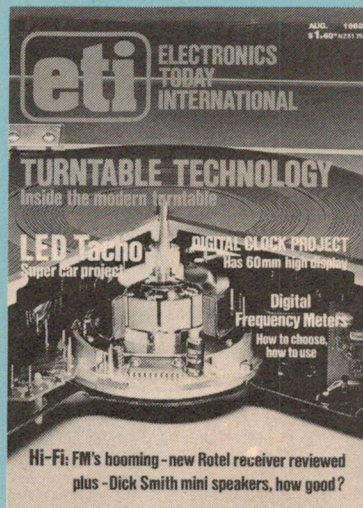

### COVER

Cutaway view inside a modern direct drive turntable. Picture courtesy of Pioneer. Cover design by Ivy Hansen.


## features

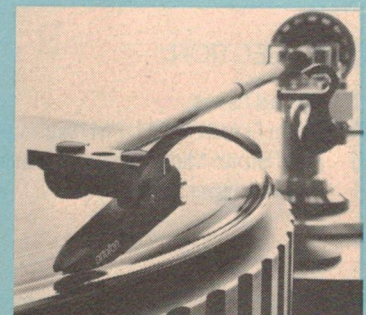
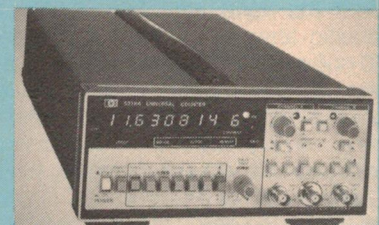
### TURNTABLE TECHNOLOGY

119

Belt or direct drive? Pivoted arm or tangential tracking? Design principles and techniques discussed, plus a review of some of the latest models.



### DIGITAL COUNTER/TIMERS

13

Handy in so many branches of electronics. How they work and how to use them.

### TOYS FOR A BORED CONSUMER SOCIETY

21

Americans go bananas! A report on the Consumer Electronics Show in Chicago — with a few caustic comments.

## news

### NEWS DIGEST

7

Talking typewriter; 100% metal tape coating; Remote controlled VCR; Negative ions, and more.

### PRINTOUT

85

Exorset 30 software development system; Fast new Z80 processor; Computerised newspaper; Apple 3 released; Micros for breeding.

### COMMUNICATIONS NEWS

99

Licence fees changed; Common channel VHF repeater; CB suggestions.

### SHORTWAVE LOGGINGS

101


New Nigerian transmitter; Guatemala goes all night; Last chance to hear Latins.

## ★ DON'T MISS SEPTEMBER'S GREAT COMPUTER CONTEST

You could win a Dick Smith System 80 for yourself — or one for your school !




## projects

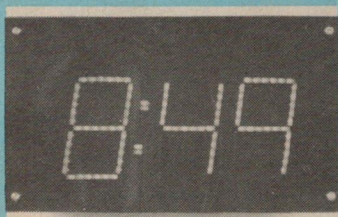

**564: DIGITAL CLOCK** 27  
Mains-driven clock with giant easy-to-read rectangular LED display.

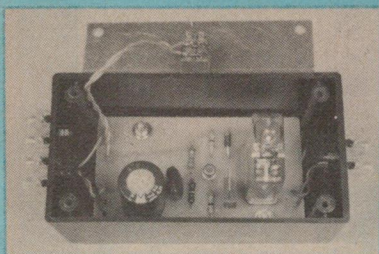**324: LED TACHOMETER** 35  
Adaptable to almost any engine, our tachometer has a bargraph display and an over-rev alarm.



**262: SIMPLE HOUSE ALARM** 42  
A straightforward, reliable circuit that will protect your property for years, without false alarms.

**LAB NOTES** 51  
Diodes in logic and other applications.

**SHORT CIRCUITS** 59



**ROTEL RX1000 FM/AM RECEIVER** 144  
Innovative design at a realistic price. Uses a single LSI chip for both power amplifier stages.

**DICK SMITH MINI SPEAKERS** 156  
Tiny loudspeakers suitable for cars, boats and other small spaces.

**REEL TO REEL TAPE OFFER** 141

## general

**IDEAS FOR EXPERIMENTERS** 69  
Circuit ideas, project modifications etc.

**SHOPAROUND** 77  
Sources for our projects, price estimates etc.

**IONOSPHERIC PREDICTIONS** 104

**MINI-MART** 164

**MAIL ORDER BOOKS FROM ETI** 166  
Beginners' books, data books, circuit books etc.

**KITS FOR PROJECTS** 168

**ETI SERVICES** 169


**DREGS** 170

**PC BOARD PATTERNS** 137

## sound

**SOUND NEWS** 111  
What does hi-fi mean? Computer controlled cassette deck; Electronic bass control on KLH speakers; Technics professional tape deck.

## next month

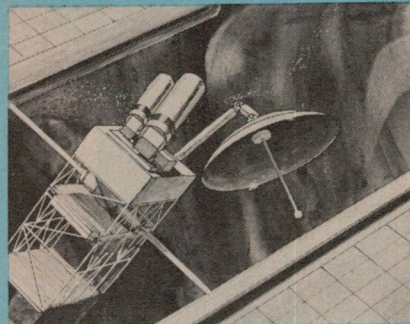

### THE COMET CHASERS

This fascinating story tells how the power of the sun may be used with ion drive motors to take our spacecraft to much greater velocities than has yet been possible. Plans have been made for such spacecraft to chase comets.



### QUALITY AM TUNER

The AM band stations have been broadcasting 15 kHz bandwidth audio for some time now, and remarkably good quality can be obtained — if you have an appropriate tuner! Our feature project is a relatively simple design, yet delivers top performance. There's life in the old AM yet!

### TAPE TEACH-IN

The popular magnetic medium — reel-to-reel and cassette tape — is often misunderstood, along with the basic techniques of recording. This article clears up the confusion, plus provides a guide to tape and recorder care products.


### CELEF SM LOUDSPEAKERS

Mini loudspeakers are popular with people who have a premium on space. These Celef 'mini professionals' are an interesting product and the review springs a few surprises.

Although these articles are in an advanced state of preparation, circumstances may affect the final content. However, we will make every attempt to include all features mentioned here.



# MAGRATHS

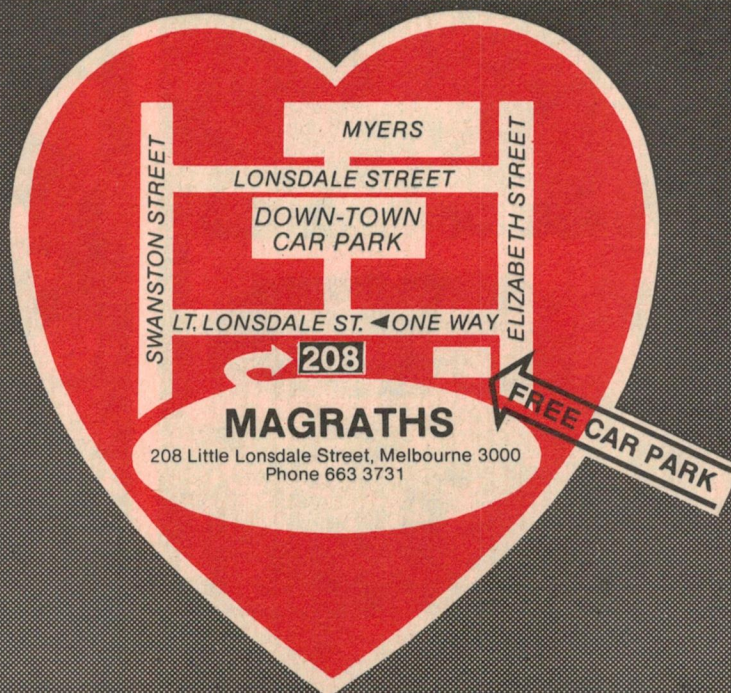

**IN THE HEART OF MELBOURNE**

## NATIONAL

Full range of National Linears, CMOS, TTL etc. All current data books.

**Even upside down**



Sonnenschein batteries can be used upside down, sideways, anyway. Full range.

## GI Diodes — Ex stock

1N 4001	1N 5061
1N 4002	1N 5626
1N 4004	GIG
1N 4006	GP30B
1N 4007	W02
1N 4145	W04

**6800 9900**

Microprocessor families from

**AMI**

## OPTO'S GENERAL INSTRUMENT

RECTANGULAR\*



MV52124  
MV53124  
MV57124

Green  
Yellow  
High Eff. Red

BAR GRAPH



MV57164

High Eff. Red

5" RECTANGULAR\*



MV57173

High Eff. Red

\*POP-INS AVAILABLE

Now available — 1980 Full Line Opto Catalogue


## DIECAST BOXES

Full range from EDDYSTONE




## TRIACS, SCR's

from TECCOR

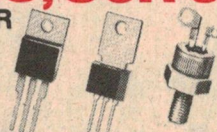

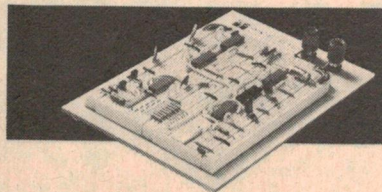
## BREADBOARDING, INTERCONNECTION & TESTING DEVICES

Full range on display from AP PRODUCTS INCORPORATED


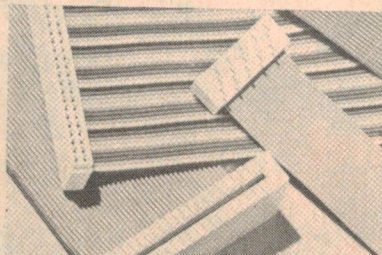
## FLAT RIBBON CABLE ASSEMBLIES AT AFFORDABLE PRICES



**FOR ALL YOUR ELECTRONIC COMPONENTS**



## Typewriter talks back !

Two researchers at Macquarie University in Sydney have developed a typewriter which 'reads back' the letters typed into it.

**Developed by Ron Aitchison, Professor of Electronics at Macquarie, and Terry Brown, a systems analyst, the typewriter enables a blind person to communicate in writing with sighted people.**


Although blind people can be taught to type just as easily as the sighted, they have hitherto been handicapped by having to rely on sighted people to point out errors. The talking typewriter, which took about 18 months to develop, solves this problem.

It is based on an IBM Selectric correcting typewriter with a standard keyboard, which the typist uses in the normal way. Whenever a key is pressed, the machine speaks the name of

the character which has just been typed, indicating whether it is a capital letter or not.

Keyboard functions like 'space', 'backspace', 'margin release' and so on are also called out as the appropriate key is pressed. To give the typist a second chance to correct errors, the machine is also capable of reading back, character by character, an entire line of text.

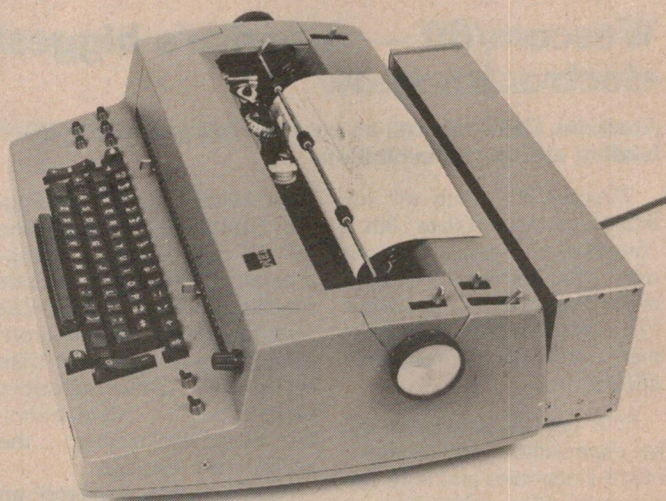A Selectric typewriter has mechanical linkage between the keys and the 'golfball' typing element. To make it talk, Aitchison and Brown have attached small magnets to each key lever and used reed relays to sense their motion. The pulses passed by the reed relays are stored in a CMOS memory for line play-



The typewriter that talks. Two researchers at Macquarie University have modified this IBM Selectric to provide a speech output corresponding to each key depressed. The box houses the electronics. All mechanical work, including modifications to the typewriter, was carried out by Ingram Paterson of the School's mechanical workshop.

back as well as being used for the real time speech synthesis.

The prototype uses a Telecentury speech synthesis board, but it is expected that later models will make use of the new single chip from Texas Instruments and thereby cut the cost by as much as \$170.

Professor Aitchison is confi-

dent that the talking typewriter can be sold commercially in its present form for about \$1500 and hopes that it will lead to more jobs for blind people. The next stage of the project is to adapt the system to computer and word processor terminals and open up even more employment opportunities.

## Tape coating breakthrough

**A new cassette tape coating process makes it possible to get better sensitivity and recording density from a magnetic layer only one-tenth as thick as normal.**

Instead of coating the tape in the normal way with a mixture of 70% resin and 30% magnetic particles, the new method developed in Japan by the Matsushita company uses a vacuum evaporation process to apply a very thin film of 100% metal.

This means that for the same thickness of polyester film substrate, cassette tape can now be made one-third thinner than was previously possible, without any diminution of its mechanical strength. In fact the makers claim that their new product is actually a little stronger than conventional tape.

Thinner tape of course allows a greater length to be wound on a given spool. Matsushita are exploiting this feature in a micro-

cassette which will be test marketed in Japan this month under the brand name of Angrom. At a recording speed of 1.2 cm per second (which is adequate for recording speech intelligibly), the new micro-cassette will run for 90 minutes in each direction, giving businessmen and other users three hours of recording time on a pocket machine.

The cobalt based metal tape coating is claimed to have a better coercivity than resin and particle mixtures, allowing a ten times higher recording density.

Matsushita's accumulated experience in the development of metallised capacitors has enabled them to overcome the problems involved in getting the

evaporated metal to adhere to the substrate and produce this novel kind of recording tape about five years earlier than the industry in general had thought would be possible.

So far the company doesn't seem to be rushing to exploit the many commercial possibilities

of their new tape. Although they have taken out patents on twelve applications in half a dozen countries in Europe and America, they have not yet decided to release even the microcassettes outside their own country.

### ERRATA JULY ISSUE

The Four-Input Preamp, ETI-467, on page 47 of the July issue had a number of errors which no doubt set a few readers scratching their heads.

Firstly, on the circuit (page 49) exchange R34 and R35. The 1k resistor, R34 should now be connected from pin 9 of IC2b to the common rail (earth, or 0 V). The capacitor across the presence control, a 4n7 marked 'C20', is actually C24. These three components are correctly marked on the overlay.

Next, on the overlay photo (page 50) IC1 and IC2 have been shown with the incorrect orientation. Pin 1 of IC1 is located diagonally opposite to where it is shown on the overlay. It should be adjacent to R1. Similarly with IC2, pin 1 should be located adjacent to R23.

On the Parts List, R35 and C24 do not appear. Add a 270R resistor and a 4n7 greencap, respectively. Finally, in the second paragraph on page 50, the maximum output is quoted as "... 200 volts peak to peak ...". In reality, it is a more modest 20 volts peak to peak. Kit and component suppliers have already been notified.



## Wescom/80 — America's biggest electronics show

Anaheim, California will be host city this year to the USA's leading electronics exhibition.

Wescom/80, which will run from September 16th to 18th, is conceived on a grand scale with over 1000 exhibitors' booths, more than 120 'Professional Program Sessions' and a film theatre showing the latest scientific movies.


Four product categories will be especially emphasised — micro-electronics and fibre optics; production, packaging and test equipment; instrumentation and control systems; and mini/micro computers and EDP peripherals.

Among the many topics co-

vered by the Professional Program Sessions, special attention will be given to the microprocessor. Other topics include satellite systems, bipolar LSI, bubble memories, semiconductor and non-volatile memories, EMI radiation, picosecond electronics, biomedical engineering... the list is almost endless.

Anyone wishing to attend can count on assistance from the US Consulate in the form of information and contacts. Enquiries to Deborah Corrigan, Commercial Section, US Consulate General, Sydney.

## Philips widen rectifier range

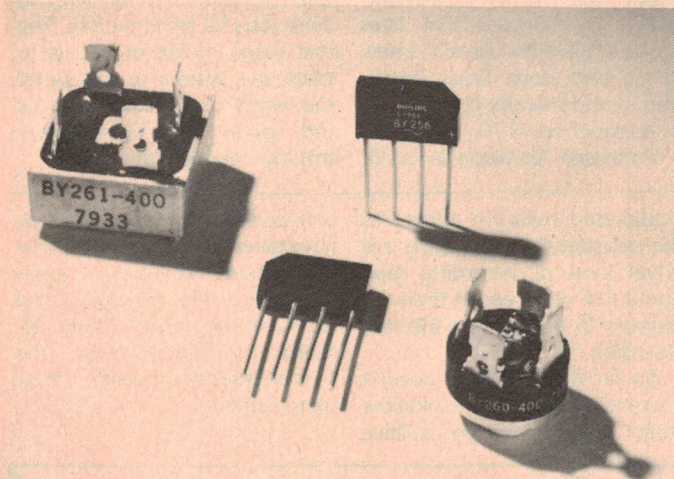

The introduction of four new types of full wave bridge rectifiers by Philips means that their range now extends from 1 A to 25 S.

The BY256 is a 1.5 A device with a maximum input voltage of 80 Vrms, suitable for equipment such as hi-fi amplifiers which use an input mains transformer. The BY257 is also rated at 1.5 A average output, but it can handle inputs up to 280 Vrms. It is recommended for colour television receivers and switched-mode power supplies up to 200 W.

The BY260 and BY261 series

are both general purpose types for industrial applications. Both series have three versions with maximum rms input ratings of 140 V, 280 V and 420 V. BY260s can handle a maximum of 12 A and BY261s are rated at 25 A.

Further information from: Philips Electronic Components and Materials, 67 Mars Road, Lane Cove 2066. (02) 427-0888.



## Ion out your problem?

**If you don't like jogging and you can't afford acupuncture, don't give up all hope of ever becoming a healthy and happy individual.**

Negative ions could just turn the trick for you! As with all 'fringe' ideas, some of the claims made for negative ions are far fetched and others more credible.

People **do** tend to get ratty before thunderstorms when the air is full of positive ions and they **are** invigorated at mountain resorts where negative ions abound.

On the other hand, the lady whose rash disappeared when she switched from nylon to cotton underwear had probably been suffering from an allergy rather than from inadequate penetration of negative ions to the flesh beneath her flimsies.

Creative Electronics are now distributing an inexpensive portable 'negion' generator for anyone who wants to settle the issue by personal experience. Their Bionaire 300 uses a cold corona discharge to create nearly 10 billion ions per second (according to their brochure). It's designed to work off a 12 Vdc supply for use inside cars.

Some drivers report striking reductions in stress and fatigue after installing the device, but since we haven't tried one out ourselves we're keeping an open mind. More info from Bionaire International, 24 Perry St, Matraville 2036. (02) 666 4000.

## World's largest earth station

**Raisting in West Germany will become the biggest satellite earth station in the world when two new antenna systems come on-line in 1981.**

The new antennas will be 32 metres in diameter and weigh 300 tonnes each. Both will operate at 4 GHz on the receive side and 6 GHz on transmit.

A new feed system, equipped for different transmit and receive polarisations, will be fitted to the existing three antennas as well as the two new ones to make the whole station compatible with the new generation of Intelsat V communications satellites which will go into service early in 1981.

Siemens, who built the existing equipment at Raisting, are once again the main contractor and the steel structure will be made by MAN, the German heavy engineering firm.



## Mitsubishi enters VCR market

A new video cassette recorder from Mitsubishi has all its functions remotely controllable by infrared transmitter.



Facilities available on the HS 300 include fast picture search at seven times normal speed, slow motion search at half speed, freeze-frame, single frame advance and automatic rewind. In the freeze-frame and single frame advance modes the machine automatically searches for the most stable adjacent frame so as to avoid the picture deterioration often found in other VCRs operating in these modes.

A flip-down front panel reveals the comprehensive timer

controls, which allow the user to record unattended up to six programmes of varying length on any station over a period of a week. Or the same programme (perhaps the news) can be recorded every night until the tape comes to an end. Special circuitry is included to guard against accidental alteration of the instructions.

Although it has been available in some countries since May of this year, it is still not known when the HS 300 will be on sale in Australia.

## Home safety system

A new home emergency warning system can bring the right kind of qualified help quickly and almost immediately.

Run by Monitor Protection Services of Melbourne, the service is so far only available in Victoria, but the company hopes to provide national coverage within six months.

The key to the system is a wall mounted transmitter in the home, which is connected directly to Monitor's headquarters through normal telephone lines. A distress signal from the wall unit activates a central computer to print out relevant medical information and emergency instructions to the service's paramedical staff.

All relevant data is provided by the subscriber when he or she joins the service, which is

claimed to be cheap enough for the average Australian family.

At the push of a 'crisis button', the wall unit will automatically dial the computer. If all the lines are engaged it will wait 32 seconds and try again, and if that fails it will dial a different number which is connected to the computer through a different Telecom exchange.

In case the crisis button can't be reached, the subscriber wears a small transmitter which can activate the wall unit at a distance of 45 metres. The wall unit optionally also includes automatic smoke and gas detectors and microwave equipment to sense intruders.

## Briefs

Philips are going all out for domination of the video disc market. They have just signed a licensing agreement with Sanyo which allows the latter to make and sell the laser pickup system developed by Philips and MCA Inc of the USA. Similar agreements have already been made with Pioneer, Sony, Sharp and Trio-Kenwood.

Amplified cordless headphones for the hard of hearing were recently released by Senheiser Electronic. A small infrared transmitter plugs into the headphone socket of a TV, radio or other audio source. Its output is modulated by the audio signal and detected by a compact receiver amplifier unit connected to the earpiece. The system is also now available to patrons of the hit musical 'Evita'.

Unl-board is a re-usable 'protoboard' designed to accommodate both discrete and integrated components. Power transistors can be mounted complete with heatsink on the same board as 40 pin ICs. An introductory kit, including an illustrated applications manual, is available for \$9.95 from the makers, Advanced Electronic Systems Pty Ltd, of Elsternwick, Vic.

Krohn-Hite tell us their 4400 oscillator, designed specifically for analysing audio equipment, generates a 7 Vrms sine wave at any frequency from 1 Hz to 110 Hz with distortion of less than 0.001 percent. Simultaneous inverted and quadrature outputs are available at the same output level and quadrature outputs are available at the same output level and source impedance of 600 ohms. Output voltage varies less than 0.05 dB over the frequency range and can be precisely attenuated up to 90 dB by vernier control.

A series of power FETs designated TIPF 101, 102 & 103 are the first in a family of such devices planned by Texas Instruments Drain-source voltage ratings are 40 V, 60 V and 80 V, with continuous drain current outputs of 3 A, 2.4 A and 2 A respectively. Suggested ap-

plications are driving bipolar switch devices, switching power supplies and as CMOS interface to power, voltage and current levels.

The Standards Association has published a new general standard, AS 1541.1, on 'fixed capacitors for electronic applications.' It establishes test methods and terminology and is to be the basis for future standards on particular types. Copies are obtainable from offices of the Association in state capitals and Newcastle. The Association is also making comment on a draft test method for fixed capacitors used to suppress radio interference. The new draft, DR 80110, aims to bring us in line with the International Standard this special area. Free copies from the Association's offices.

The Allsop 3 is a new video cassette recorder cleaner which slots into the machine like any other cassette and cleans the capstan, pinch roller, audio and video heads with a soft chamol and solvent. Available from most local video dealers.


Built-in calibrators are the leading feature of two new DMMs in the Kentron 31/2-4 1/2 digit range from Applied Measurement Australia Pty Ltd. A complete recalibration involves three adjustments and takes minutes. A 'hold probe' option is available which freezes the reading when the probe is removed from the measurement point — useful for readings in hard-to-get-at places. Phone (02) 816-2651 or (03) 25-4435 for details.

A \$25000 grant will be awarded to the winner of the 1980 Marconi International Fellowship. To qualify, candidates must have contributed to the science or technology of communications for the betterment of children. Winners in previous years have mostly been professors at prestige institutes like M.I.T. or Caltech, but hopefuls can address applications to the Marconi International Fellowship, Aspen Institute of Humanistic Studies, 1229 University Avenue, Boulder, Colorado 8-303, USA.


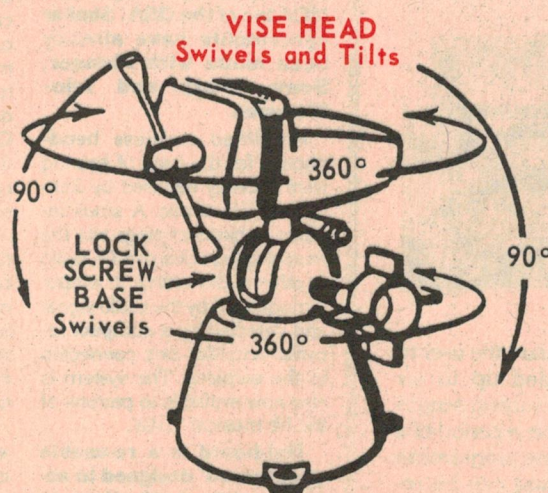
# Hold it!

Anywhere you want it.  
Scope Panavise tilts, turns and  
rotates to any position.  
(better than a third hand)




## WITH THE EXCLUSIVE STAR KNOB★

There is a PanaVise that fits your exact needs. Select the most suitable combination from the five interchangeable heads and four bases. You have the flexibility of more than one head for your base, greatly increasing your Panavise's range of usage at a modest additional cost.

Illustrated is the ORIGINAL PANAVISE MODEL 301 showing the tilts, turns, and rotations of this fine tool, all controlled by the patented single variable load control knob and split ball feature. There is nothing else like it! Electronic assemblers and camera repairmen, jewelry designers and instrument makers, gun smiths, and engravers are finding this robust little vise to be one of the most important and useful tools on their bench.

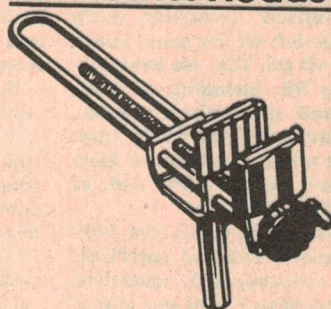
## \*Two Other Heads To Suit Your Scope Panavise ....


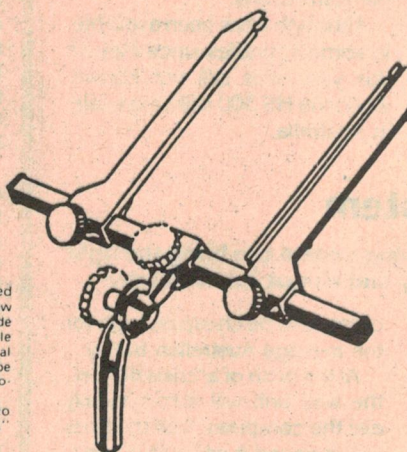
### MODEL 366 WIDE OPENING HEAD

Opens to a full 6 inches (152 mm). The contoured neoprene jaws provide a cushion over the steel jaw plates. These jaw pads are deeply ribbed on one side to firmly grip odd-shaped items. They are reversible to the wide "V" configuration for holding cylindrical objects. When working with heat, the pads may be removed. The fine thread screw permits micro-pressure adjustment.

This multi-purpose vise has a black oxide finish to reduce glare and eye fatigue. Jaw width is 1 1/2" (44.5 mm) and throat depth is 2" (50.2 mm).



### MODEL 315 CIRCUIT BOARD HOLDER

This versatile head holds p.c. boards of any size and shape, and it holds them exactly where you want them—flat or vertically, or any angle in between when used with one of the PanaVise bases. It may also be moved laterally in either direction without re-positioning the arms.

Both arms extend 6" (152 mm) from the cross bar. The "V" grip grooves hold any board to 5/32" (4 mm) thick. Found only on the PanaVise Circuit Board Holder is a second set of "V" grooves positioned laterally near the tip end of the arms. These facilitate holding exceptionally small p.c. boards and small electronics parts.

The exclusive PanaVise fingertip spring tension adjustable arm firmly holds boards yet permits the board to be inserted and removed repeatedly without further adjustment.

Please send me an illustrated pamphlet showing the complete Range of Heads, Bases and Accessories.

Name ..... Company Name .....

Address .....

Post Code .....

POST TO SCOPE LABORATORIES, P.O. BOX 63, NIDDRIE, VICTORIA, 3042. TELEPHONE: (03) 338 1566.



**THE INCREDIBLE STUDIO 1000**



*N.B. MARUNI microphones take some beating too!!!*

**MARUNI**

SUPERLATIVE HEADPHONES AND MICROPHONES

THE **MARUNI** CORPORATION

297 WILLIAMSTOWN ROAD, PORT MELBOURNE, 3207 • TELEPHONE, 645 2079 • TELEX 32571



## OPAL 1000

The OPAL 1000 can be used as a basis for expansion.

The OPAL 1000 is an 8 slot S-100 system conforming to the new IEEE standards. A Delta Products Z80a 4MHz CPU card with 2 RS232c serial and 3x8 bit parallel ports is used in conjunction with the Delta Products Disk Controller. Memory is provided by a 4 Mhz 64k dynamic RAM Board by Measurement Systems and Control. The memory board is fully bank selectable and is designed for upgrading to a multi-user system. Disk drives are 2x8" Shugart SA801R running at double density (480k/drive) and fitted with our exclusive Disk Saver which prolongs the life of the drives and floppy disks by turning off the AC power to the drives 14 seconds after the last drive select and thus reduces routine maintenance. The Disk Saver also reduces the risk of data loss due to power failures. The software is CP/M version 2.2 with Delta Product's utilities which include DTEST (for testing drives and floppy disks) and M2 (a comprehensive memory test program). The Delta PROM monitor enables fault finding to be carried out independently of the Disk Drives. The system is mounted in an attractive pressed Aluminium housing with a cast front panel fitted with reset button and key operated on/off switch. **PRICE \$4,174.00 plus sales tax.**

## MPI 88T

### SERIAL/PARALLEL PRINTER

The MPI model 88T is supplied with a dual tractor/pressure-roll paper feed system and a serial (RS232c) or parallel (Centronics) interface. (The printer is tested and supplied setup for a serial interface as detailed on the connection sheet). The tractor paper feed provides the precision required to handle multi-copy fanfold forms, ranging in width from 1" to 9.5". For those applications where paper costs are important, the pressure-roll feed can be used with 8.5" roll paper. A long-life ribbon cartridge gives crisp, clean print without messy ribbon changing. The microprocessor controlled interface has 40, 80, 96 or 132 column formatting capability while printing the 96 ASCII upper and lower case character bi-directionally at 100 characters per second.

- Full 96 ASCII character code set.
- Automatic line feed and print functions.
- Built in self-test facility.
- Any one of 5 baud rates (110, 150, 300, 600, 1200) for the RS232 serial interface. The printer is also equipped with a switch selectable parallel interface (TTL level).
- Price includes RS232c Serial cable and Parallel cable for TRS-80 with Expansion interface or standard Centronics fitting.
- The printer can print single or double wide characters.
- Any one of 8 standard forms lengths can be switch selected (default) or programmed on-line.
- Printing 6 or 8 lines per inch.
- Select any one of four character densities (number of characters per line)
- Warranty: 30 days.

**Printer \$935.00 plus sales tax**

## SPECIALS

### CROMEMCO SYSTEM Z2H

with 1- megabyte IMI hard disk drive, CDOS, Basic and other utilities. \$8,970.00 plus sales tax. Ex stock.

### VECTOR GRAPHICS MZ

with televideo 920c serial terminal and CP/M. \$5,000.00 plus sales tax.

### NORTHSTAR

48K, 2 serial ports with CP/M and a televideo terminal. \$4,700.00 plus sales tax.

### NDK S-4000

### PRINTING

### MATHEMATICS

$$F(\omega) = aT \frac{\sin \omega T/2}{\omega T/2} e^{-j\omega T/2}$$

$$e_{rms}^2 = 4KTR(f_2 - f_1)$$

$$L_1 = 10 \log \frac{1}{80} \times S_n \text{ (dB)}$$

$$A^2 + B^2 = C^2$$

$$A^2 + B^2 = C^2$$

$$F(\omega) = aT \frac{\sin \omega T/2}{\omega T/2} e^{-j\omega T/2}$$

$$e_{rms}^2 = 4KTR(f_2 - f_1)$$

$$L_1 = 10 \log \frac{1}{80} \times S_n \text{ (dB)}$$

$$A^2 + B^2 = C^2$$

$$A^2 + B^2 = C^2$$

$$F(\omega) = aT \frac{\sin \omega T/2}{\omega T/2} e^{-j\omega T/2}$$

$$e_{rms}^2 = 4KTR(f_2 - f_1)$$

$$L_1 = 10 \log \frac{1}{80} \times S_n \text{ (dB)}$$

$$A^2 + B^2 = C^2$$

$$A^2 + B^2 = C^2$$

$$F(\omega) = aT \frac{\sin \omega T/2}{\omega T/2} e^{-j\omega T/2}$$

$$e_{rms}^2 = 4KTR(f_2 - f_1)$$

$$L_1 = 10 \log \frac{1}{80} \times S_n \text{ (dB)}$$

$$A^2 + B^2 = C^2$$

$$A^2 + B^2 = C^2$$

**PRICE \$3,105.00**  
**Plus 15 percent**  
**sales tax**

# JOHN F. ROSE

## COMPUTER SERVICES PTY. LTD.

ALL PRICES SUBJECT  
TO CHANGE WITHOUT  
NOTICE


33-35 ATCHISON STREET, ST. LEONARDS, N.S.W., 2065, AUSTRALIA.  
TELEPHONE: (02) 439 1220 TELEEX: AA 27901

SEND \$1.00  
FOR YOUR EXTENSIVE  
CATALOGUE


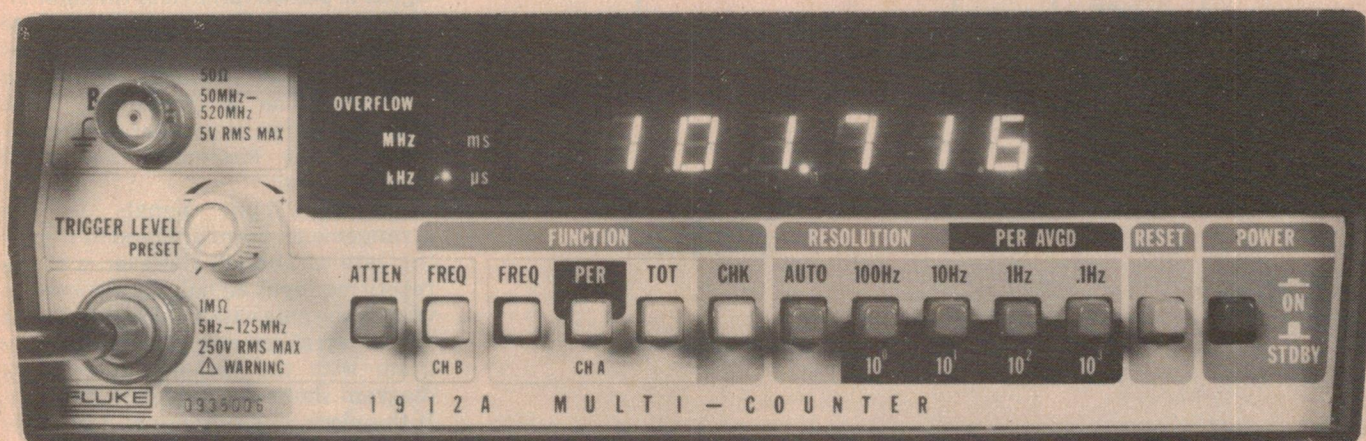
# Digital counter/timers

These instruments are very handy in many branches of electronics. Here is a basic rundown on how they work, how to choose them and how to use them.



The Fluke model 1912A is a very versatile instrument. They are distributed here by Elmeasco.

MEASURING frequency and time intervals to a known accuracy is often important in many areas of electronics: in communications, broadcasting and audio applications, in digital work and particularly in computer applications — from micros to mainframes. Digital frequency meters (DFMs), or counter/timers as they are also called, have become such an essential item of test equipment that many manufacturers are offering a diverse range of instruments ranging in price from a \$150 instrument covering the range 20 Hz to 200 MHz to many thousands of dollars for a microprocessor-controlled instrument capable of measuring frequencies well into the gigahertz region and time intervals in the picosecond range.

Frequency and time interval measurement is an area where digital

techniques come into their own. The object is to accurately quantify a measurement. Prior to the development of digital instrumentation to do this job, analogue techniques were used — often ingenious and highly refined, but laborious. Heterodyne frequency meters were used widely. These consisted of a stable, accurately calibrated, variable oscillator (VFO) driving one input of a wideband mixer, the unknown frequency being applied to the other input. The output of the mixer was monitored on headphones or an audio amplifier while tuning the VFO. As the unknown frequency was approached an audible 'beat note' would be heard, decreasing in pitch as the VFO was tuned closer to the frequency being measured. At 'zero beat' you could then read off the unknown frequency from the instrument's calibrated dial. The old BC221 will no

doubt be familiar to many of our older readers. The method was laborious, especially when you didn't even know the 'ballpark' of the unknown frequency, and to get a measurement accuracy better than several hundred Hertz ( ... maybe that's cycles/second!) was tantamount to magic: Top frequency was about 20 MHz.



These days *pocket* DFMs can measure frequency to within  $\pm 50$  Hz or better, up to 200 MHz! That's at least a factor of ten better all round than the old BC221. And readout is obtained in a few seconds or less.

Time interval measurement was, and still is, very much left to that old workhorse — the CRO. But, a CRO has its limitations and quantifying a time measurement to the accuracies required these days is best done with a digital counter. ▶


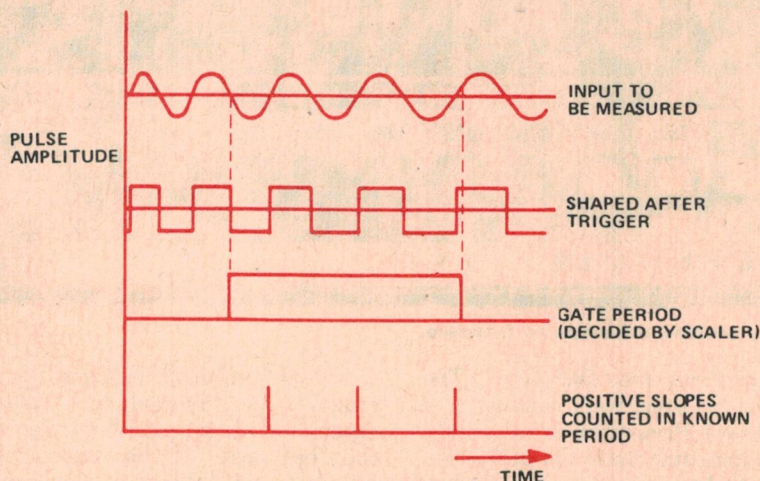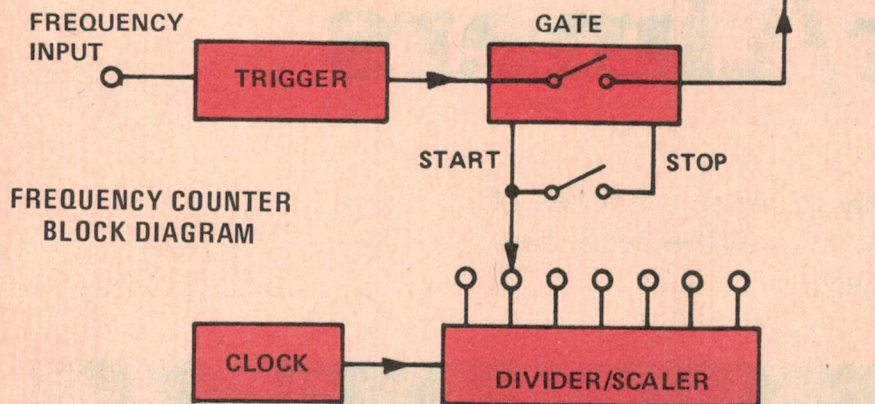
## Frequency measurement

The block diagram of a basic digital frequency meter is shown in the accompanying illustration. The input signal first encounters a 'trigger' or 'squaring stage' which ensures that the measurement always commences on the same part of the input cycle waveform. The output of the trigger then enters a gate. The gate is 'opened' for a period and allows a number of input cycles through to the counter. The period for which the gate remains open is



determined by the output from a divider/scaler driven by a very stable, accurate clock oscillator. A number of outputs from the divider/scaler may be selected to vary the period the gate is open. Usually, a number of decade steps are provided.

The output of the gate drives a counter which provides a binary coded decimal (BCD) output for the display. A 'hold' or 'latch' stage is generally added so that a steady group of numerals is displayed. (For a description of the various ways of making a digital display, see "Electronics Its Easy" — an ETI publication — Volume 3, Chapter 26).

The timing diagram below the block diagram illustrates the sequence of events. The input signal, often sinusoidal, is shaped by the trigger stage into a train of rectangular pulses. The gate allows a number of pulses through to the counter, in this case three, during the period it is 'open'. The circuit selects only the positive-going pulses in this example, though negative-going pulses from the trigger stage could equally well be used.

If, say, a gate period of one millisecond (1 ms) were selected the counter would display '3000'. In other words, the input frequency would be 3 kHz.

Practical instruments will have se-

lectable gate periods ranging from one microsecond (1  $\mu$ s) to as much as 10 seconds. The display may have five digits, though eight digit displays are more common.

Many modern digital frequency meters incorporate a high speed divider immediately following the gate, the output of this divider being used to derive the first and second digits of the display. To extend the range of the instrument, a 'prescaler' may be included. This is a high speed divider providing a fixed division ratio of ten. Its output may drive either the trigger stage or the gate directly.

## Period measurement

Measuring the period between 'events' is done by re-arranging things a little. The gate, counter and display are used as before but the gate is turned 'on' and 'off' by the input events and the clock signal is passed through to the counter. As the clock is a highly stable, accurate oscillator, the period between input events can be measured with great precision. The accompanying block diagram shows the general arrangement of the instrument for period measurement.




Separate input signals in the arrangement shown are used to trigger the gate on and off. However, a single repetitive input signal may be used to trigger the gate with a slightly different circuit arrangement. The timing diagram with the period counter block diagram shows the sequence of events. If the clock was running at 1 kHz, for example, the time interval between pulses would be one millisecond. As 17 pulses passed through the gate in the example, the period between the A input event and the B input event was 17 ms and the display would read, say, 17 000 (resolution of one microsecond).

Pulse widths can be measured with a period counter, too. In this instance, the gate is triggered on the positive-going and negative-going edges of the input pulse. However, some difficulties arise. If the input pulse had a perfectly 'square' shape, the on and off gating points would always give an accurate result because the triggering transitions would occur precisely on the rise and fall of the pulse. Trigger level would not affect the interval measured. Real-life pulses however, are seldom perfect, the edges having definite rise and fall times. In this case, the trigger level becomes critical in determining the width of a pulse. The diagram here shows why and how it is overcome. Counters are





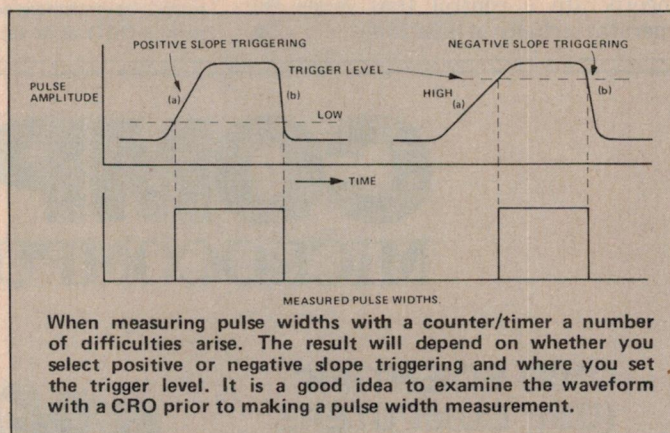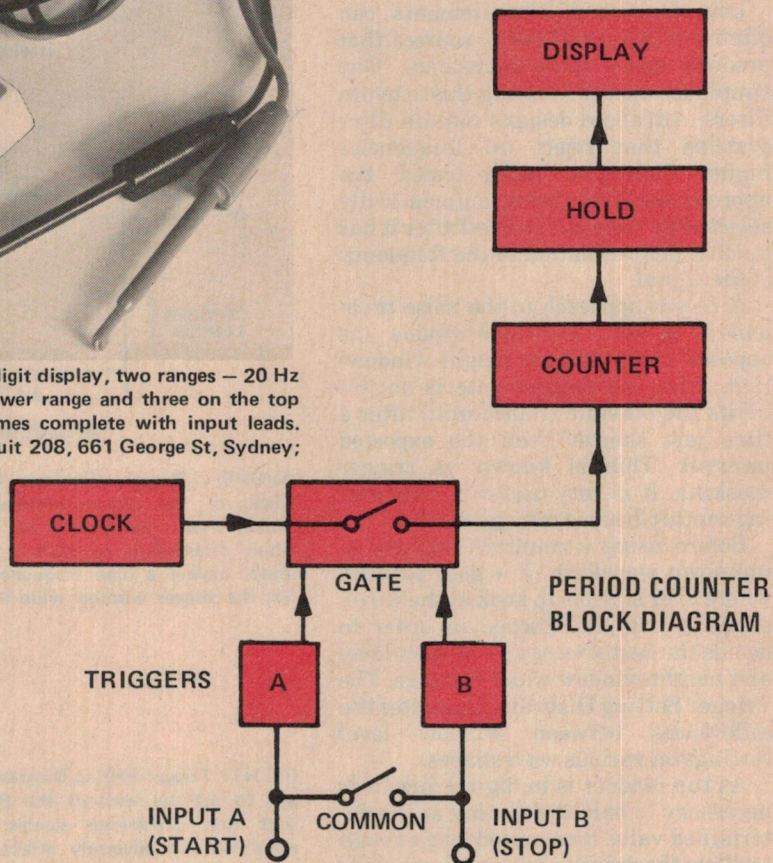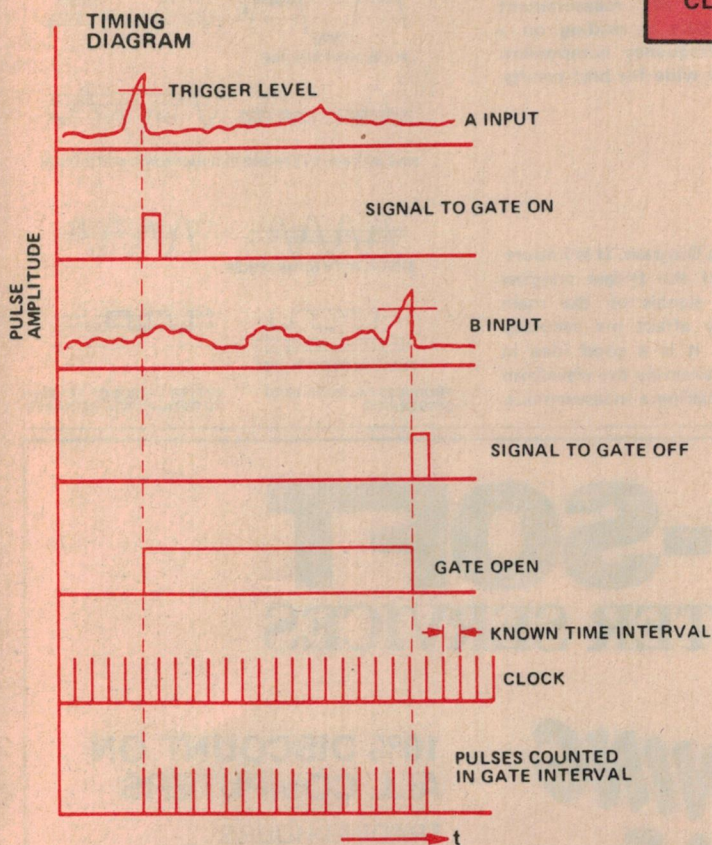This handheld DFM from Sinclair Electronics features an eight digit display, two ranges — 20 Hz to 10 MHz and 5 MHz to 200 MHz, four gate times on the lower range and three on the top range. It is powered by a single No. 216 9 V battery and comes complete with input leads. Sinclair Instruments are available through Emona Enterprises, Suit 208, 661 George St, Sydney; Phone (02)212-4815.



usually provided with a 'slope selection' control which determines whether the trigger operates on the positive or negative slope — (a), or (b) respectively in the diagram.

### Noise error reduction

The above descriptions give the basic operating modes of the various counter/timer/frequency-meter combinations. In practice, a number of refinements

may be incorporated to obtain better practical performance.

Noise can be reduced by incorporating a fixed amount of backlash in the trigger circuit; this produces what is called the 'trigger window'. On the way▶




up the trigger level is at a higher level than on the way down, as shown in the Trigger Window Diagram here. Provided the noise added to the signal has an amplitude smaller than the window width, the counter will only trigger once on the way up and once on the way down. This method works well for high-frequency measurements where the noise is usually a small percent of the signal-plus-noise signal amplitude.

Low frequency measurements can often involve interference sources that produce rapid spike transients. One simple method of reducing this is to use filters. Advanced designs contain filter systems that reject all frequencies higher than that being tested, the appropriate filter being automatically selected by the counter itself after it has made a determination of the frequency of the signal.

A recent approach to the noise problem is to set up a time-window (as opposed to the trigger height window) that, once the counter gate is on, inhibits the off-state chance until after a time just shorter than the expected interval. This is known as trigger masking. It is very useful in eliminating contact-bounce retriggering.


Before using a counter/timer on an unknown waveform, it is good practice where ever feasible to look at the wave-shape on an oscilloscope in order to decide the best strategy for trigger-level and height-window width settings. The Trigger Setting Diagram illustrates the differences between window level settings on various waveshapes.

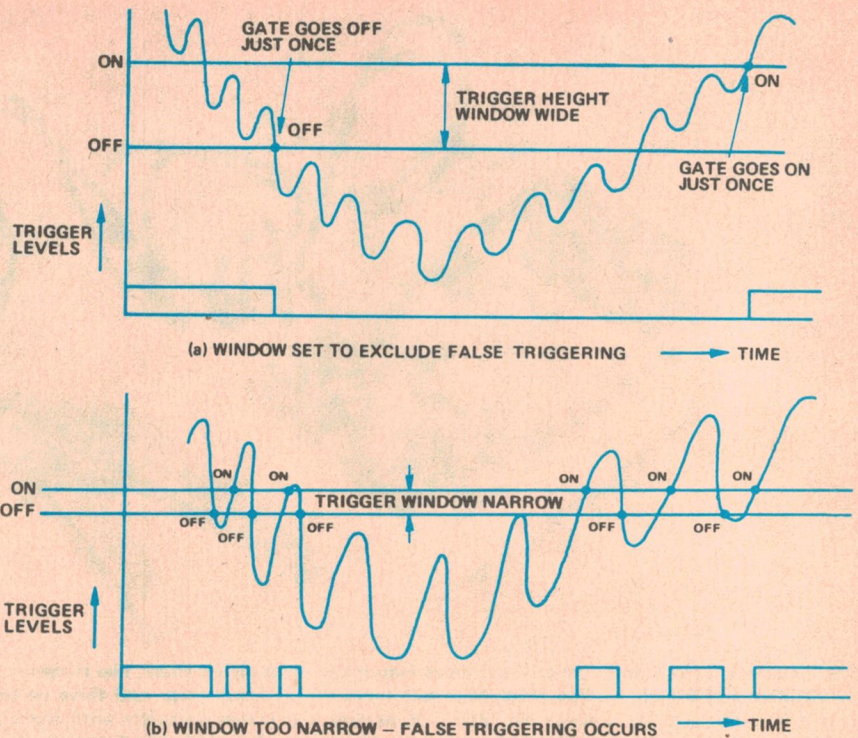As the readout is in digital form it is necessary to hold the display at the determined value for a period long enough to allow the value to be read. Some units incorporate a control that gives the operator a choice of hold time. ►



ABOVE: Trigger Window Diagram. The width of the trigger window will greatly affect the accuracy of measurement when attempting to take a reading on a signal having a high frequency component. Set the trigger window wide for best results.

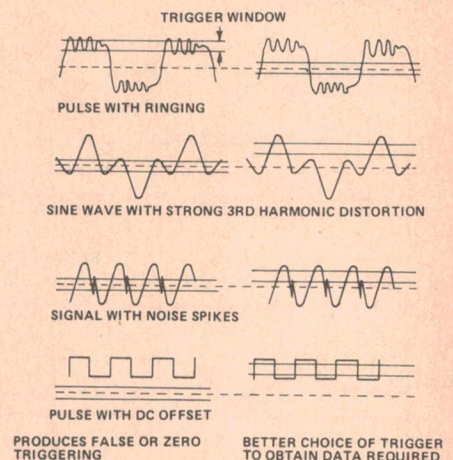RIGHT: Trigger Setting Diagram. It is important to set the level of the trigger window such that extraneous signals on the main signal do not adversely affect the accuracy of the reading. Again, it is a good idea in many circumstances to examine the waveform with a CRO prior to making a measurement.



# COMP-SOFT

## MICROCOMPUTER SERVICES

### OHIO SCIENTIFIC (OSI) COMPUTERS

- Superboard and software
- C1P • C4P
- C4P MF

# OPENING SALE

### 10% DISCOUNT ON ALL COMPUTERS

TRADING HOURS  
Monday and Thursday:  
9.30 am-5.30 pm  
Friday: 4.30 pm-8.30 pm  
Saturday: 9.00 am-12.30 pm

235 SWAN STREET, RICHMOND. PHONE (03) 428-5269.



## Economy Sized Computers™ don't stunt your growth.



A lot of small business computers are like our ads—they start out small and stay that way.

But Vector's Economy Sized Computers grow as you grow. Whenever you need to, you can have up to 4 more terminals, more power, more memory.

With Economy Sized Computers, you get data and word processing capabilities you only expect from much larger computers. All for the price of a new copying machine—

See the Vector Economy Sized Computers at your nearest computer dealer.

Because no matter how small they may look, their performance grows on you.

**VECTOR**  
VECTOR GRAPHIC INC.


Dicker Data Projects P/L

31 Cawarra Road, Caringbah, 2229.  
Ph: (02) 524-5639, 525-4707. Telex: 70182.


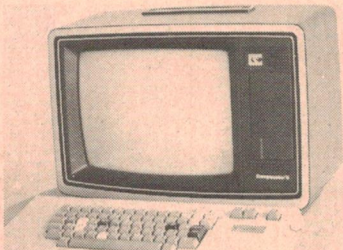
# \$ THE LOGIC SHOP PTY. LTD.

**DISCOUNT SHOPPING** for your professional Microcomputer and terminal requirements.



**COMPUCOLOR II** ex stock  
From \$2095 including tax.

Features: • up to 32K user RAM  
• Eight colour display • 32 lines of 64 characters • 5" Mini disk drive • 40 tracks, 48 TPI



**TELEVIDEO TVI 912B DISPLAY UNIT** ex stock  
From \$1256 including tax.

Features: • 24 lines at 80 characters per line • Transmission rates 75 — 19,200 Bd. • 96 character ASCII upper and lower case • 12 inch monitor.



**MICROLINE 80 PRINTER** ex stock  
From \$951 including tax.

Features: • 80 char/sec • 80 and 132 char/line • 9 x 7 dot matrix • Character or graphics printing • **Plug compatible to TRS-80.** ® Rgd. Tm. Tandy Corp.

## SPECIAL

5¼ Diskettes — \$3.95 ea. inc. tax.

\$ THE LOGIC SHOP PTY. LTD.

212 High St., PRAHRAN, VIC. 3181. Tel: 51-1950.  
91 Regent St, CHIPPENDALE NSW. 2008  
Tel: 699-4910

TRS-80 ® is a registered trade mark of Tandy Electronics.



These three counters were recently added to the range of instruments offered by AWA. Made by Marconi Instruments, each features an eight digit display and a switchable low-pass filter. First in the range is the low cost model 2430A. It covers 10 Hz to 80 MHz and has three selectable gate times. The model 2431A (middle) covers 10 Hz to 200 MHz while the top-line 2432A includes a prescaler that permits measurements to 560 MHz, plus five selectable gate times.

## In use

The input impedance of most counters that operate up to 50 MHz or so is generally 1 M with a few pF of stray capacitance in parallel, hence the actual impedance decreases at the higher frequencies. An input impedance around 1 M is generally high enough for most applications such that connecting the counter does not load the circuit to which it is connected. However, it is always wise to remember that the input impedance falls at the higher frequencies, as does the sensitivity. An input cable will significantly increase the input capacitance but a x10 CRO probe will improve matters considerably without unduly affecting sensitivity.

Prescalers for the VHF/UHF range

will have an input impedance of 50 ohms across the range and this may severely load a circuit having an impedance significantly higher. Fortunately, most instruments have a sensitivity in the tens of millivolts region and the counter can usually be coupled to a higher impedance by means of a small value series capacitor. Cable capacitance is generally not significant enough to be considered in 50 ohm systems.

The last digit in a readout will generally be 'uncertain' as a single digit is usually the limit of an instrument's resolution and the accuracy of the clock oscillator is generally of the same order, except in the high-priced highly accurate models.



When making period measurements it is best to select a gate time as long as practicable as greater precision results. Extend the gate open time to 100, 1000

or even 10 000 periods if convenient. With relatively slow events, this could be tedious — you may have to wait tens of seconds to several minutes!

Always take care not to exceed the maximum dc or ac input levels specified for your counter — such carelessness can be disastrous.

## How to choose

First, look in your piggybank! Prices for a straight digital frequency meter start at around \$150. Next step in the price/features bracket for a DFM is around \$230 - \$250. Instruments range right up to several thousand dollars, which is generally beyond most hobbyists!

Next step is to look at your applications. But, keep in mind future applications and get something a little better — if your budget will stretch that far. The number of digits in the display will certainly be a deciding factor, depending on your applications. The majority of instruments available have either six- or eight-digit displays. Next consideration is the number of ranges offered (gate time selection). Resolution is important and is related to the display, an eight-digit instrument has a better resolution than a six-digit instrument, naturally enough.

The clock oscillator stability determines the inherent accuracy of the instrument and it is instructive to compare the specifications of different makes and models when considering this parameter. Generally, a temperature range over which the accuracy is maintained will be quoted along with this specification. Accuracy will be quoted in parts-per-million (ppm) or parts in  $10^n$ . A reasonable figure for accuracy, for most hobbyist applications, would be one ppm (one in  $10^6$ ) over a temperature range of  $15^{\circ}\text{C}$  to  $50^{\circ}\text{C}$ .

Whether you get a battery operated or a mains/battery operated instrument will depend largely on your applications.

Refinements like filters, trigger window control, gate time delay, frequency ratio, totalizing etc depend entirely on your application — and your budget!



This low cost B & K Precision counter has a six digit display and a switch to select either a one second gate time or auto-ranging. B & K instruments are distributed by Parameters Pty Ltd; phone (02)439-3288 in Sydney, or (03)90-7444 in Melbourne.



Philips Test and Measuring Instruments recently added these two DFMs to their range. The upper one, model PM6667, covers 10 Hz to 120 MHz. The lower one, model PM6668, covers 10 Hz to 100 MHz and has a prescaler covering to 1 GHz. Both feature seven digit LCD displays.



# Don't throw away batteries ...& money Use GE Rechargeables

From the frontiers of space to the products in your home.

When reliable batteries were needed for missions to the Moon and Mars, General Electric was a leading supplier. Now GE's Nickel Cadmium battery leadership has pioneered a low cost system for you that can recharge all of GE's popular battery sizes (AA, C, D and 9 volt) up to 1000 times, with a single low-cost charger.

If you're tired of buying batteries, it's time for GE Rechargeables.

Rechargeable batteries make sense in today's value-conscious market. GE's proven efficiency and dependable system is rapidly attracting more and more consumers to the advantages of GE Rechargeables.

**Convenience:** Charge overnight or keep extra batteries charging, fresh and ready to use.

**Longlife:** GE Batteries are rechargeable up to 1000 times and they will last for years.

**Performance:** GE Rechargeables maintain voltage for the life of the charge to keep your products operating with steady performance.

**Warranty:** Guaranteed not to leak, with resultant damage to your product, plus all GE battery products have a full one year warranty.

**Economy:** One GE Rechargeable outlives 100 or more throwaways — even the long-life alkaline kind.

**Tests show that one GE Rechargeable Battery outlasts:**

350 Alkaline AA size batteries in a photo flash.

140 Alkaline C size batteries in a cassette recorder.

250 Carbon-Zinc D size batteries in a torch.

100 Alkaline D size batteries in a motor-driven toy.

150 Alkaline 9-Volt batteries in a calculator.

Available from leading retailers.

**Trade enquiries:**

Australian General Electric (Sales) Limited,  
86-90 Bay Street,

Ultimo, New South Wales 2007.

Rank-General Electric Housewares Pty. Ltd.

296 Ferntree Gully Road,  
Notting Hill, Victoria 3168.


plus regional offices in Capital City areas.

C. G. E. Marketing Services,  
117 Burnley Street,  
Richmond, Victoria. 3121.

Products from the Wonderful World of General Electric

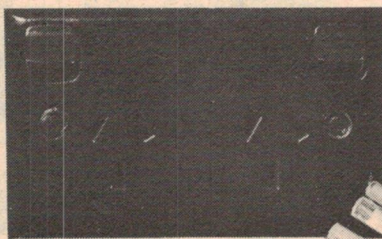**GENERAL  ELECTRIC\***

\*Trademark General Electric Company  
U.S.A. World's Largest Electrical  
Enterprise.



**Batteries that last for years!**



# Toys for a bored consumer society

Dennis Lingane

"They need all kinds of s... these days. We never needed any of it in our time." This comment by a bemused old lady sums up Lingane's feelings about the 10th Summer Consumer Electronics Show in Chicago last June.

THE GREAT electronic circus has left town. The streets of the windy city are strangely quiet and the hotel bars and foyers very, very empty.

For four days this northern metropolis has been bedlam. Over 60 000 delegates from 58 countries filled the official 35 hotels and a fleet of buses carried hung-over executives back and forth between McCormick Place, McCormick Inn, and the Pick Hotel where 600 exhibitors showed their new products for 1980/81.

Now the video companies with their attendant porn queens, the bevy of Playboy and Penthouse girls, the army of long legged models that handed out magazines, daily newspapers (four every day), brochures, and drinks in the hospitality suites that operated round the clock — all of them have gone. Seven hundred and fifteen dazed and disoriented journalists from all over the world are left to analyse what it was all about.

Jack Wayman, who organised the show says it's a "sexy industry" and so the show should be a "sexy show". Certainly the number of leggy ladies with slits up the sides of their skirts, down the back, and up the front gave it that kind of feeling.

But underneath all the hype and hysteria this is an annual opportunity for the industry to take a good look at itself and assess the past year and the potential of the future.

The economy is bad and the atmosphere during the show is one of desperate optimism. Everyone says that things will get better. Meanwhile they are all talking themselves into an economic recession.

## Video boom

The big bright star on an otherwise gloomy horizon is video. All the major film companies are now in the market place trying to jump on the band wagon.

Over 10% of the massive McCormick Pavilion convention centre was taken up by video software manufacturers. At the packed video seminar Bob Reed from the National Video Clearing House said that there are now over 30 000 titles available on video. Only 21% of that is feature films, but that share is growing almost daily.

VHS manufacturers are now offering feature laden machines with six hours play and record time. Toshiba was showing yet another format which will record two channels at once — and you can play them together or one at a time.

RCA showed its video disc player and announced that it would launch America wide in January 1981 with a massive software back up. Matsushita exhibited their JVC VHD video disc ▶

Show organiser Jack Wayman says it's a "sexy industry" and the show should be a "sexy show" — how that relates to electronics is left to our imaginations. All pictures in this article courtesy of Geoff Matthews from Convoy International.







Technology for the energy conscious — solar powered receivers

system but said that launch would not be until the end of 1981. It has signed G.E. and Thorn to back the system.

One very interesting extra displayed by Matsushita is a digital to analogue converter, which makes their video disc into an audio system as well. This seems to be the first time that PCM techniques have broken into the consumer domain.

Al Bergano from MGM (which joined the video software market only four weeks before the show) says that his The ultimate in loudspeakers? — the \$20 000 Infinity monitors. It'd be cheaper to book a lifetime subscription to the five best concert and opera venues in the world.



company will be putting film out on cassette within 90 days of it being released in the movie theatres. He's not alone — Columbia, Disney, United Artists, Paramount and 20th Century Fox have all joined in the video hysteria sweeping America.

### Audio fade-out

This year's poor relation is definitely audio. Star of the show for so many years it's now a very sorry sight. But there is the occasional show of defiance. Thorens were showing a hand built turntable for \$15 000 and Infinity had speakers at \$20 000 a pair, just stealing a march on Sony, whose best effort cost a mere \$16 000 per pair.

But by and large the mood is one of defeatism. Few dealers bothered to turn up at the Audio Seminar and Technics Vice-President Jeff Berkowitz (who chaired the meeting) was unable to resist commenting.

In an emotional attack on hi-fi retailers he warned that they could no longer expect to "hang on for the ride". He said that retailers are going broke and more would go broke this year.

"Audio is going through a rough time. The glamour is gone out of audio and so has the profit. Yesterday 700 people attended the video conference. Look around you today. Anyone walking into this meeting would agree that audio is dead".

"We must get pride back into our industry. This used to be an audio show, now all everyone talks about is video, video, video."

### TV comeback

While audio sinks to the low profile held by television for the last few years the colour TV industry looks set for a renaissance.

One star exhibit which is due for release in Australia later this year is

the new slimline National Panasonic rear projection TV, whose 45 inch (1143 mm) screen is concealed behind the doors of an antique style cupboard when the set is not in use. This giant TV has 105 channels, 23 of them for cable TV, and won't be as expensive as you might imagine. Predicted price in Australia is \$3000.

Sanyo exhibited a 26 inch (660 mm) TV on which you could draw coloured pictures with a special electronic pen, and Toshiba showed a voice controlled set.

You tell it to turn on and off, and to change channels and what volume level you want. It replies "right" after every command if it understood, and "repeat" if it doesn't understand.

The set is programmed to a selection of voices and will not work for any other voice. It's a good way to restrict viewing in a house where children put TV ahead of homework!

### Computer standstill

Calculators are a stable market, but the computer industry still doesn't quite know where it is headed.

Atari chief Ray Kassar says that instead of getting to the consumer the industry is frightening him off. "Instead of simplifying things we are making them more complicated", he told an industry seminar.

"We must put our energy and talents into simplifying things so that we can reach and communicate with the general public. They are afraid of us".

Kassar says the industry is still relying on hobbyists and small businessmen for its growth.

### Saving energy

Power factor controllers are devices that can reduce the power drawn by a fridge or other appliance using an electric motor by anything up to 60%.

They measure the amount of power the electric motor needs and when it is not under full load feed only sufficient power to do the job.

They save electricity and increase the life of the electrical motor as well. The concept was developed by NASA for the space project and the patents as a consequence belong to the American people.

So companies are free to use the technology and are doing so in increasing numbers. In fact the government has made the item tax deductible to encourage people to fit them to appliances in their houses.


One manufacturer says that if 25% of the fridges in the USA were fitted with these devices it would save the US 11 000 barrels of crude oil a day.

The units cost about \$60 and are selling like hot cakes.





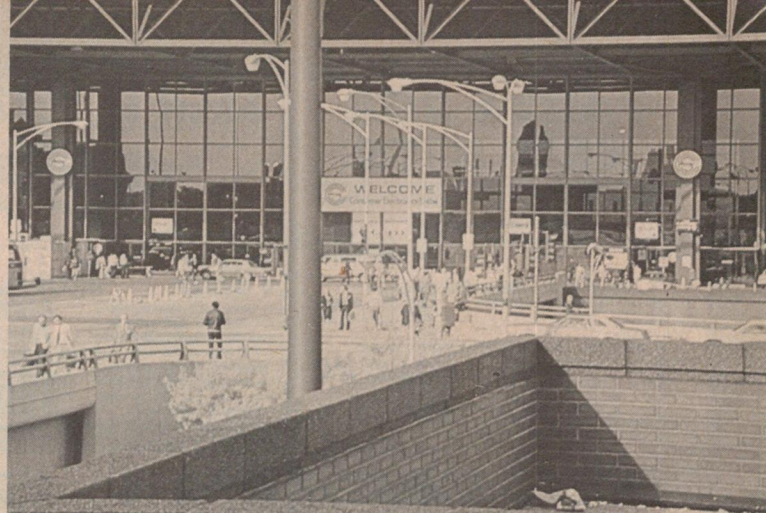Novelty audio items abound — the Bone Fone (you wear it around your neck like a scarf) being a good example.



Entrance to the vast main show venue in McCormick Place.

## Carry-around sound

Hip stereo is the big thing with the young generation. Sony recently launched a play only cassette player that hangs on the hip, and comes with a set of lightweight headphones.

They sold astonishingly well and several companies are now trying to cash in on the boom. Aiwa released a similar unit that also records, and a new company, Technadyne have a unit similar to Sony's but \$50 cheaper. Roller skating enthusiasts, cyclists, and pedestrians are hungry for these mobile lightweight stereo systems which have a very high quality sound.

AM/FM head phones are also popular and a new radio concept called the Bone Fone, which is an audio scarf that hangs around your shoulders, is selling strongly.

## Stealing scenes?

Three companies were selling satellite receivers that can pinch up to 50 TV stations off the six satellites sitting out in space.

The receiver consists of a 12 ft (3.7 m) dish which is mounted on a concrete block in your garden, and a black box that plugs into your TV. You aim the dish at whichever satellite you want to take programmes off. Units are priced under \$10 000 each.

## Remote control

The list of gadgets at the show is endless. For example I was intrigued by a remote control system for starting your car from 500 ft away. The idea is to allow the car to either heat up or cool down — depending on the weather — before you get in.

But the FBI are interested in it, and several have been sold to Europe — especially Italy where people have a nasty habit of wiring cars for bombs.

Ladies like the remote start because you can turn the car lights on as well as start the engine. So when they are approaching their car in a dark car park

they can start the car and switch on the headlights to frighten off marauders.

Remote control systems for switching domestic appliances are also gaining popularity. BSR has a unit for controlling 16 lights and appliances, which comes with an ultrasonic remote control and a timer. The light modules have automatic dimmers built in.

## What's it all about?

It was when I was trying to sort out my jumbled thoughts after four days of this sort of razzamatazz ready to do a radio report live from Chicago that these words cut through my thoughts.

*"They need all kinds of s... these days. We never needed any of it in our time."*

I looked round and there just a few steps behind me was a wrinkled old lady in a large green floppy hat, and a green suit. She was one of those people who wander around the streets talking aloud to themselves.

No doubt most people just dismissed her as a 'nutter', but her comment crystallised my own thoughts. She was right. A lot of what I had seen and would be reporting about in the next few weeks was electronic s... Toys for a bored consumer society.

Who needs a \$10 000 satellite receiver system to receive 50 channels? One TV station is bad enough. And who needs a bedside clock that tells you the time at the touch of a button when you can just look at it. Or a microwave oven that tells you everything it does?

Once it's been refined, voice synthesizer technology will be excellent, for blind people, but who really needs a humidity sensor that sounds a siren when the plant needs watering, or a TV that will plug into the telephone socket so that you can take calls through your TV without moving from your armchair?

But that is the industry we are part of. There are those massive Japanese production lines to keep rolling, and all

those bored people who want new toys, and want to keep ahead of the Joneses.

For some of us the excitement of bending the rules of physics, and making technological breakthroughs makes it all worth while but for better or worse, win or lose, the show is over for another year. Exhibitors are on the way home and their order books will tell if the show has been a success or not.

PRO Ralph Jones, who kept us in coffee and danish pastries for four days as we dashed back and forth attending almost 200 press conferences, is now getting organised for Las Vegas, the winter show.

Organiser Jack Wayman is already back in his office processing the complaints from exhibitors and he too is drawing up plans for Vegas.

For them it is a year-round job. At least journalists escape for a few months between shows and come back to the Australian sun and sanity.

## ABOUT THE AUTHOR

DENNIS LINGANE is a freelance journalist who specialises in writing about the electronics and audio industries. When asked to be rational he claims to be Irish, the rest of the time says he's English.

We do know he lives in Western Australia where for seven years he was a full time journalist with a Sunday paper. He also wrote a hi-fi column that became so successful that two years ago he retired to freelance. That column now runs to five pages regularly in the mass circulation Sunday Times.

He travels extensively and writes for such national circulation publications as Playboy, The Bulletin and ETI (when we can afford him). He has admitted to having a wife and son who, it is rumoured, he does see occasionally. Dennis has been asked often during the last two years to write similar columns for Sydney newspapers but has consistently refused because of what he describes as the "buy an ad. and we'll give you a nice write up" syndrome.

When newspapers take the industry seriously he says he will write for Sydney papers. Meanwhile, he refuses to give up his W.A. sunshine and sailing.

It has been said that Dennis is one of the most informed journalists writing on the industry. This article would tend to support that... Ed.



## PARTS FOR NEW KITS

If a kit you want to build is not listed, the parts may be available anyway. Check the Dick Smith Catalogue or call in to your nearest Dick Smith store.

### CHASER (See EA August)

Complete kit, including front panel ..... Cat K-3145 \$69.50  
PCB only ..... Cat H-8379 \$4.50

### NASA POWER CHOPPER (See EA August)

Short form kit (All components & PCB) ..... Cat K-3325 \$16.50  
PCB only ..... Cat H-8378 \$3.00

### LEDS AND LADDERS GAME (See EA August)

Complete kit inc. printed panel ..... Cat K-3390 \$15.75  
PCB only ..... Cat H-8378 \$3.00

### LED TACHO (see ETI August)

Short Form Kit (includes PCB components etc, but no case - build it into your dash board) ..... Cat K-3240 \$27.50

(Above kits are from magazines' forecasts. We will endeavour to have these kits on sale when the magazines are released; however, delays can occur! Please enquire at your nearest Dick Smith Store).

### FAST NICAD CHARGER (See ETI August)

PCB only ..... Cat H-8627 \$3.00  
(All other components in this kit are normal stock lines)

### GUITAR/PA PREAMP (See ETI August)

Short form kit PCB & components, no trans-former or case) ..... Cat K-3035 \$29.50

### 300 WATT AMPLIFIER (See EA June)

Printed Circuit Board only ..... Cat H-8376 \$9.95  
(Most other components are normal stock lines)

### TV CRO ADAPTOR (See EA May)

Complete Kit ..... Cat K-3060 \$29.95  
Printed Circuit board ..... Cat H-8375 \$3.75

## AT LAST! A CHASER!



**\$69.50**

In response to huge numbers of requests, Electronics Australia has produced a light chaser kit (see article this month). It features variable flash rate, auto reverse, auto invert, etc. It is a great companion to our popular 'Musical'. Cat K-3145

## TV CRO ADAPTOR

If you're like many people, the old B&W TV is sitting around doing nothing. And you've probably always wanted a CRO. Why not use the old TV? This simple kit from Electronics Australia turns your TV into an audio oscilloscope which you'll find very useful. The kit is complete with instructions. Compare our price with others!



**PUT YOUR OLD B&W TV TO WORK!**

**\$29.95**

Cat K-3060  
SEE EA MAY ISSUE

**AMATEURS: Don't miss our exciting new Yaesu contest!**  
Full details on page 96...

## MAJOR DICK SMITH RESELLERS

### ADVANCED ELECTRONICS

5a The Quadrant, Launceston, Tas. (317 075)

### AERO ELECTRONICS

123a Bathurst Street, Hobart, Tas. (348 232)

### AMATEUR'S PARADISE

121 Nerang Street, Southport, Qld. (322 644)

### A & M ELECTRONICS

78a High Street, Wodonga, Vic. (244 588)

### COASTAL ELECTRONICS

43 Vulcan Street, Moruya, NSW. (742 545)

### COFFS HARBOUR ELECTRONICS

Shop 3, C/H Plaza, Park Ave, Coffs Harbour. (525 684)

### CRYSTAL TV RENTALS PTY LTD

66 Crystal Street, Broken Hill, NSW. (6897)

### DECO ELECTRIC

Chr Magellan St & Brunner Hwy, Lismore, NSW. (214 137)

### ELECTRON 2000

181 Wharf Road, Newcastle, NSW. (262 644)

### ELECTROFIX

133 Malop Street, Geelong, Vic. (87 927)

### GOODWIN ELECTRONICS

123 Station Street, Blackheath, NSW. (878 379)

### HAWKESBURY ELECTRONIC CENTRE

111 George Street, Windsor, NSW. (773 411)

### HUNTS ELECTRONICS

18 Neil Street, Toowoomba, Qld. (326 944)

### HUTCHESONS COMMUNICATIONS CENTRE

5 Elizabeth Street, Mt Gambier, SA. (256 404)

### KELLER ELECTRONICS

218 Adelaide Street, Maryborough, Qld. (214 559)

### KINGSTON ELECTRONICS & RECORDS

Channel Court, Kingston, Tas. (236 802)

### KB ELECTRONICS & MARINE

361 Main Terrace, Geraldton, WA. (212 176)

### KENT ELECTRONICS

42 Stuart Highway, Darwin, NT. (814 749)

### LYREBIRD ELECTRONICS

50 Berry Street, Nowra, NSW. (25 525)

### MELLOR ENTERPRISES

Shop 2, Forrythe St, Wyalla Norris, SA. (454 764)

### M&W ELECTRONICS

48 McNamara Street, Orange, NSW. (626 491)

### NAMBOUR ELECTRONIC SHOP

Shop 4, Lowan House, Ann St, Nambour, Qld. (411 604)

### ODYSSEY ELECTRONICS

101 Main Street Bainsdale, Vic. (525 262)

### POWER N' SOUND

15 Franklin Street, Traralgon, Vic. (743 638)

### P.J. O'BRIEN ELECTRONICS

62 Wee Wee Street, Waggett, NSW. (243)

### PURELY ELECTRONICS

15 East St, Rockhampton, Qld. (21 058)

### SOUND COMPONENTS

78 Brisbane Street, Tamworth, NSW. (661 363)

### SUMMER ELECTRONICS

95 Mitchell Street, Bendigo, Vic. (431 977)

### STEVENS ELECTRONICS

42 Victoria Street, Mackay, Qld. (511 723)

### SILICON CHIP ELECTRONICS

Suite 3, 98 Bridge Street, Muswellbrook, NSW.

### TABLELAND RADIO SERVICE

2 Jack Street, Atherton, Qld. (512 017)

### TOMORROWS ELECTRONICS & HI FI

68 William Street, Gosford, NSW. (247 246)

### TRILOGY WHOLESALE ELECTRONICS

40 Frances Hwy, Fairy Meadow, NSW. (831 219)

### TROPICAL TV

249 Fulham Road, Vincent, Qld. (791 421)

### WAGGA WHOLESALE ELECTRONICS

82 Forsyth Street, Wagga, NSW 2650

### VIKING ELECTRONICS PTY LTD

3108 Gold Coast Hwy, Surfers Paradise, Qld. (388 280)

## SEEN IT YET?



**OVER 600 SOLD IN 6 WEEKS!**

**AUSTRALIA'S FASTEST SELLING COMPUTER \$695.00**

## NOW: TWO BASIC BOOKS



Cat. B-6103



Cat. B-6200

Yes - you asked for them, so here they are. Written in language anyone can understand, and they start at the basics (like how to turn it on!). Now there are two books, similar in content, but each written specifically for its own computer system. The first is for the superb Eady Sorcerer, the second is for the incredibly popular Dick Smith system 80 (but it also applies to the TRS-80). If you don't know what a computer is at all, then these books will help you understand!

## 16K UPGRADE KIT: SAVE \$30!

**SUITABLE FOR ALL COMPUTERS!**  
Incredible bargain from Dick: Save a massive \$30.50 on this pack of 8 4116 RAMs for upgrading your computer memory. YES! These are top quality 250ns types which are suitable for ALL microcomputers. We're buying so many of these that we get huge bulk buy discounts: & our savings are passed on to you. You reap the benefit. X-1186

**ALSO AVAILABLE:** Individual 250ns 4116 RAMs, also at a huge saving. Buy at Dick's low bulk prices and save!  
Cat Z-9310

## WORD PROCESSOR KEYS FOR SORCERER

11 special red keytops with word processor legends embossed on them, to replace the numeric keypad keys when using the Sorcerer as a word processor. Makes remembering the word processor functions so much easier!  
SET OF 11  
Cat X-3086

## COMPUTER MAINS FILTER

Don't lose that important program through mains spikes! This filter removes the gremlins that come down the power cord which cause programs to crash! A necessity for serious computer users! Cat M-9850



Listed below are re-sellers who stock a large range of our products. However, we cannot guarantee that they will have all items in stock or at the prices we advertise.

## THE DICK SMITH SOLDERER'S SPECIAL!



**SAVE OVER \$4!**  
STOP PRESS!  
Current stock sold out  
Next shipment due soon!

**ALL ITEMS AVAILABLE SEPARATELY**

- 1: 30W, 240 VOLT IRON**  
A budget iron for the hobbyist: beginner or expert. Ideal for all electronic assembly work. Cat T-1300. Normally \$9.75
- 2: 250g ROLL SOLDER**  
Economy pack of popular 1.25mm solder: enough to last you for many, many projects. Cat N-1619. Normally \$4.95 roll
- 3: SOLDERING STATION**  
Our incredibly popular 3-in-1 stand which holds PCB at any angle, iron and solder. Incredibly versatile: you'll wonder how you got along without it! Cat T-5700. Normally \$19.50

**ALL THREE FOR ONLY \$29.90**

## INFRA-RED BEAM

Great for hallways, doorways, (shop doors especially!) Easy installation, just connects to master alarm system. Complete with infra-red reflector.  
**\$89**



**Dear Customers...**  
Quite often, products we advertise are completely sold out within a few days. Or problems may be held up delivery of promised goods so they are not in the stores when the advert appears. Please don't blame the store manager or staff: they are powerless to solve this type of problem! What we are trying to say is that, if you are about to drive across town to pick up a particular product, why not give the store a ring first: just in case!  
**Dick Smith and Staff**

## YOU'VE SEEN IT ON TV?

The incredible Time Machine from Kambrook Turn on and off any domestic appliances when you want. Completely settable. Heaters, electric blankets, security lighting, pool filters, etc. etc. A real bargain!  
Cat X-1120



**\$24.50**


## NEW BOOKS

**TOP PROJECTS**  
Vol. 6 (from ETI). A huge selection of the best of ETI projects. 162 pages. Cat B-3649



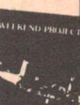**\$3.95**

**WEEKEND PROJECTS**  
For the radio amateur. A collection of quick and easy projects for amateurs from the pages of QST (ARRL). Cat B-2213



**\$4.50**

**COMPUTERS AND COMPUTING**  
Another handbook from ETI. 154 pages of articles, projects, equipment reviews etc. Good value!



**\$4.95**

Cat B-5095

## SPEAK N' SPELL IS BACK!

A lot of customers have missed out on the Speak & Spell talking game. A lot of people have been disappointed! Now they're back, but hurry, stocks are still not as good as we would like them to be! The Speak & Spell is a great aid to teaching your children letter construction and spelling. It uses a special microprocessor IC to synthesise speech electronically: no tape recordings!



## NOW THE SPEAK & SPELL IS EVEN BETTER!

Three new plug-in modules to extend the Speak & Spell's vocabulary and give it more interesting variations:  
**Vowel Power (X-1305)**  
**Super Stumper 1 (X-1301)**  
**Super Stumper 2 (X-1302)**

**\$79.50**  
each  
Cat X-1300

## PLAYMASTER GRAPHIC EQUALIZER

YES! Build your own graphic equalizer and save \$70.00! Easy to build with comprehensive step-by-step instruction manual (not just a reprint of the magazine article) With full connection details to suit your amplifier. It's easy to build: why not give it a go?



**\$99.50**  
Cat K-3500


## ANOTHER TWO NEW STORES SOON!

Yes! We're still growing, and serving you better. In the next two months we plan to open a store on Sydney's northern beaches, and then one in Melbourne's north eastern suburbs. Watch your local papers for opening dates:  
**BROOKVALE, NSW:** 531 Pittwater Rd. (Near Brookvale Oval)  
**SPRINGVALE, VIC:** Cnr Dandenong Rd and Springvale Road

# DICKSMITHELECTRONICS



399 Lonsdale Street  
Ph (03) 67 9834

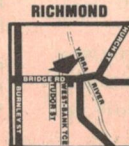

658 Bridge Road  
Ph (03) 428 1614



166 Logan Road  
Ph (07) 391 6233



842 Gympie Road  
Ph (07) 59 6255



96 Gladstone Street  
Ph (062) 80 4944



60 Wright Street  
Ph (08) 212 1962



414 William Street  
Ph (09) 328 6944

## BUYING BY MAIL?

ORDER VALUE:	P&P
\$5 (min) to \$9.99	\$1.00
\$10.00 to \$24.99	\$2.00
\$25.00 to \$49.99	\$3.00
\$50.00 to \$99.99	\$4.00
\$100 or more	\$5.50

NOTE: These charges apply to goods sent by post in Australia only. Large and bulky items cannot be sent by post.  
If you prefer, we will despatch your order by Comet Road Freight to anywhere in Australia for only \$6.00 - that's below what it costs us! Large and bulky items are normally sent by Comet unless you specify differently (eg by rail or air - you pay freight on delivery.)



## THE BARGAIN OF THE CENTURY!!!

**A DIRECT DRIVE TURNTABLE, INC. CARTRIDGE, UNDER \$200!!**

Impossible? No! Dick's incredible bulk-buying power now brings you this superb direct-drive turntable at a ridiculous price! It's so new, we haven't even taken a photo yet... stocks are due in by the time you read this. Check out the features: and the value!

- Heavy duty diecast platter with strobe
- Brushless DC servo motor with pitch control
- Semi-automatic operation
- Housed in magnificent wooden plinth with clear cover
- Complete with Shure magnetic cartridge.

AND THE PRICE:

**\$199<sup>00</sup>**

Cat. A-3078



## LEDS AND LADDERS GAME

**NEW, UPGRADED CIRCUIT AS IN EA THIS MONTH: AND IT'S \$1.00 CHEAPER THAN IT WAS IN 1976!!!!**

One of our most popular kits of the past was the intriguing 'LEDS AND LADDERS' game described by Electronics Australia back in 1976. Now EA have come up with a new version of this game which is easier to build, and just as much fun. Can you climb out of the well without being plummeted down again? And the best news of all: this kit is actually CHEAPER than it was in 1976. Yes, \$1.00 cheaper, despite 4 years of inflation!

WAS \$16.75  
IN 1976

NOW ONLY

**\$15<sup>75</sup>**

Cat K-3390



## EFFEMARISE YOUR CAR



Cat. A-6480

- FM STEREO
- AM
- STEREO CASSETTE

**\$149<sup>00</sup>**

FM has arrived. Can your car radio pick it up? Come up to the clean signals of FM with this superb Dick Smith car cassette radio featuring FM (as well as AM). Easy, do-it-yourself installation (instructions included). Recommended.

## WHAT ABOUT THE OTHER CAR?



Cat. A-5980

The second car hasn't got a radio? Here's a beauty: a powerful push button model at a low price - but not usual supermarket rubbish. Easy do-it-yourself installation.

**\$45<sup>00</sup>**

## QUALITY CO-AX SPEAKERS

While you're improving your car sound, why not install a set of co-axial speakers. They make a world of difference. A-7000



**\$39<sup>50</sup>**

## ULTRA MINI ULTRA HI-FI

- 30 WATT RATING!
- 90x90x100 mm!

They might be tiny, but they pack a real hi fidelity punch. Great for cars, vans, units, etc - anywhere that space is at a premium. And look at our low, low price:



Cat. A-2380

**\$35<sup>00</sup> pair!**

## CLEAN, CLEAR, COMMUNICATION!

That's what you get with the Philips FM320 UHF CB radio. Use it for business or pleasure, with 40 channels to choose from there's plenty of clear channel space available. Digital read-out with push-button scanning. A beauty!



Cat. D-1800

**\$330**

## UHF CB ANTENNA

Here's a roof-mounting antenna to suit the FM320. Quality low-loss construction, easy to fit.



Cat. D-4023

**\$9<sup>50</sup>**

## IC SOCKETS LEAP DOWN IN PRICE!

Why take chances with expensive IC's? Use sockets for best protection: now there's no excuse as our IC socket prices have taken a huge leap in price: DOWNWARDS! (All sockets are DIL type)

Pins	Cat No	Now:
8	P-4080	30c
14	P-4140	35c
16	P-4160	35c
18	P-4180	55c
24	P-4240	90c
40	P-4250	110c

## HANDS OFF! SPEAKER PHONE FOR HANDS-FREE TALKING

What a beauty! You've seen them on overseas TV shows: here they are in Australia. Push-button dialling with last-number memory; loud or soft volume control. Incredible value; use in place of conventional phone.



Cat. X-1177

**\$99<sup>00</sup>**

PLEASE NOTE: Although these three devices work perfectly with the Australian Telephone System, current regulations do not permit them to be used for this purpose.

## CALCUDIALLER


Great for busy executives, secretaries, - or even the home. Remembers 32 numbers, dials them for you at the push of a button. But its more than that: it's also a comprehensive memory calculator AND digital clock! All this for only



**\$179<sup>00</sup>**

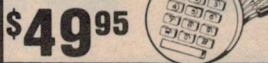
## PUSH BUTTON DIAL

Replace your rotary dial with this 20th century push-button type. Ideal for private and experimenter's systems. Simple 4 colour-coded wire installation, no soldering required. Great value! Cat X-1175



**\$49<sup>95</sup>**

## BUILD A KIT! UNIVERSAL AUDIO MIXER

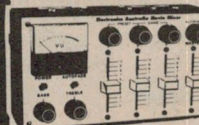

UNIVERSAL AUDIO MIXER

Here's a great kit for the audio buff: a 'universal' mixer designed to do those jobs the others can't - for example, sound on home movies! Professional quality with autotune, tone controls & VU meter. Cat K-3492

**\$49<sup>50</sup>**

## MORSE KEYS

For all hams or would-be-hams! This kit includes paddle & all components, inc. case (panel is not marked). Variable speed in correct proportion, inbuilt oscillator. Suits most transceivers. Cat K-3470



**\$39<sup>50</sup>**

## DIGITAL FREQ. METER

A 7 digit frequency meter you can build for under \$100! 40MHz bandwidth (you can change to 200MHz by adding one 95H90 IC: Z-5360 @ \$15.00)



**\$99<sup>50</sup>**

Cat K-3437

## 9kHz WHISTLE FILTER

Enjoy your AM listening without those annoying inter-station whistles. Easy to build kit adds on to almost any tuner, a must for the serious music lover. Cat K-3496




**\$19<sup>75</sup>**
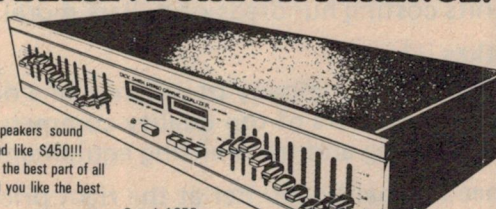
## YOU WON'T BELIEVE THE DIFFERENCE!

You won't believe the difference a Graphic Equalizer can make to your hi fi system without trying it for yourself!

They can make a set of \$50 speakers sound like \$150... or \$150 sound like \$450!!! The difference is staggering: and the best part of all is you choose the type of sound you like the best. Imagine: tailor-made sound! Just hook the graphic equalizer up to your amplifier, and adjust the slider controls. If you don't like the way a particular piece of music sounds, change it! This superb unit also features the latest LED level display: looks really impressive as it shows the level of your music.



Cat. A-1650


**\$169<sup>00</sup>**

WANT TO BUILD YOUR OWN? SEE THE PLAYMASTER GRAPHIC EQUALISER ON OPPOSITE PAGE!

## AND WHILE YOU'RE IMPROVING YOUR HI FI SYSTEM:
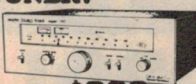
### A NEW TUNER?

Now that FM has really started, you deserve a good tuner. This one is ideal for any hi fi system: great on AM too!



**\$229<sup>00</sup>**

Cat. A-1350

### A NEW DOLBY™ DECK?

For really sparkling sound you need the advantages of Dolby™ noise reduction system. You also need to be able to use 'chrome' tapes. You can with this superb Dick Smith Dolby Deck. Front loading, easy to use and superb in quality.



**\$149<sup>00</sup>**

Cat. A-3500

## A CCTV SYSTEM FOR UNDER \$400!

- SECURITY
- SURVEILLANCE
- MONITORING
- HOME, OFFICE
- INDUSTRY

Think of the applications! Extremely simple to set up, light weight and portable (240V operated). Compare the price of this system with others: and you can still watch TV when it's not being used as a monitor!

TV Camera: Cat X-1195

12" TV Monitor: Cat X-1198

**BOTH FOR \$398**

(Items available separately: Camera \$299; TV \$99)




## DON'T THROW AWAY GOOD BATTERIES!!

Why waste money? Check out your batteries before throwing them out. They may still have plenty of life left in them. Check all standard sizes, plus fuses, globes too, ingenious!



Cat. Q-1525

# DICK SMITH ELECTRONICS

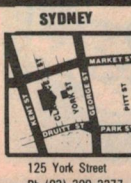


SYDNEY

125 York Street  
Ph (02) 290 3377



GORE HILL

162 Pacific Hwy  
Ph (02) 439 5311

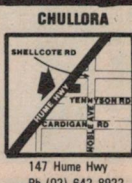

CHULLORA

147 Hume Hwy  
Ph (02) 842 8922



PARRAMATTA

30 Grose Street  
Ph (02) 683 1133



BLAKEHURST

613 Princess Hwy  
Ph (02) 546 7744



WOLLONGONG

263 Keira Street  
Ph (042) 28 3800



MAIL ORDER AND SERVICE CENTRES:  
Cor Lane Cove & Waterloo Rds, North Ryde NSW 2113  
(Monday to Friday, 9AM to 5PM only)  
SHOPS OPEN:  
9AM to 5.30PM  
MON. TO FRI.  
12 NOON SATURDAY.  
(Brisbane 1/2 hour earlier)





# A 6.5MHz Bandwidth Laboratory Oscilloscope for just \$199!

(\$183.26 Excluding Tax)

- ★ ALL NEW SOLID STATE
- ★ HIGH SENSITIVITY
- ★ COMPACT AND RELIABLE

Designed for Australia to outperform oscilloscopes costing much more! Solid state electronics throughout ensures extremely low drift and almost instant operation.

## SPECIFICATIONS:

### VERTICAL DEFLECTION

Sensitivity: 10mV/DIV

### HORIZONTAL DEFLECTION


Sensitivity: 500mV/DIV

### TIME BASE

Sweep frequency: 10Hz-100 kHz in 4 ranges. Synchronising: Internal & external

### POWER REQUIREMENTS

100/234V 50/60Hz APPROX. 10W.

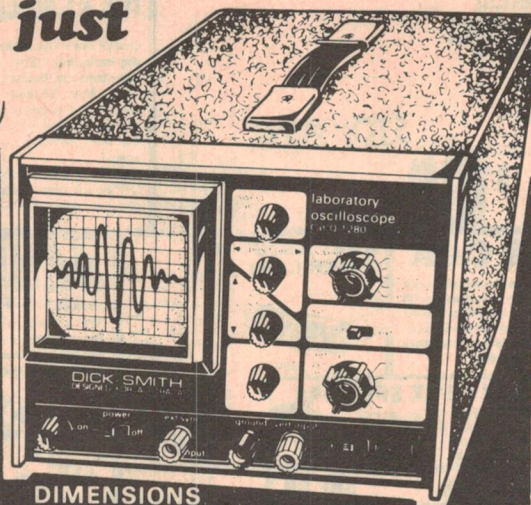


**DIMENSIONS**  
202Wx160Hx305D (mm)

**WEIGHT**  
APPROX. 3.8kg.

**COMPREHENSIVE USER'S MANUAL**  
supplied with each unit.
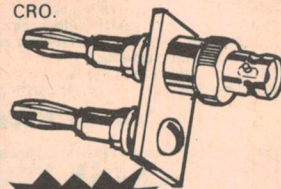
## Adaptor Plug

Converts the banana socket of the Q-1280 CRO to popular 'BNC' socket. Use a huge range of BNC accessories with your CRO.



**\$9.50**

Cat. Q-1281  
P&P \$1.00

## 100MHz Universal Probe

Make your job easier with this versatile high spec probe. Has 3 position slide switch in the lead & 1.5 metres of cable.

Complete with all accessories & comes in a deluxe plastic wallet. Use with the above adaptor (or with any CRO).



**\$34.50**

Cat. Q-1245 P&P \$3.00

★★★★★★★★★★★★

**FREIGHT ANYWHERE  
IN AUSTRALIA  
\$6.00!**

**BELOW COST!**

Cat. Q-1280

Here's what Electronics Australia magazine had to say: (June 1980)

'Our overall impression of the Q-1280 oscilloscope is that it represents good value for money'.

Ideal for the hobbyist who cannot afford an expensive CRO & yet get the performance he requires.

'The best part of all is the price - just \$199, including sales tax!'

# DON'T BE FOOLED!



Cat D-2892

A precision, 500MHz 6 digit DFM for less than \$500???

Sounds impossible — but this counter can out-perform many units costing hundreds of dollars more!

## Who makes it?

The Yaesu Musen company of Japan — one of the world's largest manufacturers of top quality commercial and amateur receiving and transmitting equipment.

If you need a quality counter at the right price, you need the Yaesu YC-500S. Ruggedly designed for years of trouble-free operation.

**High accuracy: one part per million!**

- \* Frequency range 10Hz to 500MHz
- \* Choice of high or low impedance
- \* 6 digit LED display
- \* Temperature range 0° to 40° C
- \* Dual power: 240V AC or 12V DC

PRICES CORRECT & STOCK AVAILABLE AT TIME OF GOING TO PRESS

**Amazing value at only \$475.00**  
(EVEN LESS WITHOUT S/TAX!)

# YAESU — THE PRO!

## DICK SMITH ELECTRONICS

**NSW** 125 York Street, SYDNEY Ph 290 3377  
147 Hume Highway, CHULLORA Ph 642 8922  
162 Pacific Highway, GORE HILL Ph 439 5311  
30 Grose Street, PARRAMATTA Ph 683 1133  
613 Princes Highway, BLAKEHURST Ph 546 7744  
263 Keira Street, WOLLONGONG Ph 28 3800

**VIC** 399 Lonsdale Street, MELBOURNE Ph 67 9834  
656 Bridge Road, RICHMOND Ph 428 1614  
166 Logan Road, BURANDA Ph 391 6233  
842 Gympie Road, CHERMSIDE Ph 59 6255  
**QLD** 96 Gladstone Street, Fyshwick Ph 80 4944  
**ACT** 60 Wright Street, ADELAIDE Ph 212 1962  
**SA** 414 William Street, PERTH Ph 328 6944  
**WA**



SHOPS OPEN 9AM to 5.30PM  
(Saturday: 9am till 12 noon)  
BRISBANE: Half hour earlier.  
ANY TERMS OFFERED ARE TO  
APPROVED APPLICANTS ONLY  
RE-SELLERS OF DICK SMITH  
PRODUCTS IN MOST AREAS  
OF AUSTRALIA.  
BELOW COST FREIGHT  
anywhere in Australia for \$6.00!!!



**MAIL ORDER CENTRE:** PO Box 321, NORTH RYDE NSW 2113. Ph 888 3200. PACK & POST EXTRA.



## Digital clock features huge display

Here's just the thing for the kitchen, workshop, garage or shack — anywhere in fact, you need a digital clock that just can't be missed!


**Barry Wilkinson**

ISN'T IT just what you've always wanted — a digital clock with a decent sized display? Seeing the time at a glance is convenient in many situations and that's just what this clock has been designed for. The display features three seven-segment digits for the 'minutes units', 'minutes tens' and 'hours units' plus a single column '1' for the 'hours tens' displays. Each segment in the individual displays is made up of a string of LEDs connected in series. Each vertical segment contains five individual LEDs, while each horizontal segment contains six. Overall height of the display is around 60 mm.

We used rectangular LEDs as they provided by far the best looking display compared to the more familiar round LEDs. Suitable rectangular LEDs are made by a number of manufacturers and are readily available through a variety of suppliers. A 'flashing colon' between the hours and minutes digits is provided to reassure you that the clock is going! However, as a binary divider clocking from the mains is used to drive the clock, a one-second output is unfortunately not available and so the next best output was chosen. This proved to be a division of 32 and thus, from 50 Hz, a pulse every 1.56 seconds is obtained and this is used to flash the colon.
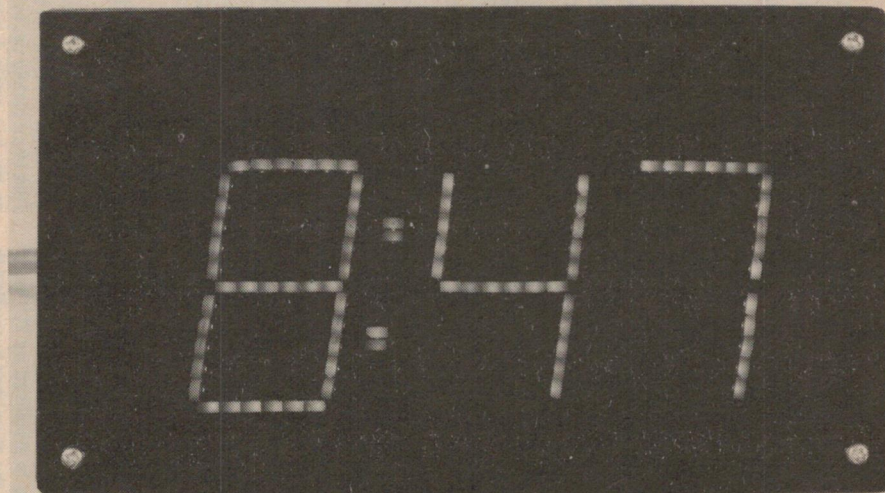
### Design

There are a number of interesting aspects to the design of this digital clock. For a start, conventional CMOS binary dividers have been used in preference to one of the special clock divider chips. The latter are very handy, no doubt about that, but they are incapable of driving a large sized display like the one used here. Firstly, the voltage drop across each segment of the




multi-LED display varies depending on the type and colour of LED used. Whilst we have used red LEDs, which have a voltage drop of around 1.6 V each, red or yellow LEDs may be used and these have around a 2.1 V drop each. The Philips rectangular LEDs type CQX10-2 are red but have a voltage drop of 2.1 V too while some of the new 'high efficiency' LEDs also exhibit a 2.1 V drop. This means that, for a horizontal segment in our display the maximum voltage drop may be as high as 12.6 V (six LEDs times 2.1 V). The clock chips available cannot readily cope with this but CMOS decoders can be arranged to do what we want.

You will notice from the circuit that the LED segments are driven by 4511 CMOS decoders which provide up to 25 mA per segment, with the actual current being determined by current limiting resistors. The current per segment in our circuit is limited to around

20 mA. However, the maximum voltage across CMOS is limited to 15 volts and a supply of around 18 volts was necessary to allow for the drop across the display segment plus the drop across the limiting resistor and the 1.5 V lost in the 4511 output circuit. To overcome this difficulty, we stabilised the negative supply rail for the CMOS to 12 volts and the negative side of all the display segments is taken to the *unregulated* negative supply. The zener action of the LEDs (i.e. there is no current flow below about 1.4 volts per LED) the outputs of the 4511s are never 'pulled' below their negative supply rail.

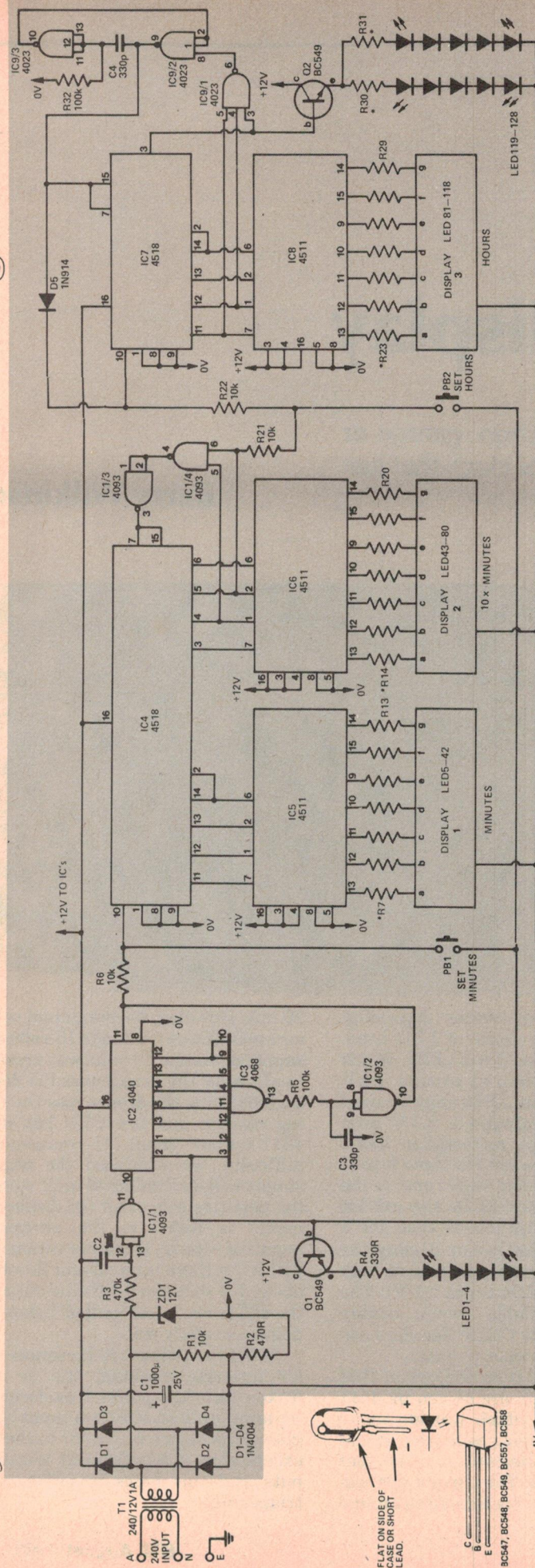To obtain a 'clean' 50 Hz square wave for accurate clocking, the ac input (taken from the power transformer) is 'squared-up' by a 4093 two-input NAND gate. This device is similar to the 4011 except that it has Schmitt trigger inputs and this helps to prevent false triggering. ▶





The power supply is simply a 12 V output transformer, full-wave rectified and filtered by C1. The IC supply is stabilised by ZD1 to 12 volts. For timing, the ac voltage is coupled to the input of IC1/1 via R3, with C2 providing some filtering to prevent false counting. The value of R3 protects IC1/1 against input damage as the ac voltage exceeds the supply rails of the ICs. IC1 is a 4093, which is a two-input NAND gate, similar to the 4011, except that it has Schmitt trigger inputs, and this helps to prevent false triggering with the output of IC1/1 being a clean 50 Hz square wave.

As the first digit is the minutes display, a division of 3000 is needed. For this IC2, 3 and IC1/2 are used. IC2 is a 4040 which is a 12-stage binary divider. The outputs of the 4th, 5th, 6th, 8th, 9th, 10th and 12th stages are decoded (when all are high) and the counter reset at that time to provide a division ratio of 3000 (binary 10111011000). This is detected by IC3 whose output goes low on that number.

After a short delay (about 30 us) due to R5/C3 the output of IC1/2 will go high, resetting IC2. This immediately causes the output of IC3 to go low but, again due to R5/C3, the output of IC1/2 will remain high for about 20 us, ensuring correct resetting and the clocking of the minutes counter.

An output of IC2 (pin 2) is used to drive the colon and to provide the clock for the fast set modes. Unfortunately, exactly one second is not available using a binary divider so we chose the 1.56 second (50/32) output.


The output of IC1/2 (a 20 us pulse once per minute) clocks IC4 which is a dual decade (10) counter. The first half is used as a ÷10 and its output is decoded by IC5 to give the minutes display. The second half is clocked by the output of the first (10 minutes) and is decoded by IC6 to display the tens of minutes. As time has yet to be decimalised (!), we have to reduce the second half from ÷10 to ÷6. This is done by IC1/4 which detects when the 2nd and 3rd

outputs are high (binary 0110) and resets it to zero.

The third output is used to clock the hours counter, IC7. This, like IC4, is a dual decade counter with the first half being decoded by IC8 and the second being clocked by the output of the first. As only a simple "1" is needed for the tens of hours (12 hour clock) no decoder is necessary, only a buffering transistor. IC9 is used to decode when IC7 reaches decimal 13 (0001 0011 binary) and this triggers a monostable formed by IC8/2,3. This is used to reset IC7 to zero hours, but, as there is no zero hour in the 12 hour system we need a reset to "1". This is done by the diode D5, which pulls pin 10 high for the duration of the reset pulse and allows it to fall back again — a few microseconds (delayed by stray capacitance) after the reset pulse, clocking it on to 1.

Fast setting is done simply by injecting, by the use of push buttons, the 1.5 second pulse directly into the minutes or hours counters.

## HOW IT WORKS ETI-564

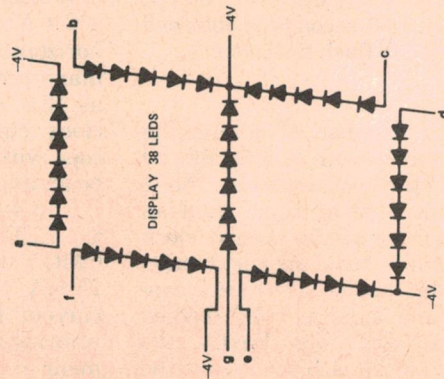

A total of 38 LEDs are used in each seven-segment display. Each of the vertical segments uses five LEDs, while the horizontal segments use six.



# PARTS LIST — ETI-564

## Resistors

- all 1/4W, 5%
- R1, R6, R21, R22 ..... 10k
- R2 ..... 470R
- R3 ..... 470k
- R4 ..... 330R
- R5, R32 ..... 100k
- R7 - R20 ..... see Table 1
- R23 - R31 ..... see Table 1

## Capacitors


- C1 ..... 1000u, 25 V pc electro
- C2 ..... 4n7 polyester
- C3, C4 ..... 330p ceramic

## Semiconductors

- IC1 ..... 4093
- IC2 ..... 4040
- IC3 ..... 4068
- IC5, 6, 8 ..... 4511
- IC9 ..... 4023
- Q1, Q2 ..... BC549
- D1-D4 ..... 1N4004
- D5 ..... 1N914
- ZD1 ..... 12 V, 400 mW zener

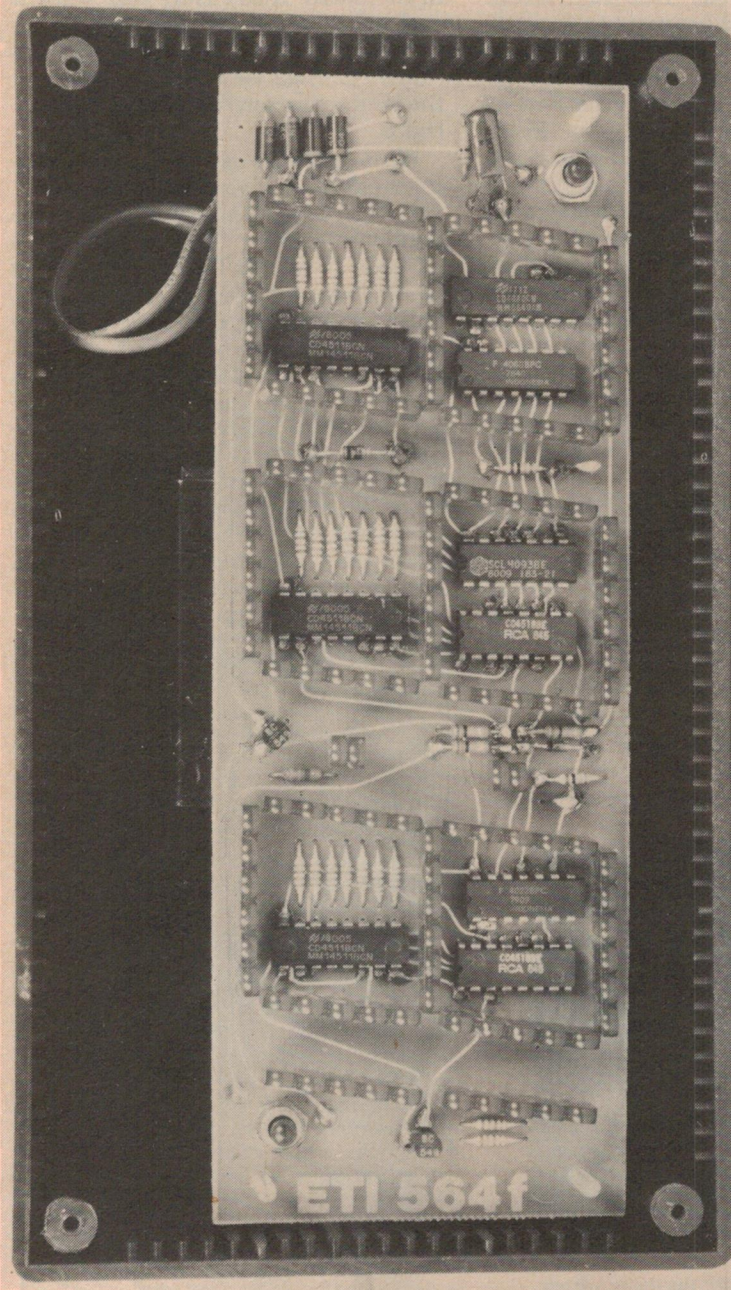
## Miscellaneous

Two push-button switches; transformer 240 V to 12 V at 1 A; sheet of polarised plastic; pc board ETI-564, case to suit; nuts; bolts etc.




The pc board patterns are on page 137

+12V AC INPUT  
FROM T1 SECONDARY

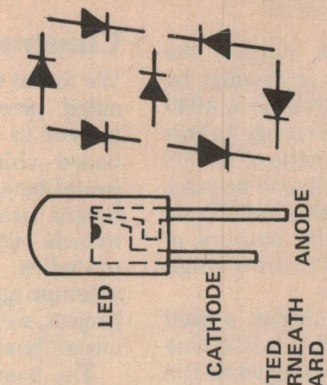

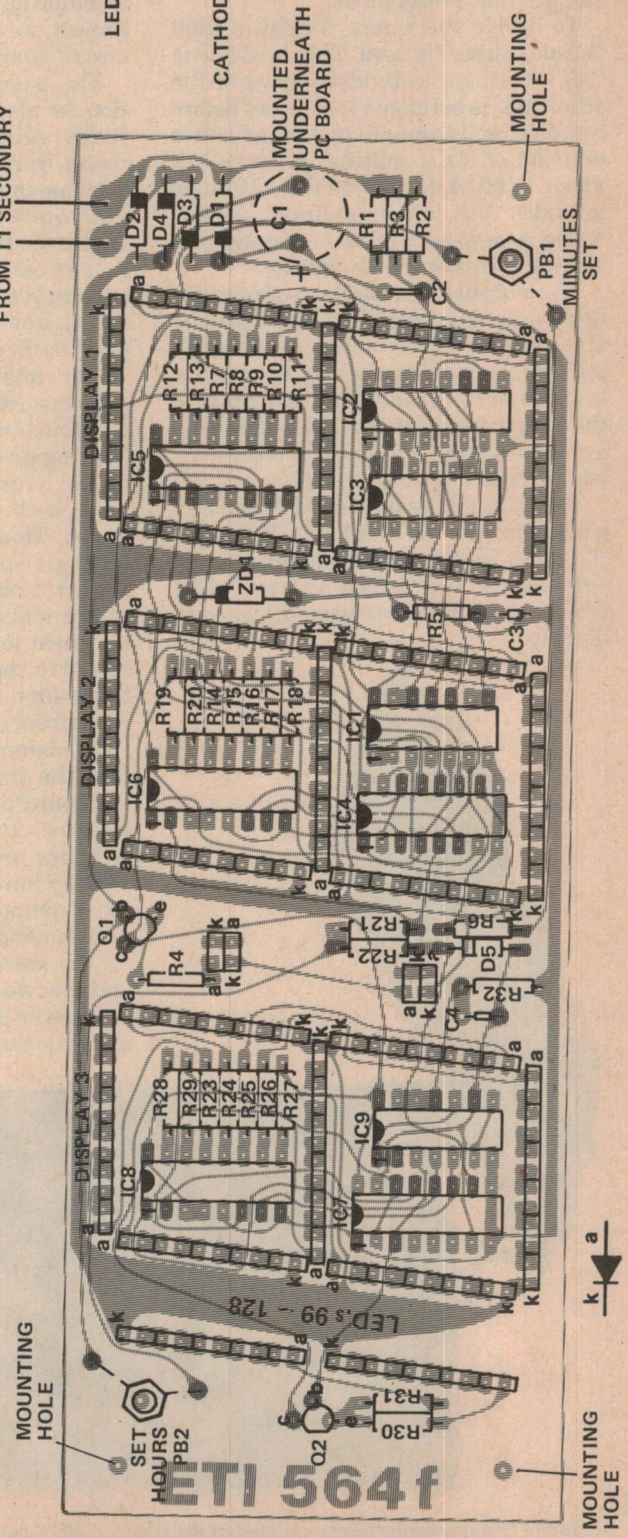Overlay diagram, looking from the components side. Note that this is a double-sided pc board.





# Project 564

To derive a 'minutes' output, the 50 Hz mains frequency is divided by 3000. To perform this division a 4040 12-stage binary counter is used. As this provides a total division ratio of 1:4096 ( $2^{12} = 4096$ ) the counter has to be reset once it reaches the 3000th count. To do this we detect when the outputs of stages 4, 5, 6, 8, 9, 10 and 12 are all high and provide a reset pulse.

To derive the 'hours' output, a dual decade counter is used. This is IC4. One half is used just to divide by 10 while the other half is arranged to be reset before completing its count to provide a further division of six, resulting in a total division of 60. A decoder on the  $\div 10$  stage provides the 'minutes units' display while a decoder on the  $\div 6$  stage provides the 'minutes tens' display.

The output from the tens-of-minutes divider (second half of IC4) is divided by six in the same way as just described to provide the 'hours units' output and this is followed by decade counter to provide the 'hours tens' output. These divisions are provided by IC7 which is reset to '1' when it reaches a count of '13'.

The hours units display is derived by a decoder from the first half of IC7 as for the other digits, but the 'hours tens' is only ever a '1', provided by a row of 12 LEDs. A buffer transistor drives this display.

## Construction

We found it necessary to use a double-sided printed circuit board for this project to avoid a large, cumbersome board which we feel sure you'd agree would be rather unattractive. To avoid ulcers, premature greying of the hair, muscle tremors and other assorted maladies that may develop from attempting to completely handwire this project, we suggest you obtain a printed circuit board as specified.

The board used in our prototype did not use plated-through holes as it is not really necessary. However, there are many fine tracks on the board and we recommend you use a soldering iron with quite a small tip. When soldering tracks on the top side of the board where a component lead connects to a corresponding track on the underside of the board, always ensure that you heat the joint sufficiently to get a good flow of solder and avoid a dry joint. From previous experience we find that many constructors tend to be afraid of overheating an IC or other components and do not provide enough heat for a good joint with the result that dry joints occur. These may work initially but often give problems some time after the project is completed and in use. Modern components will readily withstand excess heat for a short period so do not be afraid to apply the iron to the joint until the solder clearly 'wets' the area and flows freely.


To commence assembly, first check that the three mounting holes around the board perimeter and the two holes for the time setting push button switches are the correct diameter. It's awfully hard to drill the board after the other components are mounted.

Commence assembly by soldering in all the resistors, capacitors and diodes and the two transistors. You could leave the power supply's electrolytic capacitor, which mounts on the rear side of the

board, until all the other components are assembled if you wish. Take care with the orientation of the diodes, paying particular attention to the component overlay. Note that different value ballast resistors are required, according to the type (and thus the voltage drop) of LEDs chosen. Refer to Table 1 for the appropriate values.

As CMOS ICs are used, take care when inserting them that you handle the devices with due care. Carefully remove them from their packaging, taking care not to handle the pins — pick them up with your thumb and forefinger grasping the ends of the package, not the pins. Make sure you have them correctly oriented before inserting them in the board. Also ensure that you put each IC in its correct place and on the correct side of the board too! Sockets cannot be used for the ICs as many of the pins are soldered on both sides of the board.

With the LEDs used in our prototype (Siemens LD80-2 and Philips CQX10-2) we first taped the groups for each segment together. To do this, lay a group of five or six LEDs down, anodes or cathodes all facing the same way, butt their heads against a straight edge and run a strip of tape first over one side, then the other. This makes assembly much easier. Having done this, insert the LEDs into the board. The LEDs we used have a shoulder or 'step' in their leads a few millimetres from the base. We pushed the LEDs down onto the pc board until this shoulder stopped them going any further. The outside lead of each segment array was soldered and then each group checked for align-

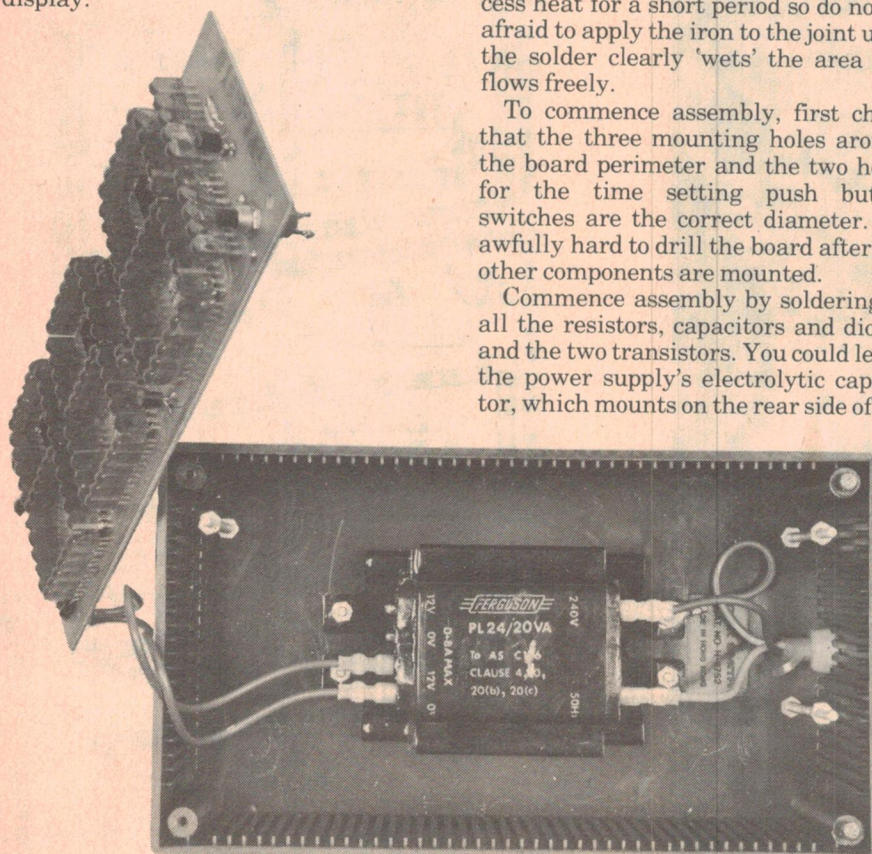

Inside the clock, showing how we mounted the transformer. Take care with the mains wiring.


## Setting the time

1. Switch on.
2. Press the minute button (the right hand one) until the minutes display is correct. To prevent multiple pulsing due to contact bounce, the button should be pressed and released when the colon is **OFF**.
3. Set the hours in a similar manner to the minutes (left hand button). If the minutes display is less than 40, again operate the button when the colon is **OFF**. If the minutes display is 40 or more, operate the button when the colon is **ON**.
4. An easy way to set the clock to the exact time is to first set it some 20 - 30 seconds fast by the push buttons, then compare it to a known time standard (you might use Telecom or a radio time signal for this). Turn off the power for the exact time difference and the clock will cease counting. The large filter capacitor will hold its charge long enough to store the last time, for up to a few minutes, until the power is turned back on. When the time signal equals the clock display, turn the clock on.



TABLE 1: Value of ballast resistor for the LEDs

RESISTOR	1.6V LEDs	2.1V LEDs
R7, 10, 13, 14, 17	180R	150R
R20, 23, 26, 29	180R	150R
R8, 9, 11, 12, 15, 16	270R	180R
R18, 19, 24, 25, 27, 28	270R	180R
R30, 31	270R	180R

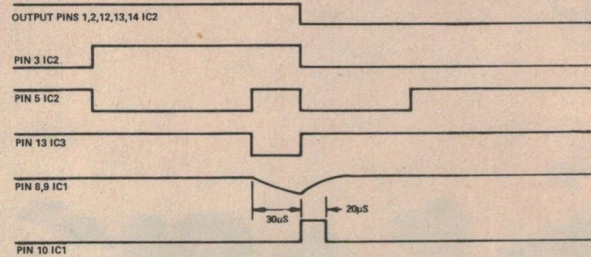

Waveforms around IC2 and IC3.

ment before soldering the other leads.

The rectangular LEDs specified measure 2.5 mm wide by 5 mm long. If you elect to use conventional round LEDs, the miniature 3 - 4 mm diameter types should be used. Many of the larger sized round LEDs will not fit this pc board as they have a shoulder around the base of the unit that measures 6 mm diameter, preventing the close packing possible with the other types.

Once you have the LEDs mounted and soldered in place, the two push button switches may be mounted. Short lengths of tinned copper wire are run from the switch lugs to the adjacent pads on the pc board.

At this stage, if you are satisfied everything has been mounted correctly, the board may be tested — *but give it another thorough check first!* In particular, look for solder 'bridges' between IC pins or across closely-spaced tracks as well as possible dry joints.

Simply apply 12 Vac to the two pins marked on the board overlay and see that the clock operates as it should. Try the 'hours set' and 'minutes set' buttons to see that they have the required effect. If all is not well, switch off and re-check the component placement and orientation, check for dry joints, etc.

We mounted our clock in a convenient plastic 'jiffy' box measuring 196 x 113 x 60 mm. The PL12/20VA 'low height' transformer is screwed to the rear of the box. The mains lead enters one side through a cable clamp. The pc board is mounted on three 58 mm long bolts with nuts positioned at a distance from the rear of the case determined by the

height of the transformer.

To drill the case, first mark the position of the holes for the pc board mounting bolts. Use the pc board as a template, laying it face down on the outside rear of the case. It's probably best to do this before loading the board. Failing that, measure the position of the holes and accurately mark them on the case. Use the photographs here as a general guide.

The board is not located centrally between the two long sides of the case. The upper edge of the board is located about 30 mm from the top side of the box. Ensure that the board does not foul the inside mounting flutes or pillars. If all is well, drill the holes and check that the board mounts properly.

Next, mark the position of the mounting bolts for the transformer, which is located under the board. Drill these and check that the transformer will mount without fouling anything. It should, there's plenty of space. The hole for the mains cable clamp should be located and drilled next.


The front panel may now be tackled. A large rectangular cutout is made in the front panel, just larger than the display. A piece of circularly polarized plastic is cut to the *outer dimensions* of the case, using the case as a template. As we chose red LEDs, we bought a piece of red plastic. For other colour LEDs, use grey. This plastic is available through Polaroid Australia. Lay the case face down on the piece of plastic and scribe around the edge. Remove the case and carefully cut around the scribe

mark. Next, place the panel over the piece of plastic and mark where the four panel mounting holes are located, then drill them. Two further holes have to be drilled in the plastic panel to permit access to the time setting push buttons. You're going to have to use a little judgement in locating these, but they don't have to be located all that accurately, just such that a match can be inserted to depress the buttons.


The plastic may now be glued carefully to the panel, or stuck on with double-sided sticky tape. As the clock dissipates some ten watts, ventilation is necessary. The easiest way to provide this is to stack some washers behind the front panel, on the mounting screws, such that the panel stands out from the case about 2 mm.

Now the clock may be finally assembled. Mount the mains transformer and secure the three pc board mounting bolts. Attach the mains cable and clamp then wire up the transformer primary and secondary. An earth lug should be mounted under one of the transformer mounting bolts and the mains cable earth soldered to it. A piece of cardboard, about 80 mm by 50 mm, should be stuck to the top of the transformer with a piece of double-sided tape. This is to insulate the rear of the pc board from the transformer case.

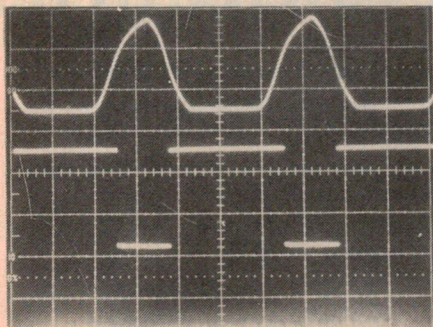
The nuts to locate the rear of the pc board should now be put on the mounting bolts and the pc board carefully secured in position. Make sure the board is held securely without it bending. Mount the front panel, plug in and you're ready to set the time!



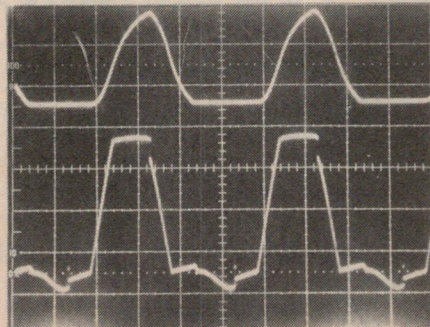Waveforms around IC1. At top is the waveform on the input, bottom shows the output.



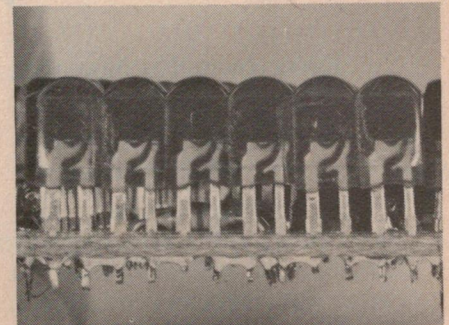Top waveform shows the input to IC1/1, lower trace shows the ac input to R3.



How the LEDs were mounted. The 'shoulders' on the leads are butted against the pc board.





# **AGC Insurances**

## **Why you should be covered by the**

You're covered by more than the terms of a policy with AGC.

You're covered by a name. A big name – AGC Insurances.

An insurance company that has a policy all its own. To give you almost more protection than you need. For less than you'd expect.

In car, home and contents, boat and trailer, and caravan, insurance.

### **Car cover that covers Australia.**

Buying car insurance from the place on the corner is fine.

But what happens when you have an accident far away?

That place on the corner is still back on the corner.

AGC covers Australia.

So wherever you go, you won't be left stranded.

And that's just one of the

beauties of insuring with AGC.

We also offer a Pay-by-the-Month plan.

And we have a no-claim bonus that reaches 60% in just four years and is cushioned so that all the bonus is not lost from just one claim.

### **Six household covers in one.**

It's hard enough getting a home together.

That's why AGC has now put 6 kinds of essential cover together.





## 'over-protective' insurance company.

In one simple policy.

It covers your home, your valuables and possessions. Also personal liability for accidents you or your family cause, covering you against court action and heavy damages.

It also covers death by accident.

And, if you employ domestic labour, workers' compensation. (Not available in Queensland.)

### **Cover for boats, trailers and caravans.**

You want to get away from it all on holiday. But you don't want to get away from your insurance company.

That's why you need AGC Insurances. Wherever you go, AGC is nearby, because we cover Australia.

### **Business protection.**

If you run your own business, AGC can tailor a policy to provide the

protection cover you need here, too.  
 Sydney: Phillip & Hunter Streets.  
 Melbourne: 31 Spring Street.  
 Brisbane: Tank Street & North Quay.  
 Adelaide: 10 Pulteney Street.  
 Perth: 250 Adelaide Terrace.  
 Hobart: 161 Collins Street,  
 and offices throughout Australia.

AGC (Insurances) Limited.  
 A division of Australian Guarantee Corporation Limited.



# ROD IRVING ELECTRONICS

425 HIGH STREET, NORTHCOTE 3070, MELBOURNE VICTORIA.

## SCOTCHCAL

### FRONT PANELS FOR ETI AND EA PROJECTS


ETI 452 Guitar Practice Amp	\$4.80
Series 4000 Any colour	\$12.50
Moving Coil Pre Amp	\$2.00
577 Power Supply	\$2.00
455 Loudspeaker Protector	\$2.70
Variable Power Supply	\$2.70
Linear Ohmmeter	\$2.50
Muscle Activity Meter Scale	\$1.40
ETI 576 Electromyogram	\$2.80
561 Metal Detector	\$2.50
EA Capacitance Meter	\$3.50
EA Flash Exposure Meter	\$4.25
EA Sound Triggered Flash	\$3.50
EA Slave Flash	\$1.20
EA Playmaster Graphic Analyser	\$8.50
EA Metal Detector 79md9	\$3.90
EA Pulse Generator	\$4.80
EA Square Wave Oscillator	\$2.50
EA RF Z Bridge	\$3.25
EA Thyristor Tester	\$2.40
EA Quartz Frequency Reference	\$2.70
EA Multi Monitor	\$1.90
EA Experimentors Supply	\$2.80
EA Quiz Master	\$3.70
EA Variable Wiper Delay	\$1.10
EA Playmate Stereo Amplifier	\$4.50

All front panels available from day of release of magazines. When ordering front panels, specify colour of lettering first, then colour of background.

### 10 TURN POTS

1/4" SHAFT. VALUES: 100, 500, 1K, 2K, 5K, 10K, 20K, 50K, 1M.

Inc tax \$6.50 ea.

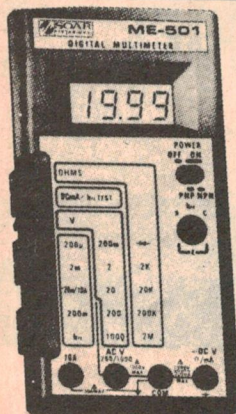

**Soar Model 501A**

**4 digit  
LARGE  
LCD  
DISPLAY**

Send for specs.

**\$69.00**

Add \$3 P&P and certified mail.

### INTERSIL LCD 3 1/2 DIGIT PANEL METER KITS

**INTERSIL ICL7106 \$32.50**

Build a working DPM in 1/2 hour with these complete evaluation kits.

Test these new parts for yourself with Intersil's low-cost prototyping kits, complete with A/D converter and LCD display (for the 7106) or LED display (for the 7107). Kits provide all materials including PC board, for a functioning panel meter. ICL7106EV (LCD)

## KITS & CIRCUIT BOARDS



(Kits of parts including quality fibreglass boards)

### ETI SERIES 4000 AMP

- Complete Kit, woodgrain sides \$179.00
- Rack Mounting..... \$185.00
- Quality front panel to suit above.....\$8.99
- ETI 470 kit of parts.....19.90
- ETI 480 kit of parts 100w (incl. bracket).....19.75
- ETI 470 PS kit of parts.....19.50 (includes relay, not transformer)
- Transformer to suit.....22.90
- ETI 471 pre-amp.....45.50
- ETI 585R ultra sonic RX.....15.95
- ETI 585T ultra sonic TX.....8.95
- EA 79 SF9 sound flash trigger.....15.00
- All parts available for DREAM computer project.
- P.C.B.'S (all quality fibreglass boards)
- ETI 574 disco strobe.....2.80
- ETI 549A metal detector.....2.75
- DREAM circuit board.....10.90

### Project Boards (Fibreglass)

ETI 043.....1.40	ETI 450B.....1.90	EA 78N6.....3.20
ETI 044.....1.30	ETI 480.....2.40	EA 78NG4.....2.50
ETI 047.....1.50	ETI 480PS.....2.40	EA 78UT4.....3.90
ETI 061.....1.40	ETI 481M.....2.00	EA 78T3.....4.20
ETI 062.....1.80	ETI 481PS.....3.50	EA 78C5.....3.90
ETI 063.....1.70	ETI 483.....2.20	ETI 470.....\$2.90
ETI 064.....1.70	ETI 484.....3.90	ETI 741.....\$9.90
ETI 065.....1.70	ETI 485.....2.90	ETI 472.....\$2.90
ETI 067.....1.80	ETI 486.....2.90	ETI 576.....\$4.90
ETI 068.....1.40	ETI 489A.....2.50	ETI 574.....\$2.80
ETI 071.....1.40	ETI 499.....1.90	ETI 473.....\$4.50
ETI 072.....1.80	ETI 528.....2.20	ETI 573.....\$2.90
ETI 081.....1.50	ETI 541.....2.20	ETI 577.....\$2.90
ETI 083.....1.80	ETI 547.....2.20	ETI 111B.....\$2.30
ETI 084.....1.70	ETI 581.....2.20	ETI 150S2 60 ETI
ETI 085.....1.30	ETI 583.....2.20	260.....\$1.90
ETI 130.....1.90	ETI 585R.....1.60	ETI 261.....\$1.90
ETI 134.....1.90	ETI 585T.....1.40	ETI 262.....\$1.80
ETI 135.....1.90	ETI 586.....2.30	ETI 263.....\$2.20
ETI 136.....1.80	ETI 603.....2.50	ETI 606.....\$2.90
ETI 137A.....2.90	ETI 604.....1.60	79se3.....\$3.90
ETI 137B.....2.90	ETI 635.....2.90	Dream 6800 10.90
ETI 139.....1.90	ETI 638A.....3.90	79sf10.....\$1.90
ETI 245.....1.60	ETI 708.....1.90	79md9.....\$2.60
ETI 417.....1.80	ETI 713.....3.90	79pg9.....\$2.90
ETI 445.....1.50	ETI 714.....1.90	79ps11.....\$2.90
ETI 446.....1.90	ETI 717.....2.90	79T111.....\$2.75
ETI 449.....1.50	EA 78A06.....2.90	79PC12.....\$2.20
ETI 450A.....1.90	EA 78TMB.....2.00	79EB12.....\$2.90

### Rod Irving Electronics Kits

Additional kits will be produced as new projects are available.

ETI 561 Metal Detector	\$29.90
ETI 041 continuity tester	3.90
ETI 043 heads and tails	3.50
ETI 044 2 tone door bell	4.10
ETI 046 500 second timer	3.90
ETI 047 simple morse, less key	3.90
ETI 048 buzz board	3.90
ETI 480 100w amp	19.50
ETI 063 electronic bongo	4.50
ETI 065 siren-less speaker	4.50
ETI 066 temp. alarm	3.90
ETI 068 LED dice	5.50
ETI 084 car alarm	10.00
ETI 470 60w amplifier	19.90
ETI 480 50w amplifier	16.00

(amplifier kits do not include heatsink)

Kits are complete with prime spec components and include assembly instructions, wire, solder, etc. All kit prices include sales tax, exempt prices on application.

## NEW PRODUCTS



**HEX KEY PAD \$24.90**

**63-key Keyboard \$55.00**

### RIE are now distributors for 3M Products, including SCOTCHCAL RANGE

8016	Blue on White Plastic	\$4.10
8018	Green on White Plastic	\$4.10
8011	Red on White Plastic	\$4.60
8012	Black on transparent Plastic	\$4.10
8013	Black on Yellow Plastic	\$4.10
8015	Black on White Plastic	\$4.10
8009	Light blue on aluminium	\$4.10
8001	Red on aluminium	\$4.10
8005	Black on aluminium	\$4.60
8007	Reversing film	\$3.75
NOTE: ALL ABOVE SHEETS 10" x 12"		
8500	Photosensitive Developer	\$4.40
3900	Clear Coating (Glossy Finish)	\$9.30
3930	Clear Coating (Matte Finish)	\$9.30
ML-3	Applicator block	\$3.90
ML-4	Developer pads	\$8.90
8002KA	Evaluation Kit	

### Attention Sorcerer and TRS 80 owners - MEMORY EXPANSION KITS AVAILABLE

We also offer full service on the popular computer projects and systems.

#### SPECIAL 4116 RAM OFFER

8 of prime spec 4116 IC's	\$79.00
16 of prime spec 4116 IC's	\$155.00
32 of prime spec 4116 IC's	\$276.00

#### STATIC RAM KIT 16K S-100

Kit form	\$239.00
Ass & tested	\$269.00



**Bankcard  
Mail Orders  
Welcome**

Please debit my Bankcard.

Bankcard No. ....

Expiry Date ..... 1980

Name.....

Signature.....

All prices current only until 7th September, 1980.

GENERAL ENQUIRIES (03) 489-8131, MAIL ORDER ENQUIRIES (03) 481-1436, RITRONICS WHOLESALE (03) 489- 7099.

HEAVIER ITEMS ADD ADDITIONAL POSTAGE, EXTRA HEAVY ITEMS SENT COMET FREIGHT ON.

PRICES SUBJECT TO CHANGE WITHOUT NOTICE. SEND 60c & SAE FOR FREE CATALOGUES.


MAIL ORDERS: PO BOX 235, NORTHCOTE, VICTORIA 3070. MINIMUM PACK and POST \$1.00



# Twin range tacho features LED bargraph display
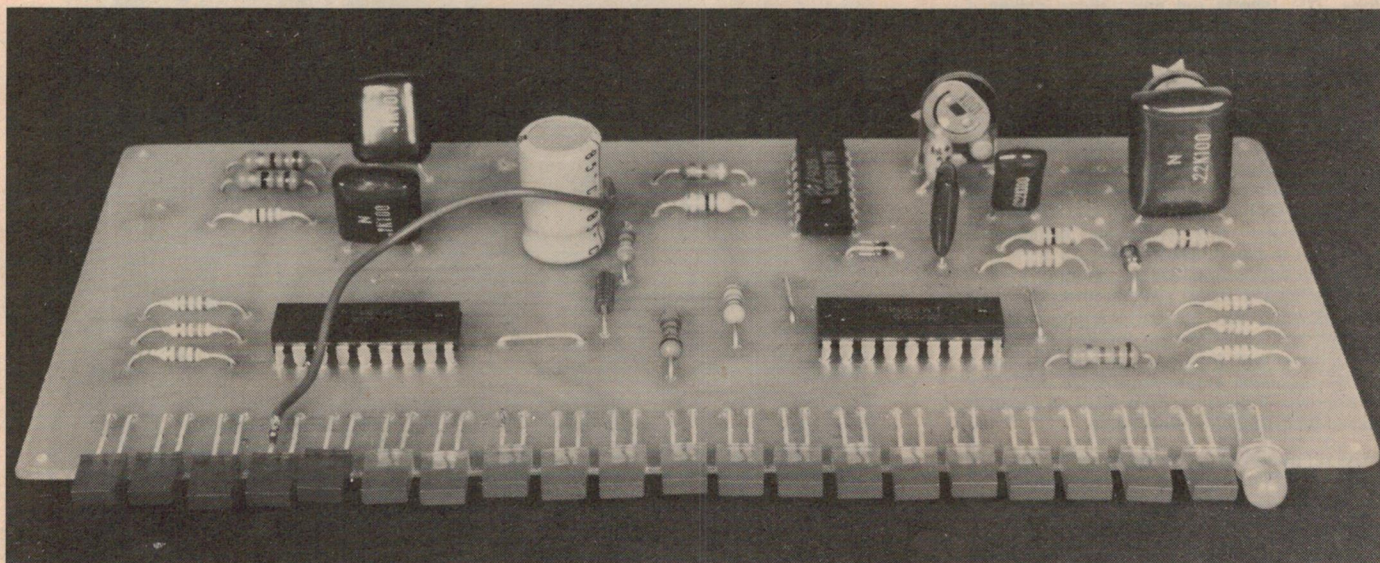
### Staff

Another in our series of projects to "update your car electronically", this tacho has many advantages over conventional types.



FEATURING a bargraph display of 20 rectangular LEDs arranged in a single line, plus one 'zero' LED, this tachometer incorporates an over-rev alarm feature and a high/low range switch. It displays engine speed in an analogue form (as with a conventional tacho) as an illuminated section of the row of LEDs, the length of the 'bar' being proportional to engine speed. This form of display indicates at a glance what your engine is doing, without the necessity of having to mentally interpret a numerical display as you would with a digital tacho — you don't have to take your eyes off the road, nor try to interpret rolling numerals during acceleration or deceleration.

This unit may be used with virtually any type of multi-cylinder petrol engine. The two speed ranges are cali-

brated by means of preset trimpots to give any full-scale speed range required. The lower range is of great value when setting or checking an engine's ignition and carburation for recommended tick-over speeds. The unit has been designed for use on 12 volt, positive or negative earthed electrical systems. It can be used with conventional (Kettering), capacitor-discharge (CDI) or transistor-assisted ignition systems — where a contact breaker system is used. Only three connections are required to install the unit — one to the positive supply, one to the negative supply and one to the contact breaker points. Protection circuitry has been included to prevent noise on the supply from causing problems and high voltage spikes from the points and coil circuit damaging the electronics.

### Design

The tacho has been designed around a frequency-to-voltage converter IC, the LM2917, driving two LM3914 LED bargraph driver chips. We covered various applications of the LM3914 in 'Lab Notes' in our March issue (page 61).

The LM3914s have an alarm facility which we have incorporated as a feature of the circuit. The triggering point for the alarm is arranged by taking a connection to an appropriate LED in the display. When the engine revs reach the point where this LED is turned on, the alarm will be triggered and the display will flash. An optional audible alarm can also be attached, the better to attract the driver's attention.

We chose a conventional (round) orange LED for the (zero) indicator in ▶



# Project 324

## HOW IT WORKS ETI-324

The circuit consists of a pulse conditioning circuit, R4 - R6, C5 and ZD1, a frequency-to-voltage converter, IC1, and two LED bar display drivers, IC2 and IC3. Each display driver is capable of driving 10 LEDs, giving a total of 20, plus one 'zero' LED. The number of LEDs illuminated is proportional to the output voltage from the frequency-to-voltage converter.


The ignition pulses from the contact breaker points in the vehicle have a repetition rate proportional to the RPM of the engine. The pulses from the points contain high voltage ringing components on the rising and falling edges of the waveform. These can be as high as 250 V at frequencies up to 10 kHz. These pulses would almost certainly damage the electronics so the input to IC1 is preceded by a pulse conditioning circuit. The 12 V zener diode, ZD1, shorts out any voltage spikes above 12 V while any remaining high frequency component is removed by R5 and C5.

The 'cleaned-up' rectangular waveform is fed to pin 1 of IC1. This is a voltage-to-frequency converter, providing an output voltage directly proportional to the frequency of the input waveform. The operating range of the IC is determined by the value of a capacitor connected to pin 2, either C1 or C2, and by a timing resistor and smoothing capacitor connected to pins 3 and 4. (RV1, C3 or RV2, C4). In our application, two preset ranges are provided by the range switch, SW1. The IC contains a constant current charging circuit for the timing capacitors (to ensure an output that is linear with frequency) and an internal voltage regulator. The network of R7 and D1 provides an input threshold level to guard against false triggering from noise.

The dc output of IC1 is fed to the inputs of the display drivers IC2 and IC3. These are LED 'bar' or 'dot' display drivers. Each IC can drive a chain of 10 LEDs and the number of LEDs illuminated is proportional to the output voltage from IC1. Put simply, the ICs act as LED voltmeters. The two ICs are 'cascaded' such that they perform as a single 20-LED voltmeter with a full-scale range of 2.4 volts. The resistors R13 to R18 are wired in series with the display LEDs to reduce the power dissipation in the two ICs. LED1 is permanently illuminated, providing a 'power on' indication and a 'zero' point for the display.

The LM3914 ICs incorporate an alarm facility. The triggering point for the alarm can be connected via a flying lead to any of the LEDs, selecting the trigger point. When the selected LED is turned on, the voltage on its cathode goes low, triggering the alarm. Capacitor C8 discharges, blanking the display. The LED is then turned off and the alarm resets. The capacitor is then re-charged, the display lights, and the alarm is triggered once again. The audible alarm will sound and display flash a few times a second. As soon as the RPM drops so the selected LED does not light, the function of the tachometer returns to normal.

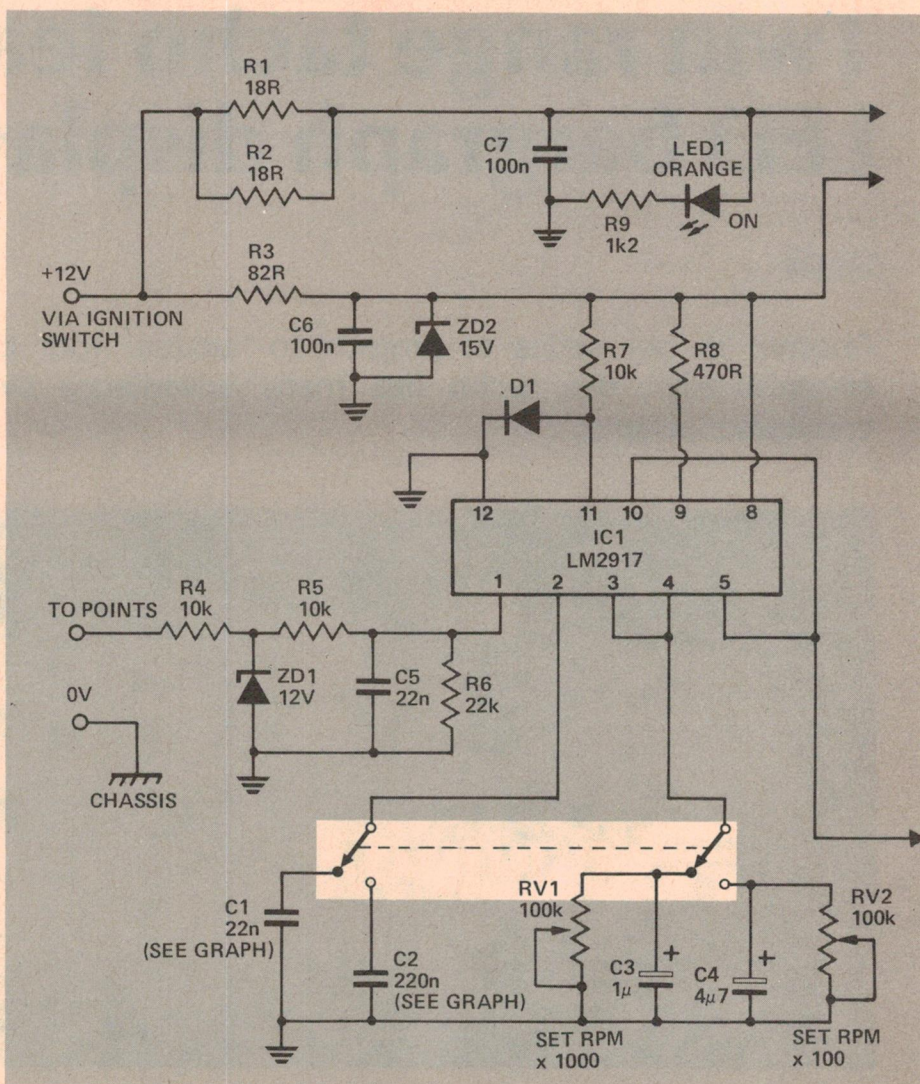Supply line filtering of noise pulses is achieved by R1 - R3, C6 and C7. Reverse polarity and overvoltage protection is provided by ZD2.



position one (it also indicates power on), rectangular green LEDs in positions 2 - 18 for the normal driving range, and rectangular red LEDs for the positions 19 - 21 giving a 'red line' area of 25% of full display. We thought this was the most convenient arrangement but you may vary it to suit your particular situation. All round LEDs may be used if you wish, but we found the rectangular LEDs provide a better looking display.

## Construction


Our printed circuit board is pretty well essential for constructing this project. The LEDs for the bargraph display are all mounted in a row down the front of the board. As you can see from the accompanying photographs, all the components with the exception of the

range switch and audible alarm are mounted on the pc board.

You will find construction easiest if you mount all the ICs, resistors and capacitors first, leaving the LEDs till last. Make sure you have the ICs correctly oriented, as well as the diodes and tantalum and electrolytic capacitors. Refer to the component diagrams and pc board overlay.

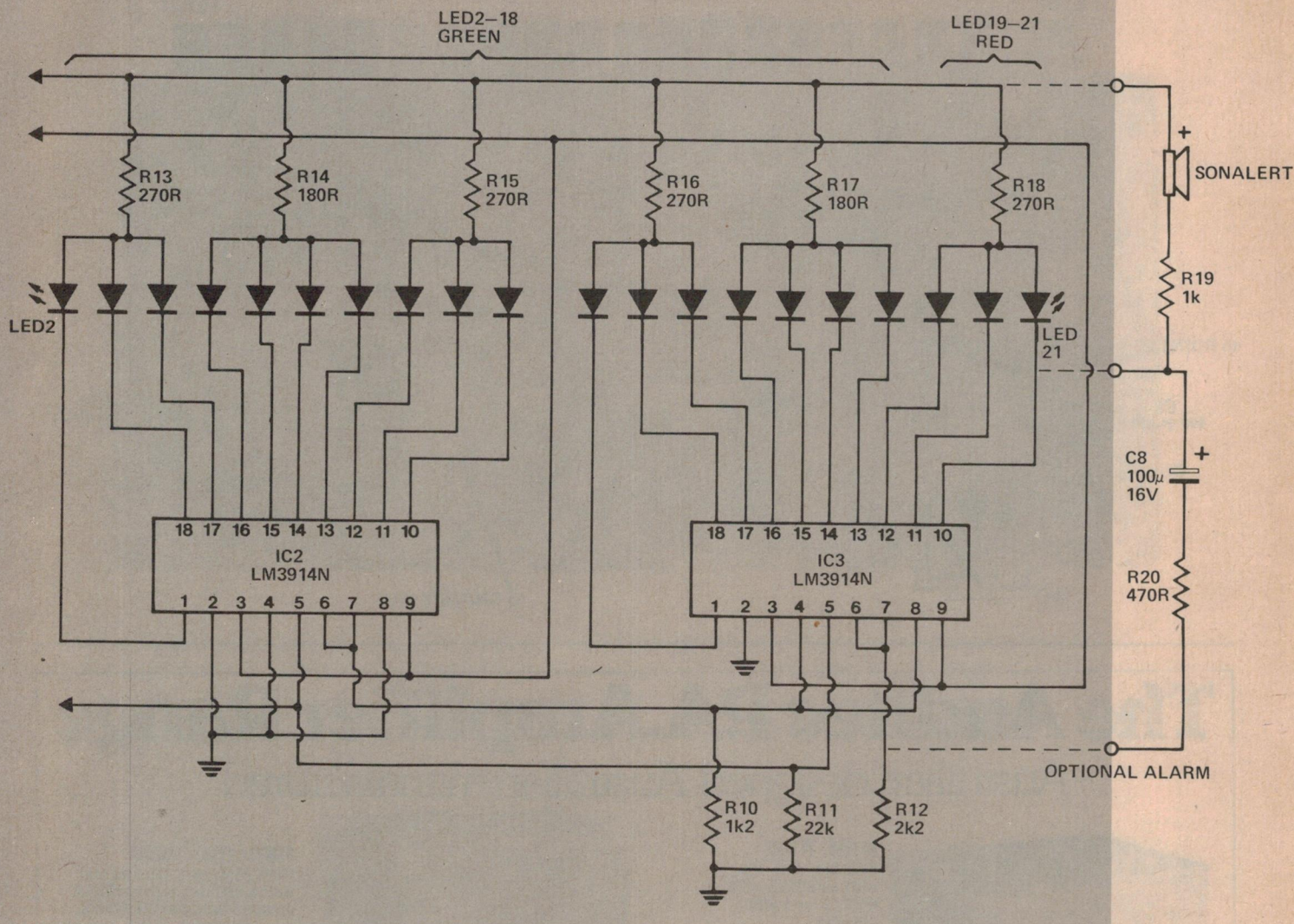When mounting the LEDs it is *most important* that they be placed in the board the right way around. One of the best ways of ensuring this is to first place them on the table or workbench in a row in front of you, with their leads all correctly oriented, just as they would be when mounted on the board. To ensure the leads are the right way around, refer to the overlay and the accompanying





The pc board patterns are on page 137

drawing showing LED orientation. Now comes the hard part — mounting the LEDs so that they're all level! Insert LED2 first and bend it such that it lies flat on the board with the base of the LED flush with the edge of the board — as shown in the pictures. Solder its leads. Bend it back upright and then insert LED3, carefully positioning it such that it is flush with LED2. Solder it in position. Proceed like this until all the LEDs are in place and then bend the whole row over, parallel to the board.

A flying lead is used to connect the alarm circuit to one of the LEDs. This determines when the display will flash and the audible alarm (if used) will sound. This lead should be left floating until the two speed ranges are set up. Attach flying leads for the

switch connections, supply and points connection.

### Mounting

Having built the unit, you'll have to consider where it is to be mounted. In fact, it may be prudent to think about this as your very first step! The tacho can be mounted such that the display is either horizontal or vertical, depending on your preference and available space in the dashboard. It is best mounted not too far from the driver's line of view so that it can be seen without his eyes leaving the road for too long, and to the side of his normal vision.

If you are brave enough, the unit can be mounted behind a slot cut in the vehicle's dash, as near to the speedometer as you can manage. Watch out that

there's enough space to accommodate the unit behind the panel before you cut, though!


If that doesn't appeal to you, the unit may be housed in a slim plastic case which is then mounted in a convenient position on the dashboard.

The range switch and audible alarm may be mounted in any convenient position, no matter where or how you mount the tacho itself, as lead length to these components is not at all critical.

Only three connections are made to the vehicle's electrical system: battery +12 V, contact breaker points and chassis (0 V). The battery connection should be taken after the ignition switch so the unit is only on when the ignition is on. The wire to the points will have to be taken through the fire wall to ►



# Project 324

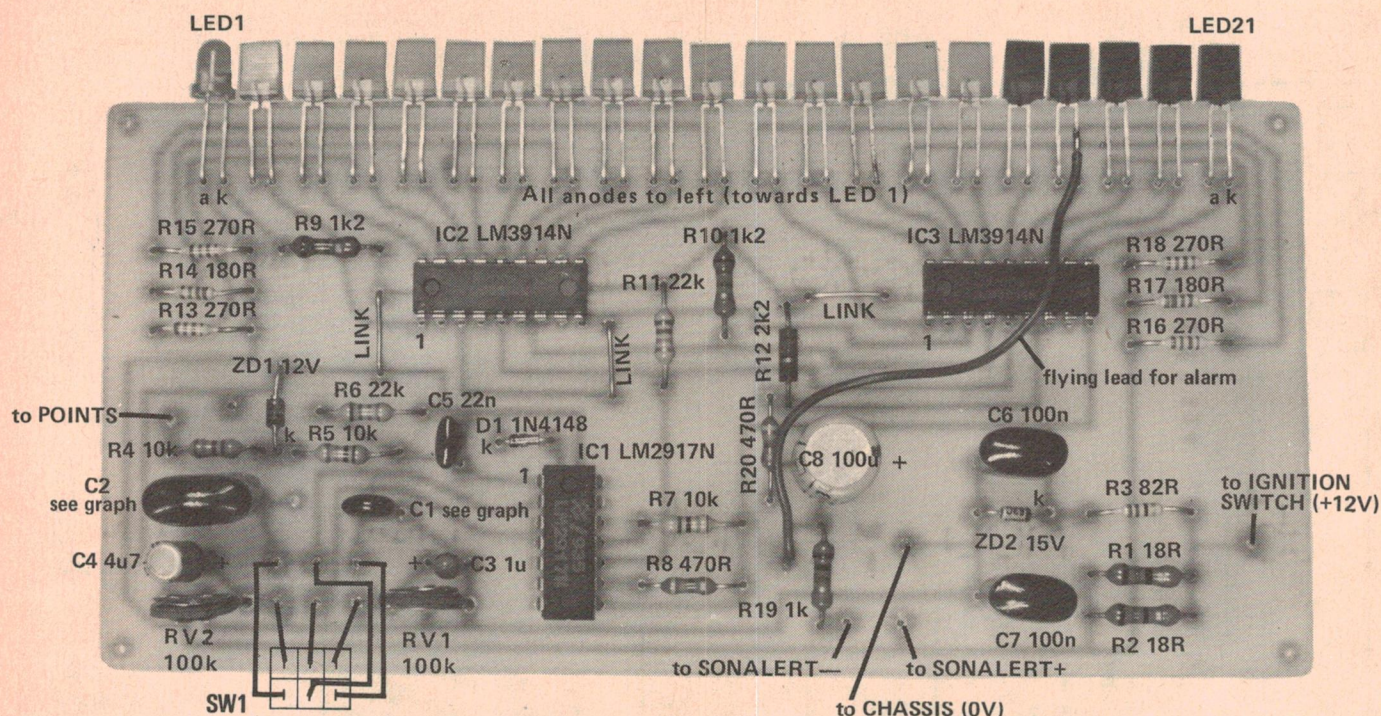

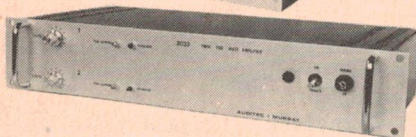
## The Auditec P.A. Amplifier Range


-Australian designed, Australian manufactured




**K104, K105**  
Free standing 120 watt amplifiers with either 2 or 4 input channels.



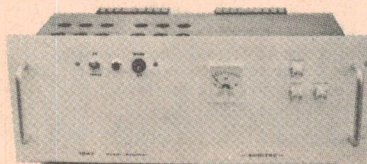**2033, 1034**  
Rack mounting 2 x 100 watt and 200 watt studio monitoring amplifiers. Where reference amplifier quality is required.



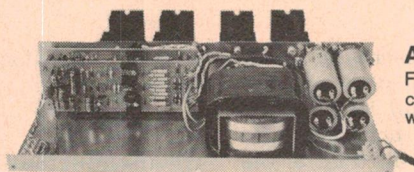**1009, 1027, 2009**  
Rack mounting 120 and 250 watt amplifiers with optional preamplifiers and VU meters.



**A-SERIES**  
For mounting into a case or cabinet. In 2 x 60 watt, 120 watt, 250 watt, 2 x 120 watt.

**There are three reasons why you should install an Auditec instead of an imported amplifier: QUALITY, RELIABILITY and PRICE.**

**AUDITEC MAJOR STOCKISTS.** VIC: ZEPHYR PRODUCTS, 70 Batesford Road, Chadstone, 3148. Phone (03) 568-2922. QLD: DELSOUND PTY. LTD., 1 Wickham Terrace, Brisbane, 4000. Phone (07) 229-6155. SA: NEIL MULLER PTY. LTD., 8 Arthur Street, Unley, 5061. Phone (08) 272-8011. WA: WILLIS ELECTRONICS, 993 Hay Street, Perth, 6000. Phone (092) 321-7609. ACT: MUSIQUE BOUTIQUE, 29-31 Colbee Court, Phillip, 2606. Phone (062) 81-5255. NT: DARWIN COMMUNICATIONS SYSTEMS, 2420 Scriven Street, Casuarina, 5792. Phone (089) 85-3184. FARMER & DAVIES ELECTRONICS, Weber Sales Bld., Fogarty Street, Alice Springs, 5750. Phone (011) 52-2967. TAS: UNITED AUDIO, 37 Elizabeth Street, Hobart, 7000. Phone (002) 34-4412.

**OTHER AGENTS.** NSW: RAY WALSH SOUND SYSTEMS, 448 Swift Street, Albury, 2640. Phone (060) 21-1502. W.M.R. ELECTRONICS, "Wirra-Willa", Belmont Road, Glenfield, 2167. Phone (02) 605-1203. DAWES SOUND SYSTEMS, 7 Mitchell's Pass, Blaxland, 2774. Phone (047) 39-4421. D.R. HI-FI & ELECTRONICS, 657 Pittwater Road, Dee Why, 2099. Phone (02) 982-7500. LANDERS MUSIC CENTRE PTY. LTD., 302 Summer Street, Orange, 2800. Phone (063) 62-6515. TRILOGY WHOLESALE ELECTRONICS, 40 Princes Highway, Fairy Meadow, 2519. Phone (042) 83-1219. R. ARCHER & SON, 107 Bungaree Road, Wentworthville, 2145. Phone (02) 631-4538. QLD: BUNDABERG HI-FI, 244 George Street, Bundaberg, 4670. Phone (071) 71-3176. KELLER ELECTRONICS, 94 Ellena Street, Maryborough, 4650. Phone (071) 21-4559.

For full details of these amplifiers phone, write or call at . . .

**AUDITEC**  
**AUSTRALIA PTY. LTD.**

10 Waitara Avenue, Waitara, NSW 2077  
(Adjacent to Pacific Highway)  
Phone (02) 48-4116



## PARTS LIST — ETI-324

## Resistors

all 1/4W, 5%

R1, R2	18R
R3	82R
R4, R5, R7	10k
R6, R11	22k
R8, R20	470R
R9, R10	1k2
R12	2k2
R13, 15, 16, 18	270R
R14, R17	180R
R19	1k

## Potentiometers

RV1, RV2	100k, miniature vert. mounting trimpots
----------	--------------------------------------------

## Capacitors

C1	22n greencap (see text)
C2	220n greencap (see text)
C3	1u, 16V electro. or tant.
C4	4u7, 16V electro
C5	22n greencap
C6, C7	100n greencap
C8	100u, 16V electro.

## Semiconductors

IC1	LM2917N
IC2, IC3	LM3914N
D1	1N914, 1N4148 or similar
ZD1	12 V, 400 mW zener
ZD2	15 V, 400 mW zener
LED1	Orange LED, round or rectangular
LEDs 2 - 18	Green LEDs, round or rectangular
LEDs 19 - 21	Red LEDs, round or rectangular

## Miscellaneous

SW1	DPDT miniature toggle switch, ETI-324 pc board, case (if required), Sonalert (if required).
-----	---------------------------------------------------------------------------------------------------


the points terminal on the outside of the distributor. The easiest way, rather than drilling a hole in the firewall, is to run the wire next to a wiring loom or the speedo cable, through an existing hole. Make sure the wire is well insulated and there is no possibility of the insulation being rubbed off, causing the points to be shorted to the chassis. The chassis connection can be made to any convenient point on the car body under the dash.

## Setting up

All that's left is to set the two RPM ranges by adjusting the two trimpots and to set the point when the alarm triggers.

The easiest way to set the RPM ranges is to borrow a friend's tacho. All good dwell angle test meters have an RPM range so it shouldn't be too hard to find a suitable unit.

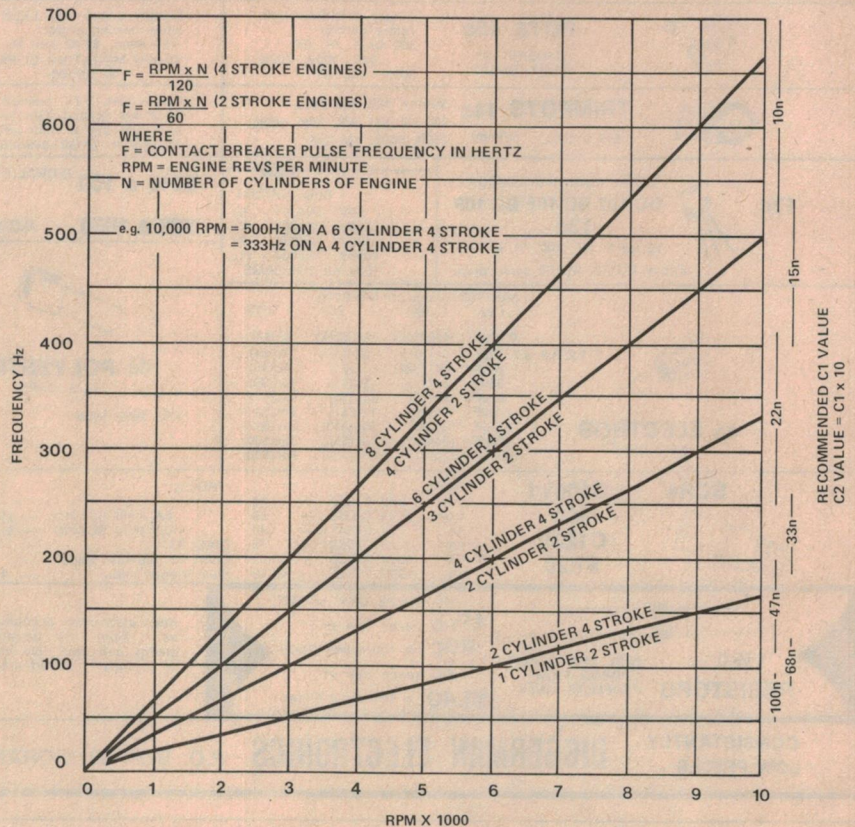Run the engine at half the required maximum RPM range and set RV1 so that the *eleventh* LED just lights. Full scale will then be *twice* the engine speed. This technique avoids having to run the engine at full RPM with no load which can be very damaging to your



## Setting C1 and C2

The values of the two timing capacitors, C1 and C2 are selected to give the desired full-scale RPM ranges.

The graph gives the value of C1 (right hand scale), for various RPM ranges (bottom scale). As the number of breaker point openings per revolution depends on the number of cylinders and whether it is a two-stroke or four-stroke engine, four lines are drawn on the graph for the eight common engine types.

Select the RPM range over which you want your tacho to operate (i.e: 10 000 RPM full scale) and draw a line upwards from the bottom scale until it intersects the line for your particular engine type. Then, draw a horizontal line across to the capacitor scale and read off the value of C1.

Since the low speed range is one-tenth the scale of the high range the value of C2 will be 10 times C1. i.e: if C1 is found to be 22n, C2 will be 220n.

If your engine is something out of the ordinary, like a five cylinder two stroke diesel (!... Ed), you will have to draw your own line on the graph! This is what the left hand frequency scale and the formulae are for. The formulae give the frequency of the points openings for all engines. Work them out for two RPM values, at say 2000 and 8000 RPM, plot the points on the graph, and draw a straight line between them. You can now work out the values of C1 and C2 as before.

If you have some entirely different use for the tacho, for example: on a piece of rotating machinery, if you know the maximum frequency, or speed, in revolutions per second draw a straight line across the graph from the frequency scale to the capacitor scale and read off the value of C1.

engine as well as you ears!

The low speed range can be set by adjusting RV2 until the 21st LED just lights at the desired engine RPM. As this is a low speed range there is no danger to the engine.

The alarm triggering point is set by soldering the flying lead directly onto a LED cathode lead. We set ours on the

lead of the second red LED. This can be made to trigger at say 6000 RPM by adjusting RV1 for a full range of 7000 RPM. If you don't need the alarm, the flying lead can be left off or the optional components left off the board completely.

That's it — project completed, calibrated and ready to roll!



Some of

# AUSTRALIA'S LOWEST COMPONENT PRICES

(Now Lower STILL!)

Note: Regular Prices not temporary specials — keep us in mind for that next order.



## POTS 40c

(LINEAR 1/4" ALUM. SHAFT

Linear potentiometers rotary carbon  
500 Ohm, 1K, 5K,  
50K, 100K, 250K,  
500K, 1M, 2M.

Quality Large red LEDs well diffused wide viewing angle.  
15c each, \$1.40 per 10, \$110/K.  
Quality MOUNTING CLIPS 3c ea. ea. \$2.70/100

## LEDs

\$12 a 100  
15c each



Best value  
No brag  
Just fact



## TRIMPOTS 14c

\$12 a 100 (10mm)

Values: 100, 500 Ohm,  
1K, 2K, 5K, 10K, 50K, 100K,  
250K, 500K, 1M, 2M

Trade/govt./S.T. exempt: welcome.  
Send for special lists (e.g. \$29 a 100 pots and \$99 a 1000 LEDs plus tax if applicable. Small quantities also.

TRADE ENTRANCE

13c



## METAL CAN TRANSISTOR BC 107 BC 108 BC 109 13c

10 for \$1.20 100 for \$11  
Epoxy BC178, BC109 same price

1 Amp. DIODES  
50V 1N4001 - 6c  
100V 1N4002 - 7c  
400V 1N4004 - 8c  
1000V 1N4007 - 11c  
10% off 100 SAME

## \$3 1/2 a 100 SIGNAL DIODE IN4148

\$29 a 1000 4c each



## 4c POLYESTER FILM CAPS

E12 10% 100V


.001 - 4c	.01 - 5c	.1 - 10c
.0012 - 5c	.012 - 6c	.12 - 11c
.0015 - 5c	.015 - 6c	.15 - 12c
.0018 - 5c	.018 - 6c	.18 - 14c
.0022 - 5c	.022 - 6c	.22 - 15c
.0027 - 5c	.027 - 6c	.27 - 16c
.0033 - 5c	.033 - 7c	.33 - 18c
.0039 - 5c	.039 - 7c	.39 - 19c
.0047 - 5c	.047 - 7c	.47 - 20c
.0056 - 5c	.056 - 8c	
.0068 - 5c	.068 - 8c	All values
.0082 - 5c	.082 - 9c	in uF
	10% off 100 same uF	

## 4c ELECTROS (UPRIGHT)



Cap.	16V	25V	50V
0.47uF	4c(\$3 1/2)	5c(\$3 3/4)	6c(\$4)
1, 2.2, 3.3, 4.7, 10uF	5c(\$3 1/2)	6c(\$3 3/4)	7c(\$4)
22uF	6c(\$3 3/4)	7c(\$4)	8c(\$5)
33uF	8c(\$4)	9c(\$5)	10c(\$6)
47uF	9c(\$5)	10c(\$6)	11c(\$7)
100uF	10c(\$6)	12c(\$7)	14c(\$11)
220uF	12c(\$8)	16c(\$10)	35c(\$17)
470uF	16c(\$12)	22c(\$16)	45c(\$30)
1000uF	22c(\$18)	30c(\$25)	75c(\$50)

## SCRs

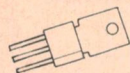

C106Y1  
40c  
C122E  
\$1.20


SCRs:  
0.8A 30V C103Y — 35  
0.8A 200V C103B — 60  
4A 30V C106Y1 — 40  
4A 400V C106D1 — 75  
8A 400V C122D — \$1.05  
8A 500V C122E — \$1.20

## TRIACS:


6A 400V SC141D — \$1.30  
10A 400V SC146D — \$1.50  
DIAC ST2 — 35  
Chart to identify leads  
Plus trigger info. — 10c

25 A 400V

SC260D TRIAC  
C37D SCR  
EA. \$2.50

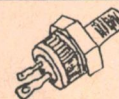

## 1 1/2c RESISTORS

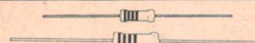

NEW TOP QUALITY  
CARBON FILM  
PERFECTS ONLY

5% E12,2.2 Ohm to 4M7  
1 1/2c each 1/4w or  
90c a 100 same Ohms  
2c each 1/2w or  
\$1.40 a 100 same Ohms

Keep electronics a hobby and not a luxury, compare our prices and buy from us. Same day turnaround service (unless swamped). All goods top quality and new. No minimum order. One P/P charge of 45c regardless of quantity. Advert current 3 months for late readers

CONSISTANTLY  
LOW PRICES

DIGGERMAN ELECTRONICS

P.O. BOX 33, CORAMBA, N.S.W. 2466



CONSISTANTLY  
BETTER SERVICE


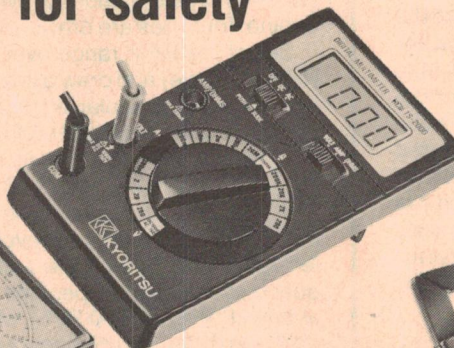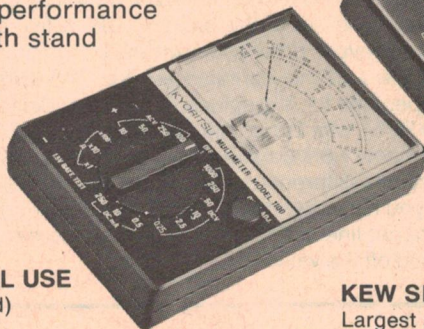
# KYORITSU TEST INSTRUMENTS — designed for safety

- No exposed metal parts
- Overload protection
- Threaded lead sockets
- Functional compact designs
- Proven field performance
- 3000V AC with stand
- Low battery consumption
- 13MM L.C.D. Display

ANALOGUE  
MULTIMETERS  
FOR INDUSTRIAL USE  
TS-1100 (illustrated)  
TS-1101




## TS-2000 (above)

- 300 VAC with stand
- 13 mm LCD display
- Low Battery Consumption
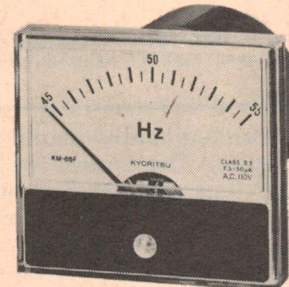
## KEW SNAP CLAMP METERS

Largest available range.  
From 100 MA F.S.D. through to  
1000 Amps.  
DC and digital models also.



Available from Electrical Wholesalers throughout Australia.

BELL

BELL INSTRUMENTS PTY. LIMITED

Garema Circuit, Kingsgrove 2208 NSW.  
PO Box 154. Tel (02) 750-6000.

74 Raglan Street, Preston 3072 Vic.  
Tel (03) 44-5021.



Facts from Fluke on low-cost DMM's

## Investigator at work: The shortcut to continuity checking.

At times like this, every minute matters. You could spend hours searching for a single short or open.

You could pack a continuity checker around with all your other gear. Or you could make your life a lot simpler and get the new 8024A Investigator from Fluke.

The Investigator is the only DMM on the market with nine functions including a built-in continuity/level detector. With  $3\frac{1}{2}$ -digit resolution, 0.1% basic accuracy and a full line of accessories, it's the most versatile handheld DMM you can buy.

When you need a quick, trouble-free continuity tester, the 8024A provides an instant visual (♦) and audible signal whenever a good connection is found. You can make



rapid-fire circuit checks while keeping both eyes on the test points and count on the Investigator's "beep" to pinpoint opens or shorts.

For active circuit checking, the level detector's "up" arrow indicates voltages above a threshold level, the "down" arrow shows signals below that point. And a pulse stretcher captures and displays signals that other analog or digital meters would never see.

Other Investigator exclusives you'll appreciate are the peak hold

feature — a short-term memory that captures and holds transient signals until you can turn back to read the display — and the ability of the 8024A to deliver direct temperature readings via any K-type thermocouple. Plus conductance lets you measure leakage and high resistance to 10,000 Megohms. All this performance at a low price.

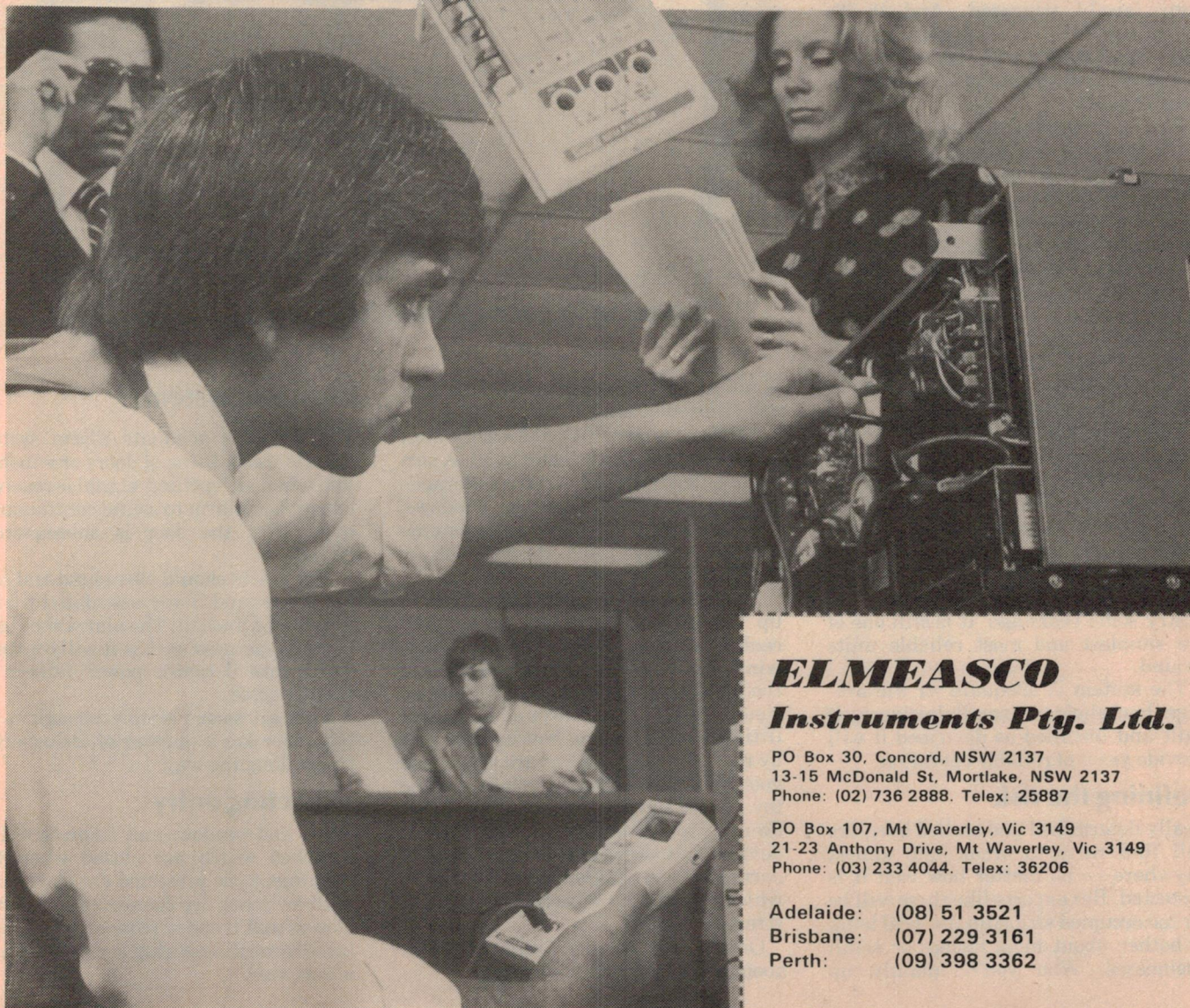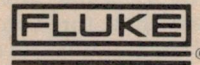For all the facts on the new 8024A Investigator, call or contact your Fluke stocking distributor, sales office or representative.



### **ELMEASCO** **Instruments Pty. Ltd.**

PO Box 30, Concord, NSW 2137  
13-15 McDonald St, Mortlake, NSW 2137  
Phone: (02) 736 2888. Telex: 25887

PO Box 107, Mt Waverley, Vic 3149  
21-23 Anthony Drive, Mt Waverley, Vic 3149  
Phone: (03) 233 4044. Telex: 36206

Adelaide: (08) 51 3521  
Brisbane: (07) 229 3161  
Perth: (09) 398 3362



# House alarm is simple to construct, features high reliability

Collyn Rivers

This project is adequate for the average household or small business and will provide years of reliable operation.

WHEN YOU HEAR a burglar alarm the chances are less than three in a hundred that the alarm has been set off by an intruder. The other 97 times it's been falsely triggered. And if it's raining at the time — especially if there's a thunderstorm — the chances of the alarm being genuine are very much smaller still.

This is a thoroughly unsatisfactory situation and one that has caused police and security organisations many headaches over the years.


False alarms are generally caused by poor installation techniques and/or the wrong choice of alarm control unit for the specific application. In the case of non-professional designs and installations the cause is usually lack of appreciation of the problems inherent in what at first seems to be a simple problem in electronic circuit design.

The alarm unit and installation techniques described in this article have been devised to combine total reliability with immunity to false triggering. Both were progressively developed over a number of years and the unit itself was produced commercially (by the author) in large quantities for the security industry some years ago. It is still one of the simplest and most reliable units around.

The system is adequate for the average household or small business. If built and installed as described it will provide years of reliable operation.
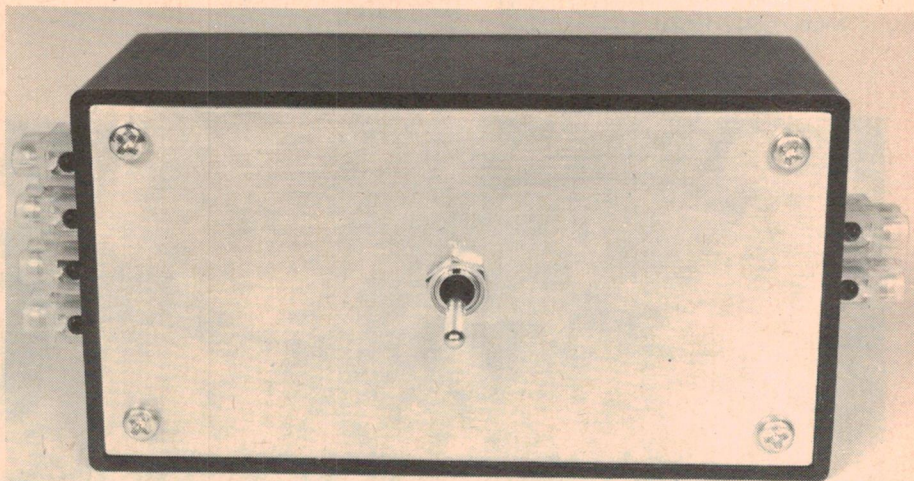
### Defining the risk

Really determined and skilled burglars will find ways to break into almost anywhere — no matter how well it is protected. But experts like these will be far too occupied sizing up the local bank to bother about most houses or small businesses. Who you're mainly up



against are 15-25 year olds with generally limited intelligence.

Figure 1 shows how and where most forced entries will be attempted. A surprising 29.2% of illegal entries are made through unlocked doors or windows. Most other entries are made by forcing with a jemmy. Only rarely is entry made by breaking glass.

So your first step should be to 'harden up' the house. Fit really strong concealed catches, especially to those windows which are not overlooked from the street or by neighbours' houses. You'll have to search around for decent fittings — the sliding bolt catches sold by most hardware stores are jokes. One good kick will tear them in half — if the toy screws supplied don't pull out first! So consider carefully how the various devices will withstand a jemmy used in earnest — and whether the woodwork to which they are attached will need strengthening.

Once this is done it's time to think about alarm protection.

### The basic system

The simplest adequate alarm system detects the opening of doors or windows and when an 'opening' signal is received causes the alarm to sound continuously even after the door is subsequently closed.

The alarm should also sound and continue to sound if any associated wiring is detected and cut. The alarm should be battery operated so that it will continue to operate if mains power fails or is disconnected.

This all seems simple enough to do but there are a number of unsuspected traps along the way.

### Detecting entry

Doors and windows may be protected by switches which are closed when the openings to be protected are closed. All such switches are connected in a series loop so that if one or more are opened, or interconnecting wiring is cut, the alarm is actuated.



# simple house alarm

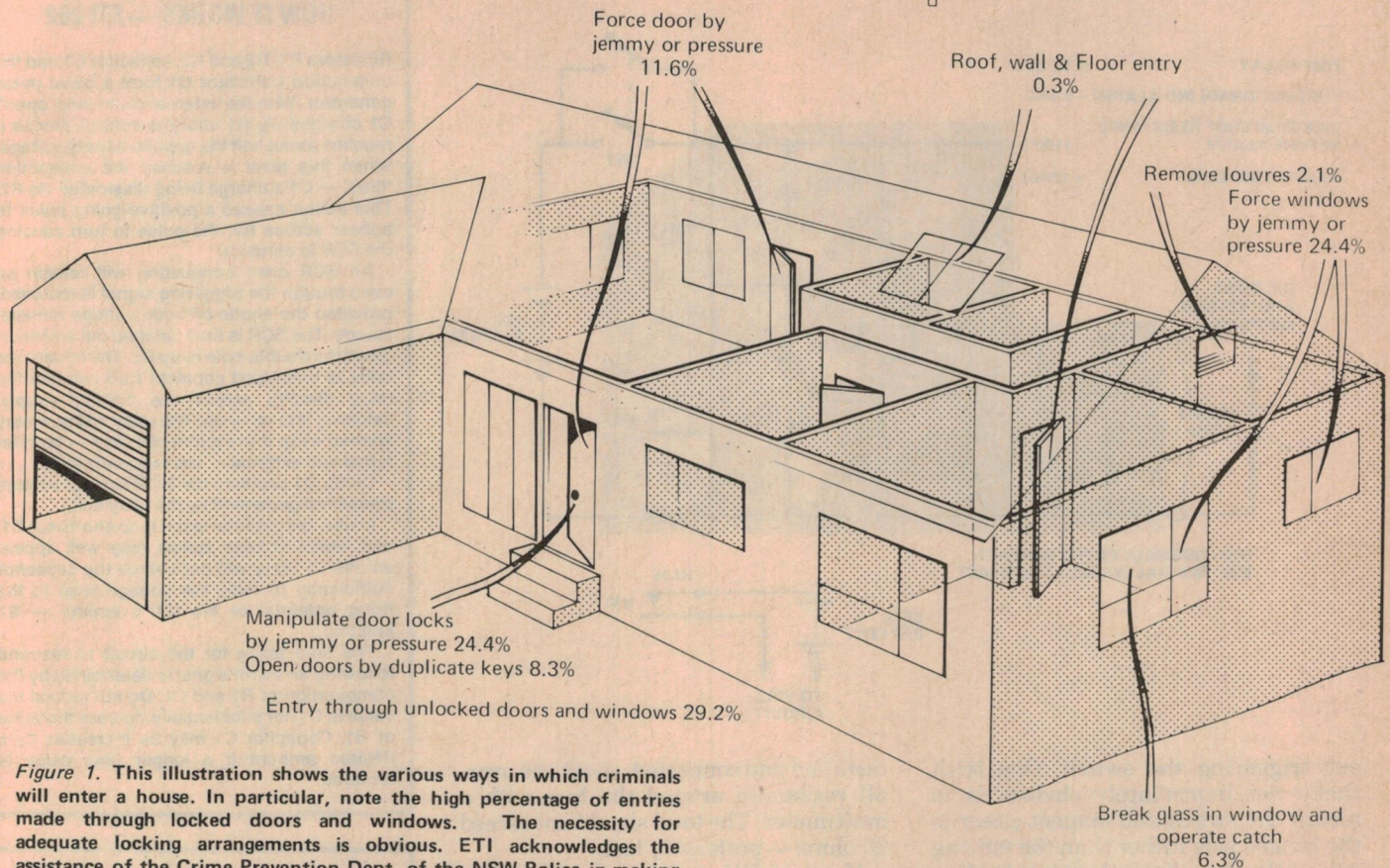


Figure 1. This illustration shows the various ways in which criminals will enter a house. In particular, note the high percentage of entries made through locked doors and windows. The necessity for adequate locking arrangements is obvious. ETI acknowledges the assistance of the Crime Prevention Dept. of the NSW Police in making these statistics available.

Many of the windows to be protected may remain closed for months — sometimes years — so the switches chosen must be absolutely reliable and resistant to corrosion. Most switches are designed so that the contacts are automatically cleaned every time the switch is operated — but this doesn't help much if the switch is actuated only once in ten years!

Another essential requirement is that the door or window must be able to open at least 20 mm before the switch is actuated. This will allow for movement caused by swelling in wet weather and rattling during storms.

The ideal device for this purpose is the magnetic reed switch. This consists of a pair of ferro-magnetic reeds and contacts, hermetically sealed in a small glass tube, and held closed by a magnet a few millimetres away. The contacts open when the magnet is moved away from them.


Commercial installers use these switches extensively but they generally keep them packaged in rectangular plastic mouldings. A neater, but more time-consuming method, is to recess them into the architrave surrounding

the opening. Whichever type is used the magnet should always be attached to the moving part of the door or window.

The reed switches *must* be designed specifically for security and similar applications — standard reed switches may not necessarily be suitable as some tend to remain closed when the magnet is removed if they've been held closed for any length of time. To be on the safe side, buy your switches from a security equipment supplier — you'll find addresses in the Yellow Pages.

The best magnets are ferritic-ceramic bar types — they're made by many companies and should not be hard to locate. They're usually round or square and sections 25 mm or so long will be fine. These will pull in the switch at a distance of 10-12 mm and will hold it closed at 15-20 mm.

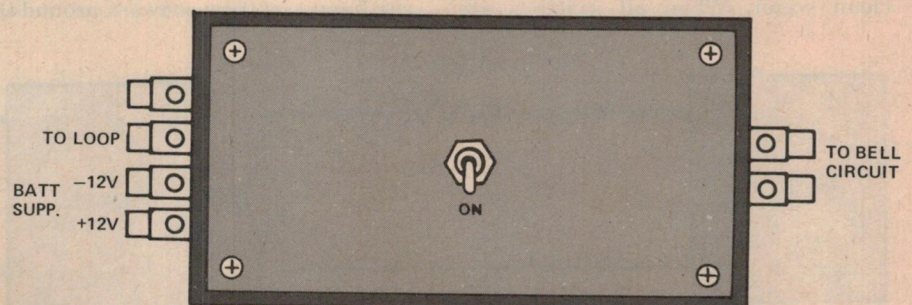Choose suitable locations and install switches and magnets as shown in the accompanying picture. Before making the final choice of position make sure that the door can open 20-30 mm with-




External connections to the unit are made via the two plastic screw-terminal blocks.


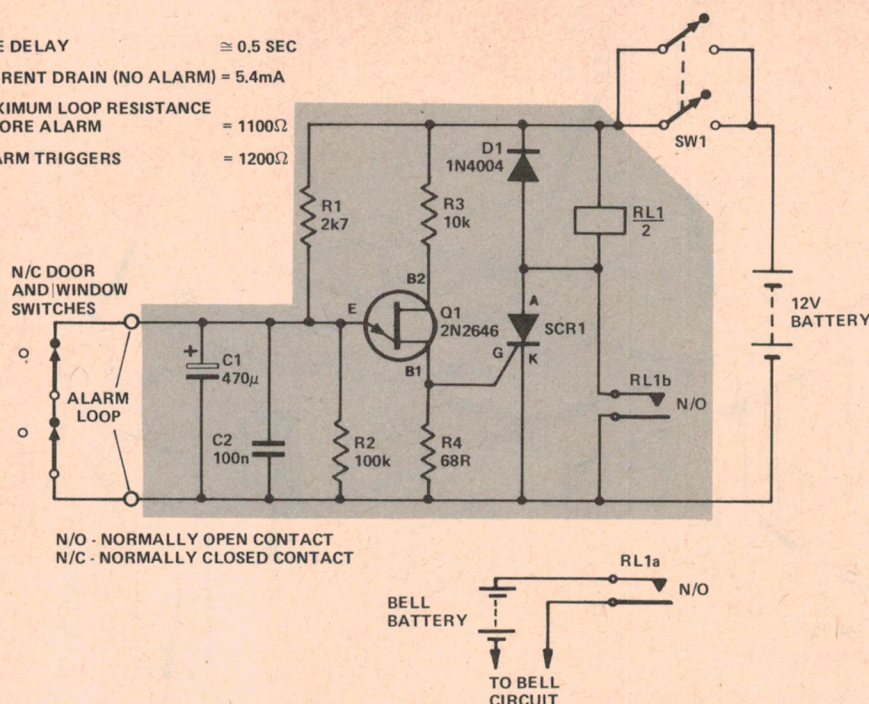
# Project 262

TIME DELAY  $\approx 0.5$  SEC  
 CURRENT DRAIN (NO ALARM) = 5.4mA  
 MAXIMUM LOOP RESISTANCE BEFORE ALARM = 1100 $\Omega$   
 ALARM TRIGGERS = 1200 $\Omega$



out triggering the switch. One trick that's not immediately obvious is to mount the switch and magnet closer to the hinged side rather than the moving side of the door. Keep the wires leading to and from the switches as far apart as possible. Leave a small amount of slack in the wiring so that building movements will not stress the wiring or connections.

It is worthwhile protecting one or two internal doors — particularly if you have one leading from a garage or carport into the house — but don't overdo the number of protected entry points. Every additional switch increases the probability of false alarms.

The switches should be connected in series using multi-strand wire (14/0076 is about right). Don't use single strand wire — it's more prone to failure if moved. Solder the wires to the switches using *non-corrosive* solder and clean off any residual flux with detergent and clean water. When all switches are

installed and connected, check the overall resistance around the loop with a multimeter. The total should not exceed 20 ohms — preferably less.

If all is OK, paint over the solder points and any bare wire with bituminous paint — or smear well with Vaseline. This may seem technical overkill but it's surprising what pollution can do to wire left bare for several years.

## The unit itself

The alarm unit should ideally be battery powered and draw little current. It should be capable of accommodating *some* resistance in the external signal loop but must *not* accept more than two hundred ohms before triggering. And that's where so many amateur and magazine-designed alarms go wrong, for in the quest for low current consumption designers plump for a high impedance input. Figure 2 shows what can happen if the woodwork around the

## HOW IT WORKS — ETI 262

Resistors R1, R2 and R3, capacitor C1 and the unijunction transistor Q1 form a basic pulse generator. With the external alarm loop 'open', C1 charges via R1 until the voltage across it reaches about half the applied battery voltage. When this level is reached the unijunction 'fires' — C1's charge being dissipated via R2. This action causes a positive-going pulse to appear across R2, the pulse in turn causing the SCR to conduct.

An SCR once conducting will remain so even though the triggering signal is removed, provided the anode-cathode voltage remains steady. The SCR is thus 'latched on' and energises the double-pole relay RL. The instant the relay is energised contacts RLb connect the relay directly across the battery supply, 'latching' the relay on. The relay will now stay latched even if the entire circuitry — both internal and external — subsequently fails.

Diode D1 protects the SCR against voltage transients generated by the relay coil.

In use, the external alarm loop shorts out C1, and whilst voltage spikes may well appear across C1, they will not charge the capacitor sufficiently to raise the voltage level to the firing potential of the UJT's emitter — B1 junction.

The time taken for the circuit to respond following an alarm signal is determined by the combination of R1 and C1. Do not *reduce* the value of C1 nor substantially *increase* the value of R1. Capacitor C1 may be increased by a desired amount if a longer time delay is required.

## PARTS LIST — ETI-262

**Resistors** all 1/4W, 5%  
 R1 ..... 2k7  
 R2 ..... 100k  
 R3 ..... 10k  
 R4 ..... 68R

**Capacitors**  
 C1 ..... 470u16 V electro  
 C2 ..... 100n greencap

**Semiconductors**  
 Q1 ..... 2N2646 UJT  
 SCR1 ..... C106D SCR  
 D1 ..... 1N4004 or similar

**Miscellaneous**  
 RL1 — cradle relay, 12 V coil with two change-over contacts (Pye, type 265/12/G2V); SW1 — DPST toggle switch; 12 V battery; pc board ETI-262; small box to suit; barrier strip terminals (six-way), plated type; suitable reed switches; magnets etc as per the article.



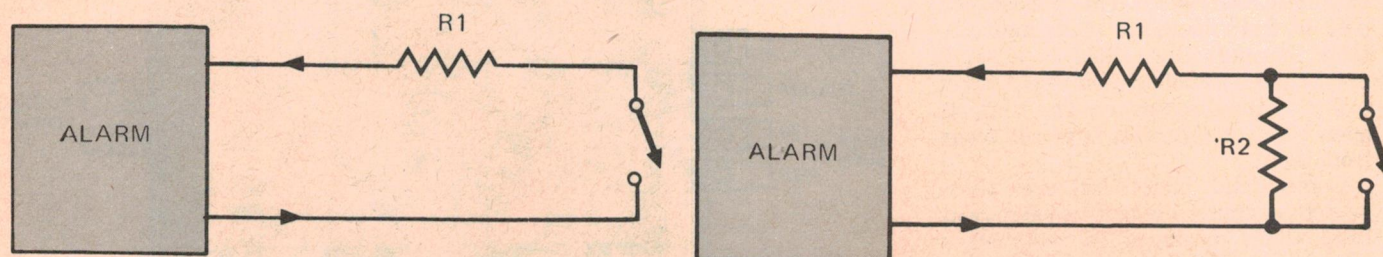



Figure 2. Resistance R1 represents series resistance of the loop (see text). Resistance R2 represents leakage paths across alarm contacts.

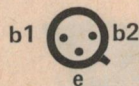

# simple house alarm

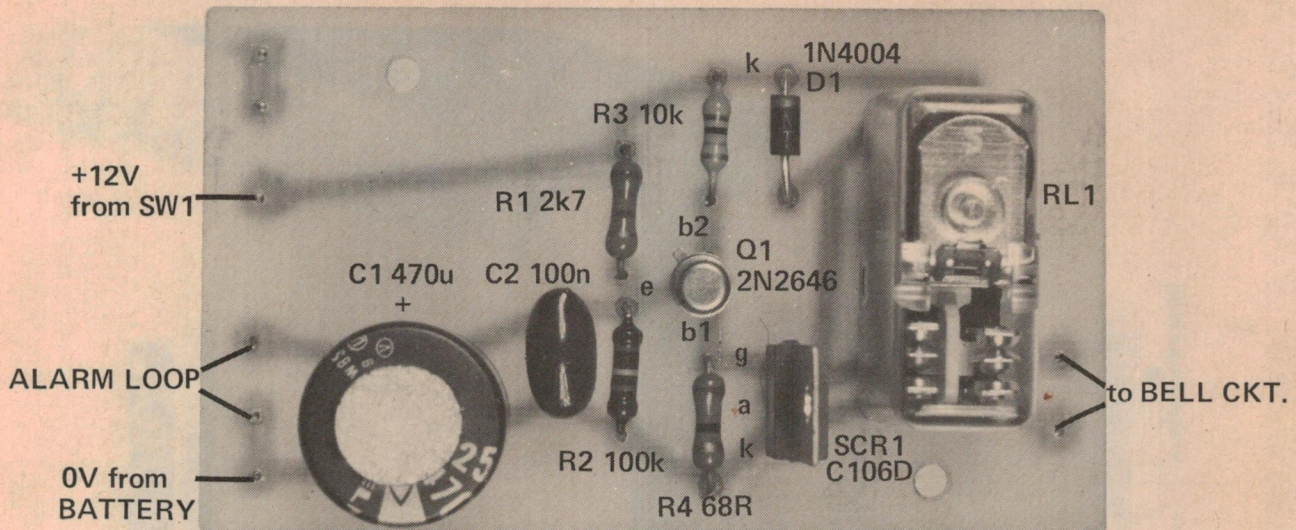

2N2646 BOTTOM VIEW

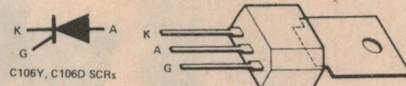

switches gets moist — a leakage path may develop in parallel with the switch (that's why you keep those leads apart) and if this happens when the control unit can tolerate more than a few hundred ohms, that switch can be opened *without triggering the alarm!*

The alarm unit must be insensitive to voltage spikes picked up by the external loop — remember that's quite an antenna you'll have there. Such voltages can be surprisingly high and are caused by lightning strikes, arc welders, faulty fluorescent lighting starters, capacitor start motors (often found in 'fridges and freezers), contactors, etc. Existing alarms can be protected to some extent by connecting two capacitors (in

parallel) across the input terminals. One should be about 10 uF, the other about 10n. Figure 3 shows how — and why you need the two.

A good test for voltage spike immunity is to wind fifty to a hundred metres of wire around a power drill. Connect the two ends to the input of the alarm unit and switch the drill on and off about fifty times. If the alarm isn't triggered by this it's a fair bet it will be satisfactory when installed. Very few alarm control units will withstand this test and those that don't will sooner or later cause problems.

Don't for a moment consider any alarm unit in which the external loop is connected directly to the gate of an SCR.

It is *impossible* to protect such a circuit if the external loop is more than a few centimetres long. Yet, incredibly, such circuits are shown time and again in electronics magazines — presumably because at first sight an SCR is (almost) a single component control unit.

Likewise, don't connect a bell or siren directly to the anode of an SCR. Voltage spikes induced in the wiring to and from the bell can and will trigger the SCR into conduction. If you have such a device at present, modify it by interposing a relay between the SCR and the bell circuit — and connect a diode across the relay coil to protect the SCR against the relay's collapsing magnetic field.

The circuit of the ETI-262 alarm con-►

## LINE FROM HOUSE CIRCUIT



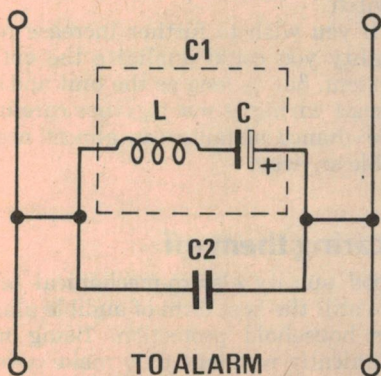


Figure 3. The large value capacitor, C1, will effectively bypass low frequency interference but its high series inductance, L, will prevent the bypassing of high frequency interference. A smaller value capacitor, C2, usually a ceramic type with a low series inductance, will bypass the high frequencies effectively.

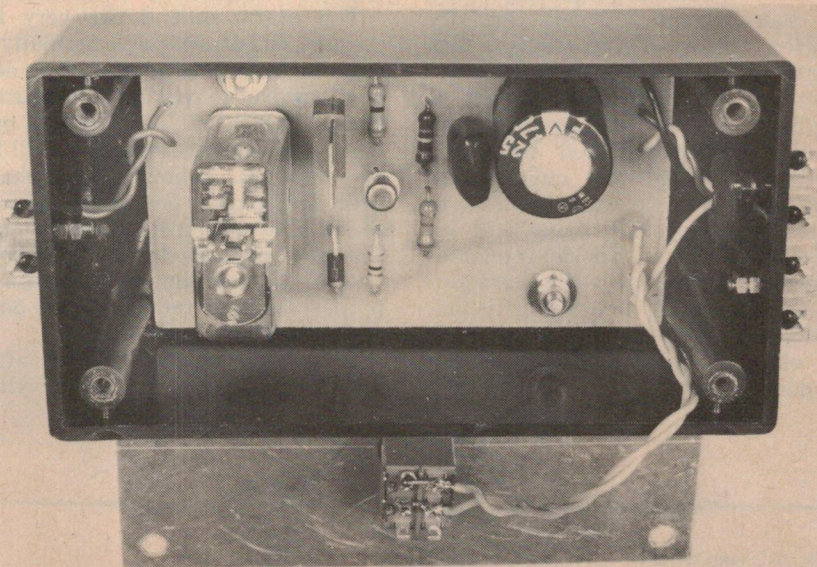

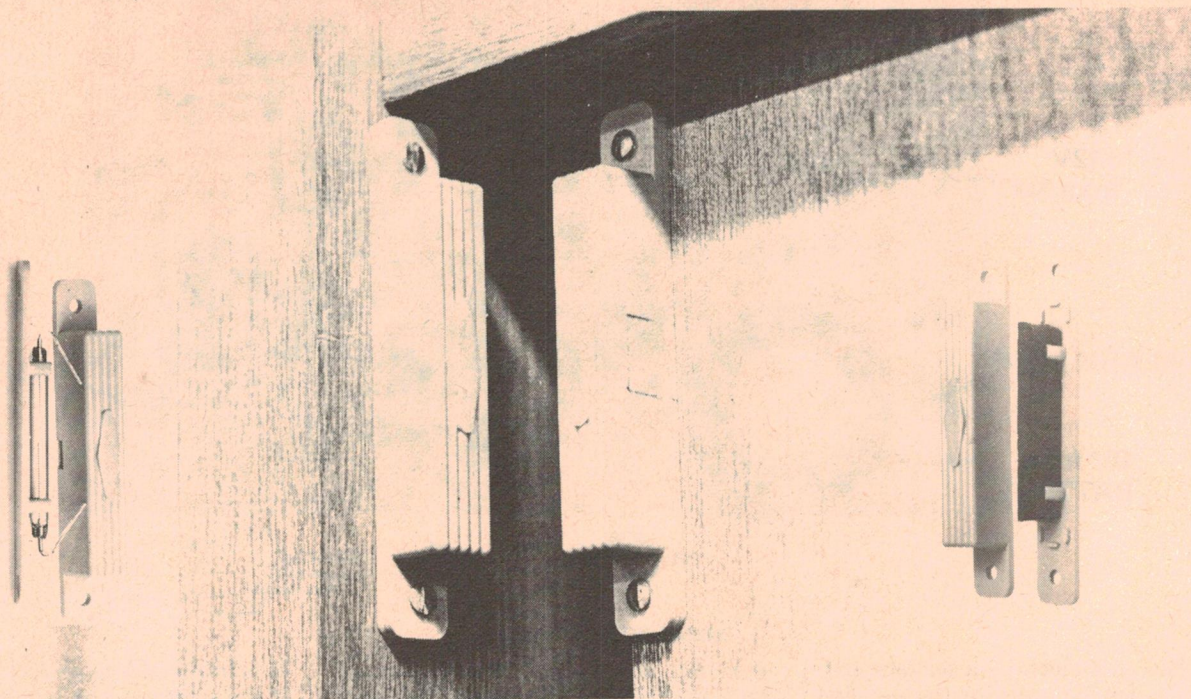

# Project 262



Reed switches and magnets for burglar alarm systems are designed for easy installation.

trol unit is shown in the accompanying diagram. It's essentially a simple circuit but one in which several components perform more than one function. The basic idea is that a unijunction pulse generator is normally prevented from operating by the closed external alarm loop. When the loop opens, the unijunction 'fires', causing an SCR to conduct and latch on, which in turn actuates the alarm relay.

The best way to construct the control unit is to use the printed circuit board shown (full size) on page 47. Make sure that C1 is inserted the right way round and that all joints are very carefully soldered. Clean off any residual flux after soldering.

Resistor R1 controls the length of time between a switch being opened and the alarm being triggered. The value shown will trigger the circuit after approximately  $\frac{3}{4}$  sec. Altering values to reduce the triggering delay will increase battery drain. The delay enables doors to rattle in a gale without triggering the alarm accidentally (it is impossible to open a door, pass through and close it again in less than one second).

Don't be tempted into replacing R1 by a potentiometer — it will rarely be moved once the alarm is installed, so that corrosion will eventually build up between the wiper and the track.

Keep the leads from the alarm unit to the battery as short as possible — 300 mm at most. Preferably build the battery in with the unit as we've shown. Use a *second* battery to power the alarm bell.

Do not delete the relay and run the bell straight off the SCR. *It will work*, but with reduced reliability and increased susceptibility to false alarms.

The alarm unit draws very little current, so batteries will normally last for nine to twelve months. It is advisable however to replace them routinely every six months. It's not worth building a mains power supply. You'll need an automatic mains/battery change-over unit to cater for mains failures — so you'll have to have a battery anyway. The best power sources for this application are six volt 'lantern' batteries. Use proper soldered terminal lugs on the ends of the battery leads.

It is worth considering powering the bell from a small Nicad battery with an

automatic charger. This is also an elegant way of ensuring that the bell cuts out after an hour or two when the Nicad has exhausted itself.


Arrange for a key operated switch to short out the alarm switch on a chosen 'silent entry' door. Suitable switches may be obtained from security equipment companies. The associated wiring should be concealed.

The main on/off switch on the unit itself should be double-pole single-throw with the contacts wired in parallel (to enhance reliability). Do not attempt to economise by fitting a cheap switch.

If you wish to further increase reliability you could duplicate the entire system, but as long as the unit and external wiring is put together carefully the chance of failure is almost negligible anyway.
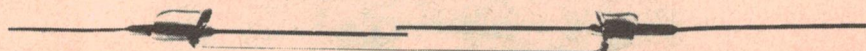
## Scaring them off

Good quality electro-mechanical bells are still the best form of audible alarm for household protection. Being mechanically resonant they make a very large amount of noise and consume little power whilst doing so. The average 12 inch bell (it's an old-fashioned industry and they still think in inches) draws less than half an amp and can be heard at least a hundred metres away.





A magnetic reed switch.


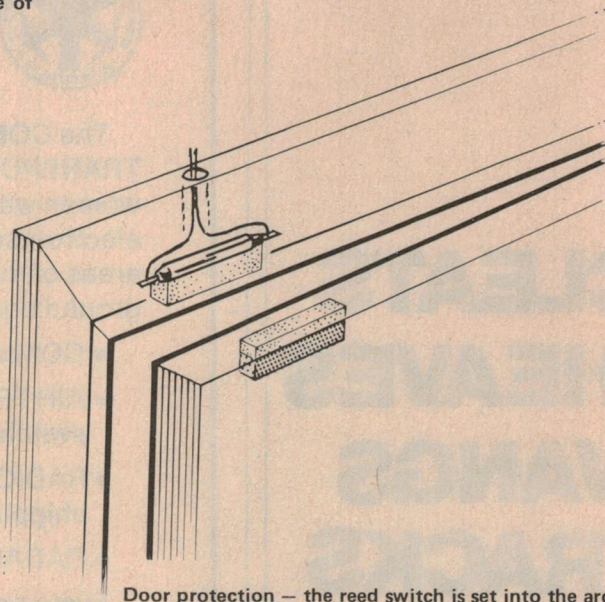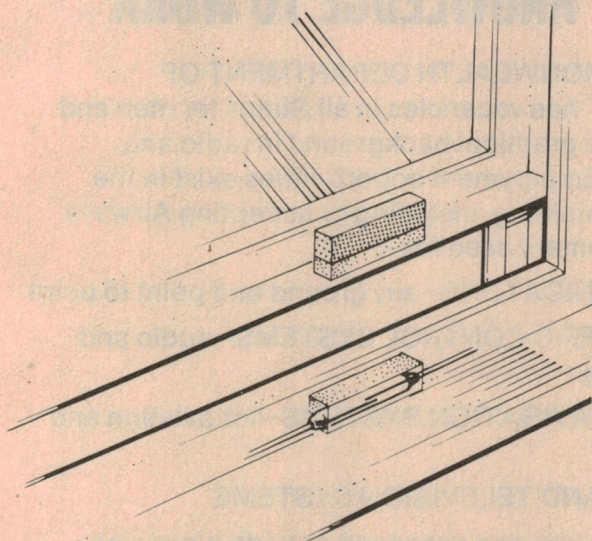
# simple house alarm

For window protection, the reed switch is recessed into the frame of the casement window. The magnet is set into the moving part.



Door protection — the reed switch is set into the architrave.

A siren has a potentially larger range but is more directional. Good ones draw a lot of power — five to ten amps or more. Small cheap sirens should not be considered. The alarm bell should be mounted unobtrusively, and high up in an inaccessible position. Leads to the bell should be totally concealed. Use 40/0076 wire to reduce voltage drop.

It is worth locating one or two spotlights in strategic positions and arranging for these to be switched on as the alarm is actuated.

Finally, don't be put off by stories about people ignoring alarm bells — burglars don't!

## Should you tell

Providing you have a good installation and a concealed bell there's a lot to be said for making it clear to intending intruders that the premises are protected.

One way of doing so is simply to place warning notices in strategically chosen windows. This is done by most professional security companies — to such effect that there's quite a strong argument for using just notices alone!


We've included a suitable warning notice in this issue — (extra copies printed on heavier paper may be obtained directly from the magazine for 50 cents each plus a large, stamped addressed envelope).

A further very worthwhile tactic is to install a circuit which flashes red LEDs set into the frames of all visible

windows and doors. The old 555 will do nicely, or those new-fangled self-flashing LEDs. Combine these with the printed notices plus the alarm circuit, just in case anyone thinks you're

bluffing, and your chances of being robbed are negligible.

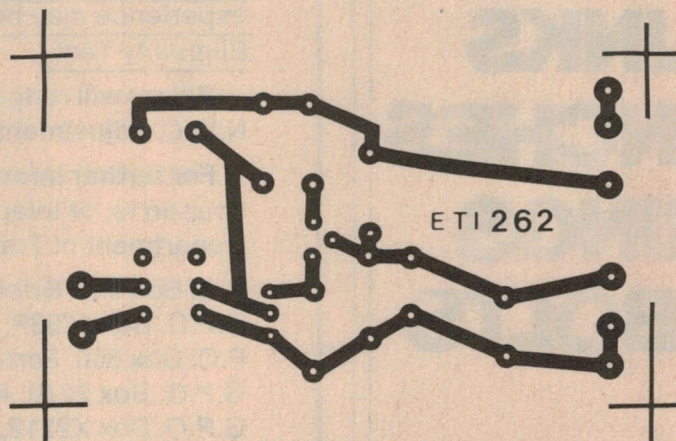One final note: no matter how good the installation, it's *useless* unless you switch it on. ●



Printed circuit board pattern.

**THESE PREMISES  
PROTECTED BY  
E.T.I. SECURITY ALARM  
SYDNEY, AUSTRALIA. **eti**262**



# **CLEATS SHEAVES VANGS TRACKS TANGS SWAGES BLOCKS LINKS WINCHES RINGS U BOLTS**

Hundreds of bits for boats in  
the 152 page Ronstan catalogue  
FREE in August issue of

Modern  
**boating**  
& Seacraft

The magazine that covers  
everything afloat.



## **PUT YOUR ELECTRONIC KNOWLEDGE TO WORK**

The COMMONWEALTH DEPARTMENT OF TRANSPORT has vacancies in all States for men and women with a practical background in radio and electronics. Employment opportunities exist in the areas of maintaining, installing or accepting Airways ground equipment used for—

- COMMUNICATIONS—air/ground and point to point
- AIR TRAFFIC CONTROL SYSTEMS—audio and switching
- RADIO NAVIGATION SYSTEMS—for aviation and shipping
- RADAR AND TELEVISION SYSTEMS

Systems in use and proposed provide a growing involvement in computers and digital techniques. The work is varied and interesting, spanning several of the above fields. Training is generally provided on new equipments. If you hold a Certificate in Electronics and Communication (Diploma in W.A.), or equivalent, with practical experience, we need you for appointment as a Radio Technical Officer. Persons without formal qualifications but with sound knowledge and practical experience may be accepted subject to passing an Eligibility Test.

Salary will range from \$9,798-\$13,923 (plus any N.W.C. adjustment).

**For further information and application form** send coupon to, or telephone, Recruitment Officer, Department of Transport in your State:

P.O. Box J93, Brickfield Hill. NSW 2000. Tel: 20929.  
G.P.O. Box 1733P, Melbourne, Vic. 3001. Tel: 6622455.  
P.O. Box 600, Fortitude Valley, Qld. 4006. Tel: 3589211.  
G.P.O. Box 2270, Adelaide, SA 5001. Tel: 2239911.  
G.P.O. Box X2212, Perth, WA 6001. Tel: 3236611.


Please forward Information  
concerning your Radio Technical  
Officer vacancies.

Name.....


Address.....

Postcode.....




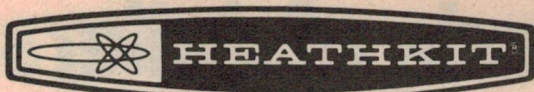
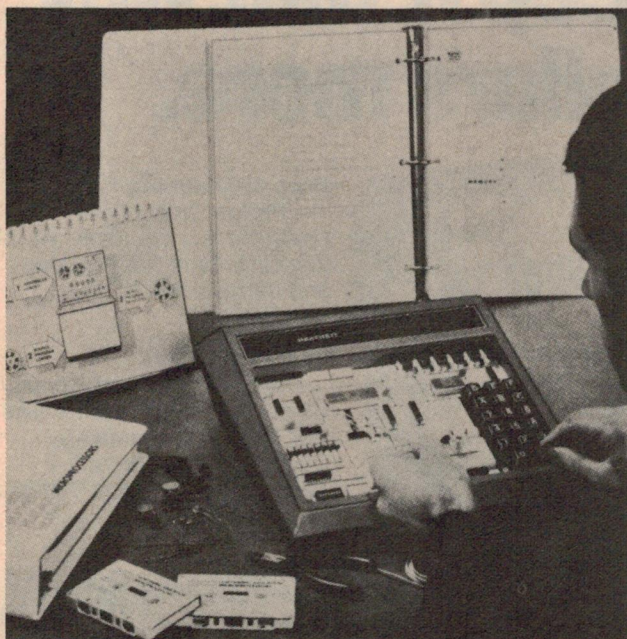
# Microprocessor Course and Computer Trainer


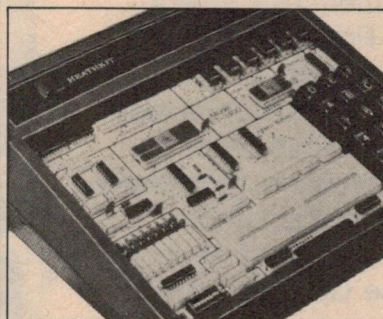
## 2 Microprocessor trainer for experimentation and design



- Uses 6800 Micro-processor
- Built in 1k ROM monitor program
- 256 bytes of RAM
- Breadboarding socket for prototyping

Use with Course EE-3401 for an up-to-date computer education

If you are involved in scientific, electronic or business pursuits, microprocessors are becoming a way of life and a dominant factor in your success or failure. The EE-3401/ET-3400 course and trainer is a low cost and effective key with which you can easily learn microprocessor theory and techniques. EE-3401 uses proven programmed learning techniques to teach programming, interfacing and much more. The ET-3400 Trainer provides the ideal platform for experimentation and later, your own prototyping and design. This is a learning package you cannot afford to miss.

## 1 Learn Microprocessor Operation, Application and Interfacing

*Covers microprocessor basics, computer arithmetic, programming, interfacing and much more*

Using Heath's proven self-instruction techniques, EE-3401 adopts a three phase approach to guide you, step-by-step, through the complexities and power of machine language programming, hardware I/O interfacing and microprocessor theory and design applications.

Element I, presented in 8 lessons, utilizes concise self-study texts to cover: Number systems and codes, micro-computer basics, computer arithmetic, introduction to programming, the 6800 microprocessor (part I), the 6800 microprocessor (part II), interfacing the microprocessor, (part I), and interfacing the microprocessor (part II).

Colourful audio and visual presentations are combined in element II's six lessons to further enhance your knowledge of such subjects as programming, designing with microprocessors and semiconductor memories. Phase III of EE-3401 provides 19 informative experiments through which valuable "hands-on" experience is gained. The ET-3400 Trainer is utilized and experiments are divided into programming and interfacing applications. Experiments cover program branches, address decoding, arithmetic and logic instructions and much more.

EE-3401 comes complete with 62 electronic components including ICs, RAMs, op-amps and a variety of other microprocessor oriented devices. No additional components are necessary to carry out the experiments provided with this program.

Course EE-3401

\$155.00

Functioning as a miniature digital computer, the ET-3400 Microprocessor Trainer has been designed to compliment your EE-3401 Microprocessor Course and provide an ideal platform upon which you may easily and enjoyably expand your knowledge of microprocessor programming and interfacing techniques. In addition, the ET-3400 provides you with plenty of breadboarding capability for experimentation, prototyping and system design.

The ET-3400 is based on the popular 6800 microprocessor and key features include: 1. A built-in 1k ROM monitor program for controlling unit operation. 2. Six digit hexadecimal 7-segment LED display for address and data readout. 3. 17-key hexadecimal keyboard for entering programs, data and control of the unit. 4. 256 bytes of random access memory (RAM), expandable to 512 bytes. 5. Breadboarding socket for prototyping, interfacing and memory circuits. 6. Eight buffered binary LEDs for display of breadboard logic states. 7. Eight SPST DIP switches for binary input to breadboarded circuits. 8. +5, +12 and -12 VDC power supply outputs. 9. All microprocessor address, data, and control busses buffered and terminated on the front panel for ease of connection to prototyped circuits. 10. Provision for a 40-pin external connector for extending memory and I/O capability.

Trainer ET-3400.

\$347.00

## ORDER BY COUPON NOW OR COME TO OUR SHOWROOM

Please rush me the Heathkit of my choice. My cheque for \$ ..... is enclosed plus \$7.00 for package and post.

☐ Course EE - 3401 ☐ Course ET - 3400

Name .....

Address .....

..... P/Code.....

Send to: W. F. Heathkit Centre

220 Park St., South Melb. 3205. Phone: 699-4999



# You spent thousands of dollars getting hi-fi. Keep it that way for a few dollars more.

To maintain the best performance from your cassette, reel to reel recorders and decks, video tape recorders and record playing equipment use Philips Maintenance Products.

Philips manufacture a very large range of maintenance aids to assist you to keep your valuable equipment in good order.

All these and many more products are available from your Philips Service Centre or dealer outlets.



**Drop In Cleaning Cassette**  
Philips Drop In Cleaning Cassette is a complete kit for cleaning, tape head guides and capstan. **\$4.20\***  
Code 38920015

**Philips RC3000**  
Hi Fi Record and Stylus Cleaner. Length pivot to pad 200 mm, arm overhang 35 mm. Complete with 2 pads, stylus brush, cleaning fluid. **\$25.46\***  
Code 39590159

## Other popular Philips Service Products.



**Philips Disco Combi Set**  
Gets down deep into the recorded grooves with a long lasting velvet pile, complete with special cleaning fluid. **\$3.89**  
Code 39590157

**Philips Hi Fi Stereo Headphones**  
Hi Fi Stereo Headphones with twelve extra membranes for spatial sound. **\$96.00\***

Technical Data (Subject to modification without notice)  
Frequency response 16-20000 HZ ( $\pm 3.5$  DB); Impedance (nominal) 2 x 600 ohm; Sensitivity 94 DB S.P.L. at 1 MW; Nominal power input 2 x 1 MW; Maximal power input 2 x 200 MW; Distortion < 1%; Weight 390 g approx.  
Code 242 47017



**Philips V.C.R. Cleaning Cassette**  
Maintains highest quality of picture and sound, removes deposits from video, audio heads and tape guides. Use every 30 hours for maximum results. **\$19.20\*** Code 39590102



**Head Renovator Cassette**  
All recorders eventually lose performance through their heads becoming gradually magnetized. Thanks to the new SBC 137 you can effectively clean and demagnetize recorder heads all in one easy operation. **\$4.85\***  
Code 39590165

\*Recommended retail price

All Philips audio and video service products are available through your nearest Philips Service Centre or selected dealers.

**Sydney:** 443 Concord Road, Rhodes, N.S.W. 2138. Telephone: (02) 73 0231. **Philips Building,** 2 Blue Street, North Sydney, 2060. Telephone: (02) 922 0181.  
**Newcastle:** 190 Parry Street, Newcastle West, 2302. Telephone: (049) 61 1631. **Canberra:** 86 Wentworth Avenue, Kingston, A.C.T. Telephone: (062) 95 0321.  
**Melbourne:** Cnr. Miles & Dodds Street, South Melbourne, 3205. Telephone: (03) 699 2711. **Hobart:** 2A Pierce Street, Moonah, Tasmania, 7009. Telephone: (002) 28 0121. **Brisbane:** 55 Forbes Street, West End, Brisbane, 4101. Telephone: (07) 44 8121. **Townsville:** 38 Punari Street, Currajong, 4812. Telephone: (077) 79 7422. **Adelaide:** 81-97 Flinders Street, Adelaide, 5000. Telephone: (08) 223 2999. **Perth:** 875 Wellington Street, West Perth, 6005. Telephone: (09) 321 5131.

# PHILIPS

# ServiceServiceService



AHEARN PSI



# Lab Notes

## Designing with diodes — tricks of the trade

The humble diode can extricate you from some difficult circuit problems, be it in logic or linear applications.

Ray Marston

THERE ARE numerous occasions when one needs a basic gate circuit or two and is faced with the possibility of having to wastefully commit an entire IC to this simple function. Alternatively, it may be the case that the inputs to a gate come from such widely separated points of a circuit that the use of an IC in a particular application will result in an excessively complicated pc board layout. In both of these instances, a simple diode gate may offer an ideal solution to the problem.

Figure 1 shows the practical circuit of a three input diode OR gate. The circuit is simple, reasonably fast, very cost-effective and can readily be expanded to accept any number of inputs by merely adding one more diode to the circuit for each new input.

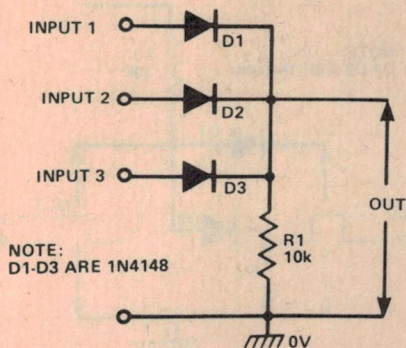


Figure 1. The diode OR gate is simple, but efficient. It can be expanded to accept any number of inputs by adding extra diodes.


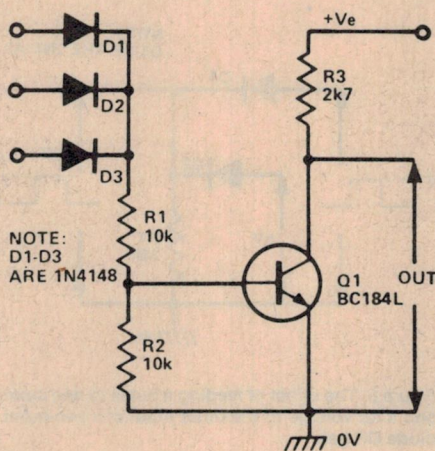


Figure 2. The diode OR gate can be converted to a NOR type by feeding its output through a transistor, as in (a) above, or through an IC inverting stage, as in (b) below.

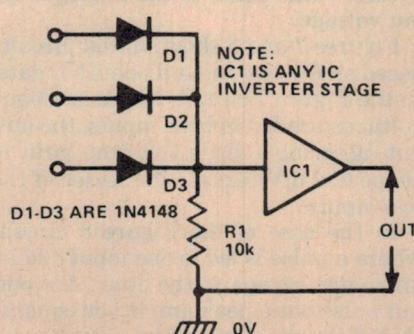

The diode OR gate can be converted to a NOR type by either feeding its output through an NPN transistor inverting stage, as shown in Figure 2a, or by feeding its output through any type of IC inverting stage that happens to be 'spare' in the circuit you are playing with, as shown in Figure 2b.

Figure 3 shows the connections for making a three input diode AND gate. The circuit can again be expanded to accept virtually any number of inputs by simply adding an appropriate number of diodes.

The AND gate can be converted to a NAND type by feeding its output through a pnp transistor or an IC inverting stage, as shown in Figures 4a and 4b respectively.

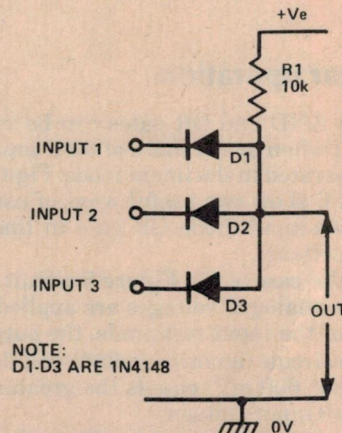


Figure 3. The circuit of a three-input AND gate. The number of inputs can be increased by adding extra diodes.



# Lab Notes

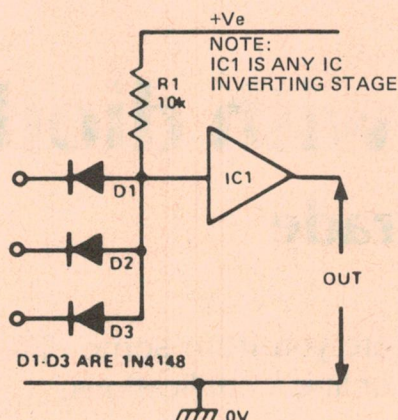
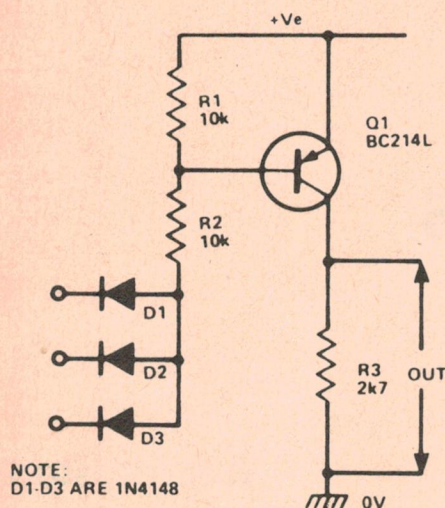


Figure 4. The diode OR gate can be converted to a NAND type by feeding its output through an inverting stage using either a transistor, as in (a) at left, or an IC as in (b) at right.

## Diode volt drops

We've mentioned above that the output of the 'analogue' diode gate may be 'within a diode volt drop' of the input signal. The magnitude of this 'volt drop' depends on the type of diode that is in use, on the magnitude of the diode forward current and on the temperature of the diode junction. All silicon diodes have a negative temperature coefficient of about  $-2 \text{ mV}/^\circ\text{C}$ .

Figures 9 and 10 show typical volt-drop curves for the popular 1N4148 and 1N4001 silicon diodes at  $25^\circ\text{C}$ . The graph of Figure 9 spans the current range  $100 \mu\text{A}$  to  $1 \text{ mA}$  and the graph of Figure 10 spans the range  $1 \text{ mA}$  to  $50 \text{ mA}$ .

Note that the 1N4148 volt drop typically ranges from  $519 \text{ mV}$  at  $100 \mu\text{A}$  to  $874 \text{ mV}$  at  $50 \text{ mA}$ , compared to the 1N4001's range of  $441 \text{ mV}$  at  $100 \mu\text{A}$  to  $744 \text{ mV}$  at  $50 \text{ mA}$ .

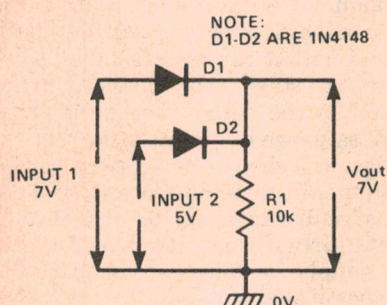


Figure 5. When a diode OR gate is used in the linear mode,  $V_{\text{out}}$  equals the greater of the two inputs.

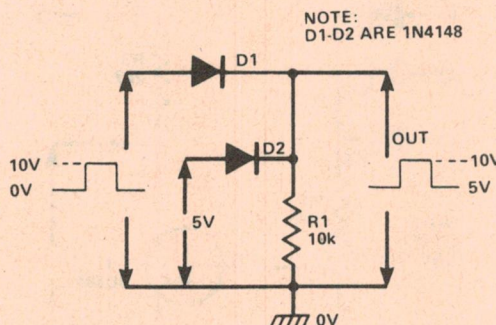


Figure 6. The effect of feeding a pulse to one input and a dc voltage to the other input of a two-input diode OR gate.

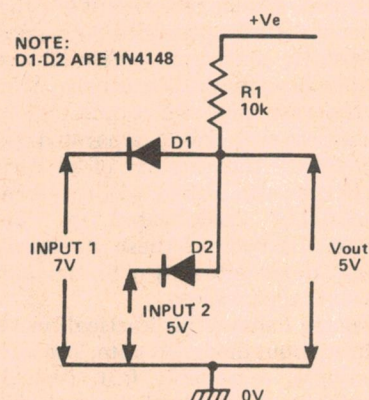


Figure 7. When a diode AND gate is used in the linear mode,  $V_{\text{out}}$  equals the less of the two inputs.

## Linear operation

Diode AND and OR gates can be very useful when one or more of their inputs are operated in the linear mode. Figures 5 and 6 show two useful ways of using the two-input diode OR gate in linear applications.

In the case of the Figure 5 circuit, in which analogue voltages are applied to both of the input terminals, the output of the circuit (ignoring a diode volt drop of about  $600 \text{ mV}$ ) equals the greater of the two input voltages.

Figure 6 shows what happens when a pulse signal is fed to one input of the OR gate and an analogue voltage is fed

to the other. The output signal comprises a pulse with a peak amplitude equal to that of the input pulse and with a 'zero' value equal to the analogue input voltage.

Figures 7 and 8 show similar circuits based on the two-input diode AND gate. In the Figure 7 circuit, where analogue voltages are fed to both inputs, the output (ignoring a diode volt drop 'gain' of about  $600 \text{ mV}$ ) equals the lesser of the two inputs.

In the case of the Figure 8 circuit, where a pulse is fed to one input and an analogue voltage to the other, the output pulse has a peak amplitude equal to that of the analogue input voltage.

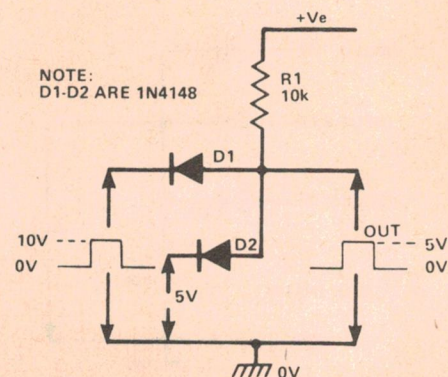


Figure 8. The effect of feeding a pulse to one input and a dc voltage to the other input of a two-input diode AND gate.



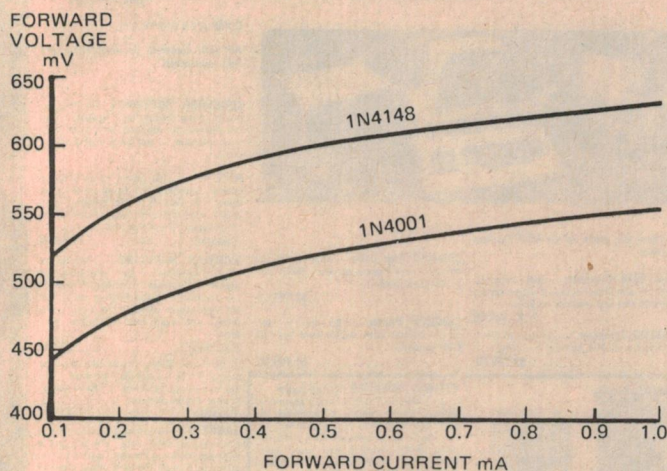


Figure 9. Diode volt-drop curves for the 1N4001 and 1N4148 diodes over the 100 uA to 1 mA current range.

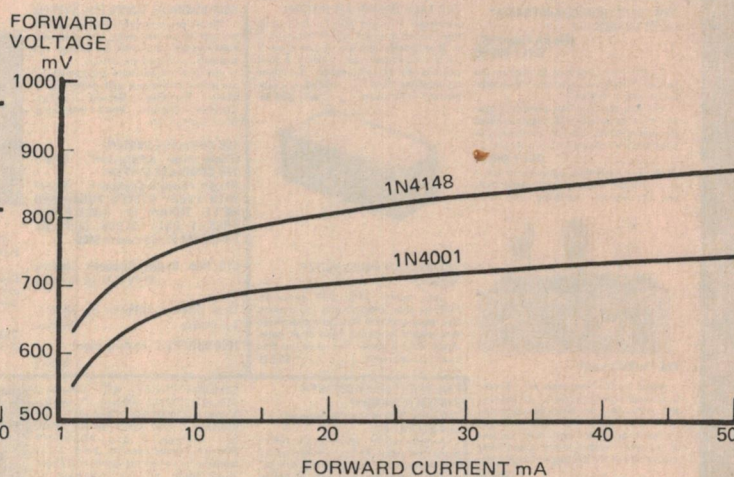


Figure 10. Diode volt-drop curves for the 1N4001 and 1N4148 diodes over the 1 mA to 50 mA current range. Note that these two diode types are the most commonly used (highest volume sales of any single component).

A point of particular note about the 1N4001 curve is that its volt drop of 714 mV at 25 mA increases by only a fraction over 4% (to 744 mV) when the forward current is doubled, to 50 mA. In other words, the diode has a voltage-to-current coefficient of about 0.04%/ in this current range. The diode can thus be used as a reasonably stable voltage reference at these current levels but has a negative temperature coefficient of about  $-0.3\%/^{\circ}\text{C}$ .

## Constant current generator

Figure 11 shows how the 'voltage reference' characteristics of the 1N4001 can be put to good use in a simple constant-current generator circuit that can be used for re-charging Ni-Cad cells or for linearly charging large capacitors, etc. Here, two 1N4001s are wired in series

and operated at a current level of roughly 50 mA. Consequently, the voltage across  $R_x$  is equal to the volt drop of the two diodes minus the base-emitter volt of Q1 (about 700 mV), which gives an  $R_x$  voltage of about 700 mV. The emitter (and hence collector) current of Q1 is thus approximately  $700/R_x$  in (mA).

To give an idea of the magnitude of things, an  $R_x$  value of 1R2 (1.2 ohms) gives an output current of about 600 mA, 3R9 (3.9 ohms) gives about 200 mA, and 6R8 (6.8 ohms) gives about 100 mA. All in all, a simple but very useful circuit.

## Diode protection circuits

To wrap up these Lab. Notes, let's take a quick look at some diode protection circuits. By 'protection' we mean circuits that are designed to insure devices against irreversible damage and

also circuits that are designed to prevent simple malfunctioning. Figures 12 to 15 show four circuits in this latter category.

In the case of Figure 12, we have a basic time constant circuit in which a rising voltage, with a time constant of about 100 seconds, is developed across C1 each time SW1 is closed. This voltage may be used to activate some additional circuitry. The problem is that, once C1 has charged up it has no means of rapidly discharging again (resetting) once SW1 is opened. If there is a load in parallel with the C-R network, as shown dotted in the diagram, C1 will of course discharge via R1 and the load but then has a very long time constant (greater than 100 seconds).

An easy way round this problem is to connect a discharge diode in parallel with R1 as shown in Figures 12 and 13.►

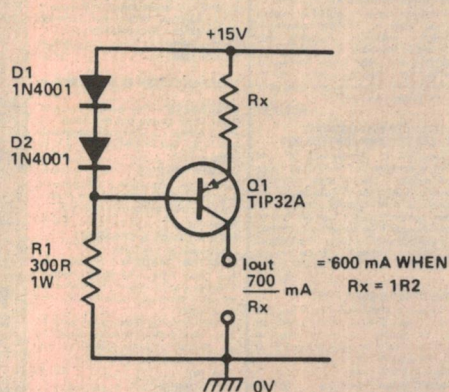


Figure 11. A simple and very useful current generator.

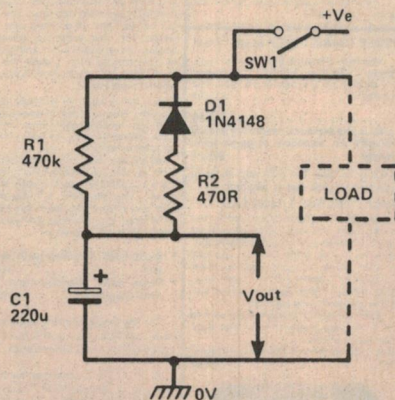


Figure 12. An example of the use of a diode to rapidly discharge a timing capacitor when the power supply connection is broken.

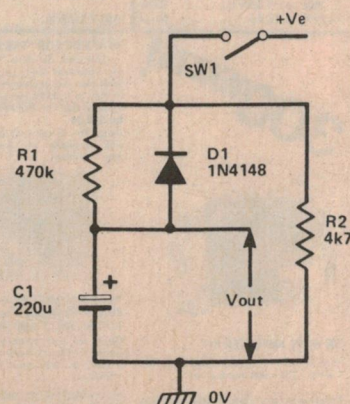


Figure 13. A modification to the Figure 12 circuit.



# Bill Edge's ELECTRONIC ENCLOSURES

New Telephone Number 745-3077,  
2 lines.

115-117 PARRAMATTA ROAD, CONCORD 2137.  
(Corner Parramatta Rd &  
Lloyd George Ave)

MAIL CHARGES	\$1.00 handling charge
\$5 - \$9.99	FREE
\$10 - \$24.99	\$1.00
\$25 - \$49.99	\$2.00
\$50 - \$99.99	\$3.00
\$100 or more	\$4.50

All heavy or bulky items (over 20 kg) sent  
"freight on" through carrier.  
Bankcard welcome - by mail, telephone,  
or over the counter.



## NEW "ELECTRONICS AUSTRALIA" LIGHT CHASER KIT

(See EA August '80)  
..... ONLY \$65.00

Exactly the same case as used in the famous "Electronics Australia" Musicolor Full details in this issue.

Our kits feature a fully pre-drilled case and front panel with high quality knurled aluminium knobs and full instructions to make this very simple to construct kit.

..... ONLY \$65.00

Absolutely everything supplied in kit - all you need is some simple basic tools like screwdriver, soldering iron, etc.



## THE "MINICOLOR"

Music to light converter kit. Similar to Musicolor but at a fraction of the cost, and only half an hour to construct.

Designed by a very competent electronics engineer and enthusiast, because of the great demand in discos and home entertainment for this piece of equipment

..... ONLY \$49.90

## FEATURES:

- One control operation.
- Quality PC fireproof board.
- PC board ready assembled and pre-tested.
- No soldering needed.
- Assembled in 1/2 hour with simple tools.
- Very simple to follow instructions.
- Doesn't take up much space.
- (160 x 100 x 125mm)

**SPECIFICATIONS:** Input sensitivity 500mV. Lamp load up to 1800 watts. Preset frequency divider. Bass 15 to 250Hz, middle 250 to 1200Hz, treble 1200 to 5000Hz.

It will suit almost any audio amplifier - you don't have to be technically inclined to get the machine working, as all the hard part has been done for you, and unlike some kits this kit is guaranteed to work.

**COLOURED**  
100 WATT SPOT FLOODS B.C.  
Red, green, yellow, blue ..... \$59.95 ea.  
Standard base for lamps ..... \$1.10 ea.  
Swivel base for lamps ..... \$1.84 ea.

## DIGITAL CAPACITANCE METER KIT

Here is an inexpensive digital capacitance meter which measures from 1pF to 99.99 uF in just three ranges. It's simple to use and features a big bright four-digit display with automatic updating and decimal points. Display digits 13mm high. Case dimensions: 184(d) x 70(h) x 160(w) mm.

..... ONLY \$59.90



## TV CRO ADAPTOR KIT

(EA May '80) ... fantastically popular - turn your old TV into a CRO.

..... ONLY \$29.40

(without power adaptor)

Two power adaptors available:  
(i) 240V to 6.75/5.9V d.c. .... \$9.50  
(ii) 240V to 9V d.c. .... \$9.95

## 300 WATTS!



## 300 WATT AMPLIFIER KIT

"The BRUTE" - develops 300 watts into 4 ohms. 200 watts into 8 ohms.

## COMPLETE KIT FOR ET1466 300 Watt AMPLIFIER MODULE


(less heatsink and power transformer), exactly as described in ET1 Feb '80, including predrilled heatsink bracket, all nuts, bolts, silicon grease etc.

..... ONLY \$63.50 per module.

All parts for ET1466 are available separately: ET1466 printed board \$7.00; MJ15003 and MJ15004 transistors \$5.00; 2500 uF/80V Caps \$3.90 ea; 1 ohm 5W Resistors 65c ea; 62 volt zener \$1.00
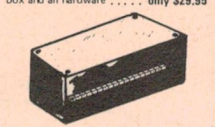
## LED TACHOMETER KIT (ET1324)

See details in August '80 ET1. A fantastic little device that will suit all cars with 2 to 8 cylinders; and will inform driver if he is revving too high - hence a good check on petrol consumption. Complete kit available from us - including zippy box and all hardware ..... only \$29.95



## LCD 3 1/2 DIGIT PANEL METER MODULE

Uses Intersil 7106 A/D converter, PCB, all caps, resistors and instructions. Has many uses and features a guaranteed zero reading for 50 volts input on all scales, direct display drive, low noise, on-chip clock and reference. .... \$42.50

## PHILIPS/ETI 4-WAY SPEAKER SYSTEM (ET14000/1)

100 watts RMS, 8 ohms impedance) (See ET1 Feb '80)

Uses the latest Philips speakers and a marvellous design by David Tilbrook, this speaker system has outstripped all projected sales figures. They sound so good, they are rivaling commercial units in the \$1,500 price bracket.

## PHILIPS/ETI 3-WAY SPEAKER SYSTEM (ET14000/2)

(100 Watts RMS, 8 ohms impedance). (See ET1 June '80). Another completely new system. Designed for those with a space problem but still require good sound.

## PHILIPS SPEAKERS

### WOOFERS

200mm(8") (AD8065/W8 or AD8065/W8) woofer, 40W RMS, 8ohm, freq. response 35Hz to 7kHz ..... \$28.50

250mm(10") (AD10100/W8) Woofer 40W RMS, 8ohm, freq. response 40Hz to 5kHz ..... \$57.50

300mm(12") (AD12100/W8) Woofer 40W RMS, 8ohm, freq. response 30Hz to 1.2 kHz ..... \$57.50

300mm(12") (AD12250/W8) Woofer 100W RMS, 8ohm, frequency response 40Hz to 2kHz ..... \$96.95

### HAVE YOUR HOME OR OFFICE UNDER SURVEILLANCE WITH THE MOST RELIABLE & SENSITIVE PROTECTION AVAILABLE TODAY - INFRARED DETECTOR - DETECTS CHANGES IN TEMPERATURE IN A ROOM - U.S. MADE.

### FEATURES:

- More reliable than ultrasonics as rustling curtains or other slight movements will not set it off - only the change in temp. when a person is present.
- Speaker design blends with household decor.
- Excitement delay.
- Internal siren with provision for external siren.
- Automatic reset.
- 7.5 metre range.
- Own battery supply.
- No installation.
- Very small size - only 125mm (h) x 225mm (w) x 135mm (d).
- Adjustable vertical coverage.

..... ONLY \$159.00

## HEATSINK FOR "THE BRUTE"

This can be done in two ways as mentioned by ET1, i.e., you can make your own out of aluminium (which is not as easy as it looks and is very critical), or you can buy the Philips 6506C Heatsink for \$29.50

(N.B. This is the only commercial heatsink available in Australia that is recommended).

## POWER TRANSFORMER TO SUIT "BRUTE"

Specially designed high power transformer ... 240V a.c. primary; Secondary: 2 x 47V @ 2A, 2 x 15V @ 1/2A (96 x 114 x 110mm) ..... \$32.50

FAN is also available (which runs directly off 94V a.c. secondary of power transformer) ..... \$29.90

CASES suitable for 300 watt Amp or wherever a large case is required:

## RACK MOUNTING ET14000 CASE

Beautifully designed (supplied in flat pack), satin anodised 1.6mm aluminium front and back panels, with surfaces suitable for screen printing etc. Top and bottom panels of hard wearing black "marvplate" with 1.0mm steel base. Side panels with chrome satin anodised aluminium with chrome handles.

Four aluminium extrusions are used to hold the top, bottom, front and back panels in position.

Size: 134mm(h) x 419mm(w) x 280mm(d) ..... \$55.00

## WOODEN SIDED ET14000 CASE

Exactly the same size and same materials as used in ET14000 rack mounting case, except side panels are made of teak wood (13mm) for a really superb looking case. .... ONLY \$45.00

## WOODEN SIDED ET14000 CASE

Exactly the same size and same materials as used in ET14000 rack mounting case, except side panels are made of teak wood (13mm) for a really superb looking case. .... ONLY \$45.00

## POWER SUPPLY TO SUIT: includes transformer and all necessary components

..... \$52.95

## CBM BUSINESS COMPUTER SYSTEM

We are proud to offer this high quality product at an incredibly low price and CBM systems are now on display and available for immediate delivery.

An array of software programmes is available for business and other applications including General Ledger, Creditors, Debtors, Word Processing, Stock Control, etc.

## 16K COMPLETE SYSTEM (Printer, Floppy & Computer) .. \$5.98

## 32K COMPLETE SYSTEM (Printer, Floppy & Computer) .. \$6.37

WITH EVERY SYSTEM PURCHASED WE'LL THROW IN, ABSOLUTELY FREE 1 ONLY STOCK CONTROL PROGRAM (disc) valued at \$400.

## C10 High Quality Computer Cassettes

..... \$1.70 ea or \$1.50 10 up.

## Blank Diskettes (133mm) by BASF - Top quality .. \$6.99 ea.

2000 SHEET 9 1/2" Fanform paper. .... \$35.00

## ET14000/1 SPEAKER KIT: Includes 2

only AD12250/W8 300mm(12") woofers 2 only AD7061/W8 178mm(7") lower midrange, 2 only AD02160/S08 50mm(2") midrange, 2 only AD01610T8 25mm(1") dome tweeters, 2 only 4-way crossover networks (designed by ETI and in kit form) plus full instructions on assembly, (box kit separate).

Mail Order: \$1.00 packing, "freight on" carrier ..... \$459 pair

## ET14000/2 SPEAKER KIT: Includes all

speakers as used in ET14000/1 system with the exception of the 178mm(7") lower midrange speakers. The crossover network is also different as it is a three way system (in kit form).

Mail Order: \$1.00 packing, "freight on" carrier ..... \$360 pair

## MIDRANGE SPEAKERS

157mm(7") (AD7061/W8) Low Midrange or Woofer 300 RMS, 8ohm, frequency response 40Hz to 3kHz ..... \$22.95

125mm(5") (AD5060/S08) Midrange 40W RMS, with recommended crossover, 8ohm, frequency response 180Hz to 10kHz ..... \$23.50

## 50mm(2") (AD02160/S08) Midrange

50W RMS, with recommended crossover, 8ohm, frequency response 500Hz to 10kHz ..... \$35.50

## TWEETERS

25mm(1") (AD01610/T8) Tweeter 100W RMS with correct crossover, 8ohm, frequency response 1600Hz to 20kHz ..... \$13.95

25mm(1") (AD01610/T8) Tweeter 100W RMS with correct crossover, 8ohm, frequency response 2kHz to 22kHz ..... \$16.95

## THE FANTASTIC ETI "SERIES 4000" AMPLIFIER KIT

Comes complete with instruction plus own specially prepared 5-page hints & advice.

This amplifier kit was originally marketed by us around August '79 and so far has surpassed all projected sales figures over 500 have been sold in all, and it still has not lost any of its popularity. The reason for this enormous interest is because the amplifier looks and performs like commercial units around the \$600 mark, and yet it sells from \$199 (with wooden sided case).

Picture shows amplifier with rack mounting case. Also available in wooden sided, with teak woodgrained 13mm pieces of wood instead of metal for sides - exactly the same otherwise.

When you buy this magnificent kit from us you are assured in writing that the kit is complete to the most minute detail - we also offer a 7 day money back guarantee if you think this kit may be a little too advanced for you, and you'd rather not attempt it.

• Series 4000 Amplifier (with wooden sided) ..... \$199.00

• Series 4000 Amplifier (with rack mounting sides) ..... \$209.00

As used in 4000 Amplifier. From 240 V A.C. input gives out + and - 40 volt rails to supply power to amplifier modules. Also gives out + and - 15 volt rails for pre-amp supply. Kit comes complete with transformer.

For the real audiophile we have also made available two transformers with extremely low hum characteristics.

Axle Low Transformer for \$10.00 extra, or a specially imported toroidal transformer for \$32.00 extra. No change is needed to amplifier circuitry to add these transformers. They are both rated at 28 - 0 - 28 volts/2 Amps on secondary and could be used in many applications where A.C. hum or in the case of the toroidal, where size is also a problem. (Save up to \$70 on locally produced toroidal transformers)

TOROIDAL TRANSFORMER ..... \$59.90 (size: 40(h) x 100(d)mm approx.)

"C" TRANSFORMER ..... \$26.50



## Items that make up the CBM Business System:

CBM 3016 Computer - 16K bytes of memory and large keyboard with separate numeric pad and graphics on keys. .... \$1,859.00

CBM3032 Computer - Identical to CBM 3016 but with 32K bytes of memory. .... \$2,249.00

## CBM3040 Disk Drive - Dual Drive intelligent mini floppy system. 341K net user storage capacity. .... \$2,329.00

CBM3022 Printer - 80 column dot matrix printer with tractor feed and full CBM graphics. .... \$1,799.00

## ET14000/1 SPEAKER BOXES (only)

Includes two professionally assembled speaker boxes exactly as described by ETI for this project - all that is required for you to do is screw speakers and crossovers (in kit form) in and mount in bond inside. Walnut finish. Dimensions: 100mm(h) x 350mm(w) x 350mm(d). Mail Order: \$1.00 packing, "freight on" carrier ..... \$300 pair

## Complete 4000/1 Speaker System

(including speakers, crossovers and boxes - everything you need to complete this fantastic pair of speakers). Mail Order: \$1.00 packing, "freight on" carrier ..... ONLY \$759 pair

## Complete 4000/2 Speaker System

(including speakers, crossovers and boxes - everything you need to complete this fantastic pair of speakers). Mail Order: \$1.00 packing, "freight on" carrier ..... ONLY \$560 pair

## CROSSOVER NETWORKS

### ET14000/1 4 WAY CROSSOVER NETWORK (Kit Form)

Crossover points: 150Hz, 750Hz, 3kHz, 100W. RMS (design by ETI) 8ohm. Size: 330mm x 246mm ..... \$170 pair

### ET14000/2 3 WAY CROSSOVER NETWORK (Kit Form)

Crossover points: 700Hz and 3kHz. 100W. RMS (design by ETI) 8ohm. Size: 210mm x 130mm ..... \$91 pair

### ADFS500/4500/8 3 WAY CROSSOVER NETWORK (Completely assembled)

Crossover points: 500Hz and 4500Hz. 40W. RMS (Philips design). 8ohm. Size: 105mm x 100mm ..... \$41 pair

## SHAPEMAKER

In studying this program you will be on your way to making effective use of the Sorcerer's graphics capability in your Basic programme.

(Cassette) ..... \$15.95

## FASTGAMMON (TM)

Makes maximum use of Sorcerer's graphics capability. An option allows you to play a game using the same rolls as the previous game. (Cassette) ..... \$21.95

## PLOT - Is a self contained and complete

plotting package which allows the Sorcerer Basic programmer to easily perform a complex high or low resolution graphics. (Cassette) ..... \$15.95

## APPLE SOFTWARE

FASTGAMMON (TM) Similar to Fastgammon on TRS80, but on diskette (24K). (Cassette) ..... \$26.95

## ASTERIODS IN SPACE

You fire at the asteroid and at the same time you have control over your spaceship. Rotate it, or move it by providing thrust. (Diskette 32K) ..... \$21.95

## FRACAS

An adventure ... humanoids, elves, dwarves, fairies and hobgoblins, plus animals - a challenge! (Cassette 32K) ..... \$21.95

## BATTLESHIP COMMANDER

Object of game is to locate and destroy the computer warships before the computer locates and destroys your warships. (Cassette 32K) ..... \$15.95

..... \$21.95

## TRS80 and SYSTEM 80 SOFTWARE

### POKER PETE

Play 5 card draw poker. Watch Peter shuffle and deal cards. He will challenge you with bluffs, raises, calls and folds. And Pete has a gun, 3 levels. (Cassette) ..... \$12.95

### RUMMY MASTER

Play Rummy against the computer. Exceptional graphics display your hand, the discards and cards that have been melded you. (Cassette) ..... \$12.95

### MATCH CARDS & BANKSHOT

Two programmes on one cassette. MATCH CARDS is a concentration type game where you match numbers, letters or graphic shapes. For one or two players. Automatic scoring rates your recall ability. BANKSHOT is a billiard game where those who think they know all angles, kick the ball into the pocket, but you must hit a wall first. (Cassette) ..... \$11.95

### FASTGAMMON (TM)

As described in Sorcerer Software, but made for TRS80 or System 80. (Cassette) ..... \$21.95

### DEBAG

As described in Sorcerer Software, but made for TRS80 or System 80. (Cassette) ..... \$15.95

### LOWBALL POKER

How low can you go? It's you against Micro Molly and the lowest hand wins. Don't take her for granted - Molly plays an excellent game. (Cassette) ..... \$12.95

### COMPUTER SOFTWARE

All with complete documentation, and fully guaranteed.

### SORCERER SOFTWARE

All top quality from leading U.S. supplier. Full documentation supplied with each software package - and very economically priced.

### NIKE II

The object is to destroy enemy bombers by firing missiles at them. If you miss a bomber, they bomb your factories and return for a second pass. 9 levels of play. (Cassette) ..... \$12.95

### MARTIAN INVADERS

Similar to "Space Invaders". Can you hold out against an invasion from Mars? Zap all the members of the landing party and another group comes after you. The longer you hold out the higher your score. (Cassette) ..... \$15.95

### DEBAG

Debug machine language programs by stepping through one instruction at a time. Relocatable. Several display options. (Cassette) ..... \$15.95

### TANKTRAP

A rampaging tank tries to run you down. You are a combat engineer, building concrete barriers in an effort to contain the tank. Four levels of play. (Cassette) ..... \$12.95

### MAGIC MAZE

A challenging maze game. Holding your lantern, you wander through a maze trying to avoid pitfalls and stay on the right path. 10 levels and automatic scoring. (Cassette) ..... \$12.95



# Lab Notes

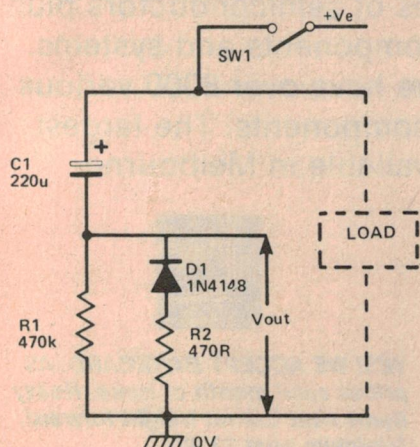


Figure 14. A basic variant of the Figure 12 circuit.

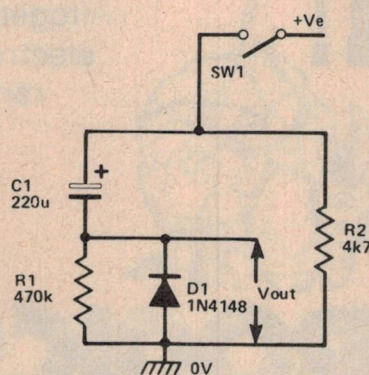


Figure 15. A basic variant of the Figure 13 circuit.

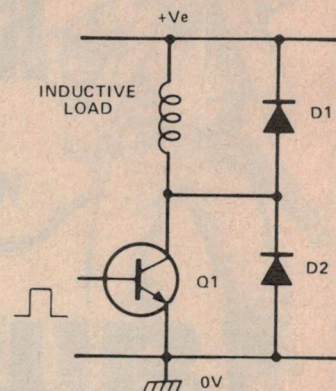


Figure 16. An example of the use of diodes to protect a pulse-driven common emitter amplifier with an inductive collector load.

If there is a low-impedance load in parallel with the C-R network a current-limiting resistor must be wired in series with the discharge diode, as shown in Figure 12. If there is no load in parallel with the C-R network then an artificial load must be provided to complete the discharge path, as shown in Figure 13.

Figures 14 and 15 show two basic variations of the above circuits in which the C and R networks are configured to give a falling output voltage across R1.

Finally, Figures 16 and 17 show ways of using diodes to protect two types of transistor circuit from destructive damage. Figure 16 shows how to protect a pulse-driven common-emitter ampli-

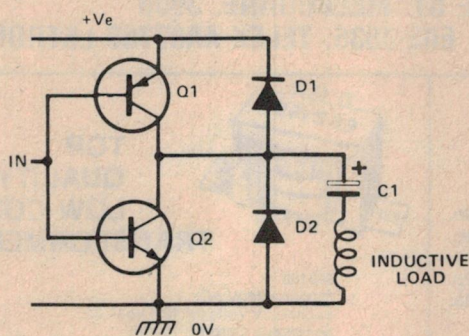


Figure 17. An example of the use of diodes to protect the complementary emitter follower output stage of a power amplifier that is used to drive an inductive load.

fier that has a highly inductive collector load, such as a transformer or a relay coil. Very high back EMFs can be generated by inductive loads and can easily


destroy transistor junctions. In the diagram D1 prevents the collector of Q1 from being driven above the positive supply rail value by these back EMFs and D2 prevents it from being driven negative.

Figure 17 shows how a similar type of protection can be given to the complementary emitter follower output stages of a power amplifier used to drive highly inductive loads. This circuit can give good protection to hi-fi amplifiers in which the speakers may be inadvertently plugged in at a moment when the amplifier is being hard driven. The protection diodes must have a current rating that is compatible with the inductive (speaker) load.
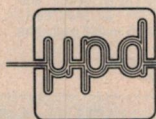
## SWITCHING POWER SUPPLIES


The California DC range of switching regulated power supplies is now available in Australia. The LR Series of open frame supplies provide size and weight savings over linear, series regulated supplies. Conservatively rated for long life, the LR Series was designed for use in computers, computer peripherals and industrial controls. They provide power for floppies, tape drives, memories and microprocessors. The range includes versions with up to four independent output voltages.

The power supplies range in price from \$170 to \$330.



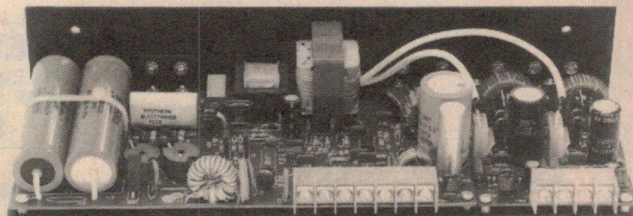**MicroPro Design Pty. Ltd.**

PO Box 153, North Sydney, NSW 2060. Phone (02) 438-1220.



### Standard features include:

- Plus/Minus 20 percent line tolerance
- Inrush limiting on turn-on
- Individual output regulation of 1 percent
- Individual output current limiting with foldback
- Thermal protection
- 50 millivolt P-P output ripple and noise
- 0-40 degrees C convection cooling without derating
- 70 percent minimum efficiency at full load





# STRIKE IT RICH!

WITH

# ELLISTRONICS

289 LATROBE ST. MELBOURNE. 3000  
PHONE (03) 602-3282, 602-3836. TELEX AA37758 LSTRON.

**FREE ELECTRONIC GIFT PACK (VALUE APPROX. \$10.00) LIMIT ONE PER CUSTOMER.**

Ellistronics now stock in excess of 2000 different types of semiconductors plus computer components and systems. Altogether we have over 8000 various electronic components. The largest range available in Melbourne



**YES! WE ACCEPT BANKCARD. All prices valid month of issue. Heavy items sent Comet freight forward. Minimum post \$3.00.**

All prices in this advertisement are tax included. Exempt prices on application.

## SUPER SPECIALS

2114.450Ns 1 to 7 .....	\$3.80 ea.
8 to 31 .....	\$3.70 ea.
32 up .....	\$3.60 ea.
2716.5v Single Supply .....	\$16.75 ea.
4116 .....	\$6.95 ea.

## FLOPPY DISC CONTROLLERS

FD 1771 .....	\$37.00 ea.
FD 1791 .....	\$62.00 ea.
FD 1793 .....	\$62.00 ea.

## MEMORIES


2758 1k x 8 5v Supply .....	\$12.50 ea.
2716 Ceramic 5v Supply .....	\$22.00 ea.
2732 .....	\$66.00 ea.
MB 8414 (2114 CMOS 250ns) .....	\$21.00 ea.
65 x 08 1k x 8 CMOS .....	\$9.00 ea.

## 8 BIT MPU'S

6802 .....	\$11.80 ea.
6808 .....	\$10.50 ea.
6809 .....	\$46.77 ea.
6821 .....	\$5.10 ea.
6840 .....	\$7.84 ea.
6845 .....	\$38.94 ea.
6847 .....	\$28.00 ea.
6850 .....	\$4.40 ea.
6852 (\$5.50) .....	\$5.50 ea.

Expansion Kit .....	\$64.00 ea.
Z80 .....	\$14.82 ea.
Z80A .....	\$14.40 ea.
Z80CTC .....	\$9.49 ea.
Z80A CTC .....	\$11.44 ea.
Z80 PIO .....	\$9.49 ea.
Z80A PIO .....	\$11.44 ea.
4116 200ns .....	\$8.26 ea.

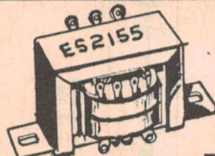ABOVE PRICES PLUS 15 PERCENT SALES TAX IF APPLICABLE.



## TOP QUALITY LOW COST TRANSFORMERS

**R-2150**  
Primary: 240V AC.  
Secondary Voltage: 12.6 volts CT.  
Secondary Current: 150mA.  
Termination: Flying leads.  
**\$3.80 ea. 10 up \$3.34 ea.**

**R-2155**  
Primary: 240V AC.  
Tapped Secondary Voltages: 6.3, 7.5, 8.5, 9.5, 12.6, 15.

Secondary Current: 1 amp.  
Termination: Solder lugs on transformer.  
**\$5.75 ea. 10 up \$5.06 ea.**

**R-6672**  
Primary: 240V AC.  
Tapped Secondary Voltages: 15, 17.5, 20, 24, 27.5, 30.

Secondary Current: 1 amp.  
Termination: Solder lugs.  
**\$7.48 ea. 10 up \$6.44 ea.**

## EXTRA SPECIAL

50 Electrolytic Capacitors from 1 uF to 4.700 uF.

**\$3.00 per pack.**




## DIAL DESK TELEPHONE

Only \$8.50 each.  
2 for \$16.

**\$2000 8" (200mm) wide range general purpose.**  
Includes transformer, mounting holes for P.A. and background use. Very smooth over-all response 45 Hz-12 KHz. Fitted to a 1.9 cubic ft vented enclosure they sound unbelievable.  
8 Ohm 8 Watt RMS 5.6 oz magnet.  
**\$6.00 TRADE, \$6.95 inc. tax**


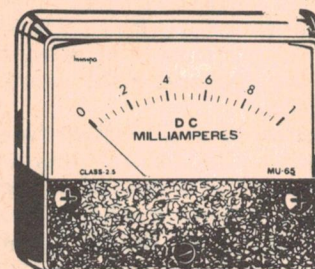
## DIRECT IMPORT PANEL METERS AT LOW, LOW PRICES



**MU-65** 1MA — 120 ohms  
100uA — 140 ohms

Dimensions: Overall — 100mm(W) x 82mm(H)  
Scale — 100mm(W) x 50mm(H)  
Mounting: Hole required — 63mm  
Bolts centres — 80mm(W) x 64mm(H)  
Nuts and washers provided

**\$10-\$18 ea. plus \$1.52 tax**



**MU-45**  
O-1MA-120 ohms  
O-50UA-140 ohms  
O-5ADC-3 Shunt  
O-20VDC-100 ohms

**\$6.91 ea. plus \$1.04 tax**

## MU-45 VU METER

VU (0dB equals 1mW into 600ohms)  
— 1,000ohm

**\$7.93 ea. plus \$1.11 tax**

## MU-45 DIMENSIONS

Overall — 58mm(W) x 52mm(H)  
Scale — 58mm(W) x 31mm(H)  
Hole required — 44mm  
Bolt centres — 38mm(W) x 38mm(H)  
Nuts and washers provided  
10 or more less 10 percent





**\$9.75 ea.**

### AUSTRALIAN MADE WELLER SP25D MARKSMAN

Mains voltage constant heat 25 watt with 5/32 tip (lightweight 185 grams). Made in Australia Weller gives you better value in soldering irons than most imported irons. Fully guaranteed.

**SPECIAL FOR THIS MONTH AT ONLY \$54.95 ea.**

### WELLER WTCPN SERIES

#### LOW VOLTAGE, TEMPERATURE CONTROLLED SOLDERING STATION


A transformer powered soldering station, complete with a low voltage, temperature controlled soldering pencil. The special Weller "closed loop" method of controlling maximum tip temperature is employed, thereby protecting temperature sensitive components while the grounded tip protects voltage and current sensitive components. The soldering pencil features a stainless steel heater construction, a non-burning silicon rubber cord and a large selection of iron plated tips in sizes from .8 mm diameter to 6 mm diameter with a choice of tip temperature of 600°F/315°C, 700°F/370°C and 800°F/430°C.

A redesigned transformer case features an impact-resistant noryl for durability and protection against accidental damage, a quick connect/disconnect plug for the soldering iron, extra large wiping sponge, tip tray to store extra tips, plus an improved off-on switch with a long-life neon indicator light, a non-heat sinking soldering pencil holder and a 2 m flexible 3-wire power cord.


The soldering iron is normally provided with a PTA7-1.6 mm screwdriver 700°F/370°C tip.
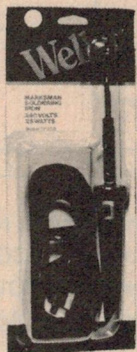
#### SPECIFICATIONS

**Power Unit** • Power input 240 Volts 50 Hz 60 Watts Int. • Transformer Output Voltage — 24 Volts (Full Load) • Power Unit Size — 113mm x 187.3mm x 92mm • 2 Metres, 3 Wire Power Cord.  
**Soldering Pencil** • Soldering Pencil Wattage — 48 Watts • Tip Voltage \*To Ground .01 Volts P-P • Pencil Weight — 50 gram (W/O Cord) • Recovery Time (From 100°F Drop) W/PTA7 Tip = 11 Sec.



### Hitachi V-302

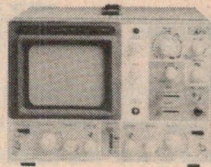

### Hitachi Oscilloscope V-302 DC-30MHz dual-trace

1. TV sync-separator circuit
2. High-sensitivity 1 mV/div (5MHz)
3. Signal delay time
4. X-Y operation
5. Sweep-time magnifier (10 times)
6. Trace rotation
7. Z-axis input (Intensity modulation)

**\$880 plus 15 percent tax if applicable**

### CS-1560AII

130 mm DUAL-TRACE

15 MHz, TRIGGERED SWEEP OSCILLOSCOPE

**SPECIAL PRICE \$520  
plus 15 percent tax**


- Bandwidth DC ~ 15 MHz
- Sensitivity 10 mV/div
- Sweep Time 0.5 μs/div ~ 0.5 s/div



### V152 15 MHz DUAL TRACE

TV sync-separator circuit  
High-sensitivity 1 mV/div (5MHz)  
X-Y operation  
Sweep time magnifier (10 times)  
Trace rotation  
Z-axis input (intensity modulation)

**\$560 plus 15 percent tax**

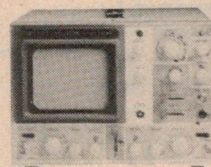


### SG-402 TRIO

RF SIGNAL GENERATOR

- Freq. Range 100 kHz ~ 30 MHz
- Output Voltage 0.1 V<sub>r.m.s.</sub>
- Modulation Method AM (internal and external)

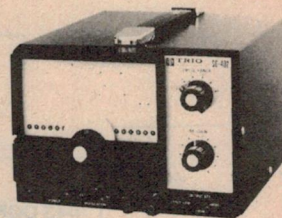**\$105 plus 15 percent tax if applicable**



### CO-1303D TRIO

5 MHz, 75 mm OSCILLOSCOPE

- Bandwidth DC ~ 5 MHz
- Sensitivity 10 mV/div
- Sweep Freq. 10 Hz ~ 100 kHz

**\$245 plus 15 percent tax**

**\$2010** PVC weatherproof re-entrant horn/speaker. Very attractive "off white" colour. 8 ohm 5 Watt RMS. Ideal P.A. use. Individually boxed.



**SPECIAL PRICE \$5.95 ea.  
exempt  
\$6.84 inc. tax**

Ellistronics are direct distributors for Weller, Hitachi and Trio. For quantity discounts etc. ask for Trade Division. If we are not No. 1 now, we soon will be.

### TRIO

- Simplified circuitry improved performance and dependability have been successfully realized with the use of ICs throughout
- A vertical amplifier provides as wide a bandwidth as DC to 15 MHz, as high a sensitivity as 10 mV/div, and a low input capacitance
- A sweep rate extends from 0.5 μsec/div to 0.5 sec/div in 19 ranges. Further, TV vertical and horizontal syncs are available for measuring video signals and, with its x5 magnified sweep, its range of application is extremely wide
- Very easy X-Y operation of high input sensitivity for Lissajous measurements
- Dimensions: 260(W) x 190(H) x 385(D) mm, Weight: 8.4 kg

### CS-1570A TRIO \$855 plus 15 percent tax

130 mm DUAL-TRACE

30 MHz, TRIGGERED SWEEP OSCILLOSCOPE

- Bandwidth DC ~ 30 MHz
- Sensitivity 5 mV/div
- Sweep Time 0.2 μs/div ~ 0.5 s/div






# ETI
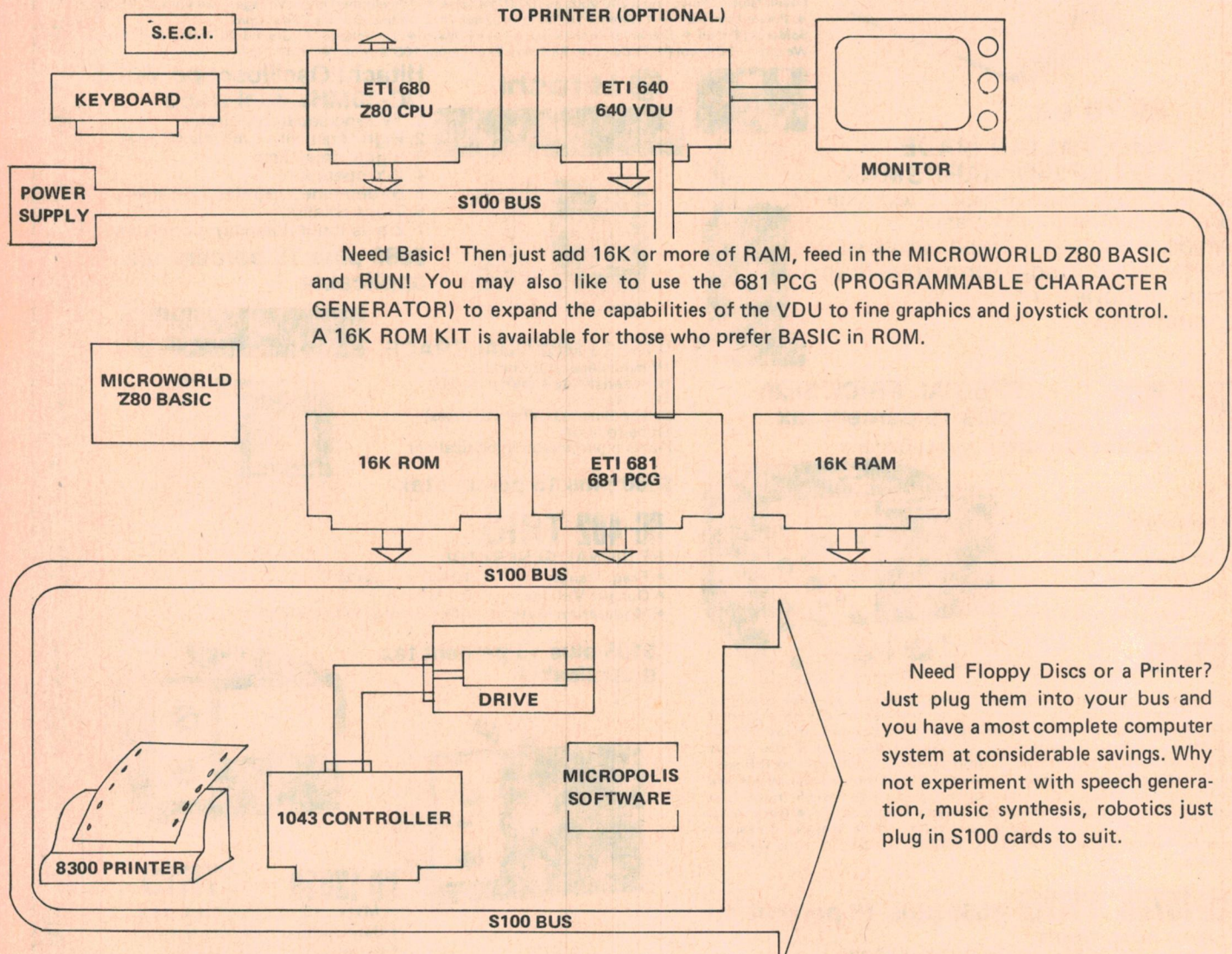
## S100/Z80 MICRO COMPUTER SYSTEM

- ★ LEARN AS YOU BUILD
- ★ START SMALL E-X-P-A-N-D LATER
- ★ AFFORDABLE - FLEXIBLE

Build up your own Z80 based home computer based on the DGZ80 described in ETI 1979. Designed by David Griffiths this is probably the most powerful S100/Z80 project described in the world to date. The big advantage of starting with the S100 bus is the flexibility. No need to pay \$400-500 for an expansion interface. Just plug in otherboards to suit your requirements. A suggested starting system is described below and is supplied with sample programs and full documentation to enable you to learn the basics of microprocessors.



KB05 Economy Keyboard	\$89.50
CLARE. C70/MGP microprocessor controlled keyboard	\$165.00
DGZ80 S100 computer board complete kit (fully socketed)	\$199.25
Assembled and Tested	\$240.00
DGOS ROM — operating system, single 5v EPROM	\$40.00
DG640 VDU Kit	\$139.50
Assembled and Tested	\$149.50
MONITOR — Converted TV for direct video	\$149.50
TCT 16k RAM (2114 RAM) Complete kit	\$285.00
Kit less RAMS/SOCKETS	\$100.00
ETI 681 PCG as described in ETI June 1980 — kit	\$140.00

TCT 16K ROM complete kit for up to 16K of EPROMS (less EPROMS)	\$105.00
Z80 BASIC — 11K Microworld basic on tape if purchased with DGZ80 (kit or assembled & tested)	\$10.00
If purchased separately	\$32.00
8300 printer with RS232 connects direct to DGZ80	\$915.00
MICROPOLIS 1043 QUAD DENSITY DISC CONTROLLER with drive, power supply and software package	\$1350.00
SECI. Kansas City Cassette Interface Kit	\$24.50
S100 Mother Board plated through with active termination	\$49.50
Card Frame with professional finish	\$49.50

NOTE — Prices include Sales Tax. Contact office for availability of Tax Exempt pricing.




**MAIL ORDERS TO:**  
PO Box 311, Hornsby 2077.  
Please add \$2.00 per order  
towards cost of post and packing.

**OFFICE/SHOWROOM:**  
1a Pattison Avenue, Waitara 2077.  
Hours: 9-5 Monday to Saturday.  
Telephone: 487-2711.



## Scratch and rumble filter

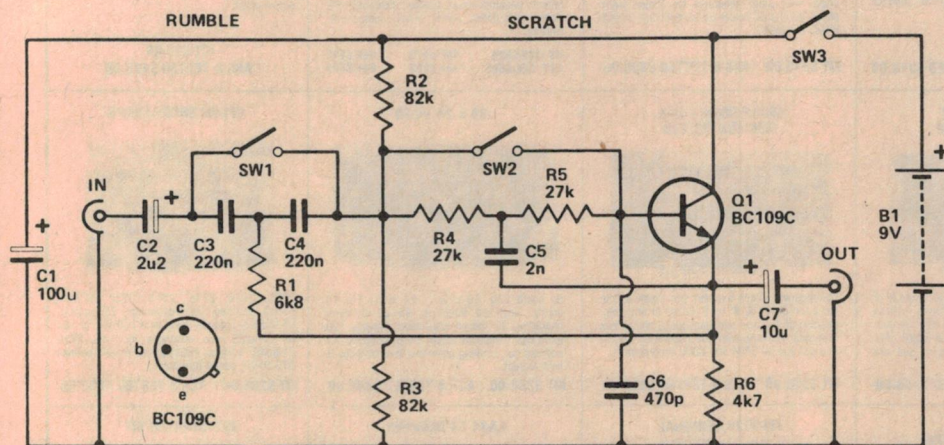

**Circuit of the Scratch and Rumble filter.** This unit may be mounted on matrix board and mounted inside your amplifier — don't forget two will be needed for stereo. If you construct it as an out-board unit it should be mounted in a metal box and connected into your amplifier system with short lengths of shielded cable. It may be connected between the "preamp out" and "main in" sockets.

SCRATCH AND RUMBLE filtering is a valuable feature in a hi-fi amplifier but is one which is absent from many designs, or if this filtering is present it may well be in the form of a relatively ineffective 6 dB per octave type filter. This circuit is a 12 dB per octave add-on scratch and rumble filter which can be connected into the 'tape monitor' circuit or some similar facility of the amplifier.

This is a conventional second order filter circuit having passive high pass filter formed by the series capacitance C3 and C4, plus the parallel resistance of R2 and R3 (the latter also being used to bias emitter follower transistor Q1). A passive filter of this type gives only a very slow initial roll off and an ultimate attenuation rate of only 6 dB per octave. A bootstrapping resistor is therefore used to improve performance.

Above the cutoff frequency, where the gain of the circuit would otherwise fall off somewhat, R1 has the effect of reinforcing the input signal from the output of the buffer amplifier based on Q1. Well below the cutoff frequency, losses through C4 result in the signal level at Q1 emitter being well below that at the junction of C3 and C4. This results in some of the signal at the junction of C3 and C4 being tapped off through R1, with C3 and R1 effectively forming a second high pass filter network. This eliminates the slow initial roll off rate (in fact there is a small and insignificant peak of about 0.5 dB above

the cutoff frequency) and speeds up the attenuation rate to a nominal 12 dB per octave.

The low pass filter works in much the same way as the high pass one, except of course the R and C filter elements have been transposed so as to give the correct filter action.

If only low pass filtering is required, SW1 can be used effectively to bypass the high pass filter components. C2 then maintains dc blocking at the input. SW2 can be used to bypass the low pass filter components when only high pass filtering is required.

With the specified component values the rumble filter response falls below unity at approximately 45 Hz, reaches the -6 dB point just above 30 Hz and then falls away at a nominal 12 dB per octave. The scratch filter response crosses the unity gain point at about 6.5 kHz, reaches the -6 dB point at approximately 10 kHz, and then falls away at a nominal 12 dB per octave. The worst-case input impedance is around 30 k to 40 k with SW1 and SW2 closed.

A BC549 or similar transistor may also be used for Q1. The circuit should be housed in a shielded enclosure to avoid hum pickup. Use shielded input and output leads. A dual circuit, with two-pole switches for SW1 and SW2, is necessary for stereo operation. ●


# ATTENTION! TRS-80 OWNERS

# SALE OF CENTRONICS 779 PRINTERS

**60 CHARACTERS PER SECOND  
FULL 132 COLUMN PRINT ABILITY  
96 CHARACTER ASCII SET**

Ring now

**92 97699**

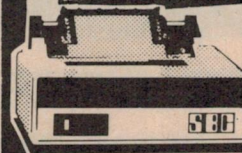

NEW OR  
USED FROM

**\$850**

## SMALL BUSINESS COMPUTER CO.

200 Pacific Highway, Crows Nest.

SB403/281



# 'THE S100 BUS STOP' <sup>TM</sup>

## SBC200



Z80 single board computer, 4MHz, 16K EPROM, 1K RAM, 16K EPROM, 1 serial port, 1 input & 1 output parallel port, power on jump, 2K monitor/2716 4 channel counter/timer, software controlled baud rate generator, modem look alike, vectored interrupt

KIT \$360.00 ASS & TESTED \$440.00


## MPB100



Z80 CPU board, switchable 2 or 4 MHz operation, power on jump to any 4K boundary, on board 2716 PROM socket, optional front panel provision, wait state generator, 2K monitor available, will suit dynamic RAMs.

KIT \$260.00 ASS & TESTED \$310.00

## 16K STATIC RAM

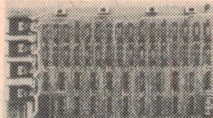

2114 low power RAM chips, 4K address boundary, standard bank select (40H) 4 MHz operation with no wait state required when using our chips, wait state generator for above 4MHz, plated thru holes, solder resist, optional 300nS RAMs available.

KIT \$315.00 ASS & TESTED \$380.00

## 32-64K DYNAMIC RAM



Bank select, 200 nS chips standard up to 4MHz speed, will accept 64K RAMs to give 256K per board, switch selectable boundaries, invisible refresh, phantom output disable, standard S100, plated thru holes, solder resist, components overlay.

KIT 32K-\$525 48K-\$670 64K-\$815  
A&T 32K-\$605 48K-\$750 64K-\$895

## 2708 EPROM



Switch selectable as 8 or 16K card 8K address boundary, wait state gen. suites industry standard 2708's standard S100, plated thru holes, solder resist.

KIT \$98.00  
ASS & TESTED \$125.00


## SERIAL-PARALLEL I/O PORT



Dual serial ports with RS232 & TTY outputs, nine programmable parallel ports, wire wrap cross link area for parallel I/O, switch selected baud rates, 9600-75 baud, 4 byte address decoding for I/O, switch selected, plated thru holes, solder resist.

KIT \$189.00 ASS & TESTED \$225.00

## SINGLE DENSITY DISK CONTROLLER

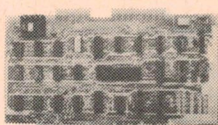

IBM 3740 soft sectored, operates standard 8" or 5" drives, single or double sided drives, utilizes FD1771 controller chip, runs CP/M disk opp software, operates with Z80, 8085 & 8080 CPU, CP/M, BIOS & diagnostic proms to suit are available.

KIT \$258.00 ASS & TESTED \$308.00

## SINGLE/DOUBLE DEN. DISK CONTROLLER



Operates with single & double den. single & double sided drives & 8" or 5" drives in any combination of 4 drives simultaneously, phase lock loop data recovery, with SDOS operating system you can run all CP/M and CDOS programmes.

KIT \$360.00 ASS & TESTED \$420.00

## 80 x 24 VIDEO



On board Z80, 80 char. x 24 lines, 7 x 10 matrix, adjustable line and character spacing, 32 special characters, optional 128 extra char composite video, for/rev scrolling, XY address cur, blinking underline reverse video & field protect.

KIT \$380.00 ASS & TESTED \$450.00

## EPROM PROGRAMMER



2708, 2758, 2716, 2516, 2732 EPROMs switch selected, 26V generator, ZIF socket, CP/M driver program, max. time 100 sec for 16K bit EPROMs mod. available for TMS 2716 EPROMs, optional PROM based driver routines STD S100, plated thru holes.

KIT \$205.00 ASS & TESTED \$255.00

## EXTENDER/TERMINATOR



True active termination, fuse prot. supply rails to extension socket, numbered test points, reset line (75) not terminated, solder resist, plated thru holes, standard S100 D.I.L. resistor packs, this board is a must for reliable operation.

KIT \$85.00 ASS & TESTED \$105.00

## WIRE WRAP PROTOTYPING BOARD



Now with plated thru holes, GND & supply rails on both sides, +5V +12V & -12V regulator provision, Hole array is .1 x .3 to suit all IC package sizes, provision for filter bypass caps, 5V reg is T03.

BOARD ONLY \$38.50


## TVI-912B TERMINAL



80 x 24 intelligent terminal, 2 page screen, printer port, dual intensity upper/lower case, 110-9600 baud, numeric pad, cursor control, XY curs block mode, self test, micro based lear siegler ADM31 look alike, full editing capabilities.

\$1295.00


## LA34 34 DECwriter

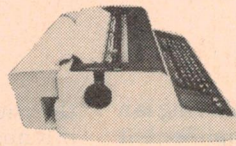

30 CPS, 128 char. set 110-300 baud 9 x 7 dot matrix, adjustable line and character spacing, opt. numeric keypad, light weight (13Ks), STD RS 232 serial com., opt. tractor feed, & paper roll holder, comes with friction feed as standard.

STANDARD VERSION \$1595.00


## Z80 STARTER KIT

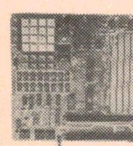

Onboard keyboard & HEX display, Kansas City cassette, PROM programmer S100 interface, 2K RAM, 4K PROM, 2K monitor, CTC timer, interrupts, 2 x 8 bit ports, wire wrap area, 120 page manual, single 5V supply, single step, breakpoints.

KIT \$350.00 ASS & TESTED \$420.00


## S-100 & 6800 CHASSIS

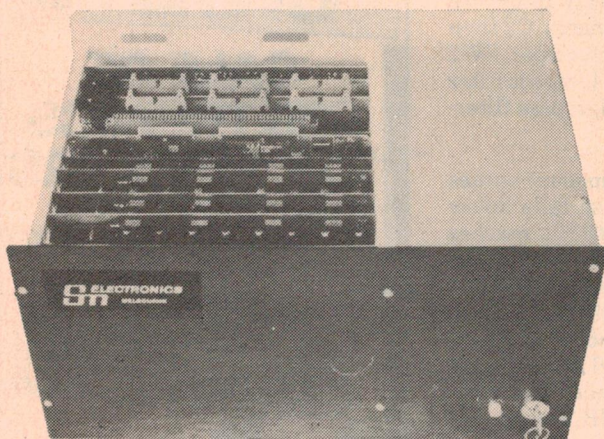

11 slot backplane, fully card guided, 15 amp power supply, fan, key switch, bench mount, rack mount, anodised aluminium, 5 edge connectors standard. S-100 Bench Kit \$345. S-100 Rack Kit \$306. 6800 Bench Kit \$370.00. 6800 Rack Kit \$330. Assembled prices add \$100.
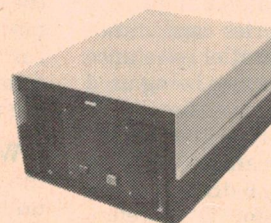
## PMS100

Introducing the PMS100 by SME Systems, an all new package microcomputer based on a Z80 CPU. This system will suit all users ranging from computer technicians, programmers and small to medium company accounting requirements.



Technical specifications are as follows:

4 Mhz Z80 CPU, 64K Dynamic memory with bank select to allow up to 8 pages of 64K each, and up to 256K of RAM on a single board, RS232 serial port and 8 bit parallel ports. Up to 16K EPROM which can be switched out after power up to allow a full 64K of user RAM per bank. Dual 8" SHUGART SABOIR drives running at single or double density. Density selection is automatically chosen by the use of double or single density formatted disks. External Mini drives can also be interfaced to the controller. The DOS supplied is compatible with standard CP/M and CDOS to allow a wide selection of software to be used, such as MBASIC, CBASIC, COBOL, ALGOL, PASCAL, FORTRAN, ASSEMBLY LANGUAGE, WORD PROCESSING, MULTIUSER, MULTITASKING, AND ACCOUNTING PACKAGES. All of which can be supplied from SME Systems.

The PMS100 is AUSTRALIAN designed and built and can be supplied as a basic system or as a complete turnkey system including terminal, printer and software.

**Sm ELECTRONICS**  
MELBOURNE  
Ph (03) 842-3666  
Trading hours: 10am-6pm Mon to Fri.

1096 Doncaster Rd. Doncaster East, Vic 3109.  
PO Box 19, Doncaster East, 3109. Telex AA37213.  
DEALER: Canberra - 81-5011. Sydney - 661-9237.

Send 66c in stamps for COMPUTER PRINTOUT CATALOGUE for more details.

ALL PRODUCTS AUSTRALIAN MADE AND EX STOCK (ALMOST).  
DEALER ENQUIRIES WELCOME.  
Prices and specs. subject to change without notice.

All prices tax free, for retail prices add 15 per cent.

**bankcard**  
welcome here

Give name, number, expiry date and signature for mail order sales.



## AC range booster for your multimeter

MEASURING small audio frequency signals is often impossible using an ordinary multimeter because most of these have a lowest ac range of about 1 V to 5 V full-scale deflection (fsd). A simple and inexpensive solution to the problem is to add an amplifier, such as the one shown here, ahead of the multimeter.

The amplifier has a switched voltage gain of 10 or 100 and would therefore boost the sensitivity of (say) a multimeter switched to the 2.5 Vac range to 250 mV and 25 mV fsd respectively. Measurements down to just a few millivolts rms can then be made with reasonable accuracy.

The circuit uses a CA3130T operational amplifier in the non-inverting mode. The non-inverting input is biased to about half the supply voltage by R1 and R2 and the input signal is coupled to this point by C1. The input impedance of


the circuit is set at over 1 M by R1 and R2 so that the unit places little loading on the circuit under test. R7 biases the inverting input and gives a quiescent output voltage of about half the supply potential.

Although IC1 has an extremely high (open loop) voltage gain, the voltage gain of the amplifier as a whole (closed loop) is much lower, and is set by the ratio of two resistances. With SW1 in the x10 position the two resistances are R7, and R3 plus R4. The voltage gain is equal to the sum of the two resistances divided by the shunt resistance (R3 + R4) in this negative feedback network. This gives almost exactly the required figure of 10 with the specified values. With SW1 in the x100 position the lesser shunt resistance of R5 and R6 is switched into circuit, boosting the voltage gain to almost exactly 100.

Capacitor C4 provides dc blocking at



the output. C5 is a supply decoupling capacitor and should be mounted physically close to IC1, C3 is the compensation capacitor for IC1 and prevents the device from becoming unstable. Note that a carefully designed layout having the input and output well isolated from one another is required or the circuit as a whole may become unstable.

Screened input and output cables should be used to prevent stray signal pickup affecting the signals. The unit has a maximum output of about 3 V rms. It should therefore be used with the multimeter set to a range of 3 V or less, or if a higher range must be used, the part of the scale above 3 V is ignored. The amplifier has a flat response up to about 30 kHz in the x100 mode, and up to about 300 kHz in the x10 mode.

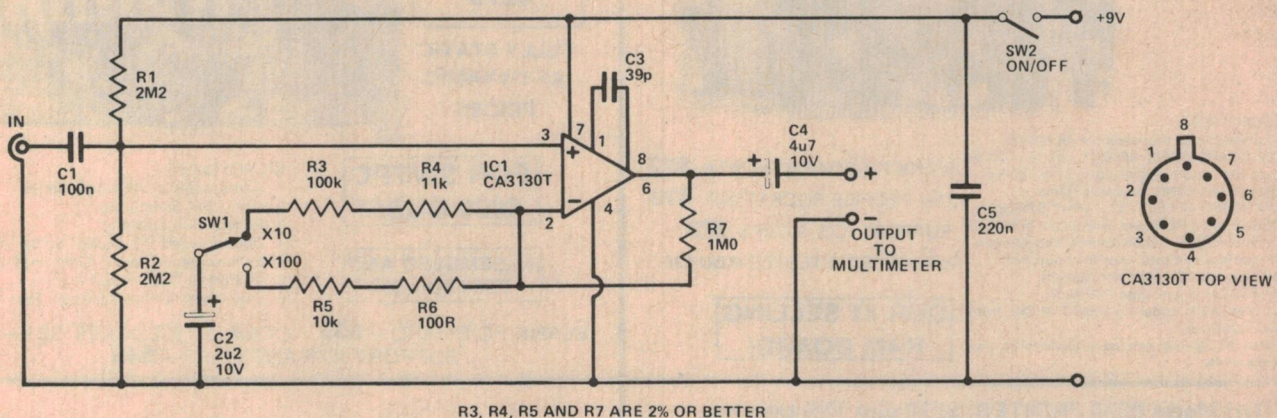



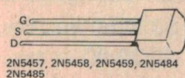
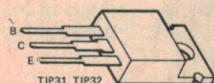
### COMMON SEMICONDUCTOR PIN-OUTS

(Cut this out, attach to strong card and stick it to your workshop wall)



LEADS ARE CLOSER TO THIS END OF THE PACKAGE

2N555, 3055 POWER TRANSISTORS

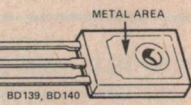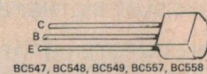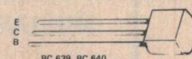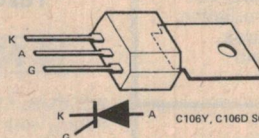




# ROD IRVING ELECTRONICS

425 HIGH STREET, NORTHCOTE 3070, MELBOURNE, VICTORIA.

## \$100 COMPUTER PRODUCTS

### 16K EPROM CARD-S 100 BUSS

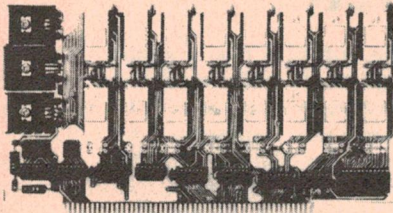

**\$89.50  
KIT**

**FIRST TIME OFFERED!  
BLANK PC BOARD - \$39**


**USES 2708's!**

Thousands of personal and business systems around the world use this board with complete satisfaction. Puts 16K of software on line at **ALL TIMES!** Kit features a top quality soldermasked and silk-screened PC board and first run parts and sockets. Any number of EPROM locations may be disabled to avoid any memory conflicts. Fully buffered and has WAIT STATE capabilities.

**OUR 450 NS 2708'S  
ARE \$8.95 EA. WITH  
PURCHASE OF KIT**

**ASSEMBLED  
AND FULLY TESTED  
ADD \$36**

### 8K LOW POWER RAM KIT-S 100 BUSS SALE

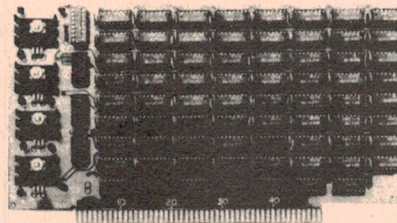

**PRICE  
CUT!**

**\$159.50**

**21L02  
(450 NS RAMS!)**

Thousands of computer systems rely on this rugged, work horse, RAM board. Designed for error-free, NO HASSLE, systems use.

Blank PC Board w/Documentation

**\$44**

Low Profile Socket Set...**13.50**

Support IC's (TTL & Regulators)

**\$13**

Bypass CAP's (Disc & Tantalums)


**77**

**ASSEMBLED AND FULLY  
BURNED IN ADD \$45**

**ALL ASSEMBLED BOARDS  
ARE TESTED AT 4MHZ.**

### 16K STATIC RAM KIT-S 100 BUSS

**KIT \$249  
A&T \$279**

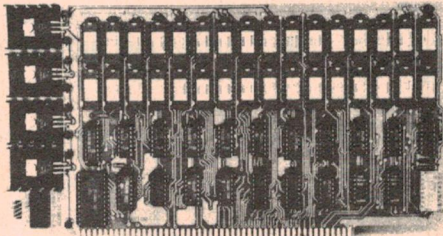

#### KIT FEATURES:

1. Addressable as four separate 4K Blocks
2. ON BOARD BANK SELECT circuitry. (Cromemco Standard!). Allows up to 512K on line!
3. Uses 2114 (450NS) 4K Static Rams.
4. ON BOARD SELECTABLE WAIT STATES.
5. Double sided PC Board, with solder mask and silk screened layout. Gold plated contact fingers
6. All address and data lines fully buffered.
7. Kit includes ALL parts and sockets
8. PHANTOM is jumpered to PIN 67.
9. LOW POWER: under 1.5 amps TYPICAL from the +8 Volt Buss.
10. Blank PC Board can be populated as any multiple of 4K.

BLANK PC BOARD W/DATA **\$49**

LOW PROFILE SOCKET SET **\$19**

SUPPORT IC'S & CAPS- **\$27**

ASSEMBLED & TESTED-ADD **\$30**


**OUR #1 SELLING  
RAM BOARD!**

### 16K STATIC RAM SS-50 BUSS

**PRICE CUT!**

**\$279**

**FULLY STATIC  
AT DYNAMIC  
PRICES**

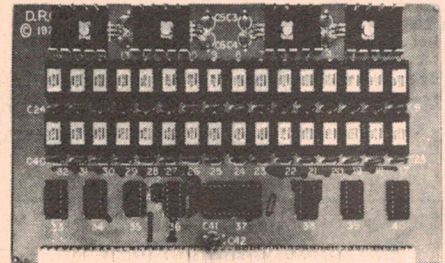

**FOR SWTPC  
6800 BUSS!**

**ASSEMBLED AND  
TESTED - \$30**

#### KIT FEATURES:

1. Addressable on 16K Boundaries
2. Uses 2114 Static Ram
3. Runs at Full Speed
4. Double sided PC Board Solder mask and silk screened layout. Gold fingers
5. All Parts and Sockets included
6. Low Power: Under 1.5 Amps Typical

BLANK PC BOARD— **\$39** COMPLETE SOCKET SET— **\$19**  
SUPPORT IC'S AND CAPS— **\$45**

### ITOH Model 8300 PRINTER. \$770 plus 15% sales tax.

This 80-column printer provides quiet operation, making it suitable for use in offices, classrooms and homes. Specifications include 125 cps, 60 lines per minute, paper loading from bottom or rear and Centronics-compatible, parallel interface.

A bidirectional, dot matrix impact printer with a print head designed for 100 percent duty operation, assuring a print life that exceeds 100 million characters. The precision sprocket-feed mechanism permits printing forms from 4 1/2 to 9 1/2 inches wide. A 96 ASCII character set prints in upper and lowercase with the added capability of producing double-width fonts in boldface. The vertical format unit provides preprogrammed/ programmable tab positions, top of form and bottom of form for complete formatting capabilities.

RITRON 8 SLOT MOTHERBOARD: KIT \$65.90 inc. tax.  
BUILT & TESTED \$80.00 inc. tax.  
RITRON COMPUTER GRADE POWER SUPPLY: +5V Reg, 10A,  
+16V Unreg. Kit of parts \$79.95 inc. tax. A&T \$99.95 inc. tax.

Write for list of other power supplies. Tax free prices also available.

### JUST WRAP KIT - JWK-6 \$39.50


• 50ft ea. blue, white, red, yellow wire • Just Wrap Tool • Unwrap Tool

Perfect for  
OEM's

### S-100 Z80 CPU CARD

**\$199.00  
Wired &  
Tested**

**4 MHZ**

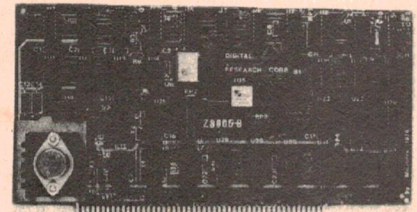

ASSEMBLED AND TESTED! READY TO USE! Over 3 years of design efforts were required to produce a **TRUE** S-100 Z80 CPU at a genuinely bargain price!

**BRAND NEW!**

- FEATURES:
- ★ 2 or 4 MHZ Operation.
  - ★ Generates MWRITE, so no front panel required.
  - ★ Jump on reset capability
  - ★ 8080 Signals emulated for S-100 compatibility
  - ★ Top Quality PCB. Silk Screened. Solder Masked. Gold Plated Contact Fingers

**SHUGART 5" MINI FLOPPY DRIVE: \$379.50 inc. tax.  
\$330.00 ex tax.**

Verbatim Products available. Please write for price lists.

Bankcard  
Mail Orders  
Welcome

Please debit my Bankcard.

Bankcard No. ....

Expiry Date.....

Name.....

Signature.....

General enquiries (03) 489-8131, Mail order enquiries (03) 481-1436. Ritronics Wholesale (03) 489-7099.

Prices current till 7th September, 1980. Heavier items add additional postage. Extra heavy items sent Comet freight on Prices subject to change without notice. Send 60c and SAE for free catalogues. MAIL ORDERS PO Box 135, Northcote, Vic 3070. Minimum pack and post \$1.25.





## The spare hand

A.J. Lowe

THIS IS one of those gadgets that, once you've made it, you'll wonder how you did without it! It is a simple, very cheap circuit board manipulator, used while fitting and soldering components into a pc board or while testing or fault-finding a board.

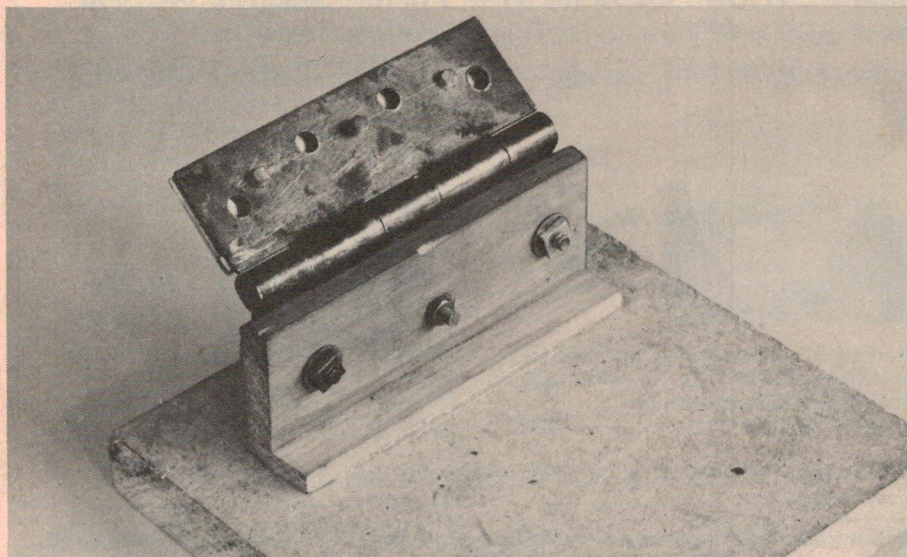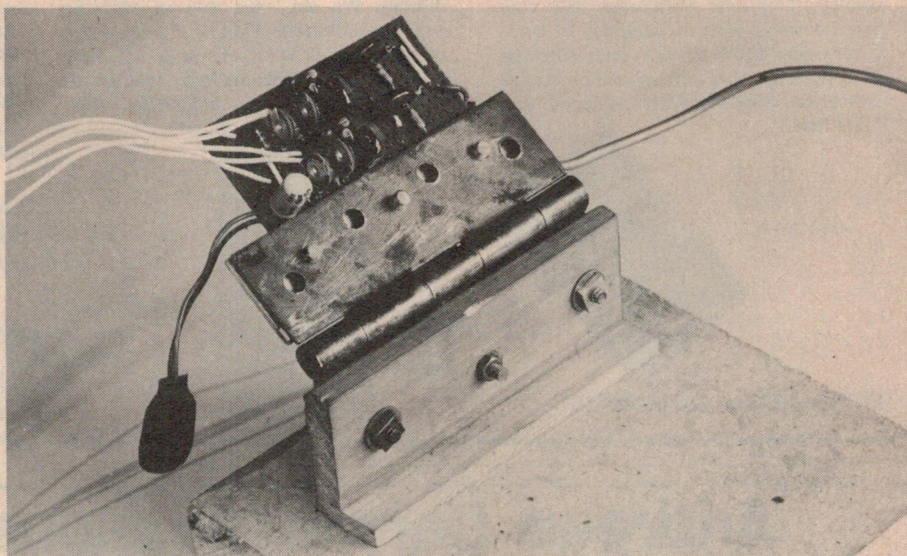The completed Spare Hand with a project securely held and tilted into the 'up' position.



The accompanying photos show the "spare hand" in the up i.e. 'load components' position, and — minus the circuit board, in the down, or 'solder' position.

The base is a 150 x 150 mm block of 20 mm particle board. The support is a strip of 12 mm timber about 45 mm high and 110 mm long. This was glued in the position shown and reinforced a little with a small strip glued alongside.

The top rear edge of the support is chamfered (see the drawing) to accommodate the hinge barrel.


The 'works' is simply a 100 mm butt hinge — the heavier the better, with wings about 35 mm wide (to the centre line of the hinge pin) and a 'gripper'

attached to the moving wing of the hinge by three clamping screws tapped into the wing.

The hinge is affixed to the support by two bolts so that the moving wing can sit firmly on the top of the support in the down position.

The gripper may be a strip of aluminium (that's what I used in the prototype), brass or steel, the same length as the hinge and 28 mm wide — nearly the width of the moving wing. The strip is actually a shallow angle — see the drawing, so that when the three screws are tightened, the gripper pivots on the short arm of the angle and grips along the front edge. The gripper can be cut from angle stock or fabricated from ►

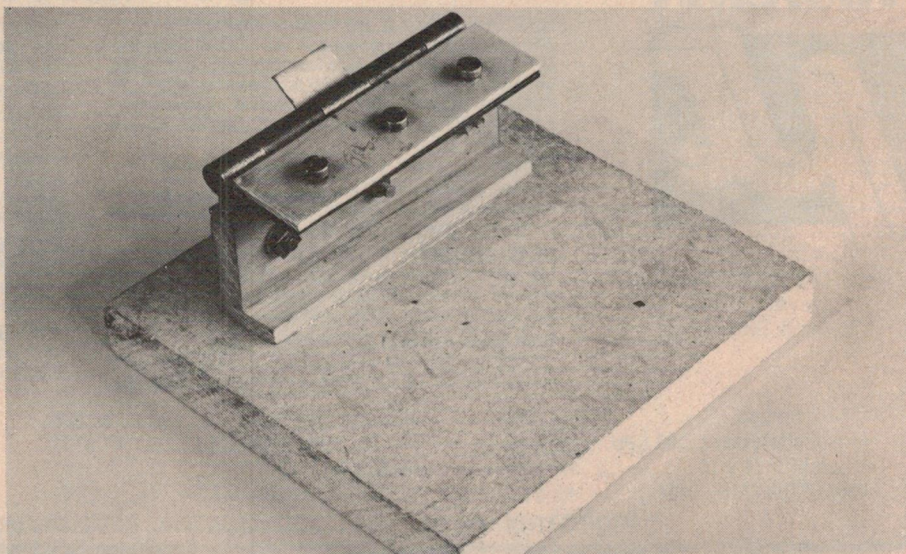General view of the unit in the 'up' position.



General view of the unit in the 'down' position with the 'stop' clearly shown.



## NEW INSTRUMENTS FROM CHRISTIE RAND PTY LTD

**'SANSEI' 2200A DIGITAL MULTIMETER**, with a 3½ digit LCD display. This new Multimeter has now been released, with an accuracy of 0.1% fs for under \$100. Other features include auto polarity, low battery and overrange indication. Supplied with Test Leads and spare fuse.


ONLY  
**\$95**  
+\$14.25 S.T.



MONEY BACK GUARANTEE


**'SANSEI' 2000A DIGITAL MULTIMETER**, with a 3½ digit LCD display. We are now able to offer an AUTO RANGING D.M.M. for the price of a normal D.M.M.. It has an accuracy of 0.1% fs and features low battery warning, and overrange indication. Test leads and spare fuse supplied.

ONLY  
**\$138**  
+\$20.70 S.T.

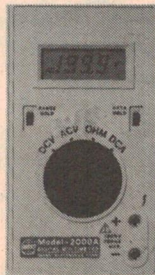

**SABTRONICS 8610 FREQUENCY COUNTER** gives you a first class high stability instrument at the hobbyists price, for a 8 digit counter. FREQUENCY RANGE guaranteed 10Hz to 600MHz (typical 5Hz to 750MHz) with a good sensitivity. Measurement accuracy 1 ppm + 1 digit or 0.0001%. Ageing rate + 5ppm/year, gate times 0.1, 1, 10 secs, Battery operated (not supplied).

ONLY  
**\$181**  
+\$27.15 S.T.

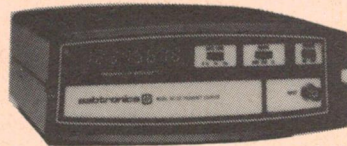

SEND TO:

**CHRISTIE RAND PTY LTD**

P.O. BOX 48, EPPING, 2121. Phone (02) 477- 5494.  
Packing & delivery \$2.00

## Andrews Communications Systems

IMPORTERS OF QUALITY COMMUNICATIONS EQUIPMENT — Ph. (02) 349.5792/344.7880

★ Bearcat ★ Regency ★ Redco ★ DSI ★ RF linear amplifiers ★ RF power transistors

### Bearcat® 220 FB



**\$475**  
20ch.  
(RRP \$567)

All VHF/UHF commercial bands inc. Australian Low Band plus Aircraft band. Searches and Scans AM/FM.

★BC210 .....\$350★Thinscans from \$179

### Regency M.100E scanner



First  
release in  
Australia  
**\$395**  
10ch.


Searches and scans Australian Low Band, High Band and UHF to 512MHz. Touch tone frequency programming.

★M400E 30ch scanner.....\$450

### REDCO FREQUENCY COUNTERS

FM.60 displays to 60MHz .....\$149  
FM.600 displays to 600MHz .....\$225  
FM.600T (TXCO) to 600MHz .....\$295

### NEW KENWOOD R1000 receiver

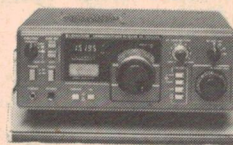


**\$450**  
(RRP \$498)

★D.S.I. 5600AK 600MHz frequency counter.....\$249

SHOP 7, GARDEN ST., MAROUBRA JUNCTION, N.S.W./P.O. BOX 33, KENSINGTON, 2033.

**microtrix**

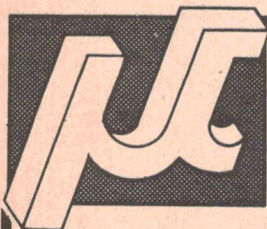

Microprocessor Systems,  
Development,  
Sales & Servicing.

## \$100 PRODUCTS

### SBC 200 SINGLE BOARD COMPUTER

Z-80 based 4 MHz microcomputer with 1K RAM sockets for 8K/16K PROM, synchronous or asynchronous serial I/O port with software programmable baud rate generator, RS232 and interfaces, parallel ports, four channel counter/timer, power-on jump, and vectored interrupt operation. Kit with 2716 PROM \$360.

### VERSAFLOPPY 1 DISK CONTROLLER

Low cost controller will operate with either mini or standard drives, single or double sided, in single density. Operates with CP/M and is Shugart compatible. Kit \$258.

### VERSAFLOPPY 2 DISC CONTROLLER

State-of-the-art controller operates with all combinations of drive types in single or double density modes, and has PLL data recovery circuit. SDOS compatible. Kit \$360.

### EXPANDORAM 2 DYNAMIC RAM

A single dynamic RAM card that will hold 64K! Page mode operation allows the use of up to eight boards for multiuser

applications. Supplied with 200 nS 2116's for 4 MHz operation. Ideal for use with Versafloppy 2 and the SBC200. Kit: 32 K \$525, 48 K \$670, 64 K \$815.

### MPB100 Z-80 CPU

Operation at 2 or 4 MHz, on-board PROM, power-on jump, can be used with or without front panel. Kit \$260.

### PROM100 PROM PROGRAMMER

Capable of programming all popular EPROMs such as 2708, 2758, 2716, and 2732. Zero insertion force socket is standard. Kit \$205.

### MST 16 K STATIC RAM

Uses 2114's with bank select, addressable as 4 separate blocks on 4 K boundaries, wait states, fully buffered, phantom signal. Kit \$299.

### VDB 8024 VIDEO DISPLAY BOARD

On-board Z-80 and CRT 5027 controller. 80 x 24 lines plus programmable characters. Kit \$380.

Z-80 Starter Kit .....Kit \$350  
Ithaco Intersystems Z-80 CPU.....Kit \$156  
Ithaco VDU 64 x 16 .....Kit \$155  
Ithaco 2708/2716 PROM .....Kit \$115

MPR 16 2708 PROM .....Kit \$95  
V/O card serial & parallel.....Kit \$189  
Monitor for SBC 100 .....\$60  
CP/M Disc operating system .....\$145

Rack mount cabinet and mother board available soon. Some other cards in design stage. Add \$50 to prices for built and tested. For mail order add \$5 for reg. post. Please write for more info on any product.

MICROTRIX, PO Box 158 Hurstbridge, Vic., 3099. Ph. (03) 718-2581 AH.



## short circuits

two strips as in the prototype. The depth of the inside of the angle must be slightly more than the thickness of the circuit board — about 2.5 mm is deep enough.


The screws were tapped into the wing of the hinge in positions to avoid the existing holes in the hinge, and to give a good grip on the circuit board. In the prototype the centre line of the screws is 10 mm back from the front edge of the hinge. The outer edge of the gripper is made to align exactly with the outer edge of the hinge.

The stop which limits the backward movement of the hinge is simply a strip of aluminium about 12 mm wide cut and bent to a suitable shape and bolted through the hinge and support.

If you have a hinge handy — make one of these right away, it'll take only an hour, and you'll be glad you did.

If you use the spare hand for testing a circuit, a strip of plastic under the gripper will prevent short circuits.

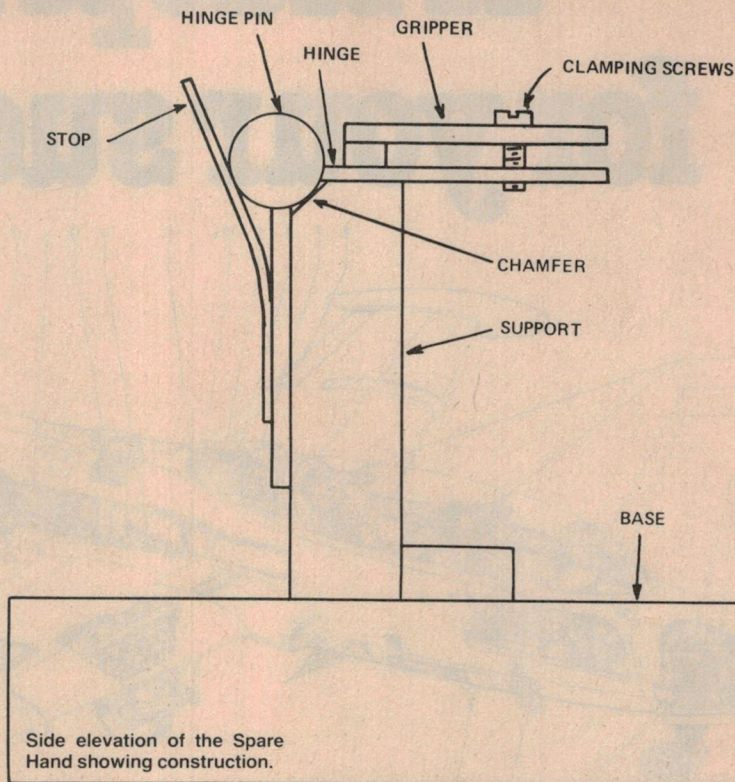For those who make large boards, the spare hand could be increased in size with two hinges attached to the support, but make sure their axes are in line. ●



# Microprocessors made easy



HP's new 5036A Microprocessor Lab is a 50 hour, hands-on course that makes it easy for you to learn about microcomputer hardware, software and troubleshooting—and at your own pace.

It comes as a 20-lesson, 454-page textbook and a microcomputer in a briefcase designed to go where you go. Makes it fun to learn

about microprocessors.

5036A Lab. \$864

Optional troubleshooting tools, \$675 to \$1150.

To order, or for full details, contact your nearest


HP sales office. Or, mail the coupon. Prices subject to change, duty & sales tax.

Name: \_\_\_\_\_

Company: \_\_\_\_\_

Address: \_\_\_\_\_

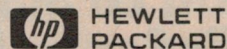Post Code: \_\_\_\_\_ Phone: \_\_\_\_\_ 90923 GM




Adelaide 272 5911/ Auckland 68 7159/ Brisbane 229 1544/ Canberra 80 4244/ Melbourne 89 6351 \_ Perth 386 5455/ Sydney 449 6566/ Wellington 87 7199

ETI August 1980 — 65



# A blueprint for your success.

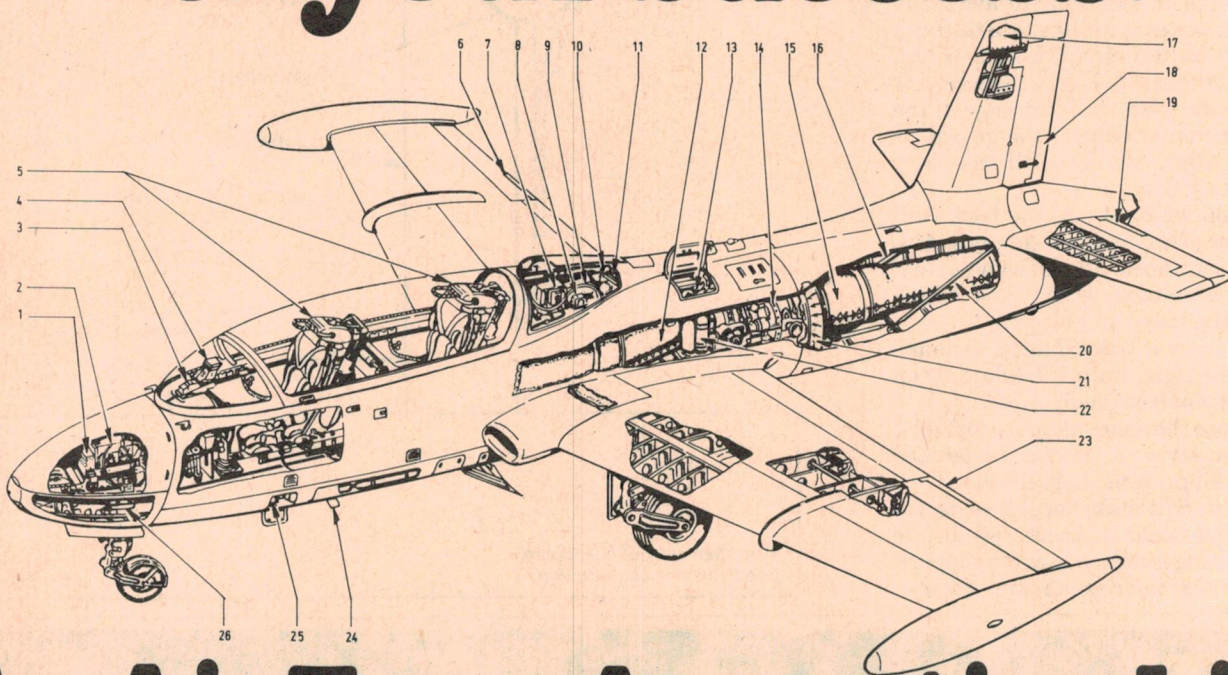

## An Air Force Apprenticeship.

**Opportunities no shop floor  
Apprenticeship can offer.**

Right now, you can take an Air Force Apprenticeship and become a specialist in Airframes, Armaments, Radar, Communications, Propulsion Systems, Flight Systems or Motor Transport.

**Full time training recognised and  
respected by Australian employers.**

For the first 2½ years, you will be taught on some of the most up-to-the-minute equipment under the expert guidance of professional instructors. In modern laboratories, classrooms and workshops.

Understandably, when you have completed your initial training we expect you to spend another 6½ years working for us. On full adult pay of course.

**It's not easy!**

Success demands application. And a disciplined approach to work. As an Air Force Apprentice you'll be required to study in your own time. And regularly sit for exams. The rewards are there. Many Apprentices go on to become Officers.

**It's not all work.**

You will have stacks of time to relax provided you're on top of your studies. At both training bases (Wagga Wagga and Laverton) excellent sports facilities abound. Gyms, football grounds, golf courses, swimming pools, tennis courts and many clubs.

**What about entry qualifications?**

You need to be 15 and under 17 years at time of entry, an Australian citizen or able to meet our nationality requirements. We also expect you to have passed (or be in the process of passing) your \*10th year of formal schooling with above-average marks in maths and science with a physics content. And be reasonably fit.

**The scope for the future is enormous.**

On completion of your Apprenticeship, you'll be part of a team servicing, repairing and testing some of the most advanced and sophisticated aircraft and equipment in the country. The technology of the future will be in your everyday working life.

**Apply now!**

Air Force Apprenticeships are very popular. So the sooner you have a chat

with a Careers Officer the better. The address is in the phone book and there's no obligation.

**Alternatively send or phone for the facts:**

Brisbane:	Townsville:	Sydney:	Newcastle:
226 2626	71 3191	212 1011	2 5476
Wollongong:	Wagga:	Canberra:	Melbourne:
28 6492	21 1100	82 2333	61 3731
Hobart:	Adelaide:	Perth:	
34 7077	223 2891	325 6222	

\* 11th year will be required for 1982 entry for Certificate of Technology Scheme.

To:  
**AIR FORCE CAREERS  
OFFICER, G.P.O. Box XYZ**  
in the capital city nearest you.  
Yes! I am interested in an Air Force  
Apprenticeship. Please send me full details.

Name: \_\_\_\_\_  
Mr: \_\_\_\_\_  
Address: \_\_\_\_\_  
State: \_\_\_\_\_ Postcode: \_\_\_\_\_  
Date of Birth: \_\_\_\_/\_\_\_\_/\_\_\_\_  
AFAP230.FP.30

**You're somebody  
in Today's Air Force**

Authorised by Director-General Recruiting Dept. Defence



# New dialer

GENTLE TOUCH DIALER  
LAST NUMBER RE-DIAL  
FLASHING LED INDIC.  
NOTE: NOT APPROVED BY TELECOM

\$29.99

DIRECT REPLACEMENT FOR  
AUST. ROTARY DIAL!

LM 309K  
5V 1.5A  
MOTOROLA  
\$1.95  
10+\*17 50+\*75  
open 7 days

# ZAP! POW!

TRY OUR PRICES

# KNOCKOUT

## VALUES

## CENTURY PAKS!

- 100 Ne-2 NEONS \$7.50
- 100 1/2W asst. RESISTORS \$1.00
- 100 asst. ELECTROS \$3.50
- 100 TAGSTRIPS asst. \$2.50
- 100 asst. KNOBS \$5.50
- 100 asst. POTS \$9.95
- 100 asst. GREENCAPS \$5.95
- 100 HOBBYISTS SPECIAL PARTS

Containing plugs, jack sockets, fuses, tests, switches, and many more items, 100 parts - \$9.95

## DECADE PAKS!

- 10 TRIMPTS \$3.65
- 10 CERMET TRIMPTS \$1.00
- 10 std. POTS \$1.90
- 10 switch POTS \$2.70
- 10 dual gang POTS \$3.90
- 10 PVC mains cable CLAMPS \$2.50
- 10 3/8" diam FERRITE RODS \$3
- 10 asst. TRANSISTOR H'SINKS \$1
- 10 asst. FUSEHOLDERS \$2
- 10 3AG FUSES \$1
- 10 asst. SWITCHES \$2.50
- 10 14 pin DIP SOCKETS \$2.00
- 10 14 pin DIP PLUGS \$1.50
- 10 16 pin DIP SOCKETS \$2.30
- 10 PL-259 co-ax PLUGS \$3.30
- 10 600 PIV 25A RECT. \$3.50

## DIGITAL WATCH



NEW LCD QUARTZ  
HOURS, MINS, SECS  
DAY, DATE, BACK LIGHT  
AND AUTO CALENDAR.

6 Months Guarantee  
With instructions and display case!

5" TV TUBE  
150C84 \$5.95  
NEW! LAST FEW. 2 for \$11.00

BUY AND SELL  
ALL TEST GEAR  
Elect. Parts  
Elect. MAGAZINES  
BACK ISSUES 1970 ON  
available, also English, American magazines  
Wanted to buy some for cash, any quantity!

MAD MAL  
P.O. Box 43, CROYDON 2132  
1a West St, Lewisham, N.S.W.  
Ph: 569-9797 POST 10% ORDER VALUE

## SUPER SAVING!

12V CAR CASSETTE  
TAPE HEAD DEMAG.  
PROBE  
RESTORES OUTPUT AND H.F. RESPONSE.

\$1.99  
Scoop! Save \$5 were \$6.99

## NEW DOLBY DECK

CASSETTE \$139  
DECK (Sent Freight On) \*SOUNDS GOOD

BSR Belt-Drive  
TURNABLE \$105  
NEW MODEL  
\*FEW ONLY!  
\*FULLY AUTOMATIC OPERATION

With base, cover and ADC mag. cart!

ECONOMY \$79  
TURNABLE \*Freight On

## PRICES CRASH!

- 1KW TVI FILTERS \$15
- 250 mixed RESISTORS \$2
- Lock-down CAR AERIAL \$3
- INTERCOMS, 2 Way \$10
- 5m SPEAKER CABLE \$50
- AYS-8500 TV Games IC Chip \$3
- Marine CB AERIALS \$18
- Traminate RF BOOSTER \$2
- 5pin DIN to 5pin DIN LEADS \$1
- Telescopic AERIALS for TVs \$1
- Stereo CERAMIC CARTRIDGE \$2
- 6x4 or 5x4 15A SPEAKERS \$2
- De-Soldering WICK \$1.25
- Sharp TV TUNER \$3.50
- 5" Hi-Fi Mid-range SPEAKER \$7
- 50 Plastic POT WASHERS \$9.50
- SWR METERS \$9.50
- FM WIRELESS MIKE \$10

## THEFT-ALERT' POCKET PAGER



UP TO 1/2 MILE RANGE!  
Designed specifically as a car, truck, boat or caravan burglar alarm system, the 'THEFT-ALERT' personal pager has 100's of uses e.g. on farms for security protection of outbuildings or equipment etc. for 'fail-safe' indication of critical remote machinery or for paging in offices or factories of key personnel of vehicles and many more!

LOW COST PERSONAL PAGER...  
The tone-selective transmitter permits many systems to be used independently on the 27MHz band without interaction or without interference to or from other transmitters.

THE BEST BURGLAR ALARM...  
When burglars strike, you usually don't know until afterwards... too late to prevent the crime. But now 'THEFT-ALERT' will do just that! Two PIERZO SENSORS (supplied) attached to each side of a vehicle or to doors, windows etc. will trigger the transmitter to alert you. You can add more PIERZO SENSORS to the bonnet and boot or to wheels etc and to other doors, windows or... anywhere. With 'Trigger Input' and 'Trigger Output' the transmit may operate an additional siren, alarm system or may be operated by an existing alarm, it's so versatile and yet so compact. EASILY INSTALLED... 300mA operation (glowstick current). No special antenna needed - uses your car radio aerial or simple 3ft long wire aerial. Takes less than 1hr to install on a car - full instructions supplied.

PRICES-Complete 'THEFT-ALERT' with pager, transmitter and 2 PIERZO SENSORS \$155. Extra PIERZO SENSORS \$15 ea. Extra pager \$50 ea. Electronic alarm siren \$19 ea. Car entry/exit delay alarm module \$45 and \$79. Power supply for 240V use \$12.50

Introductory Offer-POST FREE this month only. Large stocks avail. now!

100,000uF 16vW QUALITY ELECTROS \$9 ea

## \*NEW BIG POWER Speaker Systems

PHILIPS/ETI 4000/2 KITS  
JUNE ETI psl 3 WAY  
INCLUDING Kits are all complete with screws, wire, velcro tape - and crossover networks are wound, ready to instal. Cabinets are pre-built and ready to fit speakers.

do-it-yourself

OPEN FOR BUSINESS

## AUTO DIALER TELEPHONES

Using Dialer as above!  
DESK MODEL \$75.00  
WALL MODEL \$69.95  
(not illustrated)  
NOT APPROVED BY TELECOM  
RINGING WITH FEATURES

## NEW DE-LUXE MODEL WITH 99 NUMBER MEMORY

KAMBROOK solid-state FM Wireless INTERCOM \$45  
Use anywhere in the house or office, only \$45

## LATEST JAPANESE SEMICONDUCTOR MANUALS

1. TRANSISTOR SUBSTITUTION MANUAL
2. TRANSISTOR MANUAL
3. LINEAR IC MANUAL
4. DIODE MANUAL SOLD OUT!
5. FET MANUAL

## 240V LIGHT FLASHERS

Complete, wired with lampholder (no globe)  
HANDLES 60W GLOBE, UP TO 300W WITH H'SINK  
Ideal for Blinking Advertising signs, Discos etc. was \$5.95

## MINI H.D. RELAY

700Ω COIL, 10 AMP  
CHANGEOVER CONTACTS  
\$1 ea or 10 for \$8

EHT TRANS.  
NT3100 \$4.50  
NT3101 \$4.50  
NT3122 ONLY

## LOWEST PRICED SWITCHES SALE

B ON-(ON) SPDT 80¢ 10 for \$7  
D ON-OFF-(ON) (3P)  
E (ON)-OFF-(ON)  
G ON-(ON) DPDT 1 ea 10 for \$9  
I ON-OFF-(ON) (6P)  
J (ON)-OFF-(ON)

DPDT De-Lux TOGGLE \$1.35 \$11.50  
Mini SPST ON-OFF ROCKER 20¢  
10 for \$1.59

## 100 WATTS NEW

PHILIPS/ETI SERIES 4000/2 KITS  
FEBRUARY ETI 4 WAY SPEAKERS INCLUDING AND X'OVERS CABINETS \$460 \$698  
PR. All speakers sent 'FREIGHT'

WE HAVE MOVED... CITY →  
1a WEST ST LEWISHAM  
N.S.W. PH: 569-9797



No car  
is complete  
without one



Gregory's  
street directories  
guides and maps



G1

**Gregory's**  
will get you there.

# C70MGP

General Instrument's  
*NEW!* Thinking Cap  
Keyboard



General Instrument's Keyboard Division has combined state-of-the-art microprocessor technology with the reliability and simplicity of capacitive keys to create a highly flexible, low cost keyboard for OEM's and hobby projects.

The C70-MGP is chock full of features like 4 level ASCII encoding, serial and parallel outputs, N-Key rollover, provision for RS232 and 20MA loop connection, cursor control and user definable keys and programmable baud rates, all for around \$150, plus tax. At a dealer near you.

AUTHORISED DEALERS: **Sydney** (02) E. & M. Electronics 51-5880. A.E.D. 632-6301. Applied Technology 487-2711. G.E.S. 439-2488. **Melbourne** (03) Sontron Instruments 568-4022. Cottage Computers 481-1975. Ellistronics 602-3282. Stewart Electronics 543-3733. **Brisbane** (07) Baltec Systems 36-5183. Zero One Electronics 371-6707. **ACT** (062) Ortex 82-4995. **Adelaide** (08) Rogers Electronics 42-6666. **Perth** (09) Micro Controls 325-2444. **New Zealand** Southmark (9) 79-807.



**daneva control pty. ltd.**

66 Bay Road, Sandringham, Vic., 3191. Ph: 598-5622 Telex: AA34439



# Ideas for Experimenters



These pages are intended primarily as a source of ideas. As far as reasonably possible, all material has been checked for feasibility, component availability etc, but the circuits have not necessarily been built and tested in our laboratory. Because of the nature of the information in this section we cannot enter into any correspondence about any of the circuits, nor can we produce constructional details.

## Dual digital dice

Two identical seven-segment display driver circuits, driven from a common counter circuit, provide the numerals for this dice devised by **Russell Sharp of Belmont, Victoria.**

The counter is driven from a 2 kHz oscillator, the 4011, and generates a count sequence from 1001 to 1110. The terminal count (low on output 1111) is inverted to load 1001 into the parallel input of the 4029. When your finger is pressed on the touch pad the collectors of Q1 and Q2 go high and pins 4 and 5 on the 4511 are held high for about three seconds after your finger is removed from the touch pad. The delay is provided by C1 and R1, together with the 4081 gate. The high on pin 5 of the 4511 loads the last data present on the address inputs (A0 to A2) into the latch of the 4511, whilst a high on pin 4 releases the display from the 'blank' mode to display the contents of the latch. The number is then displayed. When pin 4 goes low again after three seconds, the display is blanked to conserve battery power.

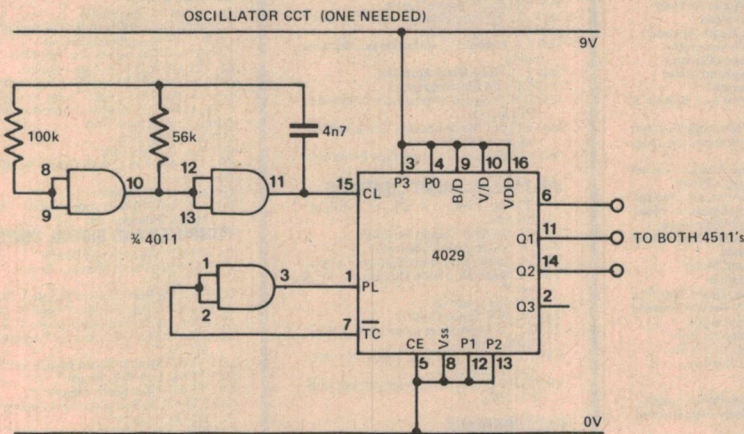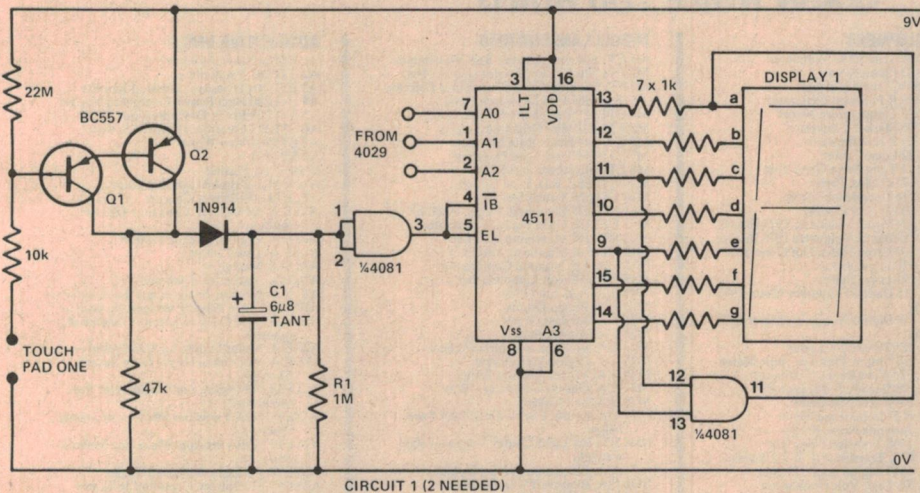
The high clock frequency ensures that the dice has a random result. Even if you attempt to touch both pads simultaneously, each die shows a different throw.


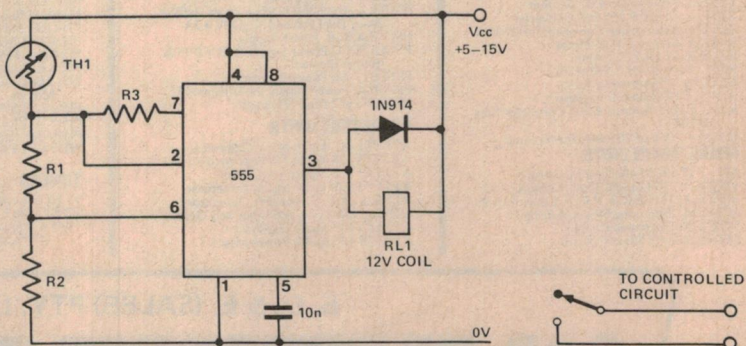
## Electronic thermostat

Yet another idea for a 555. This circuit, **from Benjamin Simons of Beecroft, NSW**, uses a 555 timer IC to switch a relay when the temperature on a thermistor reaches a preset upper level and turn it off when the temperature reaches a preset lower level. The on and off states are determined by the values of R1, R2 and R3 and on the resistance of the thermistor. You'll have to experiment to find them.

Mr Simons suggests the circuit may be used to control a ventilator, fan or chemical bath.





# ALL ELECTRONIC COMPONENTS

That's our name . . . that's our game!!!

MAJOR STOCKISTS OF ALL GENERAL RADIO AND ELECTRONIC COMPONENTS

Only "recognised brands" and top-quality components stocked. Resistors (incl. large industrial types) capacitors, semi-conductor devices, switches, meters, valves, metalwork, front panels, plugs, sockets, cable connectors, transformers, speakers, etc. Prompt and efficient attention through our mail order department. Major stockist of all ETI & EA kits — you name it — we will quote.

## ETI AND EA KITSET SPECIALISTS — TOP QUALITY, LOW PRICES LEARN WHILE YOU BUILD

### STEREO UNITS

- S1 ETI 484 Compressor Expander
- S2 ETI 482 50 watt per channel Amplifier
- S3 ETI 482A Preamp Board
- S4 ETI 482B Tone Control Board
- S5 ETI 485 Graphic Equalizer
- S6 ETI 480 50 watt Amplifier less H/S
- S7 ETI 480 100 watt Amplifier less H/S
- S8 ETI 480 Power Supply for above
- S9 ETI 443 Expander Compressor
- S10 ETI 444 Five Watt Stereo
- S11 ETI 422B Booster Amplifier including metalwork
- S12 ETI 438 Audio Level Meter
- S13 ETI 440 25 watt Stereo Amplifier including metalwork
- S17 ETI 422 50 watt per channel Amplifier \*
- S18 ETI 426 Rumble Filter
- S19 ETI 429 Simple Stereo Amplifier
- S21 ETI 417 Over led Distortion Monitor
- S22 ETI 410 Super Stereo Sound Source Width Control
- S24 ETI 427 Graphic Equalizer \*
- S25 E.A. Playmaster 10 + 10
- S26 E.A. Playmaster 128 40 watt
- S27 E.A. Playmaster 132 40 watt
- S28 E.A. Playmaster 136 13 watt
- S29 E.A. Playmaster 137 3 watt
- S30 E.A. Playmaster 143 12.5 watt
- S32 E.A. Musicolour 11 1000 w/ch
- S33 E.A. Musicolour 111 1000 w/ch
- S34 E.A. Stereo Dynamic Noise Filter
- S35 ETI 470 60 watt audio amplifier module
- S36 ETI 4000 Series 60 watt stereo amplifier
- S37 ETI 451 Hum Filter for Hi-Fi systems
- S38 E.A. Stereo Infrared Remote Switch
- S39 ETI 455 Stereo Loudspeaker Protector
- S40 E.A. Super-Bass Filter Less Power Pack

### PRE-AMPLIFIERS AND MIXERS

- P1 ETI 445 Stereo Pre-amplifier
- P2 ETI 449 Balance Mix Pre-amplifier
- P5 ETI 414 Master Mixer 8 channel
- P6 ETI 419 Mixer Pre-amplifier - 4 ch.
- Mixer Pre-amplifier - 2 ch.
- P7 ETI 401 F.E.T. 4 Input Mixer
- P9 E.A. Simple Mixer for Pick up and Microphone
- P10 E.A. Playmaster 145 Mixer
- P11 ETI 446 Audio Limiter
- P12 ETI 471 High Performance Stereo Pre-Amplifier
- P13 ETI 477 Moving Coil Cartridge Pre-amp
- P14 ETI 474 High to Low Impedance Interface

### RECEIVERS/TRANSMITTERS

- R1 ETI 711 Remote Control Transmitter Switch
- R2 ETI 711R Remote Control Receiver
- R3 ETI 711D Remote Control Decoder
- R4 ETI 711B Single Control
- R5 ETI 711C Double Control
- R6 ETI 711P Power Supply
- R7 ETI 707A 144 MHz Converter
- R8 ETI 707B 52 MHz Converter
- R9 ETI 708 Active Antenna
- R10 ETI 710 R.F. Power Amplifier
- R11 ETI 780 Novice Transmitter
- R12 ETI 703 Antenna Matching Unit
- R14 E.A. 240 Communications Receiver
- R15 E.A. 110 Communications Receiver
- R16 E.A. 160 Communications Receiver
- R17 E.A. 130 Communications Receiver
- R18 E.A. All Wave 1/C2
- R20 E.A. Fremodyne 4 Complete Kit
- R21 E.A. Fremodyne 4 RF Section
- R23 E.A. Mos Fet 52 MHz Converter
- R29 E.A. Short Wave Converter for 27 Mhz
- R30 E.A. Simple S.W.R. Meter
- R31 E.A. 27 Mhz Pre-Amp
- R32 E.A. 10-30 Mhz Pre-Amp
- R33 ETI 718 Shortwave Radio
- R34 ETI 490 Audio Compressor
- R35 ETI 721 Aircraft Band Converter (less XTALS)
- R36 ETI 726 6 or 10 meter Power Amp

### MODEL TRAIN UNITS

- M1 ETI 541 Model Train Control
- M2 E.A. 1974 Model Train Control
- M3 E.A. 1971 S.C.R. P.U.T. Control Unit
- M4 E.A. Electronic Steam Whistle
- M5 E.A. Electronic Chuffer
- M6 E.A. 1978 Train Control

### TEST EQUIPMENT

- TE1 ETI 134 True RMS Voltmeter
- TE2 ETI 133 Phasie Meter
- TE3 ETI 533C Digital Display
- TE4 ETI 129 R.F. Signal Generator
- TE5 ETI 130 Temperature Meter
- TE6 ETI 706 Marker Generator
- TE7 ETI 709 R.R. Alternator
- TE8 ETI 132 Logic Tester
- TE9 ETI 124 Tone Burst Generator
- TE10 ETI 123 C Mos Tester
- TE11 ETI 116 Impedence Meter
- TE12 ETI 533 Digital Display
- TE13 ETI 117 Digital Voltmeter 1975 Display
- TE14 ETI 117 Digital Voltmeter 1976 Display
- TE15 ETI 704 Cross Hatch Dot Generator
- TE16 ETI 120 Logic Probe
- TE17 ETI 121 Logic Pulsar
- TE18 ETI 118 Digital Frequency Meter 1975 Display
- TE19 ETI 118 Digital Frequency Meter 1976 Display

- TE20 ETI 222 Transistor Tester
- TE21 ETI 113 7 Input Thermocouple Meter
- TE22 ETI 107 Wide Range Voltmeter
- TE23 ETI 108 Decade Resistance Box
- TE25 E.A. SWR Reflectometer
- TE26 E.A. R.F. Impedence Meter
- TE27 E.A. Antenna Noise Bridge
- TE28 E.A. 1968 Transistor Test Set
- TE29 E.A. 1971 Transistor (F.E.T.) Tester
- TE30 E.A. 1977 Digital Logic Trainer
- TE31 E.A. 2 1/2 Digit Volt Ohm Meter
- TE32 E.A. Simple Function Generator
- TE33 E.A. Direct Reading Capacitance Meter
- TE34 ETI 487 Real Time Audio Analyser
- TE35 ETI 483 Sound Level Meter
- TE36 ETI 489 Real Time Audio Analyser
- TE37 ETI 717 Cross Hatch Generator
- TE38 E.A. 3 MHz Frequency Counter
- TE40 E.A. Direct Reading Ohm Meter
- TE41 E.A. Function Generator
- TE42 E.A. Transistor Tester incl. Bipolar & F.E.T.S.

- TE43 ETI 591 Up Down Pre-settable Counter
- TE44 ETI 550 Digital Dial (less case) includes ETI 591
- TE45 ETI 144 Expanded Scale R.M.S. Voltmeter
- TE46 ETI 148 Versatile Logic Probe
- TE47 ETI 724 Microwave Oven Leak Detector
- TE48 ETI 150 Simple Analog Frequency Meter
- TE49 ETI 151 Linear Scale Ohm Meter
- TE50 ETI 152 Linear Scale Capacitance Meter
- TE51 E.A. Digital Capacitance
- TE52 ETI 589 Digital Temp. Meter
- TE53 E.A. TV C.R.O. Adapter
- TE54 E.A. Zero Voltage ss. Heat Controller
- TE55 E.A. XTAL Locked TV Pattern Generator
- TE56 E.A. Decade Resistance Box
- TE57 E.A. Decade Capacitance Box
- TE58 E.A. Capacitor Substitution Box
- TE59 E.A. Tantalum Cap Sub Box

### POWER SUPPLIES

- PS1 ETI 132 Experimenters Power Supply
- PS2 ETI 581 Dual Power Supply (High Powered Version)
- PS3 ETI 712 CB Power Supply
- PS4 ETI 131 Power Supply
- PS5 ETI 119 5 volt switching regulator supply
- PS6 ETI 105 Laboratory Power Supply \*
- PS7 ETI 111 1/C Power Supply
- PS8 E.A. D.C. Voltage Reference
- PS9 E.A. 1976 Regulated Power Supply
- PS10 E.A. Dual 30-2 0-30V • 2A or 0-60V • 2A or Dual Pos and Neg 30V • 2A
- PS11 E.A. C.B. Power Supply
- PS12 ETI 142 Power Supply 0-30 V 0-15 A (fully protected)
- PS13 ETI 472 Power Supply
- PS14 E.A. Power Supply for Dream 6800
- PS15 ETI 577 Dual 12V supply

### AUDIO TEST UNITS

- AT1 ETI 441 Audio Noise Generator
- AT2 ETI 128 Audio Millivolt Meter
- AT3 ETI 112 Audio Attenuator
- AT4 ETI 102 Audio Signal Generator
- AT5 E.A. A.F. Tone Burst Generator
- AT6 E.A. Laboratory Solid State A.F. Generator
- AT7 ETI 137 Audio Oscillator
- AT8 ETI 138 Audio Power Meter

### MISCELLANEOUS KITS

- M1 ETI 604 Accentuated Beat Metronome
- M2 ETI 546 G.S.R. Monitor (less probes)
- M3 ETI 549 Induction Balance Metal Detector includes wire for search Head
- M4 ETI 547 Telephone Bell Extender
- M5 ETI 602 Mini Organ (less case)
- M6 ETI 544 Heart Rate Monitor
- M7 ETI 044 Two Tone Doorbell
- M8 ETI 043 Heads and Tails
- M9 ETI 068 L.E.D. Dice Circuit
- M10 ETI 539 Touch Switch
- M11 ETI 529 Electronic Poker Machine
- M12 ETI 236 Code Practice Oscillator
- M13 ETI 218 Monophonic Organ
- M14 ETI 701 Masthead Amplifier
- M15 E.A. I/C Volume Compressor
- M18 E.A. 240 volt Lamp Flasher
- M19 E.A. A/C Line Filter
- M20 E.A. Bongo Drums
- M21 E.A. Keyless Organ
- M22 E.A. Auto Drums
- M23 E.A. Electronic Roulette Wheel
- M25 E.A. Digital Metronome
- M26 E.A. Voice Operator Relay
- M27 E.A. Gas Detector Car Boat
- M28 E.A. Led Chaser
- M29 E.A. Sound Effects Generator \* see below
- M30 ETI 551 Light Chaser 3 channel 1000 watt/ch.
- M31 E.A. Electronic Poker Machine
- M32 E.A. Remote TV Headphone
- M34 ETI 650 STAC Timer
- M35 ETI Wheel of Fortune
- M36 ETI 557 Reaction Timer
- M37 ETI 249 Combination Lock (less lock)
- M38 ETI 814 Dinky Die
- M39 E.A. Electronic Combination lock (including lock)
- M40 E.A. Mast Head Amplifier
- M41 ETI 576 Electromogram
- M42 E.A. Prospector Metal Locator including Headphone
- M43 ETI 361 Metal Locator Less downel & tubing potplant stand

\*set as for Steam Train and Prop Plane noise

### VOLTAGE/CURRENT CONTROLS

- V1 ETI 481 12 volt to  $\pm 40$  V D.C. 100 watt Inverter
- V2 ETI 525 Drill Speed Controller
- V3 E.A. S.C.R. Speed Controller
- V4 E.A. Stage (etc.) Auto Dimmer 2 K.W.
- V5 E.A. Stage (etc.) Auto Dimmer 4 K.W. & 6 K.W. add on for above
- V6 E.A. 1976 Speed Control
- V7 ETI 592 Light Show Controller (3 ch.) (1000 w/ch)
- V8 E.A. Inverter 12V D/C Input 230V 50hz 300VA output
- V9 ETI 593 Colour Sequencer (for use with ETI 592)

### PHOTOGRAPHIC

- PH1 ETI 586 Shutter Speed Timer
- PH2 ETI 548 Photographic Strobe (less reflector)
- PH3 ETI 5148 Sound Light Flash Trigger
- PH4 ETI 532 Photo Timer
- PH6 ETI 505 High Powered Strobe (less reflector)
- PH7 ETI 513 Tape Slide Synchronizer
- PH8 ETI 512 Photographic Process Timer
- PH9 ETI 515 Slave Flash
- PH10 ETI 540 Universal Timer
- PH11 E.A. 1970 Stroboscope Unit (less reflector)
- PH12 E.A. Sync-a-Slide
- PH13 E.A. Auto Trigger for Time Lapse Movies
- PH14 ETI 558 Mast Head Strobe
- PH15 ETI 553 Tape Slide Synchronizer
- PH16 E.A. Digital Photo Timer
- PH17 ETI 594 Development Timer

### TUNERS

- T1 ETI 062 A.M. Tuner
- T2 ETI 740 F.M. Tuner \*
- T4 E.A. Playmaster 146 AM-FM Tuner \*  
\* Wooden Cabinet not included

### AUTOMOTIVE UNITS

- A1 ETI 317 Rev. Monitor
- A2 ETI 081 Tachometer
- A3 ETI 316 Transistor Assisted Ignition
- A4 ETI 240 High Power Emergency Flasher
- A5 ETI 239 Break Down Beacon
- A6 ETI 312 Electronic Ignition System
- A7 ETI 301 Vari-Wiper
- A8 ETI 502 Emergency Flasher
- A10 ETI 303 Brake Light Indicator
- A11 ETI 309 Battery Charger
- A12 E.A. 1970 C.D.I. Capacitor Discharge Ignition
- A13 E.A. High Efficiency Flasher
- A14 E.A. Dwell Meter
- A15 E.A. Variwiper
- A16 E.A. Tacho for Tune-ups
- A17 E.A. Ignition Analyser and Tachometer
- A18 E.A. Strobe Adaptor for Ignition Analyser
- A19 E.A. 1975 C.D.I. Capacitor Discharge Ignition
- A20 E.A. Mains Supply for Car Cassettes
- A21 E.A. Automatic Heavy Duty Battery Charger
- A22 ETI 318 Digital Car Tachometer (less Metalwork)
- A23 ETI 319A Variwiper Mk. 2 (no dynamic braking)
- A24 ETI 319B Variwiper Mk. 2 (for dynamic braking)

- A25 ETI 555 Light Activated Tacho
- A26 ETI 320 Battery Condition Indicator
- A27 E.A. Transistor Assisted Ignition

### GUITAR UNITS

- G1 ETI 447 Audio Phaser
- G2 ETI 413 2 x 100 watt Bridge Amplifier
- G4 ETI 408 Reverberation Unit
- G5 ETI 413 100 watt Guitar Amplifier
- G6 ETI 410 A.D.U. for your Guitar
- G7 E.A. PM 125 50 watt Guitar Amplifier
- G8 E.A. PM 134 21 watt Guitar Amplifier
- G9 E.A. PM 138 20 watt Guitar Amplifier
- G10 E.A. Waa Waa Unit
- G11 E.A. Fuzz Box
- G12 E.A. Sustain Unit
- G13 E.A. PM 135 12 watt Guitar Amplifier
- G14 ETI 452 Guitar Practice Amplifier
- G15 ETI 466 300 watt Amp module - less H/S & Transformer

### COMPUTER AND DIGITAL UNITS

- C1 ETI 633 Video Synchronizer \*
- C2 ETI 632M1 Part 1 Memory Board V.D.U. \*
- C3 ETI 632P Part 1 Power Supply V.D.U. \*
- C4 ETI 632A Part 2 Control Logic V.D.U. \*
- C5 ETI 632B Part 2 Control Logic V.D.U. \*
- C6 ETI 632C Part 2 Character Generator V.D.U. \*
- C7 ETI 632 Mother Board Including P/S \*
- C8 ETI 632 U.A.R.T. Board \*
- C9 ETI 631-2 Keyboard Encoder \*
- C10 ETI 631 A/Sch. Keyboard Encoder (less keyboard) \*
- C11 ETI 630 Hex Display
- C12 E.A. Educ-8 Computer
- C13 E.A. Cassette Tape Interface
- C14 ETI 638 Eprom Programmer
- C15 ETI 637 Cuts Cassette Interface
- C16 ETI 651 Binary to Hex Number Converter
- C17 ETI 730 Getting Going On Radio Tele Type
- C18 E.A. Dream 6800 Computer for Beginners less keyboard and cover

### WARNING SYSTEMS

- WS1 ETI 583 Gas Alarm
- WS2 ETI 066 Temperature Alarm
- WS3 ETI 528 Home Burglar Alarm
- WS4 ETI 702 Radar Intruder Alarm
- WS5 ETI 220 Wailing Siren
- WS6 ETI 219 Hee Haw Siren
- WS7 ETI 313 Car Alarm
- WS9 ETI 503 Electronic Thief Trap
- WS10 ETI 506 Infra Red Intruder Alarm
- WS11 ETI 305 Automatic Car Alarm System
- WS12 ETI 582 House Alarm
- WS13 E.A. Electric Siren
- WS14 E.A. 1976 Car Alarm
- WS15 E.A. 10 Ghz Radar Alarm

E. D. & E. (SALES) PTY. LTD., NOW

**ALL ELECTRONIC COMPONENTS**

118 LONSDALE STREET, MELBOURNE, VIC. 3000. TEL: 662-3506.



# Ideas for Experimenters

## Astable mono

This circuit idea uses half a 74C221 operating in a normal monostable mode except that it retriggers itself after a delay determined by R2 and C2. A gating facility is provided by the other input, and should be tied to the positive rail for a free running mode.


The 'on' time is determined by:

$$1.1 \times R1 \times C1$$

and the 'off' time by  $0.693 \times R2 \times C2$ .


The diode D1 ensures rapid charging of C2 when the duty cycle is less than 50%. This is not necessary for C1 since it is automatically discharged by the IC at the start of its timing cycle. Note that alternative pin numbers are shown on the circuit.

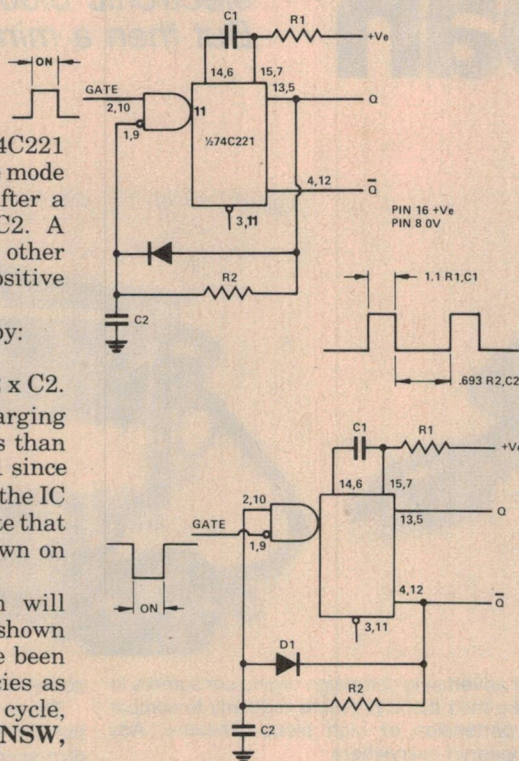An alternative circuit, which will operate from a negative gate, is shown below the first. The circuits have been used to drive a LED at frequencies as low as two Hertz at a 30% duty cycle, says **Phillip Dennis of Berala NSW**, who sent them in.


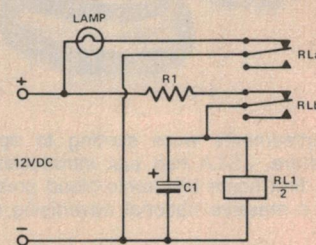
## Simple flasher

**M. Sully of Niddrie, Vic** must have devised just about the simplest circuit possible for a light flasher. A relay is wired as a pulser with a set of relay contacts breaking the power to the coil as soon as the relay operates. Normally with this connection, the relay would buzz, operating many times a second. By adding a resistor in series with the coil and a capacitor across the coil the buzzing can be slowed down to a slow pulsation. The lamp is wired across the supply, in series with a second set of relay contacts so it flashes on and off with the relay.



When the power is first applied, the capacitor charges through R1. When the voltage across the capacitor has risen sufficiently, the relay operates. Power is then disconnected from the relay coil, and C1, by the relay contacts in series with the supply and the capacitor starts to discharge through the relay coil. When the voltage across the coil falls below the 'hold in' voltage, the relay drops out. This is one flash cycle.

The capacitor is again charged through R1 for the next cycle.

Try values for C1 from 470 uf to 10 000 uf and values for R1 from 10R to 470R.

whilst the subjective loudness appears unaffected.


The circuit is adjustable in operation between 130 mV and 10 V rms input sensitivity by means of PR1. To set the circuit up, simply set the slider so that it is shorted to the output of the amp. Play some music at high volume through the system and adjust until the harshness just disappears. It's easier to do than describe, says **J.P. Macaulay of Crawley, UK**.

## 'Soft' limiter

One of the fundamental differences between valve and transistor amplifiers is their behaviour when driven into clipping. The valve amps go into so-called 'soft' clipping whilst their transistorised counterparts generate large quantities of harmonic distortion. The circuit shown simulates the soft clipping of valve amplifiers and is intended to be used between the power amplifier's input and the preamplifier's output.

Resistors R4 and R5, decoupled by C2, set a half supply reference for the non-inverting input of the op amp. Input signals are fed into the inverting input via the dc blocking capacitor and R1, the latter defining small signal gain and input impedance.

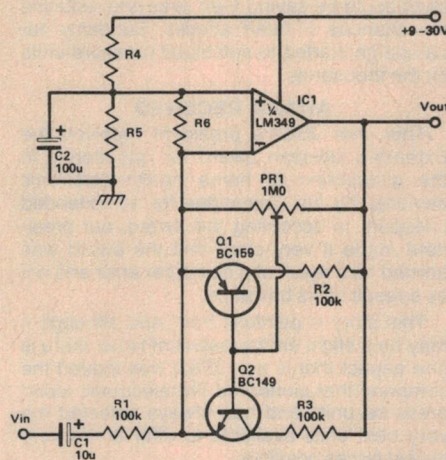For small signals, the amplifier's output is an exact unity gain copy of the input. As the signal level increases however, the time will come when the voltage across the output and slider of PR1 will be sufficient to bias Q1 or Q2 on. When this occurs the feedback in-



R4, R5 = 4k7 R6 = 22k

creases due to the shunting effect of R2 and R3.


The net effect is that musical peaks above a certain threshold are reduced in amplitude to prevent the power amplifier going into hard clipping. As a result, distortion is noticeably decreased



# Extended Lifespan

*JS&A was destined for failure when we introduced our first electronic blood pressure unit. But then a miracle happened.*

Model 310

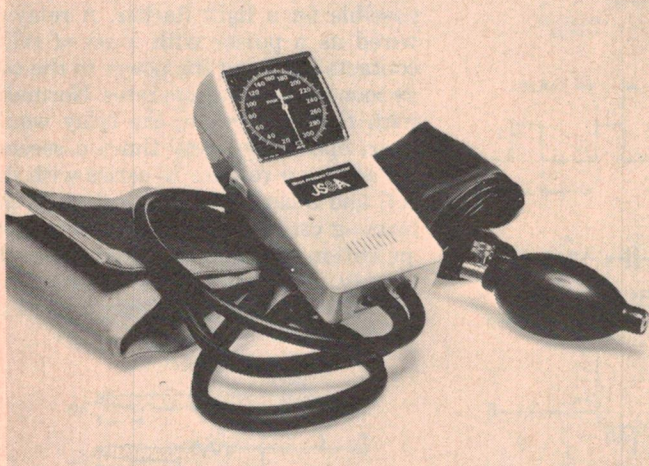

Model 410



Advertisements were starting to appear everywhere. JS&A had just introduced the world's first home electronic blood pressure unit in a massive national advertising campaign.

But something was strange. JS&A often tests its products in its catalog first before they are nationally advertised. If they sell well, we then start a national magazine advertising campaign. The blood pressure unit sold well in our catalog, but for some strange reason, it wasn't selling well in magazines.

## SHOCKING DISCOVERY

And then we found the answer. A few months earlier after our blood pressure unit appeared in our catalog, our computer manager (let us call him Ralph to protect his identity) handed us a computer printout of the catalog sales results.

Scanning the results, we discovered that the blood pressure unit was the best-selling product in our catalog—far exceeding every other product by five times.

The results were so positive that we immediately placed hundreds of thousands of dollars in an advertising campaign launched in early 1978.

Just as the advertisements were starting to appear, Ralph walked into our president's office with some startling news. "There's been a mistake," Ralph said. "The computer printout was wrong. The blood pressure unit is actually our worst selling product but a computer error gave us the wrong information."

And so our president sat back and watched JS&A advertisements appearing everywhere, knowing full well that the campaign would cost his company almost the price of a new computer.

Then came the miracle. As if by plan, the American Medical Association came out with

an advertising campaign urging consumers to take their blood pressure regularly to combat hypertension or high blood pressure. Ads appeared everywhere.

The campaign revealed that there may be as many as 25 million Americans who have high blood pressure and don't know it. Simply by taking their own blood pressure and discovering hypertension early enough, Americans could be saving their lives and reducing the chances of heart attacks. Suddenly our campaign started to sell blood pressure units by the thousands.

## AWARD RECEIVED

This year JS&A's president received the Extended Lifespan award for "pioneering in the distribution of home health electronic devices" by the Committee for an Extended Lifespan. In accepting the award, our president made it very clear that the award was earned as a result of a computer error and not as a result of his brilliance.

This story is painfully true. And although it may be a slight embarrassment to us, there is one aspect that is not. JS&A was indeed the company that pioneered the electronic blood pressure units and has always selected the very best units available to offer at the very lowest prices possible.

## NEWEST UNIT

Our newest unit shown above is another example. The model 310 sells for only **\$79.95** plus \$2.50 for post and handling. You simply wrap the velcro cuff around your arm (you can even keep your shirt on) and inflate the cuff. Both an audible tone and a visible red light will indicate your systolic and diastolic readings. The system is extremely accurate, comes with a self-bleeding air valve and can be stored in a convenient carrying case that

comes with each unit.

The deluxe model 410 functions similar to the first system except that the readings are displayed in digits, and the unit also displays your pulse reading. It sells for **\$149.95** plus \$2.50 per unit for postage, insurance and handling. If for any reason you are not completely satisfied with either unit, you may return it within 14 days for a prompt and courteous refund including your \$2.50 postage and handling. To order either unit, credit card buyers may call our phone number, or you may send your check or money order to the address below.

Both units use solid-state components, come complete with instructions and a one-year limited warranty, and should give you years of trouble-free service. If service should be required, we maintain a service-by-mail center as close as your mailbox. JS&A is America's largest single source of space-age products—further assurance that your modest investment is well protected.

If you are concerned about your blood pressure or know somebody who is concerned about monitoring his or hers, we recommend JS&A's latest units.

Incidentally, Ralph left JS&A on his own accord and bought a farm in another state. There were no hard feelings when he left. How could there be? Order your blood pressure unit at no obligation, today.

**JS&A** PRODUCTS  
THAT  
THINK®

Department ETI

66-70 Railway Road, Blackburn,  
VIC. 3130.

Phone: (03) 878-6943.

Reprinted in full with permission from JSA Inc.

© JS&A Group, Inc., 1980

Bankcard — Diners Club — American Express



# Ideas for Experimenters



## Pulse width modulation controller

This novel idea, from Donald Wallace of Bundaberg, uses a 555 IC to generate a variable width pulse to run slot cars, model trains etc or the unit may be used as a light dimmer.

The pulse width is controlled by the voltage on pin 5, set by the potentiometer. The output transistor is

switched on and off at several hundred hertz, the on to off ratio determining the speed of the motor, or brightness of the lamp.

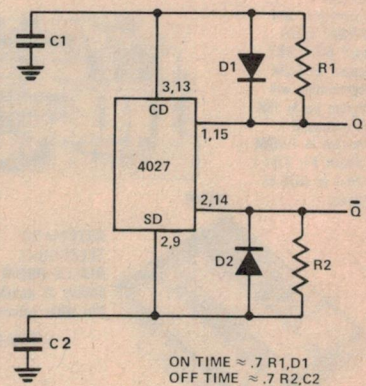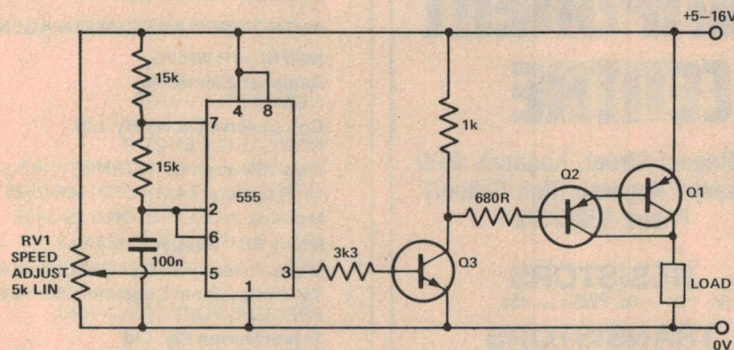The supply voltage may be 16 V maximum and the circuit can switch up to 10 A with an appropriate heatsink on the output transistor.



## 4027 Oscillator


Taking Barry Wilkinson's idea one step further (see ETI Nov '79 p. 61) an oscillator can be made using half a 4027. The 'on' time is set by R1, C1 while the off time is set by D2 and R2. Another idea from Phillip Denniss of Berala, NSW.

## Overrange for ETI 117 digital voltmeter

After building our ETI 117 digital voltmeter, S. Springett of Scarborough, WA, decided to add an overrange facility. It is an inexpensive addition which does not interfere with the normal operation of the instrument. The display will flash when overrange occurs and reset to normal when the voltage is within range.

In normal operation there is an overflow pulse between the reset pulses. The

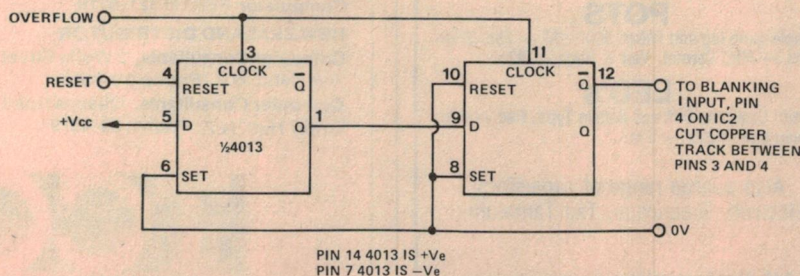first flip flop will be continuously clocked and reset. When overrange occurs there will be multiple pulses on the overflow line between the reset pulses, causing the second flip flop to change state, blanking the display. The display will re-appear after a reset pulse and the first overflow pulse. This produces a flashing display which can still be read.



## Any ideas?

Have you had a bright idea lately, or discovered an interesting circuit modification? We are always looking for items for these pages so naturally, we'd like to hear from you.

We pay between \$5 and \$10 per item — depending on how much work we have to do on it before we publish it.

The sort of items we are seeking, and the ones which other readers would like to see, are novel applications of existing devices, new ways of tackling old problems, hints and tips.





SYN-1 Single Board Computer . \$210.00  
KTM-2 CRT/TV Keyboard terminal module . \$349.00  
BAS-1 8K BASIC ROM for SYN-1 . \$149.00  
BUFFERED MOTHERBOARD for SYN-1, KIM-1 or AIM-65 systems . \$179.00





16K-8 fully tested memory board  
**WRITE PROTECT** and **BANK** switching for SYN-1, KIM-1 or AIM-65 systems . \$360.00

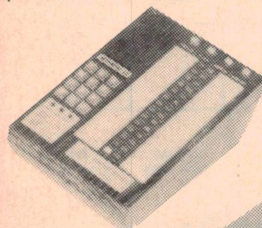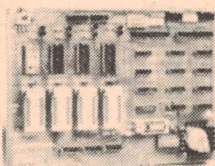EPROM Programmer and EPROM/ROM Board **MEMORY** mapped EPROM programming will program up to 16K per command firmware in PROM included. For SYN-1, KIM-1 or AIM-65 systems . \$345.00




**AUTOMATIC TELEPHONE DIALER** PROM dialling 32 numbers plus other options \$180.00

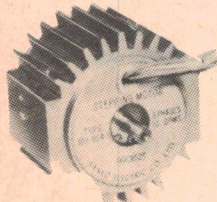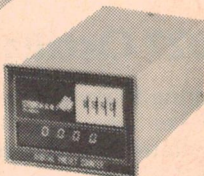**PRESETTABLE COUNTER** 5 digits suitable for counting, batching and numerical control \$150.00



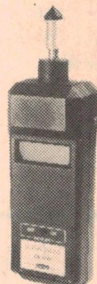**STEPPING MOTORS** wide range for N.C. Control Plotters, Variable Speed, Servo Control, Servo Motors, D.C. Motors, Tacho Generators From \$49.50



**HAND HELD TACHOMETER** \$180

**STEPPING MOTOR DRIVING CIRCUITS** for 3 or 4 phase in Mode 1 phase 2 phase 1-2 phase excitation. From . \$12.00

**THUMB WHEEL SWITCHES**  
1-4 — \$2.20 ea  
5-24 — \$2.00 ea  
25-100 — \$1.90 ea

**END PLATE** \$1.00

**PROXIMITY TRANSDUCERS** — \$15.00



Mail orders add \$3.50 for postage and packaging

**G.C.S.** 67 Blackshaw Avenue, MORTDALE 2223.  
Telephone: 570 1225

(Trade enquiries invited)



## DAVID EAST COMPONENT CENTRE

33A Regent Street, Kogarah NSW  
(Opposite Kogarah High School)  
Phone 588-5172

### RESISTORS

1/4W — 5c. 1W — 8c. PW5's — 45c.

### TRANSISTORS

BC 107, 108, 557, 558 — 33c. BC 559 — 30c. BC 547, 548 — 25c. BC 549 — 27c. BC 109 — 36c. BD 139, 140 — 95c. BC 639, 640 — 75c. 2N3055 (Motorola type) — \$1.30.

### SEMICONDUCTORS

4001, 4011 — 40c. 4016 — \$1. 4017 — \$1.75. 7400, 7402 — 45c. 7490 — \$1. 74C00, C02 — 50c.

### DIODES

IN914 — 5c. IN4004 — 8c. IN4007 — 18c.

### REGULATORS

7805, 12, 15 — \$1.25. 7905, 12, 15 — \$1.75.

### SCR's

C103B (200V, 800 mA) — \$1.16. C106DI (400V, 4A) — \$1.08. C106YI (30V, 4A) — 70c. C122E (500V, 8A) — \$2.56.

### TRIACS

SC14ID — \$1.28

### DIACS

ST2 — 38c.

### BRIDGE RECTIFIERS

All 400V, 1.5 amp to 30 amp.

### POTS

Single gang log and linear: 500R-1M — 75c. Trim-pots — 39c. Cermet, Vert & Horiz — 42c.

### LED's

5 mm Clear and Diffused Sankin Type. Red — 22c. Green and Amber — 31c.

Also a large range of capacitors, Electrolytics, Greencaps, Tag Tantalums.

All first quality components at prices you CAN afford.

## Ohio Scientific dealer network is Australia-wide

For more information and advice call on your local dealer to help you select the best system for your needs

**AUSTRALIAN DISTRIBUTOR-TCG,**  
31 Hume Street, Crows Nest, N.S.W. 2065

### AUTHORISED AUSTRALIAN AGENTS

#### NEW SOUTH WALES

Bambach Electronics  
NEWCASTLE 2-4996

Compuserve (Ncle) Pty. Ltd.  
NEWCASTLE 61-2579

Dwell Electronics HORNSBY 487-3111

Hi-Fi Gallery TAMWORTH 66-2525

Macelec WOLLONGONG 29-1455

Manly Stat. Suppliers MANLY 977-2316

Micro Visions KINGSFORD 662-4063

Tel-Professional Consulting Services  
FRENCHS FOREST 452-1540

Trevor Burton Pty. Ltd.  
BALGOWLAH 94-3861

Unique Electronics  
MERRYLANDS 682-3325

**AUSTRALIAN CAPITAL TERRITORY**  
MES CANBERRA 82-1774

#### QUEENSLAND

Dialog BRISBANE 221-4898

Johansen Systems MT. ISA 43-5582

#### SOUTH AUSTRALIA

Applied Data Control  
FULLERTON 79-9211

Ktronics ADELAIDE 212-5505

#### TASMANIA

Aero Electronics HOBART 34-8232

Eastside Computing  
EAST DEVENPORT 27-8121

J. Walsh & Sons HOBART 34-7511

#### VICTORIA

Comp Co-Ord. Services  
BORONIA 762-5937

Computerware FOOTSCRAY 68-4200

#### WESTERN AUSTRALIA

Datas. Comp. Acc. PERTH 325-5191

Micro Data EAST PERTH 328-1179

Micro Solutions SUBIACO 381-8372

Compulor PERTH 321-6319

#### NEW ZEALAND DISTRIBUTOR

Computer Consultants, 3 Wolfe Street,  
Auckland. N.Z. Phone: 79-8345

Computer Consultants, Queens Road,  
Lower Hutt. N.Z. Phone: 69-4979




TOMORROWS TECHNOLOGY TODAY

## OHIO SCIENTIFIC


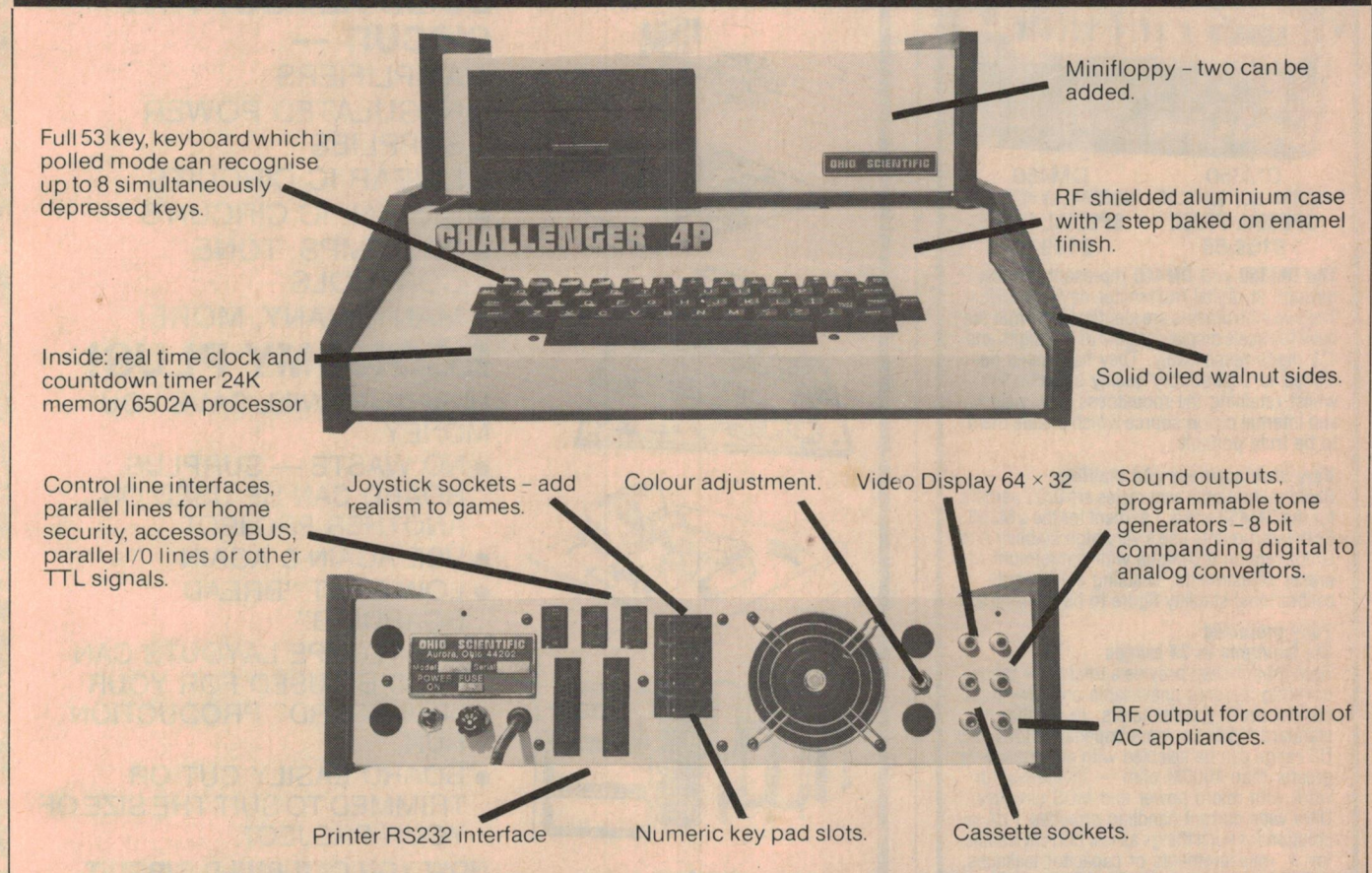
# The Challenger 4

Whichever way you look at it, no other computer offers so much for so little, and in colour!



You'd have to go a long way to get better value in a computer. It has execution speed that really separates the computers from the toys. We think the Challenger 4 is way ahead of anything you've seen so far, for a wide variety of uses including business, personal, educational and games, as well as a real-time operating system, word processor and a data base management system.

The Challenger 4 has a 2MHz 6502 processor, and if that's not fast enough we can supply the GT option with the 6502C processor, and 120 nanosecond memory which averages over one million instructions per second.

A real time clock and count down timer, a 64 x 32 display in 16 colours, including 8K memory in the cassette version, 24K for the minifloppy. A BUS structure allows easy plug in of extra memory or many more OHIO boards. The BUS means modularity. If you bought your vintage C2-4 in 1977 we can change the boards at a much lower cost than a new computer.

For the best surprise of all ask our opposition if they can provide all these facilities. When they can't, ask us!

For the complete list of dealers, please refer to listing on opposite page.

**OHIO SCIENTIFIC**  
TOMORROWS TECHNOLOGY TODAY

**OHIO SCIENTIFIC**

TCG Ohio Scientific Pty. Ltd.

31 Hume Street, Crows Nest, N.S.W. 2065

Phone: 439-6477

LOCKWOOD TCG-4616A



# sinclair

## DM350 3½ DIGIT & DM450 4½ DIGIT PROFESSIONAL QUALITY DIGITAL MULTIMETERS



DM350	DM450
NORMALLY \$210.56	NORMALLY \$271.29
<b>SPECIAL PRICE</b>	<b>SPECIAL PRICE</b>
<b>\$159.85</b>	<b>\$199.00</b>

The DM350 and DM450 represent a breakthrough in digital multimeter development. The two instruments are identical in format but have full scale display lengths of 3½ digits and 4½ digits respectively. They have been designed to a laboratory quality specification, whilst retaining the robustness, low weight and internal power source which enable them to be truly portable.

### Very high accuracy and stability.

Basic calibration accuracies are 0.05 percent for the DM450 and 0.1 percent for the DM350. Both instruments use a very high stability A to D conversion technique with a minimum of preset adjustments, enabling a 12 month calibration stability figure to be guaranteed.

### Fully protected

### Six functions in 34 ranges

Both multimeters provide a total of 34 ranges covering features unavailable on many high cost laboratory multimeters. In addition to standard 10M ohm input impedance the basic DC range can be selected with an impedance greater than 1000M ohm — invaluable for work with micro power and MOS circuitry. Ultra wide current handling provides 1 nA resolution for such things as low current transistor  $\beta$  measurements or capacitor leakages, and measurement up to 10A (20A intermittent) for work with high power circuits. A diode test facility gives direct reading of forward voltage drop. AC frequency response up to 20KHz copes with audio testing and design.

— DC voltage 10uV to 1200V (100uV on DM350)

~ AC voltage 100uV to 750V

— DC current 1 nA to 10A

~ AC current 1 nA to 10A

Resistance 10M ohm to 20M ohm  
(100 ohm on DM350)

Diode Test Forward voltage drop at 1 mA


**RADIO  
PARTS  
GROUP**

562 Spencer Street, West Melbourne.  
Phone (03) 329-7888.  
1103 Dandenong Road, East Malvern.  
Phone (03) 211-8122.

## ENTER THE 80's NOW WITH

# UNI-BOARD

## THE "UNIVERSAL" CIRCUIT BOARD

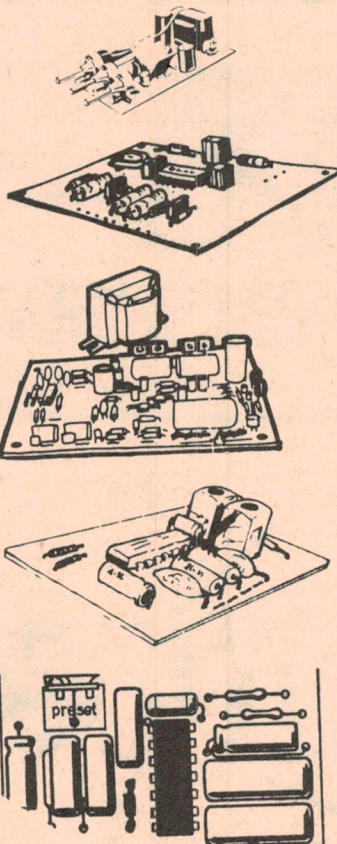

### BUILD ALMOST ANY CIRCUIT —

- AMPLIFIERS
- REGULATED POWER SUPPLIES
- LINEAR IC CIRCUITS
- DIGITAL IC CIRCUITS
- PRE-AMPS, TONE CONTROLS
- MANY, MANY, MORE!

### ECONOMY PLUS!

UNIBOARD WILL SAVE YOU MONEY.

- NO WASTE — SURPLUS BOARD CAN BE USED ON ANOTHER PROJECT
- USE AGAIN & AGAIN
- LOW COST "BREAD BOARDING"
- PROTOTYPE LAYOUTS CAN ALSO BE USED FOR YOUR "UNI-BOARD" PRODUCTION RUN
- BOARD EASILY CUT OR TRIMMED TO SUIT THE SIZE OF YOUR PROJECT.

### NOW YOU CAN BUILD CIRCUIT AFTER CIRCUIT WITH THIS SPECIAL OFFER.

INTRODUCTORY KIT INCLUDES:

- APPLICATION MANUAL
- ONE UNI-BOARD TWIN PACK
- ONE UNI-BOARD SIX PACK

REMEMBER: UNIBOARD SIX PACK IS ONE LARGE CIRCUIT BOARD WITH 6 LAYOUT "MODULES" (SUFFICIENT FOR MANY PROJECTS).

SPECIAL  
INTRODUCTORY  
OFFER!  
\$9.95  
ONLY

TO: ADVANCED ELECTRONIC SYSTEMS PTY LTD  
3 STANILAND GROVE, ELSTERNWICK 3185

PLEASE SUPPLY .....UNI-BOARD INTRODUCTORY KITS AT \$9.95 EA  
(INCL. P&P)

NAME.....  
ADDRESS.....  
POSTCODE.....



# Shoparound

THIS PAGE is to assist readers in the continual search for components, kits and printed circuit boards for ETI projects. If you are looking for a particular component or project — check with our advertisers if it is not mentioned here. Also, for a list of suppliers who stock the ETI projects published over the last few years, our "Kits for Projects" page may generally be found on the page immediately before the DREGS page (inside the back cover).

We can't deny that the **ETI-564 Digital Clock** is a *brilliant* project, a *shining* example of what can be done with solid state devices, a *dazzling* display of expertise — so on and so forth! It uses a total of 128 LEDs for the four seven-segment displays and the two flashing points.

The rectangular LEDs are relatively new on the market but all suppliers

have indicated that they will have stocks of them for project constructors. Several companies manufacture them, notably Philips, Siemens and Hewlett Packard. Be careful when you buy your LEDs to make sure that they are all of the same type from the same manufacturer because the angle and intensity of the light they emit varies from type to type.

Polarised plastic for the face of the clock is available over the counter from Polaroid Australia at Unit 3, Eden Park Estate, 31 Waterloo Rd, North Ryde, Sydney or you can write to them at P.O. Box 163, North Ryde, NSW 2113. For 12 cents per square inch, Polaroid will cut the sheet to the exact size of the box you are using for your clock or you can buy a full sheet measuring 19" x 50" (48cm x 127cm) for \$66. In either case you will have to pay sales tax of 15%. For red displays use red circular polarised display plastic; for green or



yellow displays you need grey circular polarised plastic.

The **LED tacho, ETI-324**, uses either round or rectangular LEDs. Both types are easily available from all major suppliers. It's up to you how you install the tacho in your vehicle, but if you want to house it in a slim box it's worth while checking out the range of Pactec plastic boxes from Associated Controls, 55 Fairford Rd, Padstow, NSW 2211. These come in a variety of colours which could no doubt be matched to most modern vehicle dashboards.

## Announcements

Eagle-eyed and nimble-footed Melbourne readers would have by now checked out **Rod Irving Electronics'** new store at 425 High St, Northcote 3070, just down the street from his old shop front.

The Series 4000/1 Four-Way and 4000/2 Three-Way Loudspeakers have both been popular beyond our wildest expectations. We published a note on suppliers of kits for this project in the April issue Shoparound (page 71). A new addition to the list is **Pre-Pak Electronics** of 1A West St, Lewisham NSW.

## Project price estimates

This information is published as a guide and a variety of factors may affect the actual price of projects, whether bought separately or as kits.

ETI-564 Digital Clock \$70 - \$80

ETI-324LED Tacho \$30 - \$40  
(depending on case)

ETI-262 Simple House Alarm \$13 - \$16  
(electronics only)



Do you experience vanishing video, trouble with Teletext in the TV sets in your block of units? Getting enough signal to each of the TV receivers in a distribution system can present problems, particularly in low signal areas. The Ecrafft range of distribution amplifiers, made locally by Electrocraft, have been designed to suit the wide range of conditions experienced with TV reception in Australia. Low noise figure, adequate gain, high output and good crossmodulation performance are necessary requirements in achieving good performance. The Model 27-500 for example, shown in the picture, claims a gain of 27 dB (+/- 2 dB), maximum output of 500 mV at -60 dB crossmod and a noise figure of 9.8 dB. Input and output impedance is 75 ohms to suit coaxial systems. For a brochure on Electrocraft's complete range of distribution amplifiers for TV and FM reception, write to them at 68 Whiting St, Artarmon, NSW 2064. Phone (02) 439-3266.



# TASMAN ELECTRONICS

12 Victoria Street,  
Coburg 3058.  
Phone (03) 354-5062.

## DIODES.

AAY30.....	40c
BA102.....	70c
BA244.....	22c
BP104.....	\$2.80
BYX71.....	\$1.20
HP5082.....	\$2.50
OA47.....	40c
OA90.....	20c
OA91.....	20c
OA202.....	80c
OA636.....	70c
P600G.....	90c
1N3493.....	\$1.70
1N3493R.....	\$1.70
1N4001.....	.08c
1N4002.....	.10c
1N4004.....	.10c
1N4007.....	.20c
1N4148.....	.06c
1N5404.....	.40c
1N5408.....	.80c

## ZENERS

400mW	
3V3-33V.....	19c
1 WATT	
3V3-33V.....	30c
2½ WATT	
8V2-18V.....	65c
5 WATT	
5V1,12,15V.....	\$1.20

## LINEAR IC

301.....	50c
307.....	70c
308.....	\$1.20c
310.....	\$2.60
311.....	70c
318.....	\$3.20
319.....	\$3.50
324.....	\$1.00
339.....	90c
358.....	70c
377.....	\$2.70
378.....	\$4.20
379S.....	\$6.90
380N14.....	\$1.50
381.....	\$2.30
381AN.....	\$3.96
382.....	\$2.00
383.....	\$3.20
387.....	\$1.80
388.....	\$1.38
555.....	35c
556.....	\$1.20
565CH.....	\$3.30
566.....	\$3.10
567CH.....	\$3.00
709.....	80c
710.....	80c
711.....	80c
725.....	\$4.20
739.....	\$2.80
741.....	30c

747.....	\$1.00
748.....	60c
1458.....	60c
1558.....	\$1.90
1830.....	\$2.80
2917.....	\$3.20
3089.....	\$4.20
3360P.....	\$1.40
3911.....	\$1.60
3914.....	\$4.50
3915.....	\$4.50
3916.....	\$4.50
7392.....	\$3.30
13600.....	\$2.20
CA3046.....	\$1.65
CA3080.....	\$1.90
CA3086.....	.65c
CA3130.....	\$1.50
CA3140.....	\$1.50
CA3302.....	.70c
CA3401.....	.80c
LF356.....	\$1.10
NE571.....	\$7.50
MC1494L.....	\$6.65
OM350.....	\$7.90
RC4136.....	\$1.45
SAK140.....	\$2.64
TBA641.....	\$2.40
UAF771.....	.50c
UAF772.....	.98c
UAF774.....	\$1.70

## DISPLAYS

FND350.....	\$1.98
FND357.....	\$1.40
FND500.....	\$1.40
DL747.....	\$3.50
MV57164.....	\$3.80

## SCR's

C103YY.....	.80c
C106Y.....	.65c
C106D.....	.90c
C106E.....	.70c
C122D.....	\$1.30
S4015L.....	\$1.90
S2025H.....	\$3.75

## TRIAC's

SC141D.....	\$1.30
Q4015L5.....	\$2.80
BT139-600.....	\$2.80

## TRIM CAPS

1P4-5P5.....	30c
2P-22P.....	40c
5P-65P.....	30c
5P5-40P.....	40c

MAIL ORDERS — \$1.00  
min. post & pack please.



## THE 1980 HOME COMPUTER SHOW

The major micro-event of the year. Computers in the home will soon be as commonplace as HiFi and TV. Come and see the major Home Computer Exhibition in Australia.

- Personal Computers
- Microprocessors
- Small Business Systems
- Games and Gadgetry

**Melbourne: Kew Civic Centre**  
**Cotham Road, Kew.**

Thursday, Sept 11, 10.00a.m.-6.00p.m.  
Friday, Sept 12, 10.00a.m.-6.00p.m.  
Saturday, Sept 13, 10.00a.m.-8.00p.m.  
Sunday, Sept 14, 10.00a.m.-6.00p.m.

**Bring the family!**  
**Telephone Enquiries (03) 67 1377**



# ALL TOGETHER !




— the top projects from the past few years' issues of ETI !

Assembled in one great volume, here are more than 25 projects including: the Series 4000 stereo hi-fi amplifier system; the superb Series 4000 four-way speaker system; the monstrous 300 W amplifier module; Guitar Practice Amp; Fuzz/Sustain Unit; Electronic Tuning Fork; Aircraft Band Converter; Analogue Frequency Meter; Linear Scale Capacitance Meter; Electronic Ohmmeter; Ultrasonic Switch; Radio Remote Control Unit; Transistor Assisted Ignition; Theatrical Lighting Controller; Electromyogram; Disco Strobe . . . and many more.

On sale now at newsagents and selected specialist suppliers. If sold out (highly likely), you can obtain a copy from **Electronics Today International, Subscription Department, 3rd Floor, 15 Boundary St, Rushcutters Bay NSW 2011. Send \$3.95 plus 65 cents post and handling.**



# POWER UP WITH SILICON VALLEY

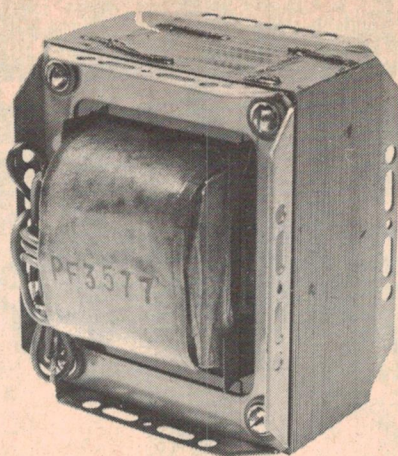

PF 3577 4 Amp  
**\$21.00**




2N3055  
**\$0.70**


Note:—

All prices shown include tax.



Trade quantities available through CEMA Electronics Pty Ltd.  
A member of the VSI Group of Companies.

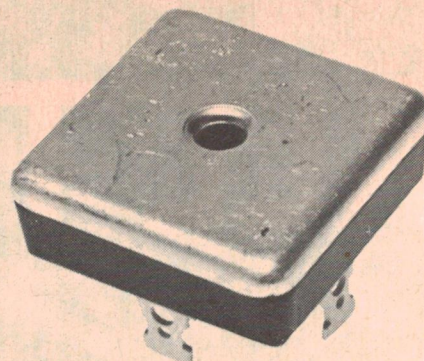

MDA 3504  
35 Amp 400 VOLT.  
**\$3.64**

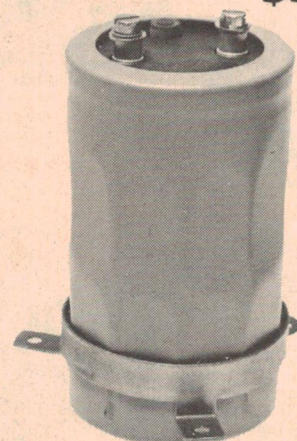

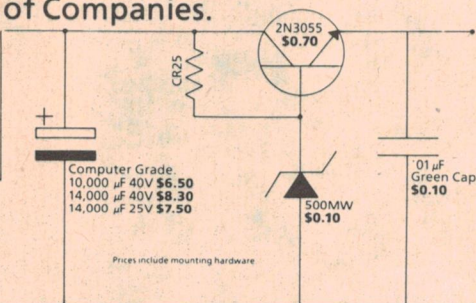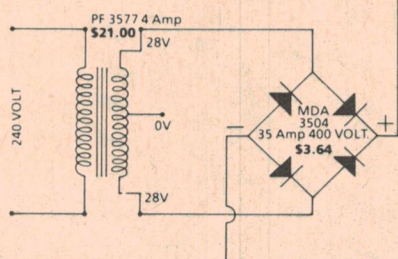Computer Grade.  
10,000  $\mu$ F 40V **\$6.50**  
14,000  $\mu$ F 40V **\$8.30**  
14,000  $\mu$ F 25V **\$7.50**



Computer Grade.  
10,000  $\mu$ F 40V **\$6.50**  
14,000  $\mu$ F 40V **\$8.30**  
14,000  $\mu$ F 25V **\$7.50**

Prices include mounting hardware

## silicon valley

**ADELAIDE:** 170 Sturt St, Adelaide  
Telephone: (08) 51.4080

**BRISBANE:** 22 Ross St, Newstead  
Telephone: (07) 52.1339

**MELBOURNE:** 208 Whitehorse Rd,  
Blackburn  
Telephone: (03) 877.5311

For all your component needs.

**PERTH:** Unit 1, 25 Brisbane St,  
East Perth  
Telephone: (09) 328.8091

**SYDNEY:** 23 Chandos St, St. Leonards  
Telephone: (02) 439.2965



## NEW APPROACH TO ELECTRONICS EDUCATION.

Dear Sir,

I would like to comment on the content of the above article. These comments are based on experience with the Victorian scene, but I do not believe that NSW is very different.

Firstly, the impression is given of private firms battling with bureaucracy in a vain attempt to lift electronics courses out of the dark ages. As a private company representative on a TAFE course committee, I can assure you that industry has plenty of opportunity to put its point of view.

It is a sad fact that many firms are reluctant to formulate their requirements in terms specific enough to base a training course thereon. If the companies who co-operated so enthusiastically with Mr. Burnett had taken the trouble to accept some of the invitations to attend, which are extended from time to time by TAFE committees, they might find that technical college courses more nearly fit their requirements.

In one area of electronic employment (Instrument Making) the NSW Education Department has conducted an industry survey in recent years, and no doubt has done so in allied areas.

Secondly, the article is written on the supposition that there is such a thing as "the electronics industry". If by that term is meant consumer electronics (and the content of the article suggests that this is so) then this should be clearly indicated. In the wide sense there is no electronics industry, any more than there is a mechanics industry.

A general electronics course will no more fit a trainee to enter many of the diversified fields in which electronic devices are now used, than a general mechanical course would enable a trainee to become, say, a car mechanic, an airframe fitter, or a toolmaker. Furthermore, there are many areas of electronic employment to which entry can only be gained via the apprenticeship system. You may think this is old-fashioned and slow, but the plain blunt fact is that this is the present legal position, and to indicate otherwise to an eager young student would be quite misleading.

Next, Mr. Burnett intends to "update his course every year". This is no doubt a laudable objective, but if carried out conscientiously will soon result in courses bursting at the seams as Mr. Burnett struggles to include the new material, while retaining as much of the old as possible. If the old is retained at the expense of the new, the course will be open to the criticism of being out of date. If the old is dropped, the course may turn out graduates who are either deficient in basic theoretical concepts, or who will be

lost if they encounter, say, a piece of valve equipment (or even something using those old-fashioned discrete components!).

Faced with this constant dilemma, technical college courses tend to concentrate on first teaching the basic concepts which govern the operation of all electronic devices, then follow this with as wide a choice of specialist subjects as it is practical to offer. Some of these are so up-to-the-minute that frequent review and re-writing is required.

A further point is that Mr. Burnett uses the "practice reinforced by theory" approach. Some people do learn most effectively this way; it is particularly useful for students whose formal academic record may not be as good as hoped. But it is by no means true for all. And in a sphere which is becoming increasingly complex, a solid theoretical grounding is very important, if not essential. As a prospective employer, I would tend, everything else being equal, to prefer a trainee well versed in theory, because they are much more capable of dealing with unfamiliar equipment or systems, by the application of basic principles combined with logical thought processes. Of the five apprentices I currently supervise, two had Leaving Certificates, one had HSC, and two had completed the first year of a Certificate of Technology (Technical Officers) course, at the beginning of their employment. Not really a "theory via practice" group.

Finally, you say that the new course had been "welcomed enthusiastically" by employers. I'm not surprised. A company employing one of Mr. Burnett's graduates will be getting a person who has completed his training (even though short of experience) at someone else's expense. And what are their future prospects? You mention positions all the way up to management. People with management potential will rise through the system, and there is no reason to believe that these trainees are at any disadvantage in this regard. But I sincerely hope that, at the start of their careers, these young people are not used as electronic cannon fodder, occupying relatively low-paid positions while technical-college trained tradesmen move up the ladder.

On the other hand, if this course helps even a few trainees to hold down jobs

when they would otherwise be unemployed, the exercise will have been well worthwhile, and it may be that, from this point of view, Mr. Burnett has filled a gap in the system.

To sum up, I have a few reservations about this approach. For a young person who is keen on electronics, but who is either not able to get an apprenticeship or traineeship, or whose academic record is not quite up to scratch, it could be just the thing. But for those with the ability and stamina to follow the more formal route, I would still recommend that way.

**Ronald F. Salter, M.I.C.A.  
MacLeod, Vic.**

Dear Sir,

I would like to thank ETI for Mini-Mart. It provides an essential forum for 'electrophiles' to pursue their interests with as little impact on financial resources as possible.

My own area of interest is audio and I was wondering when an article concerning noise reduction/expansion devices would appear. I have acquired a fairly extensive record music library and these devices offer the real saving of extending the life of the collection, thus reducing or delaying the cost of replacement.

Do you have an index of product reviews, and back copies available so that gaps in information could be eliminated?

Once again, thanks for an excellent 'umbrella' magazine that succeeds in expanding one's horizons of interest.

**Mr R. White  
Adamstown, NSW**

*Thank you for your kind remarks about Mini-Mart and the magazine in general.*

*We publish a yearly index each April. On page 95 of the April 1980 issue, you'll find all the product tests listed back to April 1979. We plan to include a ten-year index in our April 1981 issue. That should keep you busy for a little while! A cumulative index of reviews that appeared in the demised 'Hi-Fi Review' appeared in their October 1978 issue. If you turn to page 169 in this issue of ETI you'll see a coupon which you can use to order back copies of issues or photostats of articles.*

*An article on the 'ADRES' noise reduction system appeared in the July 1979 issue, page 23 and we plan to examine other noise reduction/expansion systems in forthcoming issues.*

**Roger Harrison, Editor**



# WHY IS THIS AUSTRALIA'S FASTEST SELLING COMPUTER?



**SIMPLE:**

**IT IS FAR AND AWAY THE BEST VALUE COMPUTER IN AUSTRALIA**

**It has everything the TRS-80 has, and then some . . .**

- Level II compatible BASIC as standard  
(Tandy charge extra for level II)
- Industry standard S-100 bus expansion  
(They use their own non-standard system)
- RF output: uses any TV set as a monitor  
(You have to buy a true video monitor)
- Two motor-controlled cassette interfaces  
(Theirs only has one)
- Inbuilt cassette deck (no inter-connections)  
(Their cassette is completely separate)
- Inbuilt power supply (no inter-connections)  
(Tandy power supply has to be connected up).
- AND THE BEST PART OF ALL: IT IS MUCH CHEAPER THAN THE TANDY EQUIVALENT

**DICK SMITH  
SYSTEM 80**

**Not only the best value,  
but the lowest price!!!**

**ONLY \$615**  
4k RAM MODEL, CAT X-4003  
**WITH LEVEL II BASIC**



**Compare the System 80 with the TRS-80. Notice the additional features. Then notice the lower price. Which would you choose?**

PARAMETER	SYSTEM-80	TRS-80 (level I)	TRS-80 (level II)
1 CPU type	Z-80	Z-80	Z-80
2 Speed	1.7MHz	1.7MHz	1.7MHz
3 Amount of RAM	16K	16K	16K
4 Built-in cassette recorder	Yes	No	No
5 Built-in video modulator	Yes	No	No
6 Capacity of BASIC ROM	12K	4K	12K
7 Type of BASIC supplied	Microsoft 12K Floating point	Floating point	Microsoft 12K Floating point
8 RAM expansion on-board to:	16K	16K	16K
9 Machine language programs accessible from executing BASIC programs	Yes	No	Yes
10 Full ASCII characters	Upper case only	Upper case only	Upper case only
11 Programmable graphics characters	No	No	No
12 Graphics resolution (dots)	8192	8192	8192
13 Mixed graphics/text — any format	Yes	Yes	Yes
14 Text format	16 lines x 64 or 32	16 lines x 64	16 lines x 64 or 32
15 Number of cassette interfaces	2	1	1
16 Baud rate	500	250	500
17 Time to load 8k program	2 min 30 sec	4 min 50 sec	2 min 30 sec
18 Cassette file names	Yes	No	Yes
19 Number of cassette recorders	2	1	1
20 Motor control for cassette recorders	Yes (2)	Yes (1)	Yes (1)
21 Number of string variables	930	2	930
22 Maximum length of string variables	255	16	255
23 S-100 compatible (with expansion unit)	Yes	No	No
24 Supports disc drive system	Yes	Yes	Yes
25 Cost of basic unit with 16K RAM including monitor and cassette recorder.	\$844.50*	\$989.00	\$1169.00

\* This price includes the monitor shown above. However, as the System 80 does not need a video monitor, if you have a surplus B&W TV set you can save another \$149.50 — making the savings over the Tandy system even more dramatic!

**AND REMEMBER:** All of the thousands of programs written for the TRS-80 are compatible with the SYSTEM 80 . . . you cannot lose!!!

BELOW COST  
Freight anywhere  
in Australia  
JUST \$6.00!

**SEE US AT 'DATA 80'**  
(Sydney, August 5-7)  
**& COMPUTER SHOW**  
(Melbourne, October 16-19)

**DICK SMITH  
SYSTEM 80  
16K MODEL  
ONLY \$695**  
(WITH LEVEL II BASIC)  
Cat X-4005

**HURRY! PRICES MUST RISE SOON!**

Terms are available to approved personal applicants from only 10% deposit!


**DICK SMITH ELECTRONICS**

**NSW** 125 York Street, SYDNEY. Ph 290 3377  
147 Hume Highway, CHULLORA. Ph 642 8922  
162 Pacific Highway, GORE HILL. Ph 439 5311  
30 Grose Street, PARRAMATTA Ph 683 1133  
613 Princes Highway, BLAKEHURST Ph 546 7744  
263 Keira Street, WOLLONGONG. Ph 28 3800

**VIC** 399 Lonsdale Street, MELBOURNE. Ph 67 9834  
656 Bridge Road, RICHMOND. Ph 428 1614  
**QLD** 166 Logan Road, BURANDA. Ph 391 6233  
842 Gympie Road, CHERMSIDE. Ph 59 6255  
**ACT** 96 Gladstone Street, Fyshwick. Ph 80 4944  
**SA** 60 Wright Street, ADELAIDE. Ph 212 1962  
**WA** 414 William Street, PERTH. Ph 328 6944

**MAIL ORDER CENTRE:** PO Box 321, NORTH RYDE NSW 2113. Ph 888 3200. PACK & POST EXTRA.

## DICK SMITH MONITOR

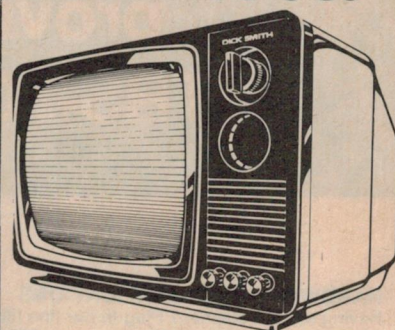


Haven't got an old TV? This 30cm monitor will give you clear, jitter-free viewing at a modest price. **And it works with all micro-computers available!**

Don't pay high prices for 'brand name' monitors when they'll perform no better! 240V AC or 12V DC operated, single 'RCA' type connection to your computer video output. And look at the price:

**\$149<sup>50</sup>!**

Cat X-1196

## DICK SMITH PRINTER

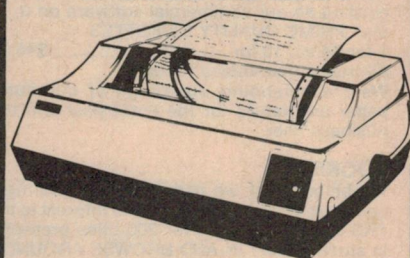

Compare the features: and the price. 9x7 dot matrix with 240mm print, at 125cps! For the best in low cost printers, you can't go past the Itoh 8300P". Cat X-3255

**\$970<sup>00</sup>!**

**NOTE:** This printer does NOT need an expansion interface; however you will need an X-4012 printer cable (@\$89.50) to connect to the computer.



**SHOPS OPEN 9AM to 5.30PM**  
(Saturday: 9am till 12 noon)  
**BRISBANE:** Half hour earlier.  
ANY TERMS OFFERED ARE TO  
APPROVED APPLICANTS ONLY  
RE-SELLERS OF DICK SMITH  
PRODUCTS IN MOST AREAS OF AUSTRALIA.



# The one-stop Microcomputer Shop providing a total service to TRS-80\* and System 80 users

\*TRS-80 is a registered Trademark of Tandy Radio-Shack

## HARDWARE AND MODIFICATIONS

Having system crashes? Plug in our line filter and get mainframe stability.....\$55.00  
Use your TRS-80 as a telephone book and automatic dialler. No hardware mods required.  
All software included.....\$59.50  
LIGHT PEN with demonstration software and full programming instructions. STILL ONLY.....\$19.50  
Lower case mod for ELECTRIC PENCIL and SCRIPSIT. Fitted and 90 day guarantee.\$49.95  
VIDEO STABILIZER CRYSTAL. Get professional stability on your VDU. CRYSTAL only \$19.95. Fitted and guaranteed.....\$39.00  
16K MEMORY KITS \$85.00. We install\$105.00  
RS-232 PRINTER DRIVER. Operates from cassette cable. Inc. software.....\$54.75  
CISA DATA DIGITIZER. Our most popular hardware product. No hardware mods required. Reads and re-records tapes normally unreadable by any other method.....\$57.50  
CASSETTE CABINET. Protect your valuable cassettes in this strong, handsome 36 cassette cabinet.....\$27.75  
DIGITAL CASSETTES. Top quality.  
C15's — 1 for \$1.65. 10 for.....\$14.85  
C20's — 1 for \$1.85. 10 for.....\$16.85  
C30's — 1 for \$1.99. 10 for.....\$18.50  
This is an entirely new product. We are so confident of this product that we are now recording all our commercial software on it.  
5¼" PRIME QUALITY DISKETTES  
1 for \$4.95. 10 for.....\$45.00  
All tracks guaranteed to load.  
We are extending our range of computer paper and labels for the enthusiast and the business user.

## BOOKS

We believe that we have the best and most comprehensive range of titles of interest to the TRS-80 owner/user. Over 200 titles presently in stock. COME IN AND BROWSE AROUND! JUST A SELECTION  
First Book of Microcomputers.....\$6.50

Pascal With Style.....\$8.50  
Basic With Style.....\$8.00  
TRS-80 Disk and Other Mysteries.....\$29.50  
Level II ROM Reference Manual.....\$24.95  
Basic and the Personal Computer (highly recommended).....\$15.95  
Basic Programming for Scientists and Engineers.....\$15.50  
The Incredible Secret Money Machine.....\$7.95  
Z-80 Microcomputer Handbook.....\$11.95  
Microcomputers for Business Applications.....\$11.95  
Z-80 and 8080 Assembly Language Programming.....\$10.00  
How to Profit from your Personal Computer.....\$12.00  
Little Book of Basic Style.....\$7.95  
Microcomputer Interfacing.....\$25.75  
Microcomputers and the 3 R's (A Guide for Teachers).....\$10.00  
COMPUTER CLASSICS  
Wirth/Algorithms plus Data Structures equals Programs.....\$29.75  
Tausworth/Standardized Development of Computer Software. Vol. I — Methods \$29.75.  
Vol. II — Standards.....\$29.75  
Klingman/Microprocessor Systems Design.....\$30.50  
Gilmour/Business Systems Handbook \$29.75  
Gane/Structured Systems Analysis.....\$26.50  
Garrett/Analog Systems for Microprocessors.....\$26.50  
Rhyne/Fundamentals of Digital Systems Design.....\$26.95

## TRS-80\* AND SYSTEM 80 SOFTWARE

Ecology Simulations 1 and 2 (disk and cassette) each.....\$24.95  
Mission Impossible and Voodoo Castle (disk).....\$24.95  
Adventureland and Pirate Adventure (disk).....\$24.95  
Investment Analysis (disk or L2 cassette).....\$49.95  
Sargon II (cassette).....\$37.50

Strategy Games (5) (cassette).....\$7.95  
Space Games (4) (cassette).....\$7.95  
5 Adventures (cassette) each.....\$14.95  
Advanced Statistics (disk or cassette).....\$24.95  
U Boat (cassette).....\$8.50  
Basic Monitor (cassette).....\$19.95  
Micromazing (games cassette).....\$7.50  
RPN Calculator (cassette).....\$14.95  
PLUS MANY MORE

We stock and highly recommend all RACET COMPUTES professional standard system programs.

Infinite Basic.....\$49.95  
Infinite Business.....\$29.95  
Remodel.....\$24.95  
Remodel plus Proload.....\$34.95  
GSF.....\$24.95  
DOSORT (sorts disk files).....\$34.95  
COPSYS (copies system tapes).....\$34.95  
NEW DOS FROM APPARAT

35 Track.....\$99.00  
40 Track.....\$110.00

This DOS emulates many mainframe capabilities. Has features usually restricted to much larger systems.

TARANTO and ASSOCIATES

General Ledger.....\$155.00  
Accounts Payable.....\$155.00  
Accounts Receivable.....\$155.00  
Print Invoice.....\$99.00  
Complete Business System.....\$500.00

This is professional quality software and really provides a superb business system for the TRS-80. Software maintenance is available to purchasers of the complete system at \$15 per hour, to tailor the programs to your specific needs.

## PLUS MANY MORE

We are the Australian agents for many first class U.S. software houses. Send for our full catalogue.



Remember, for all your TRS-80\* and System 80 needs, phone, write or call  
Showroom: Ground Floor,  
GIO Building, 159 Kent Street,  
Sydney 2000.  
(Opposite IBM Building)  
Phone (02) 241-1813  
Trade enquiries welcome.





# Print-out

Flabbergasting flexibility

## — that's the EXORset 30!

The latest addition to Motorola's family of EXORciser microcomputer equipment is a software development system called EXORset 30, which is designed to fill the gap that previously existed between limited low-cost systems and expensive EXORciser-based machines.

**The EXORset 30 can communicate with EXORciser systems via a serial port, or it can be used as an EXORciser terminal, and is compatible with the whole range of Motorola Micromodules.**

A standard parallel printer interface allows connection to a printer of any selected performance and external storage of programs on microcassettes is also provided for.

A single console incorporates a full size ASCII keyboard with 16 user-assigned function keys, a dual mini-floppy disk drive and a 230 mm CRT which is capable of displaying 22 lines of 80 characters each or a combination of a 320 x 256 dot graphic image and 16 lines of 40 characters each.

The standard RAM provision is 48K bytes, but this can be extended to 56K using extra memory modules. Twelve EPROM/ROM sockets will accept up to 24K bytes of user firmware. The two disks give 160K of mass storage.

The memory map is defined by a PROM, which allows users to reconfigure the system quite easily.

The heart of EXORset 30 is an MC6809, Motorola's latest 8-bit microprocessor. Standard disk-resident software enables this chip to perform the functions of an editor/assembler and a compiler/interpreter.

### The Compiler

An improvement in speed of one or two orders of magnitude over standard BASIC interpreters is claimed by the manufacturers. The compiler generates

executable codes, which can be used independently of the compiler itself, at a rate of 100 lines per second.

Programming possibilities are extended by the use of BASIC-M, a compatible extension of BASIC which is said to have several advantages over its parent.

Individual bits of a specified byte can be accessed in BASIC-M; 'byte declaration' allows a specified byte location in memory to be assigned a variable name; 'integer declaration' names a 16-bit integer starting at a specified location.

REAL variables have an allowable range from  $10^{-38}$  to  $10^{+38}$  with nine significant digits and CHAR or STRING variables may run up to 31 ASCII characters.

ARRAYS of the same type of data may be as large as 255 x 255 (or 65535 elements) and there is a set of twelve instructions for inputting, outputting and performing operations on MATRIX elements.

For disk input and output with sequential organisation, BASIC-M allows random access to fixed length records or sequential access to records of variable length. Indexed files may have their record lengths defined by the user and can be accessed by means of keys.

There are several new control statements. WHEN... THEN instructs the machine to test the WHEN condition on each subsequent line of the program and execute the THEN clause if the condition is met.

A family of instructions with the basic form ON... THEN executes the THEN clause in case



of a specified external event, which may be a keyboard entry, NMI, IRQ, FIRQ or a runtime error, as specified.

PRINT USING is a statement which allows the output to be formatted in one of seven different ways. New system commands available include automatic line numbering, re-naming of variables, patch, and list erroneous statement.

### Disk Control

The disk operating system, known as XDOS, permits random file organisation and has system call routines that are compatible with MDOS, the standard Motorola disk operating system.

A wide repertoire of commands includes backup duplication of disks, copying from disk to disk, disk to device or device to disk, and copying from memory to disk.

XDOS can search the directory for prescribed file names and display them, or delete a file name from the directory and free the corresponding disk space. It can display the total content of any physical sector or display the number of available directory entries and disk sectors.

File names and suffixes in the directory can be altered and soft sector addressing information can be rewritten. Two or more files can be chained together to make a single new file.


### Debugging

Extensive debugging facilities are provided by the EXORbug monitoring system, which is on-board in ROM.

Sixteen separate debugging functions are listed in the manual, including memory read and change, memory initialise and block move of ▶



# Print-out

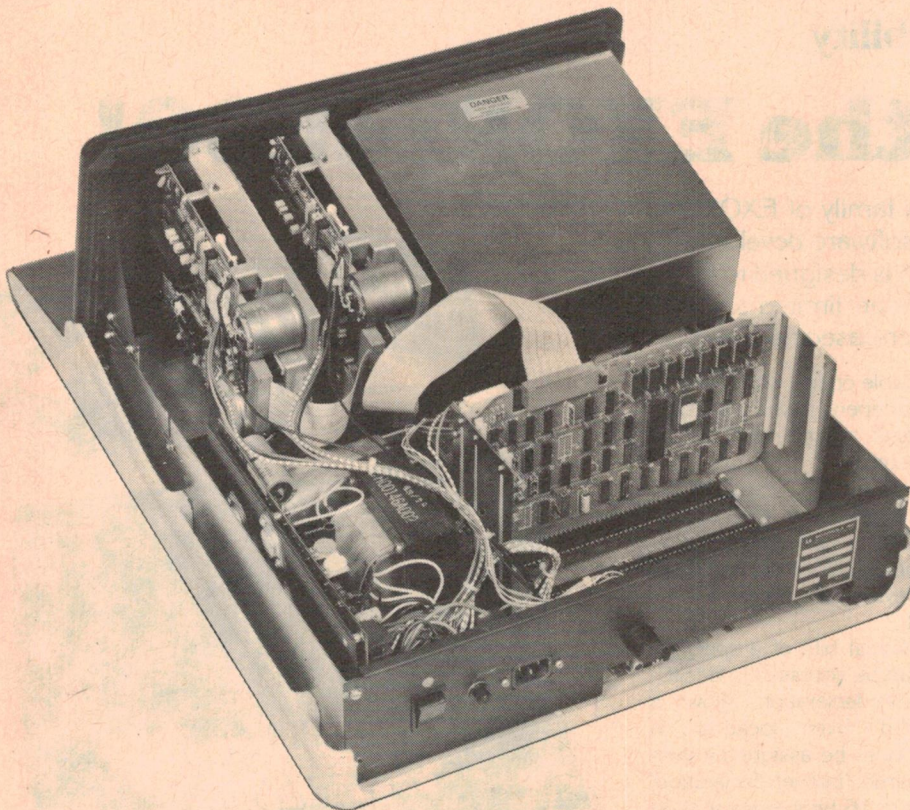

Inside the EXORset 30. Note the expansion card cage behind the enclosed VDU. Interface buss at lower right.

memory. Users can search for a specified 8-bit pattern, read and change the MPU register, trace with printout of a selected memory location or trace to ending address.

Up to 4096 hardware breakpoints are available within a 4K address range, in RAM, ROM,

and in any selected cycle of instruction, with real time execution at full speed between breakpoints.

In addition, the EXORbug operating system controls the screen and printer functions, transfers and verifies between audio cassettes and memory,

and controls the operation of EXORset 30 as an EXORciser terminal.

We were fortunate enough to have one of these machines to play with for a short while recently, along with some software on disk and a set of manuals. Pity that the period we

## Hewlett Packard donation

**Hewlett Packard Australia has donated \$35 000 to the Royal Melbourne Institute of Technology towards a computer upgrade of the administration of the college.**

The HP 3000 Series 2 is being upgraded to the Series 3 to provide one Megabyte of memory.

RMIT has developed three data base systems for use in Colleges of Advanced Education and Technical Colleges.

These include a Staff/Establishment system to provide management information on staff salaries, classification and personal information, a Finance System, and a Student/Academic Administration system which is used to assist student enrolments.



### Specifications


Microprocessor:	MC6809	Programmable timer module:	Yes
Clock Cycle Time:	1 MHz.	Software:	EXORbug monitor
Keyboard:	Full ASCII		XDOS operating system*
	16 function keys		ASM09 assembler*
Display Type:	9" CRT monitor		Text editor*
Display Format:			BASIC-M compiler/interpreter*
Alphanumeric	22 x 80 characters		BASIC-M runtime package*
or	16 x 40 characters		*disk resident
Graphic	320 x 256 dots	Power Supply:	100 - 130/200 - 250 V
Mass storage:	Dual mini-floppy disk drives	(jumper-selectable)	45 - 100Hz
Disk capacity:	2 x 80K bytes		100W
RAM capacity:	48K expandable up to 2-56K bytes	Overall dimensions:	
	(Additional 2K reserved for alphanumeric display)	length	640 mm (25.2")
Connectors:	2 Micromodule-compatible board connectors	height	280 mm (11.0")
Printer interface:	Parallel Centronics-type	width	465 mm (18.3")
Serial I/O:	RS-232C (or current loop with use of MM11)	Weight	22.2 kg (49 lb)

had the machine was so short, really, else we'd have a great deal more to say about it... no one on staff is all that familiar with 6800 machines and Motorola software so we couldn't rip straight into.

However, the graphics capability of the machine, from what we saw from the demonstration disk, is extraordinarily powerful. The on-board mass memory capability, quite apart from the available user RAM and ROM, makes the machine very versatile — more so when you consider the expansion capabilities. Just from our short first look — "... we think it 'mazing". And for something over \$6000, it's got to be a steal in its price/performance class. Maybe we can have one back to play with later... hmmm?

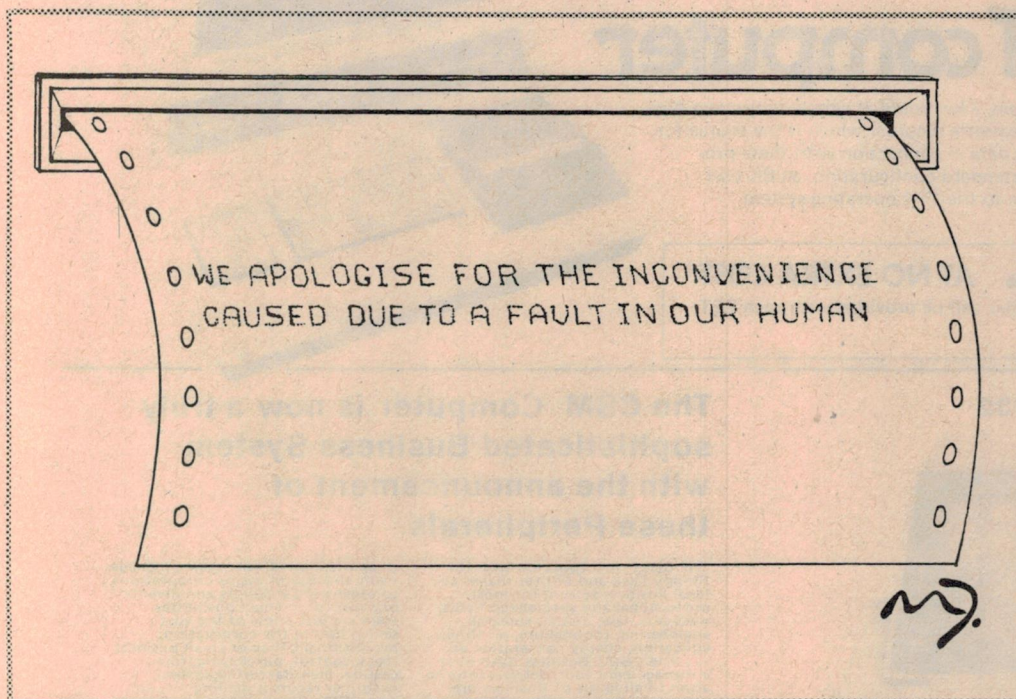More information from Rank Electronics, Sydney — 12 Barcoo St, East Roseville NSW 2069, (02)406-5666; Melbourne — 60 Rosebank Ave, Clayton South Vic 3169, (03)541-8444.





## TAFE courses

The IREE Microcomputer Interest Group are organising ten week computing courses which will begin in Brisbane the first week of September.

Three of the courses are hardware oriented and are entitled Digital Electronics and Logic Circuits, Introduction to Microcomputers, and Microcomputer Systems. A fourth course, called Microcomputer Software, deals with programming concepts in machine code and the use of assemblers. Last in the series is Introduction to Computer Programming, which will use the computer facilities at the various Brisbane colleges of Advanced Education.

Enrolments will be taken from August 11th and further details can be obtained from the QLD TAFE on (07) 224-7847 or 224-7839.

## Philips to push minis/micros

Philips Data Systems France are using the new 16-bit NMOS based P800 microprocessor at the heart of four new minicomputers and one microcomputer in an effort to expand their business machine market.

The computers have a cycle time of 650 ns and the cheapest machine, the P853 with 32K of memory will sell for around \$5000. The top of the line P859 has 16 registers and 1M of memory.

## New generation Z80

Zilog announce that refinements in process technology enable the latest version of their Z80 microprocessor to run at a clock rate of 6 MHz.

This is 50% faster than the Z80A and more than twice as fast as the original Z80 which runs at 2.5 MHz.

The Z80B is completely pin and software compatible with its predecessors and is said to be ideal for users who are currently

in Z80/Z80A design activities but need additional speed for specific applications.

The new microprocessor is priced at \$20 in plastic and \$31.85 in a ceramic package, for quantities between 10 and 100.

## Apple 2 enhancement

Apple computers with at least 48K of memory and a disc drive can now handle programs written for Z80 and 8080 based computers with a new card which fits in one of the buss slots.

The card is made by Microsoft Consumer Products of Bellevue, Washington. It is used with two diskettes — one for the CP/M operating system from Digital Research and the other for Microsoft's Disk Basic.

## Cobol for the TRS80

Tandy has announced the introduction of a Cobol interpreter suitable for the TRS80 Model 2.

The Vice President of Radio Shack, the US parent company, says that the Cobol language offered is an enhanced Level 2 ANSI '74 which has been adapted for the TRS80 and is similar to a minicomputer language rather than a more limited microcomputer version.

He states that although it is not suitable for use on the TRS80 Model 1, because of its limited memory, a condensed package will be introduced for this machine sometime in the future.

We have no information as to when it will be available here.

## Computerised newspapers

On the heels of the journalists' strike comes the announcement of Australia's first computerised metropolitan daily newspaper — the Advertiser of Adelaide.

The paper uses eight minicomputers and 30 microcomputers together with 138 video display terminals (VDT's) to automate the preparation of features, news and classified advertising.

Journalists type their copy on the VDT, storing the complete article on magnetic disks.

The editing stage is conducted by calling the file name on the editor's terminal and al-

tering the article on the screen.

A similar procedure is used for classified advertising.

Layout is performed easily on an enlarged screen called a 'page view terminal' (PVT) where the articles are called from the computer memory and moved around to achieve maximum visual effect on the page. When the editor is satisfied, the whole page is typeset photographically.



# commodore

## the PET computer

The Pet has a television screen, a keyboard as simple to use as a typewriter and a self-contained cassette recorder which is the source for programmes and for storing data in connection with these programmes. And it has, in its standard configuration, an 8K user memory. (This is in addition to the 14K operating system resident in the computer).

### **SPECIAL AT NO EXTRA COST**

\$200 value of programmes will be provided with each PET purchased



2001-16/32



## The CBM Computer is now a truly sophisticated Business System with the announcement of these Peripherals.

The CBM, incorporated with the Floppy Disk and Printer makes an ideal business system for most professional and specialized fields, medicine, law, dental, research, engineering, toolmaking, printing, education, energy conservation etc. . . . The CBM Business System as a management tool, delivers information to all levels of Business previously attainable only with equipment many times more expensive, the CBM Business system is one of the most cost efficient business tools today. It offers a wide range

of applications from logging management strategy in major corporations to organizing accounts and inventory control of small businesses. Here are just a few of the cost saving uses in the corporation, professional office or small business stock control, purchasing, forecasting, manufacturing, costing, customer records, mailing list, etc. The CBM Floppy Disk and Printer, a compatible business system at a reasonable price — Take a closer look at these Peripherals.



2040

## Dual Drive Floppy Disk

The Dual Drive Floppy is the latest in Disk technology with extremely large storage capability and excellent file management. As the Commodore disk is an "intelligent" peripheral, it uses none of the RAM (user) memory of the CBM. The Floppy Disk operating system used with the CBM computer enables a programme to read or write data in the background while simultaneously transferring data over the IEEE to the CBM. The Floppy Disk is a reliable

low cost unit, and is convenient for high speed data transfer. Due to the latest technological advances incorporated in this disk, a total of 340K bytes are available in the two standard 5 1/4" disks, without the problems of double tracking or double density. This is achieved by the use of two microprocessors and memory I.C.s built into the disk unit. Only two connections are necessary — an A/C cord and CBM interface cord.



2022

## Tractor Feed Printer

The Tractor Feed Printer is a high specification printer that can print onto paper (multiple copies) all the CBM characters — letters (upper and lower case), numbers and graphics available in the CBM. The tractor feed capability has the advantage of accepting mailing labels, using standard preprinted forms (customized), cheque printing for salaries, payables, etc. Again, the only


connections required are an A/C cord and CBM connecting cord. The CBM is programmable, allowing the printer to format print for: width, decimal position, leading and trailing zero's, left margin justified, lines per page, etc. It accepts 8 1/2" paper giving up to four copies. Bidirectional printing enables increased speed of printing.

CONTACT YOUR LOCAL DEALER FOR FURTHER INFORMATION, PRICING AND DEMONSTRATION.

Distributed by  
**HANIMEX LTD.**  
Commodore Business Machines Division.



# Print-out

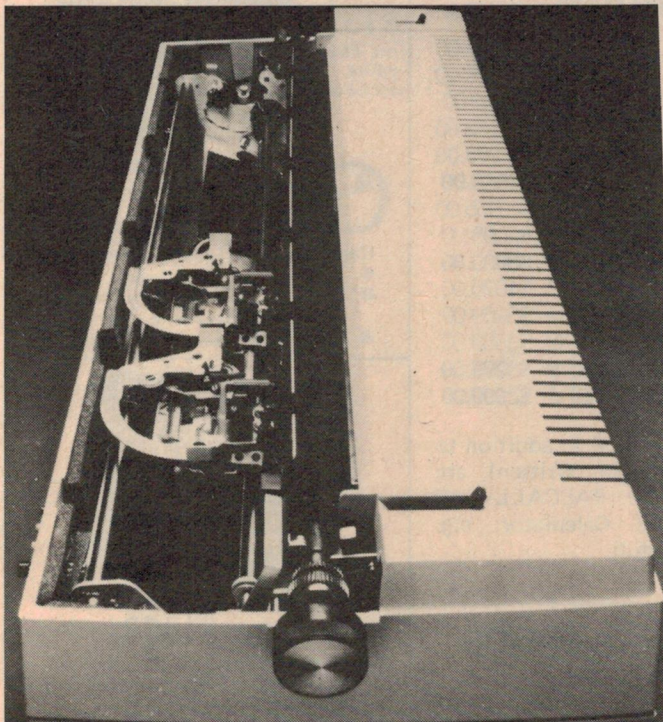

## Two heads are better than one

**A new twin-head character printer, the Qume Twin Track, has been introduced into Australia by ADE.**

This printer enables printing in two independent columns simultaneously.

Both heads use daisy wheels whose founts may be independent. This means that it is possible to include Greek or mathematical characters in text printed in normal typeface, as is required for instance in scientific documents.

It is also possible to print text in, say, English and Japanese

side by side. The Twin Track can be used to print at twice the normal speed of a single print head. Printing is also bi-directional to provide fast throughput.

The print area is 388 mm wide and printing speed is 45 characters per second. Further information can be obtained from Anderson Digital Equipment, P.O. Box 294, Ryde, NSW. (02) 808-1444.

### ERRATA ETI-681 PCG PROJECT (June issue)

There were a number of minor errors in the Programmable Character Generator, ETI-681, published in the June issue. Firstly, in Table 1 on page 69, the heading at the top of the left hand column should read "Value of Rp" as the values of RV1 and RV2 are fixed at 5k. On page 70, IC27 has a pin at the bottom marked "18" when it should be 15 — it's only a 16-pin chip, anyway! On page 73, in the parts list, R3 is listed as 1k9, 2%. A 1k8, 5% resistor is OK here. On page 74, under "Dip switch No.2:", second paragraph, the lines "We recommend that you put the joystick port at hex 'FF...' should say "... put the joystick port at hex 'EF...'". The joystick setup procedure is correct as it places the joysticks at EF.

In addition, a number of typographical errors appeared on the circuit diagram on page 70. Address lines A11, A13 and A14 were shown as going to pins 27, 35 and 36 respectively. This is incorrect. A11 goes to pin 87, A13 to pin 85 and A14 to pin 86.

## Eyes and ears for your PET

**Edible Electronics are importing a new analogue to digital input conversion system for the popular PET microcomputer.**

Known as PETSET, the system will give PET users an interface between their computer and the real world, allowing them to monitor up to sixteen physical variables at a time. One of the inputs may be used for a joystick control which is provided as part of the package.

Two input modes are possible — ratiometric and absolute. In the ratiometric mode the PETSET gives a digital output which corresponds to the ratio of the actual input to its

maximum value; in the absolute mode, raw voltages in the range  $-0.3\text{ V}$  to  $+5.4\text{ V}$  produce a digital output of one pulse per 20 mV input.

The number of potential applications is enormous, since the ratiometric mode allows almost any kind of transducer to be used. One good suggestion by the manufacturers is to use the PETSET for monitoring temperature, humidity, light intensity, soil moisture and pH in greenhouses.

Edible Electronics (03)41-5708.

## Siemens ink jet

**Siemens has introduced an ink jet version of their impact printer, the PT80i.**

It uses an 8085 microprocessor to control the bi-directional printing mechanism and ensures that the print head covers as few empty spaces as possible to triple the speed to 270 characters/second.

The 12 vertically arranged ink jets can produce up to 125

different characters in a 12 x 9 point matrix. The machine uses normal paper and can be switched for normal, cursive, or wide character printing.

With appropriate character generators, the PT80i can produce national alphabets as well as ASCII standard characters.

## Recycling by computer

**The computer owned by the Southwestern Bell Telephone Company of Abilene, Texas made rather a blunder when it was listing the Yellow Pages of this year's telephone directory.**

More than 70 000 phone books were distributed with a tasteless error in the entries in the category of "Frozen Foods-Wholesale": a local funeral parlour was featured! Yuk.

The same computer sought to compensate the same company by including its subsidiary which sold life insurance in the category "Funeral Homes"!

Note that this was not the same computer which almost recycled us all when it scrambled the US airforce in a false missile alert in June.

## PET gets new handler

**MicroPro Design has become an authorised dealer of Commodore products such as the PET microcomputer and the CBM business system.**

The engineers and programmers at MicroPro Design will offer maintenance, custom interfacing and applications software. They have already developed a number of interfaces for the Commodore

IEEE 488 buss which are manufactured locally.

For further information contact MicroPro Design, P.O. Box 153, North Sydney NSW. (02)438-1220.




# Buy Direct from the Independent Importer



**\$950**  
inc. Tax
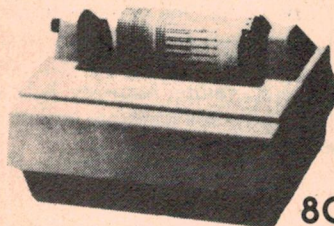
## Amp 88T

- Selectable Character Densities 80, 96 or 132 Characters per line
- 96 Character ASCII Set
- Upper and Lower Case
- 7 x 7 Matrix
- Bi-directional
- 100 Characters/second
- Parallel and Serial Interfac




801

## IMPACT DATA

- Impact Matrix Printer
- 132 C.P.S.
- High Quality
- Heavy Duty
- 7 x 7 Dot Matrix
- Use with Apple, TRS-80, PET, Ohio Scientific
- Available ex-stock

**\$899**  
inc Tax

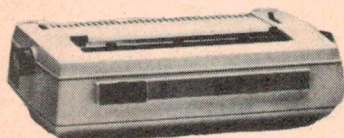

## Qume®

### Daisywheel Terminal

- Typewriter quality print
- 96 Printable Characters and Symbols
- Six to Ten Copies

## TI 810

**\$2495**  
inc. Tax

- Bidirectional
- 256 Ch. Buffer
- 9 x 7 Dot Matrix
- Up to Five Copies
- Adjustable Wide Carriage up to 132 Column
- Rear or Bottom Feed
- Full ASCII Character Set
- 150 C.P.S.

## Ohio Scientific

### New Range

ex TAX

SUPERBOARD II	@ \$ 369.00
CIP (8K)	@ \$ 499.00
CIP (MF)	@ \$1555.00
NEW CIP II (18K Ram/Rom)	@ \$ 589.00
NEW 630 Board (Colour & I/O CIP)	@ \$ 289.00
NEW CIP II (MF)	@ \$1649.00
C4P	@ \$ 865.00
C4P (MF) Mini-Floppy	@ \$2095.00
NEW C4P (DF) Dual 8" Floppy	@ \$3099.00
C8P	@ \$1075.00
C8P (DF) Dual 8" Floppy	@ \$3269.00
C2 - OEM	@ \$3559.00
NEW C2-D with 8" Hard Disk (10MB)	@ \$8295.00
NEW C3-D with 8" Hard Disk (10MB)	@ \$8999.00

NEW SOFTWARE AVAILABLE in addition to Business Packages (Australian Written) are SARGON (CHESS), USCD PASCALL and FORTRAN and Universal Calculator. e.g. (VISI-Calc. but more powerful); Prices available on request.

## IMS Business Systems

### IMS 8000

This attractive business Computer is an S - 100 based system incorporating a Z - 80A 4MHz C.P.U. card with 2 RS232C Serial Ports. Disk Storage is via 2 Shugart SA800/801 disk drives providing up to 960 K bytes/drive. Comes complete with 32K static RAM (expandable to in excess of 500 k bytes). Operating System is either CP/M™ or UCSD PASCAL Software System.

### IMS 5000

Features 5¼" disk drives and can expand to three disk drives in same cabinet.

### Software

These transportable software packages run on any machine using the standard CP/M™ operating system and CBASIC 2™. Designed in Australia using standard Australian Accounting practices and Australian Date Formats.

#### Systems Available:—

- General Ledger
- Accounts Receivable
- Accounts Payable
- Inventory
- Payroll
- Direct Mail
- Word Processing

~~\$1466~~

**\$1395**


inc Tax while stocks last



## SOROC IQ 120
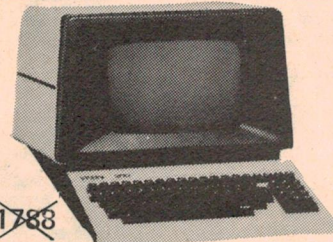
### Remote Video Display Terminal


- Upper and Lower Case
- 24 Line Screen, 80 characters per line
- Numeric Keypad
- 1920 Character Screen Memory



~~\$1788~~

**VISUAL 200 \$1688** inc. Tax

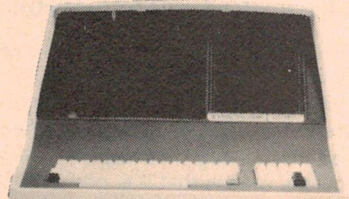- Self contained Micro-processor based terminal
- Numeric Keypad
- Full ASCII Keyboard
- Standard features include Line drawing, Switchable Emulations Background/Foreground Modes
- Programmable Function Keys



**SUPERBRAIN™ \$3995** inc. Tax

- Two 5¼" Double Density Mini Floppies
- 64K RAM
- 12 Inch CRT
- CP/M Disk Operating System
- Full ASCII Keyboard with numeric Pad and user-programmable function keys.

## TI 825

**\$1995**

inc. Tax

- 132 Columns
- Upper and Lower Case
- Bidirectional
- 9 x 7 Dot Matrix
- 75 C.P.S.

KSR Versions of TI810/825

DEALER ENQUIRIES WELCOME


# THE ELECTRONIC CIRCUIT

SUITE 414, 4th FLOOR, 20 DUNCAN STREET, FORTITUDE VALLEY - 528455  
BRISBANE'S CALCULATOR/MICRO-MINI COMPUTER CENTRE

\*Prices Subject to Change without notice and while Stocks last.



## Logic with memory

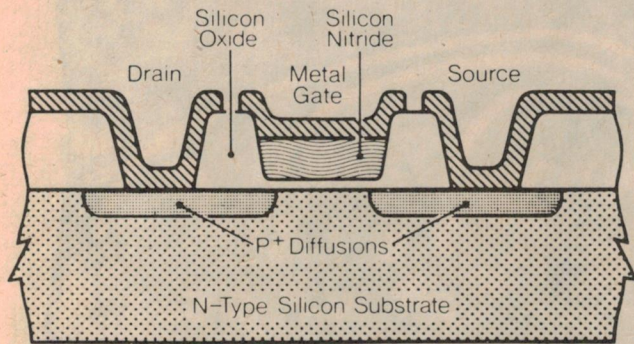

**A range of non-volatile logic products using MNOS FETs has been introduced to Australia by Plessey.**

The MNOS FET construction prevents stored charge under the gate of a FET from leaking away through surface effects, which is the problem with conventional chip construction.

Charge may be stored for up to one year at the interface between the silicon oxide/silicon nitride interface under the gate (see diagram).

The range of devices using this technique include a 4-bit

data latch with output enable, (MN9102) a four decade BCD counter with 16-bit memory and a 4-bit latch (MN9105), the MN9106 6-bit counter with 24-bit memory and multiplexed output, and the MN9107/8 which are adaptations of the MN9106 for use in timer applications. Further details can be obtained from Plessey, P.O. Box 2, Villawood, NSW 2163. (02) 72-0133



## New disk will store 6.3M

**Shugart Technology of California has developed a new 133 mm (5") Winchester disk drive which will store 30 times more data and transfer it 20 times faster than a standard mini floppy.**

The Shugart ST506 uses standard Winchester head technology to store 6.3M of data in unformatted form. The disks have 153 tracks and access time is 170 ms on average.

The US price is \$1500 /drive.

Shugart have also introduced two new 203 mm (8") fixed disk drives into Australia. These are

designed for use in microcomputer systems and provide the user with 5M or 10M of storage. Data transfer rates of 4.34 Mbits/sec for the SA1002 and SA1004 fixed disks are specified, using double density recording.

These "low cost" disk drives and further details can be obtained from Warburton Franki.

## New Apple

**Apple Computer of the US have released details of their new Apple 3 micro which is aimed at the serious hobbyist and small business user.**

The computer has two versions: the 'Information Analyst' and the 'Word Processor'.

The Information Analyst is designed to be used as a tool for business planning, modelling, forecasting, scheduling, budgeting and costing. It has 96K of RAM, a 133 mm (5") minifloppy disk drive and a keyboard with two extra keys with program-defined functions to enable commands to be executed with a single key stroke.

The peripheral options include a thermal printer or letter-quality printer, and 305 mm CRT monitor or colour monitor for colour graphics.

Software includes a Mail List Manager, Business Basic, Visicalc 3 and the company's Sophisticated Operating System.

The Word Processor differs from the business version in the provision of a second disk drive and alternative software.

The Apple 3 can be expanded up to four disk drives and up to 128K of random access memory. The prices for the Australian market have yet to be announced but will be around \$4000 for the Information Analyst and \$5400 for the Word Processor.

## Budget micro for novices

**At \$550 the Series 2 C1P is designed specifically to appeal to people buying a computer for the first time.**

The makers expect its low price and versatility will make it attractive to schools and other educational institutions, who will be able to purchase two or three C1Ps for the price of one of their more expensive competitors.


The standard system has 8K of memory and a cassette input, but plug-in boards are available which can expand the memory to 32K, allow the computer to accept inputs from two floppy disks, and drive a printer. In addition there is a minifloppy version of the C1P, the MF Series 2, which offers a dual floppy disk facility.

Both the standard and the minifloppy versions can be used with an I/O Expander to give colour displays, remote keypad operation, dual joystick control and programmable sound and musical effects.

A wide range of support material is offered, in the form of educational, entertainment and small business programs, and a data base management system option allows users with no knowledge of programming to store information on diskette for instant recall.

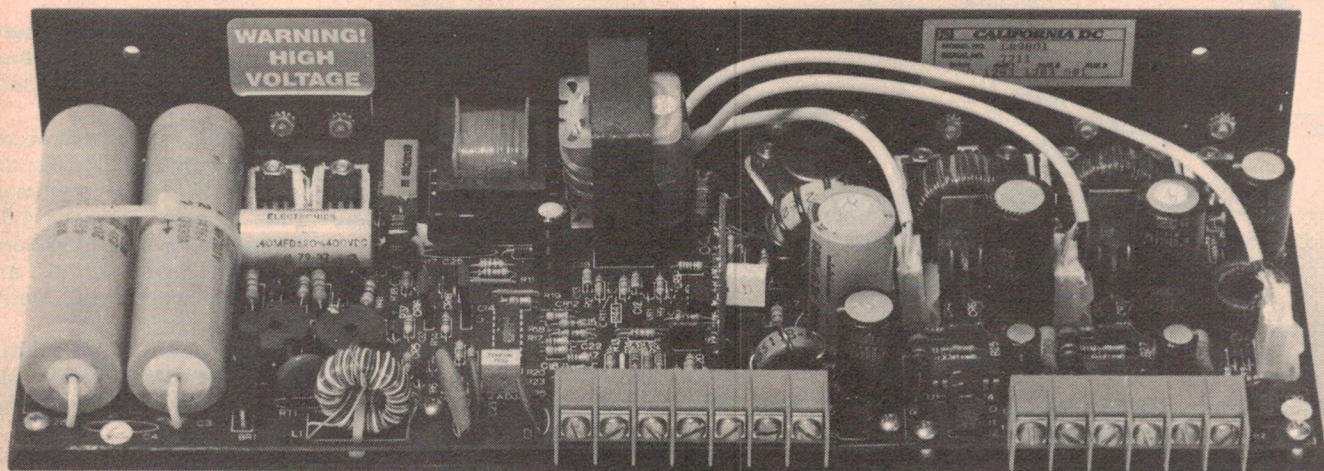Enquiries to Systems Automation Pty Ltd, 31 Hume St, Crows Nest NSW 2065.





## New power supply

A new range of switching regulated power supplies, designed for use in microcomputers, disk drives and industrial controls, was recently introduced by MicroPro Design.

The supplies are smaller and lighter than linear, series-regulated supplies. The MicroPro LR range includes versions with up to four independent output voltages.

The California DC range of switching power supplies available from MicroPro Design range in price from around \$170 to \$330.

Standard features include 20 percent line tolerance, thermal protection, 50 mV peak-to-peak ripple and noise and 70 percent minimum efficiency at full load.

Further enquiries to MicroPro Design, P.O. Box 153, North Sydney 2060 NSW. (02) 438-1220.

## Renaissance software

The Logic Shop are now selling the following software packages for the CompuColor 2: (the "Renaissance Machine") a Word Processor (\$75), Basic Tutorial Lessons (\$36), Fortran Compiler (\$92), and Inventory (\$100).

The Word Processor includes the usual edit functions, right margin adjust, automatic paragraph indent and spelling corrections. The tutorial lessons in Basic are aimed at the beginner and it is claimed that even school children should be able to program after the series of ten lessons.

The inventory package allows the storage of up to 900 goods classifications on a minifloppy disk. It should therefore be suitable for many small businesses including the corner store, maybe! Further details can be obtained from The Logic Shop in Melbourne (03) 51-1950, or Sydney (02) 699-4919.

## Computers out to stud

Computerland of Melbourne have released a set of programs written in Basic which may be of interest to the farming community who have access to an Apple microcomputer.

The 'stud book' programs enable the listing, for up to 100 animals, of information such as family trees, offspring of any animal, all information for any animal, animals born or sold within a period of time, select animals with a combination of characteristics and find animals with a certain characteristic.


The programs require an Apple II micro with 48K of memory and a disk drive. The programs have been developed in Australia to suit the requirements of breeders here and it is hoped to develop further programs for rural applications over the next 12 months.

For precision soldering  
Light weight. High power.

### ADCOLA STANDARD

No frills. Just high performance.

3mm S 30 5mm S 50

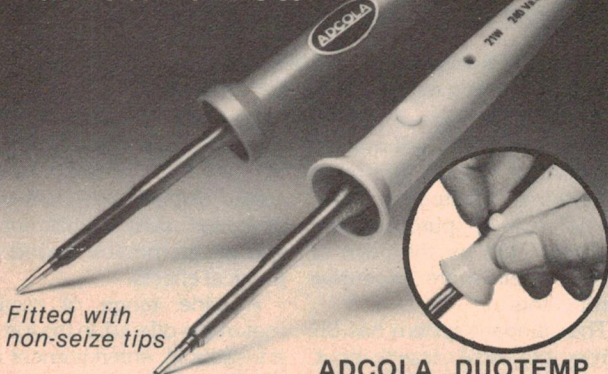

Fitted with  
non-seize tips

Fully automatic  
'THERMATIC'  
also available.

### ADCOLA DUOTEMP

Temperature control at  
your fingertips.

3mm D 30 5mm D 50

From your radio parts supplier or :

**Royston Electronics**

N.S.W. (02) 709 5293 Q.L.D. (07) 391 8011  
VIC. (03) 543 5122 S.A. (08) 42 6655  
TAS. (002) 34 2233 W.A. (09) 381 5500


**ADCOLA**

SD2D







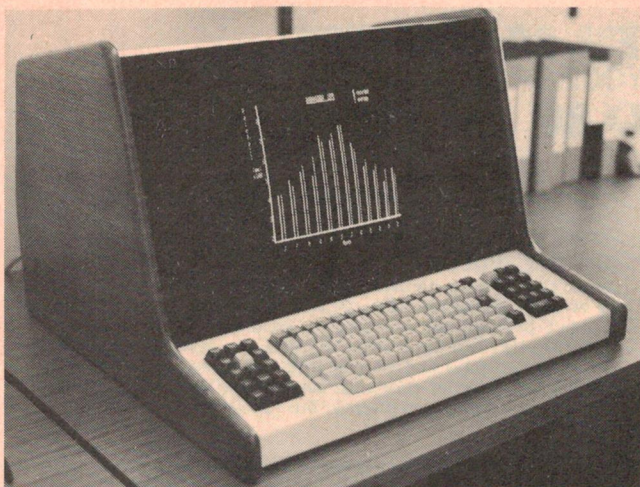

**STANDARD ARE ALL THE FEATURES YOU WOULD LIKE BUT WERE AFRAID TO ASK THE PRICE OF.**

- WIDE, 16 MHz BANDWIDTH.
- 160 x 96 GRAPHICS FOR BUSINESS AND TREND ANALYSIS, CURVED BAR CHARTS ETC.
- HALF TONE, UNDERLINE, BLINKING, STRIKE THRU, REVERSED VIDEO, BLANK OUT, OR ANY COMBINATION OF THE SCREEN AT ONCE.
- SHARP, GREEN PHOSPHOR SCREEN.
- CONTRAST ENHANCING FILTER.
- SUPERB, SCULPTURED WORD PROCESSING KEYBOARD.
- STRONG WELL ENGINEERED HOUSING SCULPTURED FROM SOLID TIMBER AND METAL.

**ALSO WE CAN PROVIDE 256 x 256 OR 512 x 256 HIGH RESOLUTION GRAPHICS AS AN OPTION.**

## THE INCREDIBLE A.E.D. S100 Terminal

# THE UN-SERIAL

**MORE FEATURES! MORE SPEED!  
MORE SALUBRIOUS THAN ANY  
SERIAL TERMINAL WE KNOW.**

**CAN OUTPERFORM SERIAL  
TERMINALS PRICED ABOVE \$2300.**

**YET ONLY \$1350 + SALES TAX  
FULLY INCLUSIVE.**

**'CP/M' PATCH SOFTWARE  
AVAILABLE FROM A.E.D.**

**THE TERMINAL YOU DESERVE!**

This memory mapped terminal can be configured to have the intelligence of top serial terminals such as Hazeltine, Lear Siegler, Soroc 'etc' without the eye strain and sludgy slow speed.

**WE ARE NOW GAINING A NAME FOR OUR 8" DISK SYSTEM FOR**

## SORCERER

- 8" IBM SINGLE AND DOUBLE DENSITY.
- 600K BYTES PER DISK — ALMOST TWICE AS MUCH AS QUAD DENSITY 5" SYSTEMS.
- MORE SPEED AND DATA RELIABILITY THAN 5".
- CP/M PROVIDED FULLY INTEGRATED WITH THE SYSTEM.
- CAN READ AND WRITE SINGLE DENSITY AS WELL AS 256, 512 OR 1,024 BYTE DOUBLE DENSITY FULLY TRANSPARENT TO THE USER.
- PRICED GENERALLY LESS THAN MICROPOLIS 5".
- INCLUDES SHUGART DRIVE(S), CABINETS, CABLE AND CONTROLLER + CP/M DISK OPERATING SYSTEM.

**PRICED FROM \$1285.20+ SALES TAX**

*DESIGNED BY GEORGE MORROW, THE GUY MOST  
INSTRUMENTAL IN WRITING THE IEEE SPEC FOR S100*

## SEE US ALSO FOR:

- SYDNEY'S BEST VALUE IN STATIC RAM ALSO BY GEORGE MORROW.
- VIDEO CARDS, I/O CARDS ETC.
- PROTOTYPING BOARDS, SOCKETS WIRE WRAP "SLIT AND WRAP".
- DRIVE CABINETS FOR YOUR RENEX, OR SHUGART OR SEIMENS DRIVES.
- KEYBOARDS AND ENCLOSURES.
- S100 CABINETS.
- COMPUTER FURNITURE.
- VIDEO MONITORS "WIDE BAND WITH GREEN PHOSPHOR".

**IN FACT, ALL YOUR S100 NEEDS.**




# MICROCOMPUTER PRODUCTS

123 Military Road, Guildford,  
NSW 2161. Phone (02) 632-6301  
(02) 632-4966. Telex AA25958.



# Here at last !

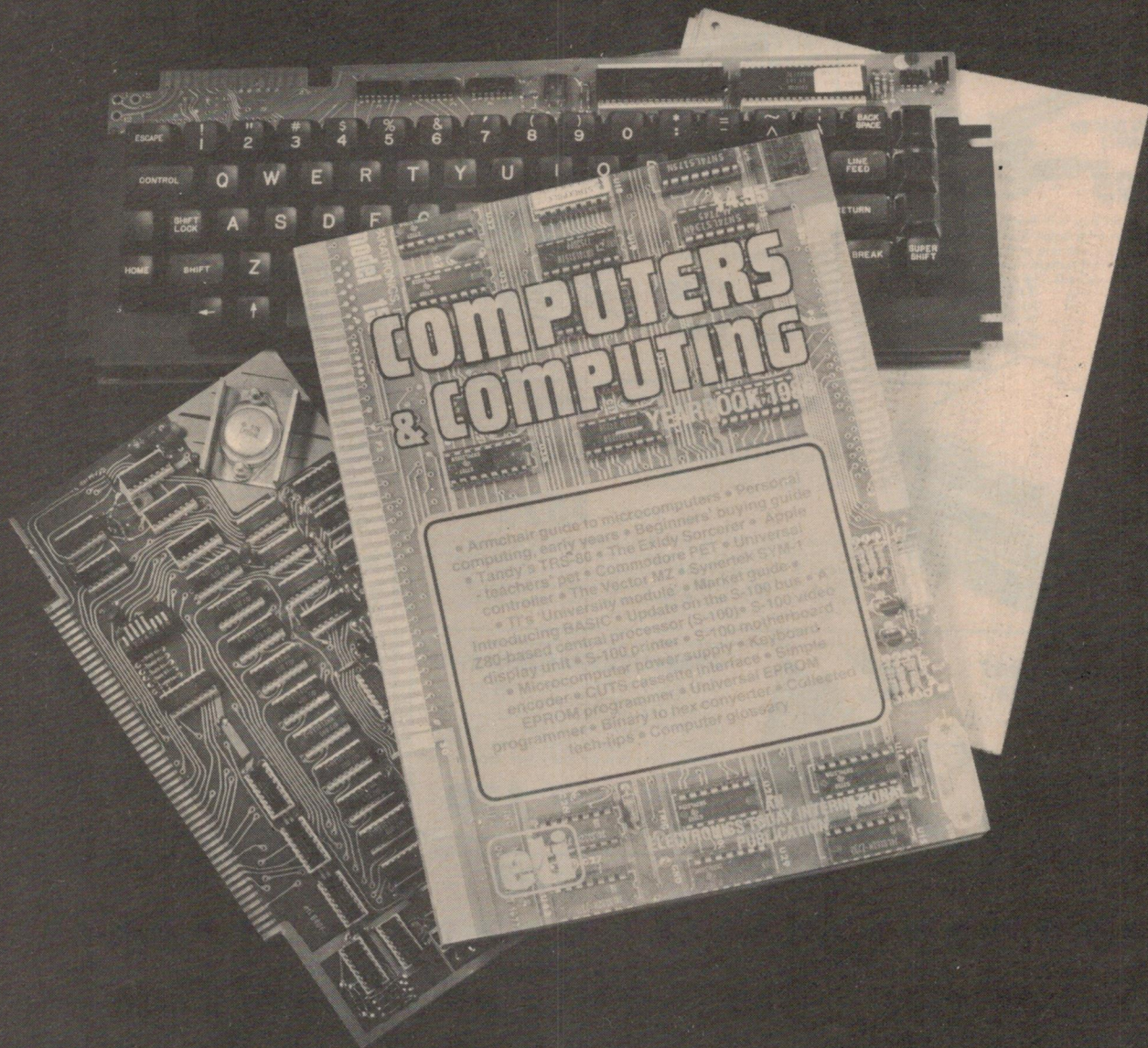

A book on computing that takes you from *what-is-all-this-fuss-about-computers* through a thorough *beginners'-buying-guide* to *building-your-own-computer*.


When faced with the awesome task of choosing or assembling a computer system — whether you want a “learning aid” or a “working tool”, a “ready rolled machine” or “project kit”, you’ll find very few places to go. This book rolls it all into one. Assembled from articles published in Electronics Today International over the past few years, *with additional material to aid the newcomer*, it’s an invaluable reference work. Running to 156 pages, this book contains 16 articles on various aspects of computing and 10 construction projects.

On sale now at newsagents and selected specialist suppliers, or direct from **ETI Subscription Department, 3rd Floor, 15 Boundary St, Rushcutters Bay NSW 2011**. Price: \$4.95, plus 65 cents post and handling.



# HARDWARE
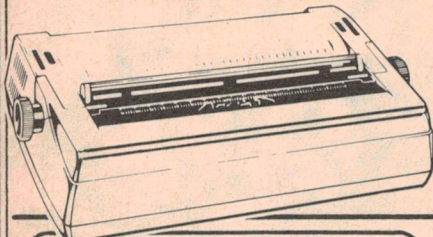
## PROFESSIONAL DAISY WHEEL PRINTER FOR WORD PROCESSOR SYSTEMS



This superb unit is a self-contained printer with in-built asynchronous serial interface conforming to the established RS-232C standard. It prints on business stationery up to 380mm wide at the rate of 45-55 characters per second - three times faster than golf-ball typewriters. Top quality office systems printer that is below competition prices.

**\$3,390.00**

Cat. X-3260

## LIGHT PEN FOR TRS-80 OWNERS

TRS-80  
LEVEL II  
ONLY

FOR SYSTEM 80  
AS WELL

**\$9.95**

Use this light pen with the TIC-TAC-TOE cassette shown below or with the SKETCH 80 (see opposite page). Comes complete with plug for insertion into your cassette and battery snap for 9V transistor type battery (not supplied).

### TIC-TAC-TOE

Just insert this program cassette into your computer cassette player and enjoy playing the game with your light pen.

**\$11.95**



## MICROPOLIS™ QUAD DENSITY DISC DRIVE


The Micropolis mod 2 drive with controller enables you to store 315,000 bytes on just 1 disc. By adding the mod 2 add-on drive (up to 3) you can obtain up to a maximum of 1.26 Megabytes! Complete with all software to enable you to be up and running in a very short time.

Model 1043/mod 2 with controller.

Cat. X-3205 **\$1,350**


Model 1023/mod 2 add-on

Cat. X-3208 **\$750**

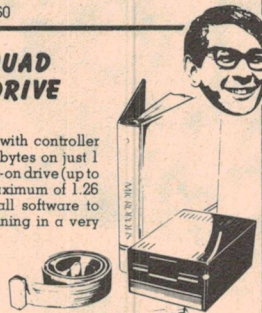
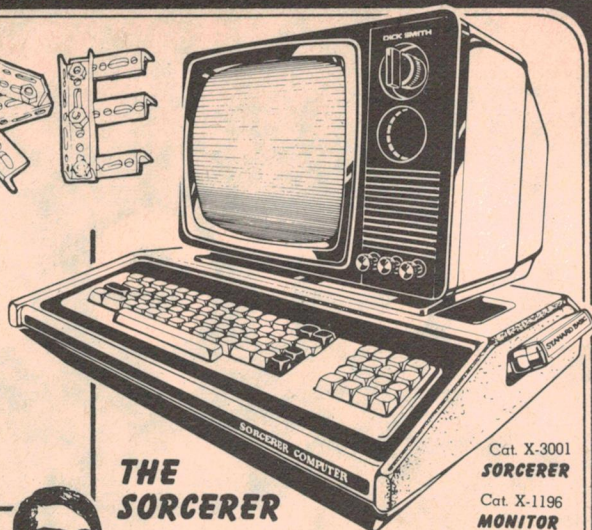
## THE SORCERER

Cat. X-3001  
**SORCERER**  
Cat. X-1196  
**MONITOR**



The Sorcerer is the expandable Z-80 based micro-computer that allows you to add peripherals to take it from basic computing through to advanced office business systems.

● 16K RAM expandable to 48K (on board) ● Serial I/O and Parallel I/O ● S-100 BUS compatible ● Cassette I/O for two recorders at speeds of 300 or 1200 baud ● Video I/O - 1920 characters full screen ● Full ASCII 128 characters (64 defined characters and 64 undefined characters) ● Graphic resolution 122,880 pixels ● Includes 8K BASIC plug-in ROM PAC™ in MICROSOFT™ ● Dimensions 490 x 330 x 100mm ● Weight 6 kilograms.

(Ask for our FREE comparison chart between the Sorcerer and other well known computer brands).

Dust cover to suit  
Cat. X-3005 **\$3.95**

**\$1,395.00**

## VIDEO MONITOR

This is a superb 30cm black and white video monitor that can be used on AC and DC. Simple connection to your computer. Features jitter free and distortion free characters. Can be used with most computers on the market.

Cat. X-1196

**\$149.50**

## WORD PROCESSOR PAC

Remove the plug-in BASIC PAC™ and replace it with the powerful WORD PROCESSOR PAC™ and you will have the basis of an office computer system.

Features: ● Automatic text wrap ● Automatic checking of drastic commands ● Powerful search function ● Auto commands ● Macro programming - all this plus extensive user instructions.

Cat. X-3085

**\$275.00**

## SPECIAL WORD PROCESSOR KEYS

To enable you to use the Sorcerer's Word Processing function more readily we can supply specially embossed keys (11 units) to replace the normal beige keys. The colour allows you to identify the special keys immediately. Just another touch of professionalism for the Sorcerer owner.

Cat. X-3086

**\$14.95**

## FAMOUS 'BLUE BOARD' PLUG-IN CARD MODULES FOR THE S-100 BUS...

And now for the famous 'Blue Boards' from SSM in the US of A. Three boards available for your S-100 unit in ready built form or as kits with comprehensive instructions.

### 2 PARALLEL & 2 SERIAL I/O BOARDS

2 serial I/O ports (2 in and 2 out) with full handshaking status from UART's and 2 latched I/O ports (2 in and 2 out) using 8212 latch buffers. Independent DIP switches for setting address of serial and parallel port blocks. Ideal for the person who wishes to control a number of appliances in the home, office and factory.

Built unit Cat. X-3300 **\$250.00**

Kit form Cat. X-3301 **\$190.00**

### MUSIC SYNTHESIZER BOARD

A fantastic synthesiser with a frequency range of 15Hz to 25KHz with a nine octave frequency change via software. Attack and sustain can be defined by user. Includes "MUS-X1" a high music interpreter which can drive up to 8 boards at once - even includes a music program to get you up and going fast!

Built unit Cat. X-3305 **\$310.00**

Kit form Cat. X-3306 **\$250.00**

### 8K & 16K PROGRAMMER & 4K/8K EPROM BOARD

Now you can program your EPROM's (2708 or 2716) and also have the facility for on-board 4K of 2708 or 8K of 2716 EPROMs. This extends the capabilities of your computer system and provides a powerful unit for those who wish to do their own programming on EPROMs.

Built unit Cat. X-3310 **\$250.00**

Kit form Cat. X-3311 **\$190.00**

## EXIDY S-100 BUS EXPANSION


By using plug-in cards with the S-100 BUS and your Sorcerer you can use many other manufacturers peripherals (see our special 'Blue Board' cards on this page). The world of computing has been made even more exciting through the S-100 BUS. Comes complete with in-built power supply, ribbon cable and connector.

Cat. X-3010

**\$575**

● Allows up to 6 plug-in cards ● Connects directly to Sorcerer's 50-way expansion socket via supplied cable ● All S-100 lines fully buffered ● Separate 2.000MHz crystal clock provided for S-100 cards which cannot use the  $\phi 1$  and  $\phi 2$  clock signals derived from the Sorcerer's 2.106MHz clock ● Provision for mounting up to six 25 pin "D" connectors for additional I/O ports, etc.

## C.I.TOH BRAND DOT MATRIX PRINTER

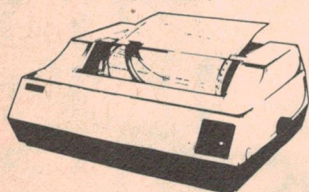

The model 8300P dot matrix printer is a non-sense unit that can churn out the full 96 character ASCII at a brisk 125 characters per second on standard fan-fold paper. Character spacing of 80, 40 or 132 columns which are software selectable. A quality unit that costs less than \$1,000!!

Cat. X-3255

**\$970.00**

## JABEL COMPUTER MAINS FILTER

Having trouble with memory crashes? Then the answer is the Jabel Mains Filter - it will remove those annoying spikes from the 240V mains and thereby protect your memory!

Cat. M-9850

**\$75.00**

## SERIAL DATA CABLE

Connect 2 cassette recorders to your Sorcerer and be able to control them both from your computer keyboard.

Cat. X-3110

**\$34.50**

## PRINTER INTERFACE CABLE

Connect your Sorcerer to the C.I.TOH printer or any Centronics compatible printer.

Cat. X-3112

**\$49.50**

## DYNAMIC EXPANSION KITS

These are top quality ICs that can expand your basic 16K Sorcerer to 32K or even 48K (expands the 8K to 16K etc). They can also be used with the TRS-80 level I and II and the Apple II computers to expand their on-board RAM. Superb value and complete with installation instructions.

SAVE **\$30.50** NOW **\$79**



## CASSETTE RECORDER

For cassette storage of data, or for loading programs into your Sorcerer you need a quality cassette recorder that has been tested and found to be reliable. The National Panasonic was tested by us along with other units and came out as the best unit available in its price range. Works on AC or DC and can be controlled from your Sorcerer.

Cat. A-4095

**\$79.95**



## NEW NEW NEW DUE IN SHORTLY

### COGNIVOX™ VOICE INPUT & OUTPUT FOR THE SORCERER

- ★ Recognizes up to 16 words.
- ★ 16 word voice response vocabulary
- ★ Easy two pass training
- ★ Up to 98% recognition accuracy
- ★ Generates music & sound effects
- ★ Excellent software support
- ★ Connects directly to Sorcerer

Cat. X-3150

**\$199**



# SOFTWARE



## FOR YOUR SORCERER

### MAGIC MAZE

A challenging game with 10 levels of play - wander through the maze and meet many obstacles. Automatic scoring on screen.

Cat. X-3620 ..... **\$14.95**

### PLOT

Get superb graphics in both super high resolution mode and quick low resolution mode.

Cat. X-3621 ..... **\$17.95**

### Z-80 DISASSEMBLER

Decode machine language programs, including Sorcerer's monitor and ROM PACs. Written in BASIC the instruction mode prints out machine code and Zilog mnemonics in standard format. Or use the ASCII mode which converts machine code to ASCII.

Cat. X-3622 ..... **\$17.95**

### SHAPE MAKER

On screen character editor for special characters and shapes. Lots of fun and includes 12 page manual with examples.

Cat. X-3623 ..... **\$17.95**

### DEBUG

Debug machine language programs by stepping through one instruction at a time. Relocatable. Several display options. Multiple break points. Modify memory and registers.

Cat. X-3624 ..... **\$17.95**

### FASTGAMMON

Backgammon players will find this program a skillful opponent. Has ultra sharp screen graphics and comes complete with an 8 page booklet with rules of the game.

Cat. X-3625 ..... **\$22.95**

### MARTIAN INVADERS (NEW)

Similar to the very popular 'Space Invaders' you find in amusement parlors.

Cat. X-3626 ..... **\$17.95**

### NIKE II (NEW)

Fight off bombing attacks with your missiles and protect the city from heavy casualties.

Cat. X-3627 ..... **\$14.95**

### TANK TRAP (NEW)

Render the marauding tank harmless but watch out for slow drying cement and unarmed citizens!!!

Cat. X-3628 ..... **\$14.95**

### GRAPHIC GAMES

Land on the moon in a LEM, lob a pie, nuclear reaction, bounce, checkers and dodgem - games of skill, games for fun.

Cat. X-3631 ..... **\$14.95**

### SMART ALEC

Answer over 200 questions that the computer gives you and let it decide whether you're a genius or not.

Cat. X-3632 ..... **\$14.95**

### ADVENTURELAND

Recover the 13 treasures from the enchanted world, but watch out for the unexpected.

Cat. X-3633 ..... **\$12.50**

### MISSION IMPOSSIBLE

Enter the world of suspense as you try and save the world's first automated nuclear reactor.

Cat. X-3635 ..... **\$12.50**

### VOODOO CASTLE

Rescue the Count from his castle after he has had a fiendish curse placed on him - you're his only hope!

Cat. X-3636 ..... **\$12.50**

### THE COUNT (NEW)

Another exciting game for you and your Sorcerer to play.

Cat. X-3638 ..... **\$12.50**

### WILDERNESS (NEW)

Trudge through uncharted lands fighting off with swords and sorcery the foul monsters that live there.

Cat. X-3639 ..... **\$12.50**

### BLACKJACK

Play the table in this ever popular game of 21's, pontoon, blackjack. Whether you win or lose, it's a fantastic game.

Cat. X-3602 ..... **\$9.95**

### WUMPUS

This is a great game of hunt the Wumpus through 20 rooms with a bent bow and arrow!!!

Cat. X-3604 ..... **\$9.95**

## SKETCH 80

### For the TRS-80 and System 80

A program tape that allows you to sketch on your VDU - the light pen becomes a real writing tool with this tape program.  
SEE THE LIGHT PEN ON PREVIOUS PAGE

Cat. X-3646 ..... **\$17.95**

## FROM

# DICK SMITH ELECTRONICS



<b>NSW</b>	125 York Street, SYDNEY Ph 290 3377	<b>VIC</b>	399 Lansdale Street, MELBOURNE Ph 67 9834
147 Hume Highway, CHULLORA Ph 642 8922	656 Bridge Road, RICHMOND Ph 428 1614		
162 Pacific Highway, GORE HILL Ph 439 5311	166 Logan Road, BURANDA Ph 391 6233		
30 Grove Street, PARRAMATTA Ph 683 1133	842 Gympie Road, CHERMSIDE Ph 59 6970		
396 Lane Cove Rd, NORTH RYDE Ph 888 3200	96 Gladstone Street, Fyshwick Ph 80 4944		
263 Keira Street, WOLLONGONG Ph 28 8000	60 Wright Street, ADELAIDE Ph 212 1962		
613 Princes Highway, BLAKEHURST (Opening Soon)	414 William Street, PERTH Ph 328 6944		

**MAIL ORDER CENTRE: PO Box 321, NORTH RYDE NSW 2113. Ph 888 3200. PACK & POST EXTRA.**

**SHOPS OPEN 9AM to 5.30PM**  
(Saturday: 9am till 12 noon)  
**BRISBANE: Half hour earlier.**  
ANY TERMS OFFERED ARE TO  
APPROVED APPLICANTS ONLY  
RE-SELLERS OF DICK SMITH  
PRODUCTS IN MOST AREAS

## FOR YOUR TRS-80 COMPUTER

### TIME TREK

For TRS-80 4K level I and II. Hunt the Klingons through space and fight an intergalactic war. Has nine levels of play.

Cat. X-3650 ..... **\$17.95**

### STIMULATING SIMULATIONS

For TRS-80 4K level I and II. 10 games on one cassette from monster chase to nautical navigation and lost treasure - it's great fun.

Cat. X-3652 ..... **\$17.95**

### ELECTRIC PAINTBRUSH

TRS-80 4K level I and II. Create dazzling real time graphics. Commands let you draw lines, turn corners, change white to black, repeat previous steps or call other programs.

Cat. X-3654 ..... **\$17.95**

### BLOCKADE

TRS-80 4K level I and II. Many variations whereby you and your opponent try and make each other collide with a wall.

Cat. X-3659 ..... **\$17.95**

### BRIDGE CHALLENGER

TRS-80 16K level II. Practice and improve your game of Bridge.

Cat. X-3656 ..... **\$17.95**

### MICRO CHES

The computer is programmed to beat you at chess and you are trying to beat it - absorbing and educational.

Cat. X-3658 ..... **\$22.50**

### SIMUTEK 1

Contains 5 games that would normally cost \$19.50 each! Great fun for all the family and friends. For TRS-80 4K level I and II.

Cat. X-3685 ..... **\$17.95**

### DOS PATCH

Extends the TRS-80 to take advantage of the 40 tracks on the Dick Smith Disc Drive for TRS-80 computers (Cat. X-3230 only \$379). Also enhances TRSDOS in other ways as well.

Cat. X-3550 ..... **\$19.50**

### "TINY" PASCAL

Cassette tape for developing and debugging or running programs on your TRS-80. Provides powerful subset of standard Pascal statements. Comes complete with comprehensive manual.

Cat. X-3670 ..... **\$49.50**

## FOR YOUR TRS-80

### C10 COMPUTER CASSETTE

Dick Smith special grade cassette tape with 5 minutes per side and 38K capacity per side.

Cat. X-3500 ..... **\$1.95**

### 'DUMB TERMINAL'

Program which enables you to use your Sorcerer as a 'dumb terminal' with another computer or another dumb terminal. Operates in full or 1/2 duplex mode, software selectable - output through the RS-232 port.

Cat. X-3637 ..... **\$9.95**

Store data the easy, convenient way. . .

## COMPUMAX ACCOUNTING DISCS

For the small business, a book and disc that will assist in the running of the accounts department. Discs suitable for use with the Micropolis Quad Density Disc Drive and the Sorcerer computer.

**MICROLEDGER** - General ledger, chart of accounts, journal, trial balance, posting, audit trail of transactions, profit and loss statement and balance sheet.

Cat. X-3700 ..... **\$169.00**

**MICROPAY** - Accounts payable, statements by vendor and by date, cash requirements, prints cheque and mailing stub, journalizes A/P transaction into MICROLEDGER.

Cat. X-3702 ..... **\$169.00**

**MICROREC** - Accounts receivable, aged trial balances, prints invoices, statements by customer and by date, cash projections, journalizes A/R transactions into MICROLEDGER.

Cat. X-3704 ..... **\$169.00**

## SYSTEMS SOFTWARE DISCS

CP/M Floppy Diskette Operating Systems from EXIDY.

CP/M PLUS MICROSOFT BASIC for Micropolis quad drives ..... Cat. X-3710 ..... **\$445.00**

CP/M PLUS MICROSOFT BASIC for Micropolis dual drives ..... Cat. X-3711 ..... **\$445.00**

CP/M for Micropolis quad drives

Cat. X-3715 ..... **\$149.00**

CP/M for Micropolis dual drives

Cat. X-3716 ..... **\$149.00**

Also available is a Word Processor Linker for Micropolis quad drives Cat. X-3720 at only **\$99.00** and also for the Micropolis dual drives Cat. X-3721 at **\$99.00**. (Both of these need CP/M as well).

### THE COMPLETE MICROCOMPUTER SYSTEMS HANDBOOK

Written by E.L. Safford Jr for the beginner through to expert. Goes from basics to advanced subjects such as magnetic bubble memories.

Cat. B-2345 ..... **\$9.95**

**AND NOW!** A program tape for the TRS-80 - 16K level II - a cassette version of the book. Why not buy the book and the cassette and have a lot of fun.

Cat. X-3665 ..... **\$19.50**

### SOME COMMON BASIC PROGRAMS

Fantastic book containing 76 programs in BASIC.

## NEW SORCERER BOOKS

A new series of books containing programmes that will make your Sorcerer even more versatile!

Small business ..... Cat. B-6110 ..... **\$49.95**

Educational & Scientific Cat. B-6112 **\$37.95**

Fun & Games No 1 Cat. B-6114 **\$17.95**

Fun & Games No 2 Cat. B-6116 **\$17.95**

Home & Economics Cat. B-6118 **\$27.95**

Fantastic value for everyone with a Sorcerer.

### Sorcerer Technical Manual

Cat. B-6100 ..... **\$14.95**

### Sorcerer Word Processing Manual

Cat. B-6105 ..... **\$17.50**

### Sorcerer Development Tour Manual

Cat. B-6106 ..... **\$17.50**

### Sorcerer Software Manual

Cat. B-6108 ..... **\$14.95**

### NEW QUAD DENSITY HARD SECTOR DISKETTE

- suitable for use with the Micropolis Cat. X-3205 and Cat. X-3208 drive systems.  
Cat. X-3514 ..... 1-9 **\$6.95 ea** ..... 10 up **\$6.50 ea**

See us at the  
**DATA 80**  
show in  
Sydney from  
the 5th to 7th  
of August 1980





## AIM, SYM, KIM OWNERS

KIM 4 Bus compatible products.  
Same shape and size as KIM, SYM.

### MEMORY PLUS \$225 A&T

8K low power RAM. All IC's socketed. 8K EPROM sockets and programmer for Intel 2716, 6522 I/O and plus 5V and plus 25V regulators.

### VIDEO PLUS \$293 A&T

Upper/lower ASCII. 80 characters by 24 lines. 128 additional user programmable characters. Keyboard and Lightpen interfaces. 2K display RAM, expansion to 4K. On-board regulators, provision for 6502. All IC's socketed.

### DRAM PLUS \$353

Complete with 16K of 4116 socketed and tested to 32K.

### PROTO PLUS \$47

Double sided, plated through holes, professional quality. Provision for 40 off 14/16 sockets, 4 off 24/40 sockets, 3 off voltage regulators.

### MOTHER PLUS \$98 A&T.

Fully buffered and decoded. Add up to 5 additional boards.

### CARD CAGE PLUS \$28

Compatible with Mother Plus.

### PROTO PLUS \$48

Transparent Refresh with 4K segment addressing. 4 sockets for 16K or 32K bit ROMs. 4K memory segment addressing. EPROM programmer to suit. 2 off I/O for 32 I/O lines and 4 off 16 bit times proto type area.

P&P \$3.50. Prices plus sales tax if applicable.



PO BOX 31, GOODNA 4300  
PHONE (07) 288-2757

Prices subject to change without notice.

SAE for  
Datasheet

## TRY THIS EXCITING HOBBY!

Build your own Organ, at  
half the cost of a  
ready-built Organ.

## WITH WERSI ORGAN KITS

Wide range of models:  
COMBO to large CHURCH ORGANS



Also

- STRING ORCHESTRA
- BASS SYNTHESIZER
- ELECTRIC PIANO
- and the famous  
WERSIVOICE  
ROTATION SOUND

All available from:

### CLEFTRONICS PTY. LTD.

9 Florence St., Burwood, Vic. 3125  
Phone: (03) 288-7899

Catalogue 104 pages in colour — \$3.00 (incl. postage).  
Klaus Wunderlich Demonstration Record, music only with  
jacket notes — \$7.00 (incl. postage).



## OHIO SCIENTIFIC COMPUTERS

1. 4K RAM Memory Expansion Chips, 2114 450nS, \$52.
2. RF Modulator, 5 to 9 volt, all channels, \$19.95.
3. Superboard 11 Cover/VDU Stand, \$18.95.
4. Superboard 11 Computer, 8K ROM, 4K RAM, \$389.
5. Challenger C1P Computer, 8K ROM, 4K RAM, \$489.
6. Challenger C4P Computer, Sound/Colour, \$946.20.

### SOFTWARE

We regret PRICE RISE due to shipping costs. All previous (54) advertised Cassette Software up \$2.00. Instructions (14 sets) are still the same price. 01 is now replaced by an updated and enlarged C1 at \$2.95.

### New Programs for Ohio Software

#### UTILITIES

U.15. Disassembler — 4K	\$10.95
U.16. Filename, for cassettes	\$8.95
U.17. Trace	\$12.95
U.18. Packer — (K saver)	\$14.95
U.19. Cursor — C2/4	\$13.95

#### INSTRUCTIONS

I.12. 32 x 64 Character Display	\$12.95
I.13. Wp 6502 Word Processor Book	\$3.95
I.14. Disassembled ROM, with Inbuilt References	\$13.95
I.15. Sound — S II/C1P	\$6.95
I.16. G.T. Conversion, X2	\$2.95
I.17. Saving Data on Tape	\$6.95
I.18. C1P Tape Control	\$6.95
I.19. C1P Beeper	\$5.95
I.20. C1P/ Base 2 Printer	\$6.95
I.21. Morse Code Converter with tape	\$16.95
I22 supplement to I12 32x64 character display.	
100 percent hardware	\$4.95

#### BUSINESS

B.4. Savings & Loan Package	\$14.95
-----------------------------	---------

#### DISPLAY

D.2. Flashboard, your advert	\$10.95
------------------------------	---------

#### GAMES

G.25. Alien Invaders (Like Space Invaders)	\$10.95
G.26. Orbital Lander	\$11.95
G.27. Escape from Mars, 2 tapes	\$18.95
G.28. Death Ship, 2 tapes	\$18.95
G.29. Startrek	\$7.95
G.30. Air — Sea Battle	\$7.95

#### BOOKS/MAGAZINES/CATALOGUE

T.1. The First Book of OSI	\$19.95
T.2. Aardvark Journal (6 issues)	\$12.95
T.3. Basic Handbook, David Lien	\$15.95
T.4. Personal Computing, Monthly	\$1.95
C.1. Catalogue describes all software and hints plus free programs	\$2.95

Postage: 1 or 2 \$1.00  
(Software) 3 — 5 \$1.50  
6 — 9 \$2.00  
10 or more \$2.50

PLUS MANY MORE NEW LINES  
OF SOFTWARE — ENQUIRE.

MAIL ORDER: Cheque or Bankcard.

Looky Video: PO Box 347, Richmond Vic.  
3121. Shop, 418 Bridge Road, Richmond.  
Ph (03) 429-5674.

All prices subject to change without notice. All  
prices INCLUDE sales tax.

## HERE'S VALUE !

## TOP PROJECTS

FROM ELECTRONICS TODAY INTERNATIONAL  
VOLUMES PRICES\$3\*

Over 20 of our top projects for the princely sum of \$3 ! A collection of some of the 'Best from ETI' projects, including: The Induction Balance Metal Detector; Accentuated Beat Metronome; Marine Gas Alarm; Shutter Speed Timer; CB Power Supply; Ultrasonic Switch; Photo Strobe; House Alarm & many more ! How do you get it ! . . . . .

Send \$3.00, plus 65 cents post and handling, for your copy to:

ETI, Subscriptions Department  
3rd Floor, 15 Boundary St,  
Rushcutters Bay NSW 2011

## ATTENTION YOUNG COMPUTER BOFFINS!



Dick Smith Electronics is planning to extend the support of its microcomputer products like the highly successful Exidy Sorcerer and System 80, by setting up a 'hot line' advisory service.

To assist with this service we are looking for a bright young computer enthusiast; someone who is around 19 or 20, but bursting with knowledge about, and enthusiasm for, personal computers.

If you think you answer this description, write to our Technical Director, Jim Rowe, at the address below, giving brief details of yourself and an idea of the salary you would expect.

**DICK SMITH ELECTRONICS**  
PO Box 321, North Ryde, NSW 2113.





## Licence fees changed

There will be a large drop in many radiocommunication licence fees as the result of changes announced in June by the Minister for Post and Telecommunications, Mr Tony Staley.

**"In many cases radio equipment is essential for safety and in the case of private, or non-commercial harbour and land mobile stations and private ship stations, the Government has agreed to cut licence fees by more than half", the Minister said.**

"Taxi owners and most small businesses which use radios will also benefit by lower licence fees."

For the first time the new scale of fees differentiates between private or non-commercial use, and non-private use. The Minister said that this corrected an anomaly in the old system where there had been no distinction between different uses. The new fees will operate from July 1 and there will be a discount of 10% where the fees are collected by clubs and submitted for renewal in a group.

"This should provide an incentive for people to work through clubs", the Minister said.

The Minister said that harbour mobile station fees would drop from \$37 a year to \$15 a year for private radios and \$37 to \$32 for non-private. Radio licence fees for ships would drop from \$50 a year to \$20 a year for the private (non-commercial) category and from \$50 a year to \$32 for the non-private category.

A new category "Marine Rescue Station" has been created at a minimal \$2 fee, for radios provided by clubs and organisations mainly for safety of life.

Fees paid by private users of the Citizens Band Radio Service will reduce to \$20, but will increase to \$40 for non-private use.

Although radios used solely for life-saving, rural fire fighting and ambulance services must be licensed, there will be no fee for these licences in future.

The Minister said that although fees for both private and business users of radio facilities had dropped in many cases some fees had risen.

Those which have risen are: Novice amateurs, up from \$6 to \$10; Limited and Full amateurs, up from \$12 to \$15 and Radio-determination stations, up from \$25 to \$60. As the Department

is likely to make stuff all out of an increase in amateur licence fees, why increase them at all? It smacks of pettifoggery pedantry (or is that pederasty?) from the beastly bureaucracy.

## CB review bait attracts many bites !

**The P & T Department's call for submissions on the CB radio service with a view to reviewing the allocations and regulations has attracted quite a response.**

Australia's two largest CB user organisations, the National Citizens Radio Association (NCRA) and the Citizens Radio Emergency Service Teams (CREST), have submitted lengthy documents along with a host of submissions from CB clubs and a number of private individuals.

A number of clubs and associations are still preparing submissions, but it seems the response shows that there's plenty of life left in the CB movements.

From what we have seen to date, most submissions argue for: retention of the 27 MHz band beyond 1982 (the originally proposed cutoff looms up in

June, 1982), more channels on both HF and UHF, provision for phone patching, the permission to work both local and overseas DX (with other countries having similar CB regulations on 27 MHz), permission to use beam antennas, point-of-sale licensing, continued licensing for older 23 channel equipment and the removal of business activities from the CB bands.

There is strong support for the retention of a dual (HF and UHF) CB service for Australia, citing the usefulness of HF for country and remote areas and the convenience of UHF for local and urban working.

More details when the fight gets hot !

## Common channel VHF repeater

**Plessey has designed a portable automatic VHF repeater which can receive and transmit simultaneously on the same frequency.**

This was hitherto been considered impossible because of interference between transmitter and receiver.

The Groundsat PTR 3411 has already won a British Design Council award and the 1980 Duke of Edinburgh's Designer's prize for its unique design.

Designed primarily for military applications, it can be carried easily, concealed and left unattended, remaining on

standby until required. By contrast, two-frequency repeaters are bulky and need to be continuously manned, which makes them prime targets in battle.



As well as its military uses, a common channel repeater clearly has great potential for civil applications, where the available frequency bands are already overcrowded.






**This Service Monitor sets the standards for what a Communications Test Set Needs to be!**


# FM/AM-1000S

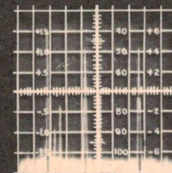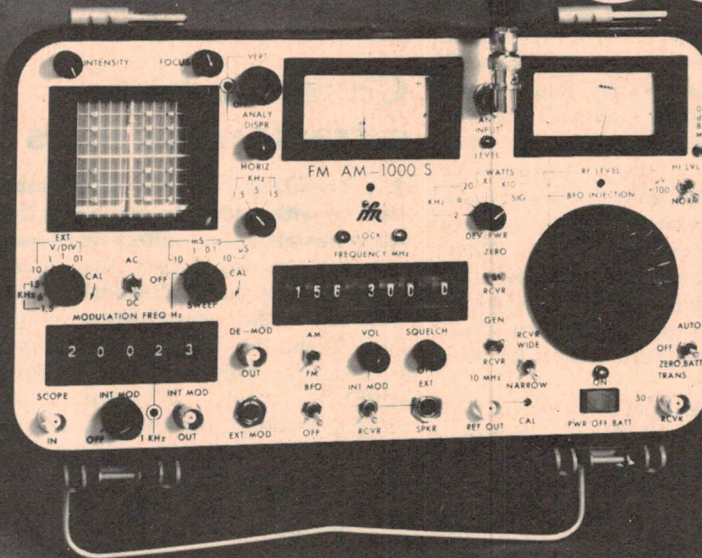

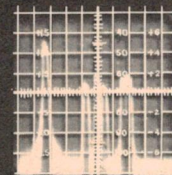**WIDE DISPERSION:**  
Analyzer sweeps  $\pm 5$  MHz from selected frequency (10 MHz span)



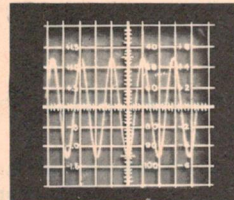**NARROW DISPERSION:**  
Analyzer sweeps  $\pm 0.5$  MHz from selected frequency (1 MHz span)



**OSCILLOSCOPE:**  
Oscilloscope features DC to 1 MHz frequency response

**We gave you the features you needed and the performance you expected to get the job done... on the bench and on the go!**

The FM/AM-1000S is a compact, light weight, completely portable test set which is easily and efficiently used with no sacrifice in versatility. Its ruggedly constructed circuits are housed in a deep-drawn, heavy gauge metal case, allowing it to withstand the rigors of portable operation as well as being a highly functional bench instrument.

As a generator, the FM/AM-1000S features continuous frequency coverage from 100 Hz to 1 GHz, AM or FM modulation, internal variable audio tone generator, 1000 Hz fixed tone generator, and 0 dBm RF output level into 50 ohms.

Automatic switching to monitor mode occurs at 100 MW, allowing measurement of transmitter frequency, FM deviation or % AM modulation, and RF power throughout the operating range of the test set.

A sensitive receiver allows measuring the characteristics of radiated signals, including SSB and DSB. The Beat Frequency Oscillator features variable injection level and is phase-locked to the master oscillator for precise suppressed carrier frequency measurement. The 15 kHz Narrow IF selectivity allows monitoring a desired signal within 25 kHz of adjacent channel interference without difficulty.

The Oscilloscope/Spectrum Analyzer operates simultaneously with all other indicators to provide detailed analysis of monitored signals. The 70 dB dynamic range of the analyzer is equal to that of many individual analyzers.

**Features...Performance...Portability.** The FM/AM-1000S Communications Service Monitor has them all — plus it's priced below comparable, competitive test equipment.



SYDNEY: 339 PACIFIC HWY, CROWS NEST  
PH 436 2766

MELBOURNE: 68 EASTERN RD, STH MELBOURNE.  
PH 699 6700



## New transmitter for Nigeria

Test transmissions have been noted in Melbourne from a powerful new shortwave transmitter located at Kaduna in northern Nigeria.

**The broadcasts are in English and a local language, presumably Hausa, and are currently heard in our early mornings up to sign-off at 2315.**

The frequency being used is 4770, in the 60 metre tropical band. These broadcasts identify as being from the Federal Radio Corporation of Nigeria, Kaduna.

Kaduna is the capital city of Kaduna State, and the Federal Radio Corporation has for some years operated a powerful shortwave transmitter from that city on the 49 metre outlet of 6090.

Unfortunately for Australian listeners, 6090 is also used by the ABC shortwave domestic service from Sydney. During our winter months, the best we can hope for is to hear a weak signal from Kaduna underneath our strong ABC station.

With the current broadcasts on 4770, this has changed dra-

matically, and good reception is noted up to 2315 of the Kaduna station. A relay of the English news from Lagos, Nigeria's federal capital, is taken at 2300, when 4770 may be heard in parallel with Lagos station on 4990.

The Kaduna 4770 transmitter gives much stronger signals than Lagos on 4990, and as the Lagos transmitter is rated at 50 kilowatts, it is thought that the new Kaduna outlet may be using a transmitter of at least 100 kilowatts, if not 250 kilowatts. Kaduna's transmitter on 6090 is rated at 250 kilowatts.

Current test broadcasts on 4770 are part of Nigeria's extensive plans to upgrade the country's communications network, using funds available thanks to major oil finds along the Nigerian coast in recent years.

DXers will recall the test



VOICE  
of  
NIGERIA

transmissions on 4755 by the Federal Radio Corporation during 1979, made on behalf of the Imo State Broadcasting Service in Owerri, which were well heard throughout Australia in the 2100 to 2305 time period.

Each Nigerian state (there are 19 states) is now responsible for broadcasting and communications within their boundaries. The Federal authorities, following test transmissions, have

handed over the 4755 transmitter to the Imo State radio, and no doubt the transmitter on 4770 will also eventually be handed over to the Kaduna state broadcasting authorities following the current test transmissions.

Reception reports of the current test broadcasts could be sent to the Federal Radio Corporation of Nigeria, Kaduna, Kaduna State, Nigeria.

## Guatemala all night

**La Voz de Guatemala at Guatemala City has recently been broadcasting 24 hours on 6180 in the 49 metre band.**

For many years, La Voz de Guatemala broadcast from their morning sign on at 1100 through until sign-off at 0500.

Australian DXers, especially on the east coast, had the best opportunity to hear Guatemala at their sign on at 1100, which is during our evening, when a darkness path meant signals reached us across the Pacific Ocean.

In recent weeks however, La Voz de Guatemala has been

broadcasting on 6180 right throughout their former 0500-1100 silent period.

Signals have been strong on 6180, with Spanish announcements and distinctive marimba music of Guatemala.

Station identification is often given, sometimes for La Voz de Guatemala, and sometimes as Radio Nacional de Guatemala. Reception is best between about 0800 and 1200, as noted from Melbourne.

## Portugal move

**Radio Portugal in Lisbon is currently well heard in east Australia using the North American service between 0500 and 0530 daily, on both 9575 and on 11 925.**

Another Radio Portugal English service well heard here, although not directed to Australia, is that beamed to Europe daily from 2030 to 2100 on both 6025 and 9740.

Meanwhile, Portugal's broadcast in Portuguese, directed to Macau and Australia, is heard daily on 21 735 plus the new outlet of 21 645 (replacing 21 700) between 0925 and 1055.

## Last chance for 90 metre Latins!

**August should prove the last chance for east coast DXers to log Latin American signals on the 90 metre band.**

These signals are an exciting feature of mid-winter DXing along the east coast.

All stations on the 90 metre band in Latin America are fairly low powered Home Service and commercial stations, usually broadcasting to their small local region or even their local town.

Here is a list of some of the stronger Latins on 90 metres you might hear, but make sure you get the household to turn off that colour TV before you tune down to 90 metres as this sort of low frequency DXing and colour TV interference just don't mix!

**ECUADOR:** Strongest of the 1980 crop of Latins on 90 metres is Radio Iris at Esmeraldas on 3380. Reception is sometimes very strong between 1100 and 1140, with popular Ecuadorean music and Spanish announcements. The station identification is usually given as "Esta es Radio Iris" (This is Radio Iris).

HCJB the Voice of the Andes in

Quito, transmits their Home Service programmes in Quechua (the language descended from the Incas) on 3220, and is audible from 0930 to about 1130. There is interference from Radio Morobe in Papua New Guinea, which also uses 3220, but HCJB's signal often dominates on the channel.

**GUATEMALA:** The religious broadcaster TGNA Radio Cultural, is often heard with strong signals on 3300, from 1100 to past 1130, with Spanish religious talks and prayers. Interference from a utility station is sometimes present.

**NOTE!** All times are given in Greenwich Mean Time (GMT). To convert to Australian Eastern Standard Time, add 10 hours (11 hours for Daylight Saving Time). To convert to Central Time, add 9.5 hours and for Western Time add 8 hours. All frequencies are in kHz.

Shortwave Loggings is compiled by Peter Bunn on behalf of the Australian Radio DX Club (ARDXC). Further information on DXing or the activities of ARDXC may be obtained from PO Box 79, Narrabeen NSW 2101, for a 30c stamp.





# ANNOUNCING A GREAT NEW CONTEST



## WIN A TRIP TO HONG KONG!

Yes! A trip to magnificent Hong Kong, with your flight and accommodation paid for!!! That's the prize in our exciting new Yaesu/Dick Smith Competition: and you could be the winner!

## OPEN TO ALL PURCHASERS OF YAESU AMATEUR GEAR FROM DICK SMITH

### Here's how it works:

We at Dick Smith Electronics want to know what you, the amateurs of Australia want from your hobby: the amateur radio service. And we want to know how we, as a company, can serve you and Australia best for the benefit of Australia. So we're asking you to tell us, in fifty words or less, 'The best way that Dick Smith Electronics can promote the fantastic hobby of Amateur Radio to the benefit of Australia'

Entry to this competition is only open to purchasers of any Yaesu equipment from Dick Smith stores or authorised Dick Smith Yaesu re-sellers, between August 1, 1980, and November 1, 1980.

If you think about it, your chances of winning this trip are very, very good: the number of entries cannot be all that high — all it takes is a little originality and constructiveness of comment from you, and you could be going to Hong Kong: free!

Entries will be judged initially by a panel from Dick Smith Electronics to produce five finalists: these will be judged by Neville Williams, MIREE, Editor-in-chief of Electronics Australia magazine.

The winner will be notified by Dick Smith, and will be announced in Electronics Australia and Electronics Today International.

So if you're thinking about buying Yaesu, why not buy it in the next three months: of course, only from Dick Smith Electronics or authorised Dick Smith Yaesu re-seller!

**Remember: we're the number one supplier of Yaesu amateur gear in the Southern Hemisphere!**

### HERE'S HOW TO ENTER: RULES AND CONDITIONS

Entries will only be accepted on the official entry form, which is available only with the purchase of any item from the Yaesu range from a Dick Smith store or a Dick Smith authorised re-seller.

All entries must show the model number and serial number of the item purchased, (if applicable), and be signed by the store manager or authorised person.

In the space provided on the entry form, write in one paragraph of not more than 50 words.

**'The best way that Dick Smith Electronics can promote the fantastic hobby of Amateur Radio to the benefit of Australia'**

Post your entry to:

Amateur Radio Contest,  
Dick Smith Electronics  
PO Box 321,  
North Ryde, NSW, 2113.

Entries close at 5PM on Monday, 3rd November, 1980.  
Entries received after this date will not be considered.

Final judging will take place on 10th November, 1980.  
The judge's decision will be final and no correspondence will be entered into.

As this flight departs from, and returns to Sydney, the winner must travel to Sydney at his/her own expense.

All entries become the absolute property of Dick Smith Electronics Pty Ltd, who may use such entries as they see fit.

# NOW, MORE THAN EVER, IT PAYS TO BUY YAESU FROM DICK SMITH!




# Micro Computers From INDUSTRIAL MICRO SYSTEMS DON'T LET ITS SMALL PRICE AND SIZE FOOL YOU
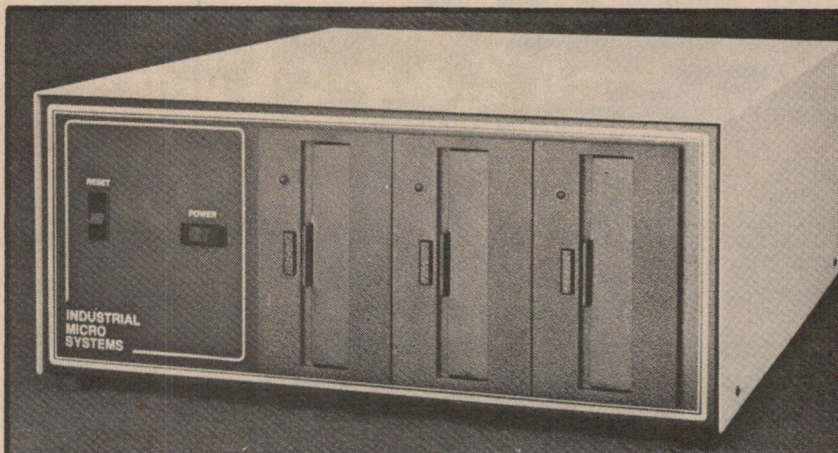
## SERIES 5000

The Series 5000 System requires very little money or space. But there's nothing small about the way it performs. Regardless of the size of machine you choose, there's room inside for up to 256k of IMS RAM with memory management. And the integrated floppy disk capacity is pretty impressive too — more than a million bytes! You can start with a single 5.25" drive, then install one or two more when you need them — all in the same cabinet. The Series 5000 System's power supply and disk controller are made with this kind of expansion in mind so growing is simple. And our Z-80 computers have features like serial and parallel I/O's, clocks, PROMs on board so that less slots are used on the S-100 12 slot motherboard, giving more space for extra RAM or special purpose boards.

Because the system is S-100 and CP/M based you can run all of the programs written for use with CP/M systems. (Like CBASIC, FORTRAN, COBOL, PASCAL, C, ALGOL, WORDSTAR etc.) And you can go multi-user as well!  
CALL US FOR MORE INFORMATION ABOUT THIS SYSTEM OR ITS BIG BROTHER WITH THE 8" DISKS — THE SERIES 8000.



# SIGMA INTERNATIONAL PTY LTD

GPO BOX 72 SYDNEY 2001

92 PITT ST SYDNEY

(02) 231 4091

232 6804

XEROX DIABLO 3200



## APPLICATION SOFTWARE (CUSTOMISED, INSTALLED AND FULLY SUPPORTED)

### ACCOUNTS PAYABLE AND GENERAL LEDGER SYSTEM

Purchase journal, cheque writing, accounts payable ageing and cash forecast. General ledger reports including: G/L budget trial balance, working trial balance, chart of accounts. Financial reports including: balance sheet, income statements, budget reports, and budget schedules.

### PAYROLL SYSTEM

Automatic pay processing, instant employee information, full tax calculation, full deduction reporting, optional cheque production, labour distribution reports and group certificates.

### SALES AND INVENTORY ACCOUNTING SYSTEM

Order entry and invoicing, stock control, back ordering, sales analysis, cash receipts, age trial balance, debtors ledger and statements.

### WORD PROCESSING

Screen based system, document oriented word processor, full access to data processing files, powerful merge and print queuing facilities which operate in "background mode", leaving the operator free for editing and revision. Printer options to handle plastic or metal daisy wheel, letterheads, continuous stationery, automatic sheet feeding and custom stationery.

## WE ALSO DISTRIBUTE:

- **INTERTEC COMPUTERS** — twin Z80's using full business software plus language options of Basic, Fortran, Cobol, APL, PASCAL, etc. Hardware fully expandable.
- **C.B.M. SYSTEMS** — with standard software.
- **APF HOME COMPUTERS.**
- **COMMODORE PET.**

For calculator prices see July ETI.

## SPECIALISED APPLICATIONS INCLUDE:

Insurance brokers system, law firm accounting/word processing, accountant's client accounting, medical group accounting, real estate/property management, motor dealers system — including finance and insurance applications, contractors/builders job costing, manufacturer's bill of material and requirements planning, pharmaceutical system, production planning/manufacturing job costing, textile/clothing industry system, newspaper management and transport management system.

XEROX  
DIABLO 3000



## CALCULATOR AND COMPUTER DISTRIBUTORS

INCORPORATING EXCLUSIVE CALCULATORS & COMPUTERS  
and ELECTRONIC CALCULATOR DISCOUNTS

PHONE (02) 624-8849

MAIL ENQUIRIES  
PO BOX 106, BAULKHAM HILLS  
2153




# PREDICTIONS SEPTEMBER 1980

Covering 3 to 40 MHz, these predictions show the times radio contact is possible between the areas designated beneath each graph, as well as the possible 'mode' and reliability. Vertical columns indicate time — commencing at 0000 UT on the left, to 2300 UT at right. For reliable predictions follow the times and frequencies indicated by the F character.

Complete information on using these predictions can be obtained by sending a stamped, self-addressed envelope to:-

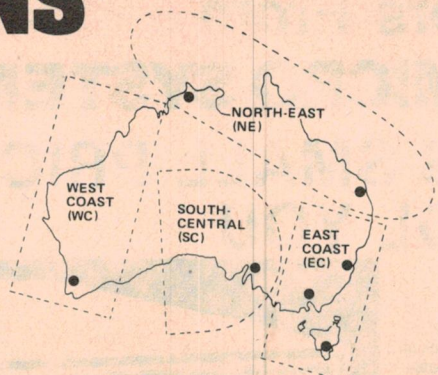ETI — Predictions  
3rd floor 15 Boundary St  
RUSHCUTTERS BAY NSW 2011.



These GRAFEX style computer generated predictions are provided courtesy of the Australian Ionospheric Prediction Service.

## KEY TO SYMBOLS

A blank area means no normal propagation is possible.

%..... path open 50 - 90% of days in month.

F..... path open at least 90% of days in month.

B..... propagation possible via E and F layers over 90% of days. Overrides 'F'.

M..... propagation possible by both 1st and 2nd F-layer modes. Expect strong fading.

S..... propagation possible by 2nd mode (also 3rd and mixed E and F modes). Expect strong fading, weak signals.

A..... High absorption indicated. Expect weak signals.

40	..XZXX..	..XZXX..	40	..XZXX..	..XZXX..	40	..XZXX..	..XZXX..	40	..XZXX..	..XZXX..
39	..XZXX..	..XZXX..	39	..XZXX..	..XZXX..	39	..XZXX..	..XZXX..	39	..XZXX..	..XZXX..
38	..XZXX..	..XZXX..	38	..XZXX..	..XZXX..	38	..XZXX..	..XZXX..	38	..XZXX..	..XZXX..
37	..XZXX..	..XZXX..	37	..XZXX..	..XZXX..	37	..XZXX..	..XZXX..	37	..XZXX..	..XZXX..
36	..XZXX..	..XZXX..	36	..XZXX..	..XZXX..	36	..XZXX..	..XZXX..	36	..XZXX..	..XZXX..
35	..XZXX..	..XZXX..	35	..XZXX..	..XZXX..	35	..XZXX..	..XZXX..	35	..XZXX..	..XZXX..
34	..XZXX..	..XZXX..	34	..XZXX..	..XZXX..	34	..XZXX..	..XZXX..	34	..XZXX..	..XZXX..
33	..XZXX..	..XZXX..	33	..XZXX..	..XZXX..	33	..XZXX..	..XZXX..	33	..XZXX..	..XZXX..
32	..XZXX..	..XZXX..	32	..XZXX..	..XZXX..	32	..XZXX..	..XZXX..	32	..XZXX..	..XZXX..
31	..XZXX..	..XZXX..	31	..XZXX..	..XZXX..	31	..XZXX..	..XZXX..	31	..XZXX..	..XZXX..
30	..XZXX..	..XZXX..	30	..XZXX..	..XZXX..	30	..XZXX..	..XZXX..	30	..XZXX..	..XZXX..
29	..XZXX..	..XZXX..	29	..XZXX..	..XZXX..	29	..XZXX..	..XZXX..	29	..XZXX..	..XZXX..
28	..XZXX..	..XZXX..	28	..XZXX..	..XZXX..	28	..XZXX..	..XZXX..	28	..XZXX..	..XZXX..
27	..XZXX..	..XZXX..	27	..XZXX..	..XZXX..	27	..XZXX..	..XZXX..	27	..XZXX..	..XZXX..
26	..XZXX..	..XZXX..	26	..XZXX..	..XZXX..	26	..XZXX..	..XZXX..	26	..XZXX..	..XZXX..
25	..XZXX..	..XZXX..	25	..XZXX..	..XZXX..	25	..XZXX..	..XZXX..	25	..XZXX..	..XZXX..
24	..XZXX..	..XZXX..	24	..XZXX..	..XZXX..	24	..XZXX..	..XZXX..	24	..XZXX..	..XZXX..
23	..XZXX..	..XZXX..	23	..XZXX..	..XZXX..	23	..XZXX..	..XZXX..	23	..XZXX..	..XZXX..
22	..XZXX..	..XZXX..	22	..XZXX..	..XZXX..	22	..XZXX..	..XZXX..	22	..XZXX..	..XZXX..
21	..XZXX..	..XZXX..	21	..XZXX..	..XZXX..	21	..XZXX..	..XZXX..	21	..XZXX..	..XZXX..
20	..XZXX..	..XZXX..	20	..XZXX..	..XZXX..	20	..XZXX..	..XZXX..	20	..XZXX..	..XZXX..
19	..XZXX..	..XZXX..	19	..XZXX..	..XZXX..	19	..XZXX..	..XZXX..	19	..XZXX..	..XZXX..
18	..XZXX..	..XZXX..	18	..XZXX..	..XZXX..	18	..XZXX..	..XZXX..	18	..XZXX..	..XZXX..
17	..XZXX..	..XZXX..	17	..XZXX..	..XZXX..	17	..XZXX..	..XZXX..	17	..XZXX..	..XZXX..
16	..XZXX..	..XZXX..	16	..XZXX..	..XZXX..	16	..XZXX..	..XZXX..	16	..XZXX..	..XZXX..
15	..XZXX..	..XZXX..	15	..XZXX..	..XZXX..	15	..XZXX..	..XZXX..	15	..XZXX..	..XZXX..
14	..XZXX..	..XZXX..	14	..XZXX..	..XZXX..	14	..XZXX..	..XZXX..	14	..XZXX..	..XZXX..
13	..XZXX..	..XZXX..	13	..XZXX..	..XZXX..	13	..XZXX..	..XZXX..	13	..XZXX..	..XZXX..
12	..XZXX..	..XZXX..	12	..XZXX..	..XZXX..	12	..XZXX..	..XZXX..	12	..XZXX..	..XZXX..
11	..XZXX..	..XZXX..	11	..XZXX..	..XZXX..	11	..XZXX..	..XZXX..	11	..XZXX..	..XZXX..
10	..XZXX..	..XZXX..	10	..XZXX..	..XZXX..	10	..XZXX..	..XZXX..	10	..XZXX..	..XZXX..
9	..XZXX..	..XZXX..	9	..XZXX..	..XZXX..	9	..XZXX..	..XZXX..	9	..XZXX..	..XZXX..
8	..XZXX..	..XZXX..	8	..XZXX..	..XZXX..	8	..XZXX..	..XZXX..	8	..XZXX..	..XZXX..
7	..XZXX..	..XZXX..	7	..XZXX..	..XZXX..	7	..XZXX..	..XZXX..	7	..XZXX..	..XZXX..
6	..XZXX..	..XZXX..	6	..XZXX..	..XZXX..	6	..XZXX..	..XZXX..	6	..XZXX..	..XZXX..
5	..XZXX..	..XZXX..	5	..XZXX..	..XZXX..	5	..XZXX..	..XZXX..	5	..XZXX..	..XZXX..
4	..XZXX..	..XZXX..	4	..XZXX..	..XZXX..	4	..XZXX..	..XZXX..	4	..XZXX..	..XZXX..
3	..XZXX..	..XZXX..	3	..XZXX..	..XZXX..	3	..XZXX..	..XZXX..	3	..XZXX..	..XZXX..

East Coast to Japan  
(Also serves N.E. and S.C.)

East Coast to South Pacific

East Coast to North America  
(Also serves N.E. and S.C.)

East Coast to South America  
(Also serves S.C.)

East Coast to North Africa  
(Also serves S.C.)

East Coast to South Africa  
(Also serves S.C.)

East Coast to Europe  
(Short Path)

E.C. and S.C. to Europe  
(Long Path)

East Coast and S.C. to Persia

North East to South Pacific  
(Also serves S.E.)

North East to North Africa

North East to South Africa

North East to Europe  
(Short Path)

S. Central & W.C. to Europe  
(Short Path)

West Coast to North America

West Coast to Japan

West Coast to North Africa

West Coast to South Africa



# BAD T.V. RECEPTION

IMPROVE YOUR PICTURES BY FITTING A MAST-HEAD AMPLIFIER, PLUS A GOOD QUALITY CABLE. SUCH AS:—

Coaxial or open-wire feeder cable. Your present signal can be increased by a minimum of 3 times if you use one of the following amplifiers.

HILLS	Input	Output	Gain	Ratio	Cost
MH.1	300	300	10dB	3.1	\$46.66
MH.2	300/75	75	20dB	10.1	\$66.68
MH.4	300/75	300/75	25dB	17.1	\$75.78
MH.4 / 10 or 20dB down on Ch's 3-4-5A					\$81.95

LABGEAR	Input	Output	Gain	Ratio	Cost
6060	75	75	28dB	25.1	\$59.98
6059	75	75			\$57.30
approx 15dB down on ch's 0-6					

Ecraft. Line Amplifiers VHF-UHF	Input	Output	Gain	Ratio	Cost
175D16	75	75	16dB	6.1	\$45.00
275D12	75	75	12dB	4.1	\$52.79
375D10	75	75	10dB	3.1	\$53.70
475D10	75	75	10dB	3.1	\$54.29
175D25	75	75	25dB	18.1	\$53.65
275D21	75	75	21dB	11.1	\$60.45
375D19	75	75	19dB	9.1	\$61.45
475D19	75	75	19dB	9.1	\$61.95

KINGRAY					
D15/600	75	75	15dB	6.1	\$53.55
D30/600	300	75	25dB	18.1	\$61.20
WN30/600300		75	38dB	25.1	\$68.63
D42/600	75	75	42dB	126.1	\$94.86
D12/1500	75	75	15dB	6.1	\$94.86
MH20	300	75	20dB	10.1	\$74.97
MH20WN	300	75	20dB	10.1	\$81.08
CROWN Remote control Antenna Rotator					\$99.00

Ecraft Double Screened Coaxial cable  
2045 3.5dB loss at 216Mhz per: 30M .47c per metre  
2063 2.05 loss at 216Mhz per: 30M 1.08 per metre  
Open-wire feeder 1.5dB loss at 200Mhz per 30M .70c per metre  
Masting. Telo-masts. Guy fittings. Outlet plates.  
Splitters. Balun fly leads etc: Belling-lee type plugs lots of 10 -.51c each.  
Gold Detectors Bounty Hunter range.  
840 VLF/TR Discriminator \$337.00 2 only TR1000D VLF/TR  
were \$445 now only \$339.00. Red baron RB7 VLF/TR/SPD  
Ground reject discriminator \$595.00. ETI Kits May 77  
Build your own detectors to clear \$49.00  
PL259 50 Ohm plug .60c. Jumper lead 125mm  
2-PL259 fitted \$2.00



## ELECTRORAFT PTY LTD

68 Whiting Street, Artarmon NSW  
Telephone 438-4308 ext. 6  
or 438-3266 ext. 6

WE ARE SPECIALISTS  
30 years in the antenna business.  
Hours: 8am to 5pm.

Prices subject to alteration without notice.



## PLESSEY COMPONENTS

PO Box 2, Villawood, NSW 2163  
Telephone 72-0133

## NI-CAD PACKS

Plessey SAFT present high-reliability Ni-Cad Battery Packs.

- 1.2V to 24V (1.2V steps)
- 100 mA to 10 AH
- Long life of over 2,000 charge/discharge cycles.
- Rapid recharge capability fully recharge — 3.5 hours

Available ex stock:

- 5V 500 mA Standard package  
5/500 28 mm x 28 mm x 50 mm
- 6V 500 mA Standard package  
6/500 42 mm x 28 mm x 50 mm
- 9V 500 mA Standard package  
9/500 55 mm x 28 mm x 50 mm
- 12V 500 mA Standard package  
12/500 85 mm x 28 mm x 50 mm

These standard packages are supplied in insulated packages with fly leads 0.3 metre long. Other package configurations available.



NON  
VOLATILE  
LOGIC

### Features

- Data retention for one year in the absence of applied power
- Simple to use
- Standard power supplies only (plus 5V, minus 12V)
- CMOS/TTL compatible
- 14-lead DIL package
- Typically ten million SAVE operations

## DEVICES AVAILABLE

### MN9102

The MN9102 is a non-volatile 4-bit data latch which uses MNOS\* transistors as memory.

### MN9105

The MN9105 is a 4-decade BCD counter which counts up or down on negative transitions of the Clock input. In parallel with the counter is a 16-bit non-volatile MNOS memory into which the contents of the counter can be written. When data has been written into the memory it can be retained in the absence of applied power, and subsequently be recalled from the memory to preset the counter.

### MN9106

The MN9106 is a six-decade up counter in parallel with a twenty-four-bit MNOS memory which can provide non-volatile data storage of the current count position.

### MN9107, MN9108

The MN9107 will count up to 99 hours, 59 minutes, 59 seconds, while the MN9108 counts up to 9999 hours, 59 minutes or 9999 minutes, 59 seconds.

### APPLICATIONS

Applications for NOVOL are found in all forms of metering, security code storage, back-up storage for microprocessor-based systems, elapsed time indicators, electronic counters, latching relays and many other general industrial areas.

### Plessey Agents and Distributors:

<b>SYDNEY</b>	
Martin De Launay	29-1066
<b>MELBOURNE</b>	
Zephyr Products	568-2922
<b>BRISBANE</b>	
L.E. Bougmen	36-1277
<b>ADELAIDE</b>	
K.D. Fisher & Co.	269-2544
<b>TOWNSVILLE</b>	
Electronic Communications	72-3450
<b>PERTH</b>	
H.J. McQuillan Pty. Ltd.	458-7111

# RADIO DESPATCH SERVICE

869 George Street,  
Sydney, NSW. 2000.  
(Near Harris Street)  
Phone 211-0816, 211-0191.

## OSCILLOSCOPES

Models available

## HITACHI

Includes Sales Tax

X125 15MHz Dual Trace .....	\$644.00
X302 30MHz Dual Trace .....	\$1021.20
V550 50MHz Dual Trace .....	\$1920.50
Large 6" screen (Probes extra)	

## LEADER

LBO — 512A DC or 2Hz to 10MHz .....	\$459.00
Single Trace 5" .....	
LBO — 508A DC or 2Hz to 20MHz .....	\$809.00
Dual Trace 5" .....	
LBO — 520 DC or 2Hz to 30MHz .....	\$1245.00
Dual Trace 5" .....	

	Excluding sales tax	Including sales tax
Little Professor		
(Electronic Learning Aid) .....	\$17.40	\$19.00
Dataman		
(Math Learning Aid) .....	\$23.63	\$26.15
Spelling B		
(Electronic spelling aid) .....	\$46.20	\$51.15
Speak and Spell		
(Talking learning aid) .....	\$68.60	\$75.95
Speak and Spell word modules	\$20.00	\$21.95
Mr. Challenger .....	\$43.40	\$48.05
Language Translator .....	\$245.73	\$272.05
(Shows and tells how to pronounce foreign words etc.)		
Language Translator modules	\$45.56	\$50.00
Spanish French English		
TI.30 S.P. ....	\$20.00	\$22.10
TI.1750 .....	\$16.40	\$18.15
TI.B.A. II .....	\$40.97	\$45.35
TI.50 .....	\$36.40	\$40.30
TI.55 .....	\$53.35	\$59.00
TI. Programmable 58C .....	\$132.00	\$149.00
TI Programmable 59 .....	\$265.00	\$299.90
PC100 C Printer .....	\$210.00	\$237.00
Specialty Pakettes .....	\$8.30	\$9.10
Library modules .....	\$33.32	\$36.90

We specialize in P.C. Boards for ETI and E.A. projects. Scotchcal front panels for recent ETI and E.A. projects.

WRITE TO US FOR SPECIAL PRICES

### MAIL ORDER CUSTOMERS

\$1.00 packing plus 5 percent of order value up to \$80.00, thence a flat \$4.00 for postal items. Carrier — freight on.

OPEN: Mon-Fri 8 am to 5.30 pm.  
Thursday night late shopping till 8.30 pm. Saturday 8 am to 11.45 am.



# "I have always wanted a really good loudspeaker system."



Today the cost of excellent turntables, cartridges, tape decks and amplifiers has fallen to the point where the average family man can afford equipment of a quality and performance-level that was impossible ten years ago.

But good loudspeakers have remained extremely expensive and, in most domestic hi-fi systems, the rest of the equipment can dramatically outperform the speaker.

Philips have set out to correct this imbalance.

In co-operation with Philips Elcoma Division, a leading Electronics magazine has developed the ETI 4000/1 speaker system.

The ETI 4000/1 is available in kit form which means you save money by assembling it yourself.

A total kit, including:

- 8 loudspeaker drivers (4 per box)
  - 22 element crossover networks
  - pre-assembled boxes.
- For around \$798.00 per pair. (\$300.00 less, if you build your own boxes)!

The ETI 4000/1 is comparable to systems selling for twice the price.

See your Philips dealer today or send for complete details including a free reprint of the original construction article. Further information on Philips loudspeakers; a list of Philips dealers and a free 4-speed stroboscope card for checking the speed accuracy of your turntable.

**Philips Electronic Components and Materials**

P.O. Box 50  
LANE COVE, N.S.W. 2066

Please send me complete information on the ETI 4000/1 loudspeaker system plus my free 4-speed stroboscope card and further information on loudspeakers.

NAME \_\_\_\_\_  
Please Print

ADDRESS \_\_\_\_\_

STATE \_\_\_\_\_ P'CODE \_\_\_\_\_

ETI




**Electronic  
Components  
and Materials**

# PHILIPS

AHEARN EL 30





# esound

<b>FEATURE:</b>	● MODERN TURNTABLE TECHNOLOGY	119
<b>REVIEWS:</b>	● ROTEL RX1000 FM/AM RECEIVER	144
	● DICK SMITH MINI SPEAKERS	156





A dream come true  
demands music  
as true as the dream  
- Nakamichi





For further information contact Convoy International Pty Ltd 4 Dowling Street Woolloomooloo NSW 2011  
Telephone (02) 358 2088



# The dawn of a new recording era

## Auto Azimuth Alignment

Undoubtedly the most advanced and sophisticated cassette recorders in the world today, the ZX Series launches a new era in high-fidelity cassette recording. These revolutionary transports feature exclusive Nakamichi Discrete-Head technology, 4-Motor, Dual-Capstan, Asymmetrical, Diffused-Resonance Transport, Random Access Music Memory, and Auto Azimuth Alignment. For the first time, you can be assured of perfect azimuth alignment – on any cassette – at the touch of a button. Unprecedented frequency response – to 22kHz at standard speed, to 15kHz at half speed! The culmination of Nakamichi's commitment to excellence in the fine art of recorded sound.



### 680ZX

The premier Model 680ZX – half-speed response that rivals that of other decks at full speed! And, at standard speed, a full 22kHz! High-resolution wide-range FL level indicators and 18 program RAMM. Choose your speed, choose your program. The 680ZX does it all!

### 670ZX

Full off-tape monitoring facilities with Double Dolby and two complete sets of electronics. Single-speed operation to an astounding 22kHz! Nine program RAMM and wide-range peak-responding meters. Outstanding performance.



For further information contact Convoy International Pty Ltd 4 Dowling Street Woolloomooloo NSW 2011 Telephone (02) 3582088



## What is hi-fi ?

The Australian Hi-Fi Industries Association is on the point of completing a \$20 000 research programme to define hi-fi, according to the chairman of the Association, Mr Les Black.

**Addressing a meeting of Pioneer dealers in Perth recently (he is also managing director of Pioneer Electronics), Mr Black said the words "high fidelity" were "meaningless".**

He says there are still a good many electronic systems, and trillions of three-in-ones, that do not meet what is generally accepted as hi-fi standards.

But as there is no definition of hi-fi, these items can be advertised as hi-fi without any recriminations.

A definition of hi-fi is long overdue and many industry people wanted the matter looked into several years ago when England and America set down a legal definition.

But, although our Australian standards are late in being drawn up, Mr Black says that they are far more comprehensive than overseas efforts to define hi-fi.

He says that in America, the hi-fi definitions were limited to specifications relating only to amplifiers and receivers.

The Australian standards will cover all components sold and related to hi-fi equipment, including cassette decks and turntables.

The research programme, to cost \$20 000, started 18 months ago and is within three months of being completed. A rough draft is already finished and it is now only a matter of formalising the definitions.

**What will the definitions mean to the public, and how will they be used?**

A special sub-committee headed by Philips executive

Arno Rieuwers is looking at ways to use the \$20 000 standards.

One obvious way to give the standards some real meaning is to get the Federal Government to accept them as a standard and pass legislation accordingly.

Then anyone advertising sound equipment that doesn't meet the specifications as hi-fi could be prosecuted under the Trade Descriptions Act.

This would make life much easier for the consumer.

However, the Federal Government may be reluctant to accept the fact that there are two standards of sound equipment. If they do then the industry would be able to push for abolition of tariffs on a wide range of products.

The government currently doesn't differentiate between public address quality sound equipment and hi-fi quality sound equipment. So while there are companies in Australia making P.A. equipment we have to pay heavy protective tariffs on hi-fi equipment.

It's going to be a hot potato and will keep Arno Rieuwers quiet for a while because if the industry association pulls it off it will mean the loss of millions of dollars to the Federal Government funds.

Tariffs currently stand at around 37% and the hi-fi industry is worth around \$100 million a year. The only exception to the tariff protection system is the cassette deck. This was cleared on its by-law 18 months ago and prices fell dramatically overnight. Because of it, sales have boomed since.



## Audax Kit 51 speaker prices

**Our review of these speakers in the July issue missed out on a price breakdown and we feel readers may be interested to know the details.**

The recommended retail price of the completely assembled speakers is now slightly lower than quoted in the review and is now \$719.

As a kit, complete with all components, cabinets and drivers, the price is \$459. The cabinet kit alone costs only \$169. Enquiries to Audax Loudspeakers, 32 Wilson St, Oakleigh Vic 3166. (03) 579-5196.

## Pointing in the right direction

**A new design of rear shelf speaker from Pioneer cuts down the high frequency losses which are common in car interiors.**

The trouble with normal car speaker designs is that high frequency sound is very directional. For the driver of a car to hear good treble the axis of the speaker should be pointing more or less towards him.

Ideally this means mounting the speakers on the windows or the roof, both of which are ruled out by considerations of visibility and headroom. So car speakers are usually fitted in the rear shelf or the front doors, with the result that most of the high frequencies are sent in the wrong direction.

Pioneer have got round this problem in the design of their TS-1600 unit. This has a cross-axial arrangement with the tweeter axis inclined at 60° to that of the woofer. When the unit is mounted on the rear shelf with the woofer pointing upwards, the tweeter directs most of its output at the heads of the front seat occupants.

The TS-1600, nicknamed the Music Director for obvious reasons, also incorporates a diffuser in front of its 57 mm tweeter cone to give a wider horizontal spread of sound.



## Computing Cassette Deck

Nakamichi has just released an extraordinarily sophisticated cassette deck.



**The 1000ZXL has a microprocessor which independently controls tape head azimuth, bias, recording level and equalisation to optimise these parameters for the particular tape actually running in the machine.**

By compensating for the small differences that can exist even between different tapes of the same type and brand, this system is claimed to give an astonishingly flat frequency response of  $\pm 0.5$  dB from 20 Hz to 20 kHz.

Fine setting of all the variables is a multistage process. First of all the processor sets the azimuth, then it fixes a rough level and determines the peak bias. After testing the frequency response, it trims the bias and sets up a first approximation to a

proper equalisation. Then the processor rechecks the frequency response, trims the equalisation, checks again and finally sets the level.

The whole process takes about 20 seconds, including the time taken to rewind the tape. Adjustment data can be stored in one of four memories in case the same tape is used again.

Another interesting feature is the improvement in erasing ability which has been achieved by abandoning the standard practice of using the same oscillator frequency for biasing and erasing. Although low frequencies are best for erasing and high ones for biasing, a single compromise frequency of about 80 kHz is generally used to avoid beats.

Nakamichi have improved on this practice by using a quartz-

locked master oscillator to generate the bias frequency of 105 kHz. A frequency halving circuit, which is phase locked to the master oscillator, is used to drive the erase head at 52.5 kHz.

The 1000ZXL is promoted as a long term investment that should not become obsolescent with future developments in tape technology. To this end the machine is provided with a bias set switch that can shift the entire range of settings inherent

in the microprocessor adjustment system up or down by 12.5% in case tapes of the future require bias settings outside the range of today's.

Nakamichi expect this machine to supercede their older Model 1000 and once more place the company 'head and shoulders' above the rest of the market. Enquiries to Convoy International, 4 Dowling St, Woolloomooloo NSW 2011. (02)358-2088.

## TDK cassettes


**The TDK advertisement on page 91 of the July issue suffered on a slight problem of missing copy.**

The column on the right hand side of the advertisement referring to the OD, AD and D tapes had the column heading missing — it said "Normal Position Tapes". We thought it prudent to explain the problem in case some readers though the Optimum Dynamic (OD), Acoustic Dynamic (AD) and Dynamic (D) tapes appeared to be included in TDK's list of High Position tapes.

— to page 115. ►



# MARANTZ ROLLING THUNDER CAR STEREO

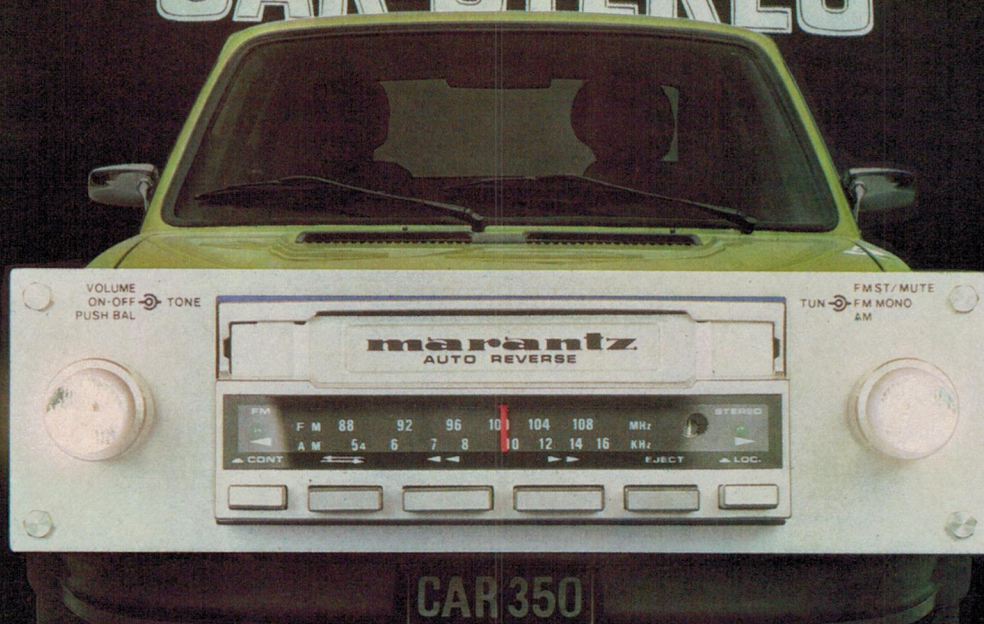

ALFASUD: Car of the Decade, 'Car' Magazine, Jan '80

Marantz, makers of the world's most uncompromising hi-performance, hi-fi components, hits the highways with the new Rolling Thunder Car Stereo range.

Tailored sound, precision engineered, with a performance equal to the high fidelity you expect from quality home audio equipment: dynamic, clear, soft and sweet. Or bold and gutsy. Take your choice.

Rolling Thunder Radio Cassette-players' features include auto reverse, AM/FM pushbutton selection, powerful 12 watts total power output, locking fast-forward and rewind controls. And you get it all through Rolling Thunder speaker systems — an extensive range of round and oval types from a space-saving 4" to the sophisticated 5-way SS 569 shown, with all but a few having 20 oz. magnets. And every one designed for maximum performance.



Pack the powerpunch with the sensational SA 230 Integrated Amplifier. Individual bass and treble controls and 40 watts total power give you the liveliest rock venue on wheels. It's also compact and easy to instal.

Or, if at 80 k's you can still hear the siren behind you, turn on to the SA 247 7-band super powerful Equalizer-Amplifier. You get 60 watts of clear highs and punchy bass, you colour it to car or concert effect.

And you can connect it to almost any car stereo receiver.



Rolling Thunder is different. You'll hear that difference. Even feel it.

**marantz**  
Now you're listening.



MARANTZ (AUST.) PTY. LTD.  
32 Cross Street, Brookvale, N.S.W. 2100

Please send me more information on Marantz Rolling Thunder range of car stereo.

NAME .....

ADDRESS .....



# The Sony Casseiver.

A name like  
no other for a system  
like no other.

Never before has such a high quality system been so reasonably priced. The Casseiver by Sony. The Casseiver combines a front-loading Dolby\* cassette deck, with twin LED displays and soft-eject mechanism; a built-in amplifier delivering 15 watts/channel RMS; a sensitive 4-band AM/FM/SW1/SW2 stereo tuner and a full-range speaker system with passive cone radiators. And with provision to add on other components, such as a turntable, the Sony Casseiver is truly a system like no other. Recommended retail price \$499.

\*Dolby is a registered trademark of Dolby Laboratories.



The PS-212A turntable (pictured) is an optional extra. Recommended retail price \$210.00.



AP3412

**SONY**  
AUDIO





## Hi-fi consoles from Hitachi

**Hitachi have recently introduced a range of consoles which will accommodate most of their hi-fi units.**

Model VC 1 is a 'vertical' design which will hold any of their four turntables, a cassette deck and a stereo receiver. The taller VC 2 will take a record deck, cassette deck, AM/FM tuner and a separate stereo amplifier.

Two 'horizontal' styles of console are also available. The HC 1

has space for three units and the HC 2 will house similar units to the VC 2.

All the new consoles have generous storage space for records and cassettes, are attractively styled and reasonably priced. The VC 2 for example retails for a little less than \$50.

## High speed Technics tape deck


**The latest open reel tape recorder from Technics is designed for professional recordists and features a tape speed of 76 cm/sec.**

The RS 1800 has a three motor direct drive tape transport system which will also run at speeds of 38 or 19 cm/sec. A quartz synthesizer pitch control system allows speed variations of up to 9.9% in increments or decrements of 0.1%. Nominal speed and variation are displayed digitally.

Rather surprisingly for a studio quality deck, the RS 1800 uses quarter inch tape. The standard model is two-track two-channel record and reproduce but Technics can supply four-track head assemblies as well.

The heads themselves are made from an improved version of the Sendust alloy called SX, which is claimed to have improved wear and resistance as well as better magnetic characteristics.

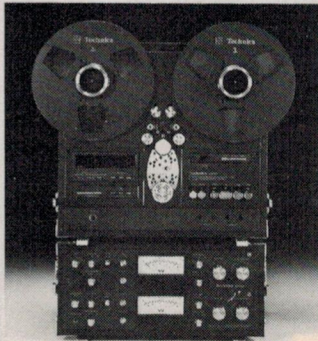The amplifier is completely separate from the tape transport unit and has its own power supply. Both the playback and



the recording amplifiers are designed to preserve every aspect of a waveform by accurately reproducing the relative phases as well as amplitudes of the various frequency components.

An integral oscillator provides automatic equalisation at set frequencies of 100 Hz, 1 kHz, 10 kHz and 20 kHz and an automatic bias adjustment system allows virtually any tape formulation to be used. For total control, manual bias and equalisation adjustment is also provided.

## Improving speakers is easy as ABC !

**A new range of speakers from KLH are equipped with sophisticated equalisation and overload control.**

The control circuitry is contained in a separate module which the makers call an Analog Bass Computer, or ABC for short. Each of three sizes of speaker in this range has its own version of the ABC, which is specifically matched to the characteristics of that speaker's enclosure and drivers.

ing the drivers. Two methods are used to prevent this.

Very low frequency (bordering on subsonic) transients caused by surface irregularities or turntable rumble are eliminated by a steep cut high pass filter. Musical bass transients cannot of course be dealt with so simply, and this is where the



Equalisation to improve linearity of the perceived sound output at low frequencies has long been employed in professional monitor speakers, but it's rare to find it on systems intended primarily for domestic use.

The Analog Bass Computer which provides this equalisation on the KLH-1, KLH-2 and KLH-3 speaker systems is basically an extra amplifier whose gain varies with frequency. Above 70 Hz the gain is unity; at frequencies below this the gain increases to compensate for the reduced efficiency of the speakers.


This method of compensation, which is also known as bass pre-emphasis, carries with it a considerable risk of distortion or damage from overload-

description 'Computer' begins to be justified.

To prevent the woofers from exceeding their maximum safe displacement on very loud bass passages of a piece of music, the Analog Bass Computer incorporates a special signal processor network. This processor detects the voltage present at the speaker terminals and modifies the input voltage to the equalising circuits as a function of this voltage and the electro-mechanical characteristics of the driver. KLH claim the processor responds so quickly when it senses a potential overload that distortion is very unlikely.

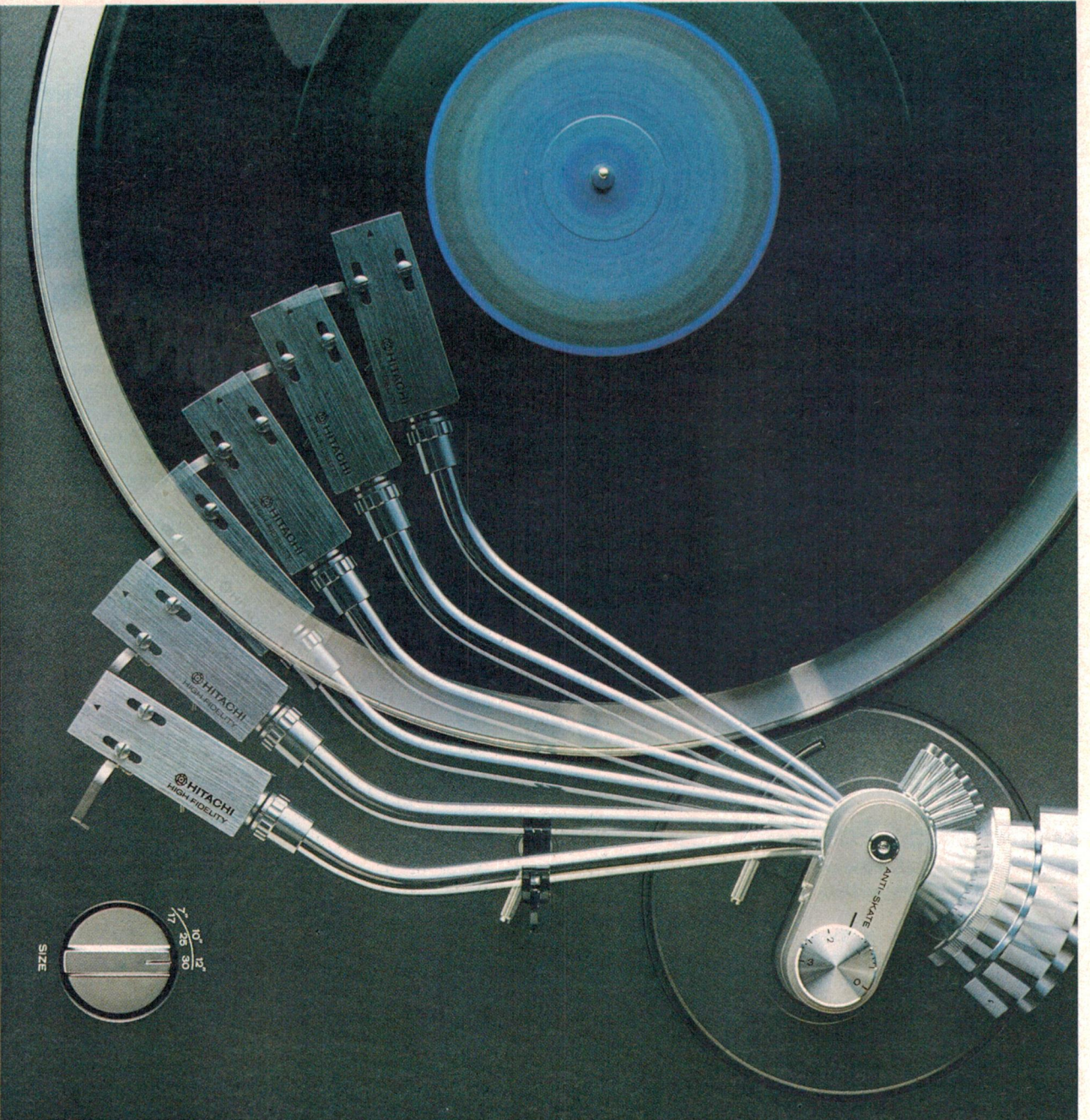More details can be obtained from the distributors, Concept Audio, P.O. Box 422, Dee Why NSW 2099.





HITACHI  
UNTORQUE  
QUARTZ LOCK  
DIRECT DRIVE AUTOMATIC TURNTABLE model HT-660

REPEAT  
START/CUT  
DOWN  
UP

SIZE  
10"  
12"  
15"  
17"

# sound engineering



## Hitachi's Photo Sensing Tone Arm

### Optically-activated return eliminates side force to make the HT-660 Turntable the accurate choice.


The photo sensing tone arm is sound engineering. Precision engineering. It's a remarkable design concept that achieves unsurpassed turntable accuracy. Because with photo sensing return, the side force of conventional systems doesn't exist. And in the HT-660 Turntable, it's joined by Quartz-locked Unitorque that makes every revolution of the platter perfectly smooth.

The benefits of non-contact switching are readily apparent — every time you play a record. Distortion-producing mechanical parts have been eliminated. Instead switching is activated by a light beam. And because unnecessary side force doesn't exist, the arm requires far less tracking pressure.

Unitorque direct-drive with Quartz further contributes to the unit's fine sound reproduction. Wow and flutter is a low, low 0.025% WRMS.


Of course the system is fully automatic, but all auto functions are independently powered so there's no drain on the main drive motor. And the controls for those functions are right up front. You never have to lift the dust cover to get to them.

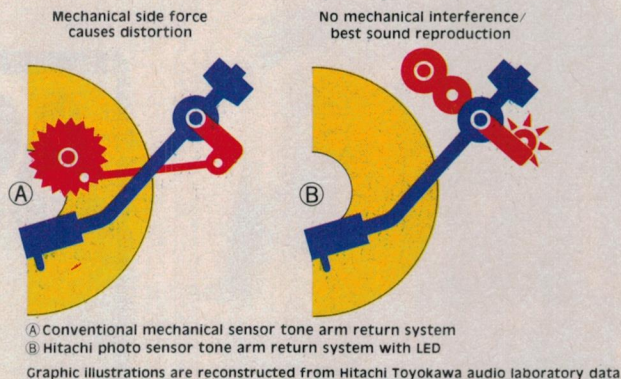Hitachi technology is at work to bring you greater turntable accuracy through advanced electronics. The HT-660 Turntable with the photo sensing tone arm system and Unitorque with Quartz is the result of those efforts. Listen to the soundness of Hitachi engineering today.



Professional sound through sound engineering

# HT-660

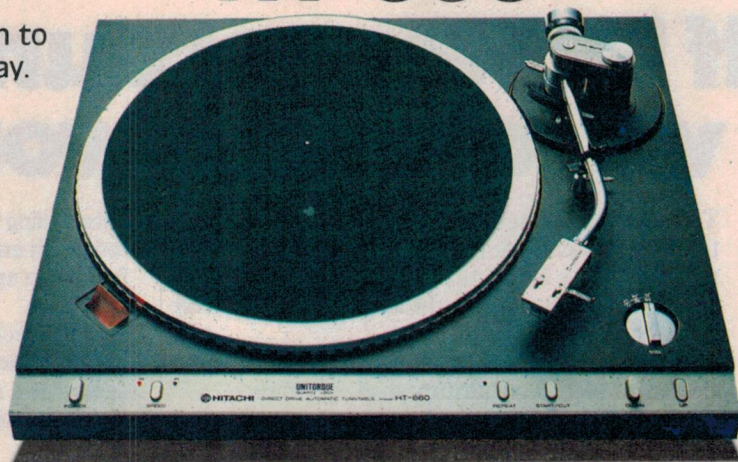





# If he were around today we know he would use it.

Throughout his career as a composer and performer, there is no doubt that Franz Liszt went first class all the way. So it's logical to suppose, if he was around today, he would choose a chromium dioxide tape for recording and playback.

If you want to go first class too, choose Agfa Stereochrom and get unsurpassed recording characteristics, high frequency replay response,

outstanding H.F. output and dynamic range, clearer tone with enhanced presence. Even the cassette features a special mechanism for better tape transport.

Agfa Stereochrom C60+6 and C90+6 cassettes are available at hi-fi specialists, music stores and photo dealers.




\*Registered  
trademark of  
AGFA-GEVAERT  
Antwerp/Leverkusen.



# Modern turntable technology

Here we look at the requirements of the modern record player and discuss how advanced electronics can provide 'the ultimate' in this branch of hi-fi. We also consider the products of the major manufacturers and some of the special facilities offered in high quality decks.

**Brian Dance**

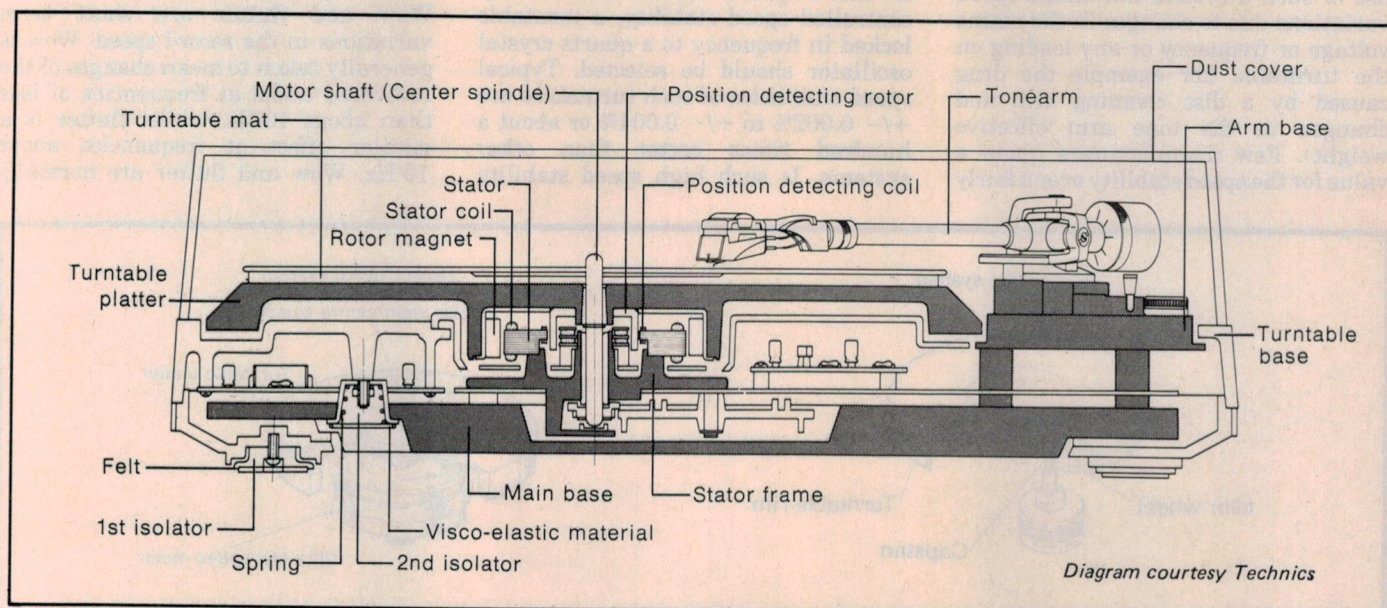

**THE BASIC REQUIREMENT** of any record player assembly is that the turntable shall rotate noiselessly, at the required speed without any short-term or long-term variations in this speed. This sounds a simple enough requirement, yet sophisticated, modern players contain quite complex circuitry with large numbers of integrated circuits and discrete components; indeed, the circuitry is too complex for us to reproduce in full for any of the latest players mentioned in this article!

Turntable mechanisms have evolved a very long way from the purely mechanical gramophones of about fifty years ago where one had to wind up a spring motor with a handle. All of the audio power came from the mechanical interaction of a large steel needle with the surface of the revolving record; the steel needle moved a mica diaphragm at

the narrow end of a flexible horn which provided suitable acoustic coupling to the air. The weight of the moving arm part of the horn seemed almost enough to push the needle through the record! However, it is this old type of gramophone which has set the pattern for the modern record player of today.

## Turntable speed

The rate of rotation of the turntable directly controls the frequency of the audio signal reproduced from the record track. Any slight increase or decrease in the rate of rotation will produce a proportionate increase or decrease in the pitch of the recovered audio signal. Most modern recordings are made for use at either  $33\frac{1}{3}$  or 45 revolutions per minute. How accurately must the player match these speeds of rotation in order to be acceptable? This is not a

question to which one can give a definite answer, since so much depends on one's hearing, on the listening experience one has had previously and on the amount of hard cash one is willing to spend in order to obtain a constant rate of revolution. (See April 1980 ETI, p.108.) (One might even add that it could even depend on how much one is willing to spend to be able to praise one's equipment to one's friends and neighbours!)


Most of the fairly economical turntables employ a strobing system which enables the rate of rotation of the turntable to be set quite accurately to the required speed. The cheapest strobing system employs a lamp (normally a light emitting diode) which flashes at the mains frequency of 50 Hz. However, if one uses the mains frequency as one's standard, any ►



changes in the mains frequency will produce errors. This problem can be avoided by driving the lamp from an astable multivibrator circuit which is operated from a stabilised supply voltage.

In the simplest systems the lamp may be placed under the edge of the turntable so that light passes through a pattern of bars on the edge; the speed is correct when the bar pattern for that speed remains stationary as the turntable rotates.

To stabilise rotation speed a tachometer and an F/V converter can be used to give a voltage proportional to rotation rate. The difference between this and a reference voltage is used to adjust the speed of rotation so that the error voltage is reduced almost to zero. The use of such a system minimises speed variations due to changes in the mains voltage or frequency or any loading on the turntable (for example the drag caused by a disc cleaning arm and changes in the tone arm effective weight). Few manufacturers quote a value for the speed stability over a fairly

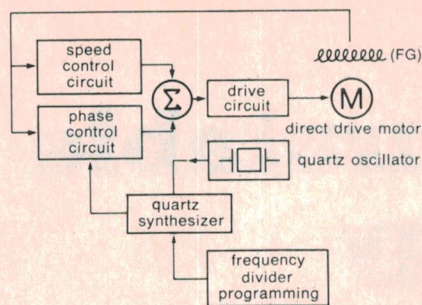

Block diagram of a quartz stabilised turntable drive circuit, as devised by Technics.

long period for such equipment, but generally a few tenths per cent speed variation is reasonable.

### Quartz stabilised

If one requires much more closely controlled speed stability, a turntable locked in frequency to a quartz crystal oscillator should be selected. Typical speed stabilities of such turntables are  $\pm 0.002\%$  to  $\pm 0.004\%$  or about a hundred times better than other systems. Is such high speed stability


necessary? Only you, the user, can answer this question after prolonged listening to both quartz stabilised and other equipment.

In some quartz stabilised equipment one cannot vary the turntable speed at all without switching the quartz control out of use. In others the crystal reference frequency is divided by different factors to enable the speed of rotation of the turntable to be varied without losing the advantages of quartz control. Some manufacturers of top quality decks offer quartz control systems with a digital display of the platter speed. Changes in speed of a quartz controlled system with temperature can be as low as 0.2 parts per million per centigrade degree.

### Wow and Flutter

Wow and flutter are short term variations in the record speed. Wow is generally taken to mean changes of the recovered audio at frequencies of less than about 10 Hz, whilst flutter is a similar effect at frequencies above 10 Hz. Wow and flutter are normally


Rim drive system

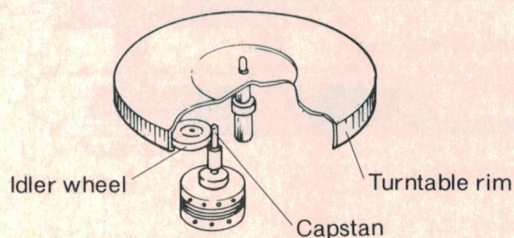


#### Rim Drive

In this system the motive power provided by the drive motor is applied to the inner or outer edge (rim) of the turntable by means of a capstan on the shaft of the motor. Since a high speed motor is used, one or more idler wheels are inserted between the capstan and the rim to reduce the speed and achieve the desired ratio to obtain the correct platter speed. (This system is also known as 'idler drive'). The rim drive system is relatively low in cost, permits the use of a low torque motor and allows mechanically simple speed changing. Its main disadvantage is rotational instability due to slippage occurring between the capstan, idler and rim.

Speed change of rim drive

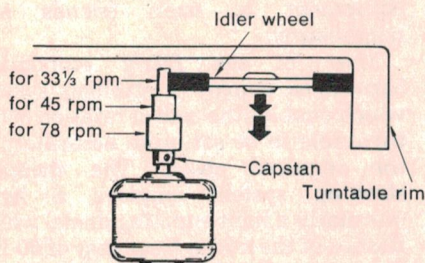


Direct drive system

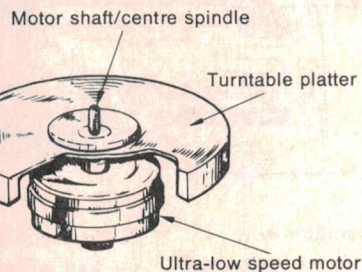


#### Direct Drive

As the name implies, this system uses no speed reduction devices to transfer the motive power from the motor to the turntable platter. Rather, the shaft of the platter is set in the centre of the motor itself and is driven directly. The motor rotates at exactly the required speeds (33 1/3 or 45 rpm) and its rotational accuracy is maintained by any one of a variety of electronic servo mechanisms. The slower rotational speeds and very high rotational accuracy of this system have brought both rumble and wow and flutter specs to levels seldom if ever before achieved. Since the introduction of the first direct drive turntable by Technics in 1970, this system has rapidly become very popular and many manufacturers have entered the market with their own models.

Speed change of belt drive

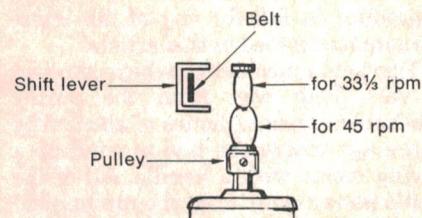

Belt drive system

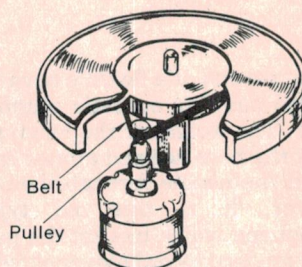

#### Belt Drive

This is a very common drive system like the rim drive. A relatively high speed motor is used and coupled to the turntable platter by a compliant belt. By moving the belt up or down over different diameter sections of the motor shaft pulley, speed changes may be effected. One of the big advantages of this system is that the belt serves to dampen motor vibrations, thereby reducing noise and rumble. Polyurethane is the preferred belt material because of its resistance to heat, humidity and oil and its low elasticity. The problems encountered with belt drive are instability due to belt slippage and a relatively large amount of vibration due to the high rotational speed of the motor.



measured together as a total percentage, but a form of weighting network is often used which attempts to take account of the degree of annoyance to the listener so that wow and flutter of particularly annoying types produces a larger contribution to the percentage figure than a similar amount of other types.

Wow and flutter can be measured in various ways. If one uses a test record, replay cartridge and tone arm, one will usually obtain a higher percentage figure than if one measures the fluctuations of speed in the turntable more directly with a tachogenerator. Many of the Japanese manufacturers employ the tachogenerator technique to obtain a percentage figure for wow and flutter expressed as a WRMS figure (weighted root mean square). The German standard DIN (Deutsche Industrie Normal) is a peak weighted figure expressed as a percentage which is a *third* figure to catch the unwary.

It has been agreed that DIN peak weighted wow and flutter percentages of less than about 0.1% are probably undetectable in normal listening. However it has recently been shown that intermodulation products which can be generated by pitch fluctuations can impair the recovered audio signals, so it is wise to select a system with the minimum wow and flutter percentage figures you can afford. The percentage figures quoted are normally in the range 0.01% to 0.1%. (See also, April 1978 ET, p.108).

Table 1 shows wow and flutter percentage figures for the Philips AF877/AF977 and AF677/AF777 turntables measured in various ways for comparative purposes. The lower values obtained for the AF877 and AF977 are due to improved control circuitry and differences in the mass of the turntable.

## Cogging

Most turntable motors are dc electric motors which employ Hall Effect cells for commutation instead of the conventional brushes and copper commutator ring. Brush sparking can

generate much noise; the use of Hall Effect cells for detecting the changes of magnetic field and for generating the switching pulses eliminates brush noise.

However, the problem remains that the energy is given to the motor in small discrete pulses as each coil passes through one of the magnetic fields. The uneven running due to this effect is known as 'cogging'; it can result in appreciable rumble combined with wow and flutter. Technics have developed a 20-pole, 30-slot brushless dc motor to minimise the effects of cogging. Hitachi employ their 'Unitorque' motor which incorporates a 200-pole rotary magnet. The coils are arranged 22.5° physically or 90° electrically out of phase with each other. The torque produced by a single coil fluctuates in a linear mode between a maximum value and zero. When the coils are out of phase at a given rotor angle, the sum of the torque produced is equal to the maximum torque of a single coil. This results in a motor action which has a uniform torque which is completely free from cogging.

## Other effects

Various other effects can cause minor variations in turntable rotation. One of these is 'platter wobble' in which the turntable wobbles on its axis. It may be reduced by the use of a large diameter centre shaft, but Pioneer employ a hanging rotor system in which the main bearing is placed at the centre of gravity of the rotating system at the top of a fixed motorshaft. This provides a kind of gyrostatic action, increasing the stability and allowing the platter and the attached 'hanging cup rotor' to glide without any wobbling.

The actual recorded groove can cause small fluctuations in the speed of rotation of the platter. Figure 1 shows a stylus tip following a heavily modulated signal. It can be seen that the pressure of the stylus on the one wall of the groove acts as a variable braking effect on the rotation of the turntable. This problem can be reduced by using a turntable of high moment of inertia, but in turn this involves the use of a high

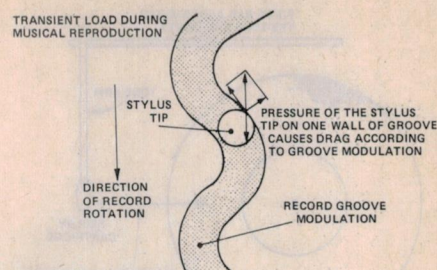


Figure 1. The groove modulation can apply a variable braking effect on turntable rotation.

torque motor which can bring the turntable up to its correct speed reasonably quickly.

Vibrations from the motor, transformer and acoustic waves from the speakers can also affect the rotational stability of the platter.

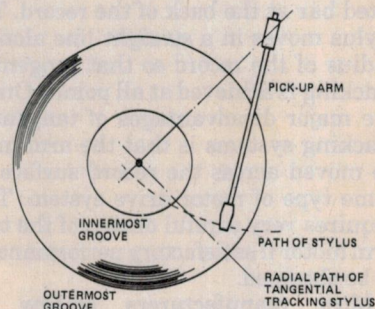


Figure 2. The path a conventional tone arm traces across the record is different to the path taken by the cutting arm of the original disc cutter. Thus, the stylus is not always tangent to the groove. Tangential tracking arms were devised to overcome this.

## Tangential tracking

The conventional tone-arm moves across the record in an arc of a circle so that the path of the stylus is as shown in Figure 2. When a record is being cut, however, the cutting arm moves inwards along a radius towards the centre of the record. Thus the cutting path is a straight line unlike the arc of the replaying stylus. This leads to the important point that the direction of the motion of the recording head relative to the record surface is a tangent to the recording groove at all times. A conventional stylus cannot move at a tangent to the record groove at more than two places. At all other points there will be a small angle between the direction of relative movement and a tangent to the groove.

Many people feel that a stylus which follows the path of the cutting head across the disc as accurately as possible is likely to achieve a more faithful reproduction of exactly what is on the disc than a stylus which moves at an angle to the direction of movement of the cutting head. A few record decks are now coming onto the market in which 'tangential' or 'parallel' tracking is achieved.

AF877- AF977	AF677- AF777	Measurement technique
0.05	0.08	% DIN using test record, cartridge and tone arm.
0.03	0.05	% WRMS using test record, cartridge and tone arm.
0.02	0.04	% WRMS measured directly at output of tachogenerator (thus eliminating effects due to the test record, cartridge and tone arm).

Table 1. Wow and flutter figures for Philips turntables measured in three ways.



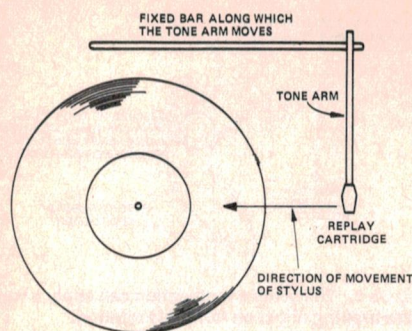


Figure 3. The basic arrangement of a tangential tracking turntable system.

The basic idea of the tangential tracking system is shown in Figure 3. The tone arm does not swing in an arc, but moves from right to left along a fixed bar at the back of the record. The stylus moves in a straight line along a radius of the record so that tangential tracking is achieved at all points. One of the major disadvantages of tangential tracking systems is that the arm must be moved across the record surface by some type of motor drive system. This requires very careful design of the tone arm motor if satisfactory performance is to be obtained.

Most manufacturers employ an optical feedback system to control the tone arm motor. In the normal or equilibrium position a beam of light from a lamp is blocked off by a shutter on the tone arm so that it cannot reach a photo-resistive cell. If the record now rotates so that the stylus is closer to the centre of the record, the position of the tone arm will be changed by a small amount so that the shutter no longer prevents the beam of light from reaching the photoconductive cell. The current through this cell activates the tone arm motor which moves the arm inwards towards the centre of the record until the shutter again blocks the beam of light.

A successful optical system of this type must be very accurate, since the record grooves are very small and close together. The tone arm motor system must also be carefully designed to prevent 'hunting' in which excessive or

inadequate movement of the tone arm takes place and the system hunts for the correct position.

Tangential tracking systems generally provide tracking angles to within a few tenths of a degree of the desired angle, whereas conventional systems may have angles of up to a few degrees at some point on the record. But what is the practical effect? Tracking error angles tend to introduce second harmonic distortion which, whilst obviously undesirable, is not nearly so objectionable as third harmonic distortion. There seems to be some controversy as to exactly how much distortion is introduced by such tracking angle errors. Pioneer state that reduction of crosstalk between channels can be achieved by the use of tangential tracking.

In a tangential tracking system the effective arm length can be relatively short and the equivalent mass low even if strong materials are used to obtain a highly rigid arm. This can bring the advantages of minimum vibrational levels and small resonance patterns and hence of cleaner reproduction.

In spite of their important advantages, tangential tracking decks must be very carefully designed if they are to be better than conventional systems. Designers have not yet had extensive experience with linear tracking, so the intending purchaser would be well advised to try any linear tracking equipment very thoroughly before committing himself to purchase. However, it may well be the system of the future for top-of-the-market systems.

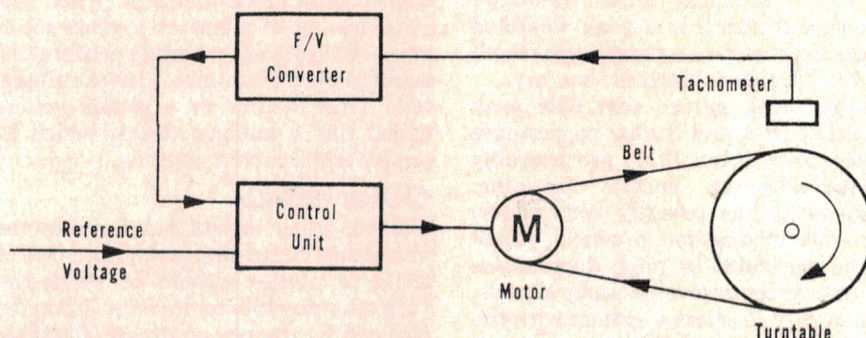


Figure 4. The Philips 'direct control' system employs belt drive for the platter and servo feedback to the motor control circuitry via a tachometer sensing the platter speed.

The pickup arm of a conventional system will tend to 'skate' towards the centre of a record unless the correct amount of bias compensation is applied. If no bias or an incorrect bias is applied, the inner groove is likely to receive more force from the stylus which will result in signals of an unequal amplitude in the two channels and which is likely to cause the inner groove to wear at an increased rate. These problems are said not to arise in tangential tracking systems, whereas in conventional systems the application of bias is only a compromise, since the required bias varies with the position of the tone arm on the record and with the modulation levels.


## TURNTABLE SURVEY

We will now review various turntables and will stop to examine any unusual features offered in specific types. As the Japanese seem well ahead in this market, most of the models considered are Japanese.

### Philips turntables

The Philips AF685 turntable is at the low-price end of the market and has electronic speed control with belt drive. The AF677 features 'direct control' and has about half the wow and flutter level of the AF685. The AF777 is rather similar to the AF677, but has automatic record diameter selection and arm

Figure 5. Block diagram of Philips' quartz-PLL speed stabilisation system.

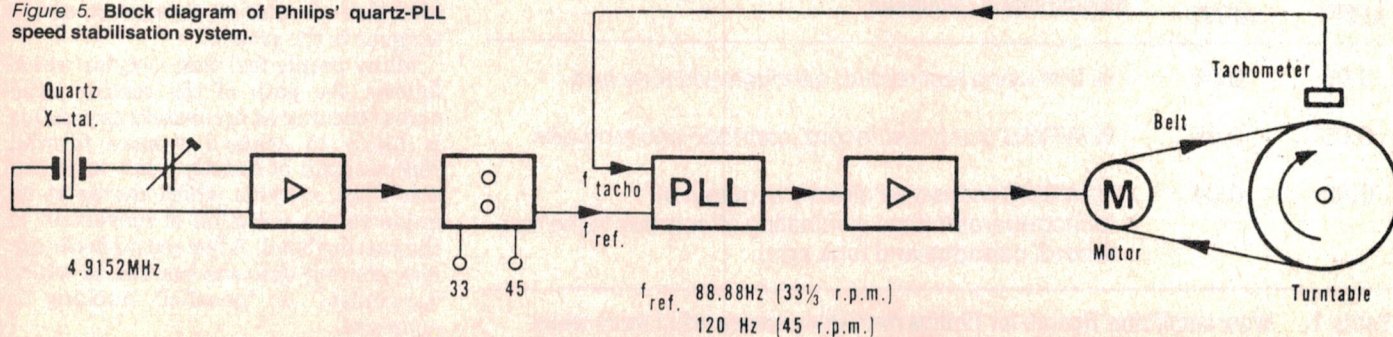



positioning, variable pitch controls with a LED speed display, etc. The AF877 offers lower wow and flutter (see Table 1) and completely silent operation is achieved by the use of touch control switches; at the end of each disc, a photo-electronic sensor detects the acceleration of the arm as it follows the run-out groove and the arm is automatically returned to its rest. The AF977 employs a quartz stabilised speed system.

Let us look at the Philips 'direct control' belt drive system which is said to provide similar specifications to direct drive systems without the expensive constructional techniques required in direct drive systems to avoid rumble, etc. The direct control system is shown in Figure 4. Unlike servo control systems, in direct control the feedback signal is obtained from the turntable itself and not from the motor. Thus, stabilisation is related to the speed of the turntable itself — which is what matters most of all. Any slackness in the belt will have a much smaller effect than if the tachometer were connected to the motor. Fine control of the turntable speed is effected by varying the reference voltage with which the feedback voltage is compared.

The AF977 deck employs a quartz stabilised circuit of the type shown in Figure 5. The 4.9152 MHz signal from the crystal controlled oscillator is divided by a suitable factor, the value of which depends on whether one requires the 33 $\frac{1}{3}$  or 45 rpm speed. The resulting reference frequency is fed to a phase-locked loop (PLL) circuit together with the speed frequency fed back from the tachometer. The output from the loop is used to control the motor speed. Thus, the phase of the tachometer generated signal is continually compared with that of the reference frequency and very high stability is obtained.

### Trio-Kenwood Turntables

Japanese manufacturer Trio-Kenwood produces the KD-600/650/750/850 range of quartz/phase-locked loop stabilised turntables and the electronically speed controlled types KD-3100 and KD-4100. This manufacturer emphasises the importance of using a turntable of a high moment of inertia to prevent transient changes of speed due to load variations. The turntable bases have been developed from a limestone-resin-concrete mixture to reduce low frequency resonance problems to a minimum. Brushless 20-pole, 30-slot dc motors are employed to minimise cogging and to provide DIN weighted rumble levels of -75 dB. Electronic braking is employed to minimise resonance effects. The tone arm wiring



Philips' AF977 turntable features 'state of the art' specifications, digital speed indication, automatic operation and direct readout of the adjustable stylus force.

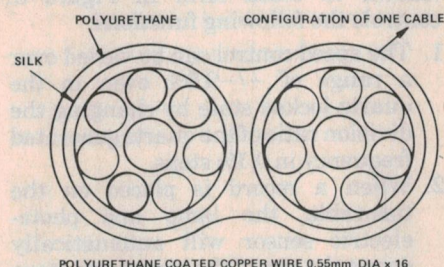


Figure 6. The Trio-Kenwood low capacitance tone arm wire.

in these models consists of 'Penta-Litze' wire of the cross section shown in Figure 6; this has a very low capacitance and therefore signal losses and cross talk are minimised.

The model KD-850 has a fully automatic tone arm controlled by a digital-optical electronic system; it is both completely silent and error proof even if the arm is operated manually whilst set for automatic operation. ►

The Trio-Kenwood KD-850 fully automatic direct drive turntable.





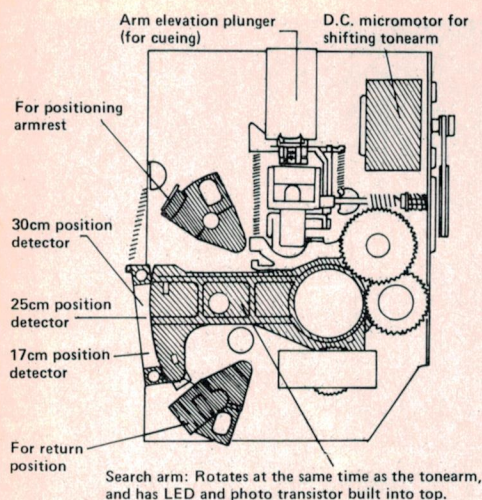


Figure 7 (a). The automatic mechanism of Trio-Kenwood's model KD-850 turntable.

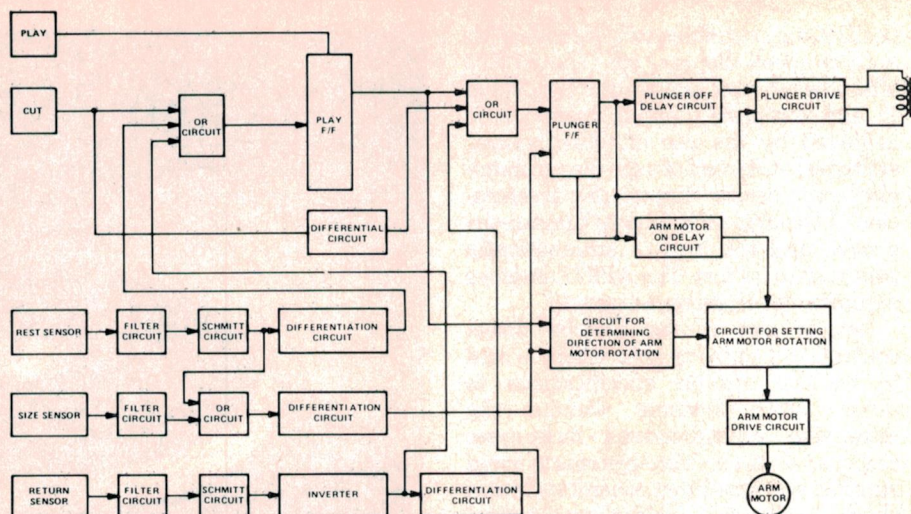


Figure 7 (b). Block diagram of the logic system employed for automatic operation in the Trio-Kenwood KD-850.

The automatic mechanism is shown in Figure 7. A photo-sensing system automatically selects the record size for the tone arm by sending a light beam to any of the prism slots in the platter not covered by records so that the information is signalled back to the disc size selector. The KD-4100 also employs an electronic system for automatic tone arm control, but the turntable is not locked in frequency to a quartz oscillator circuit.

## Hitachi Turntables

Hitachi manufacture a range of turntables, including the HT324 and HT354, with electronic speed control, the HT356, HT353, HT550Q (semi-automatic) and the HT463 and HT660 (fully automatic) quartz crystal stabilised types. Perhaps the most

interesting model, however, is the new HT-860 microcomputer controlled, quartz stabilised, fully automatic turntable.

The microcomputer control system (shown in block form in Figure 8) controls the following functions:

1. The speed control can be varied over a range of  $\pm 9.9\%$  even in the quartz locked state by changing the division ratio of the quartz generated frequency in 0.1% steps.
2. When a record is placed on the turntable, the lamp and photo-electric sensor will automatically detect the size of the record and move the tone arm into the correct position.
3. The speed is automatically set on detection of the record size, except in

the case of 300 mm, 45 rpm and 170 mm,  $33\frac{1}{3}$  rpm records.

4. Optical sensors are used for moving the tone-arm in this fully automatic deck.
5. A repeat function allows the automatic replaying of any record up to nine times.
6. The tone-arm can be swung to any position by front panel button operation.
7. A safety mechanism prevents damage to the stylus under error conditions (such as operating the start button with no record on the turntable).
8. A fluorescent tube display indicates the turntable speed, any pitch variation, the record size and the number of repeat cycles.


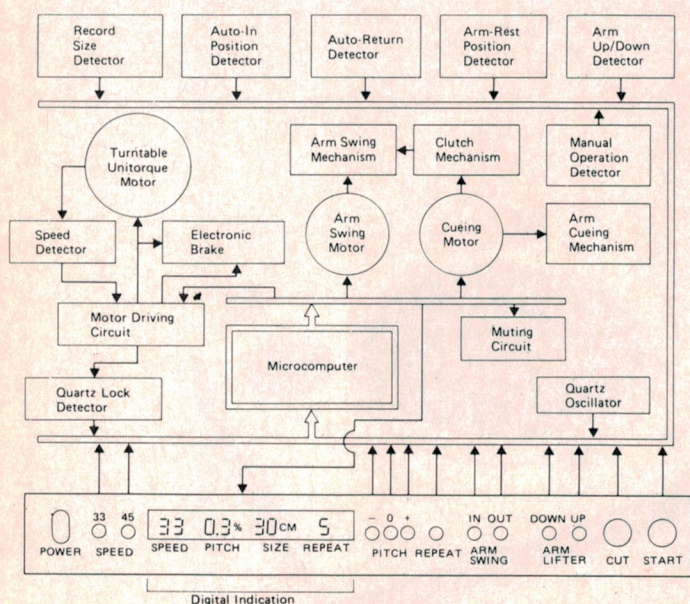


Figure 8. Block diagram of Hitachi's HT-860 microcomputer controlled deck.

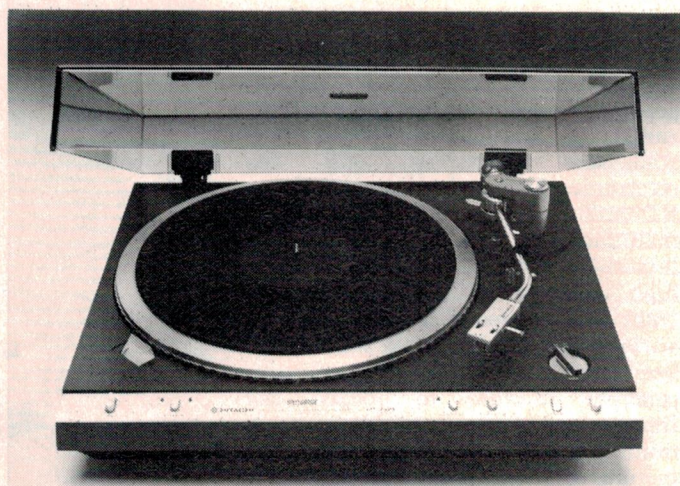

The Hitachi HT660 quartz locked, fully automatic deck features optical sensing for the tone arm return and electronic platter braking.



## Sharp Optonica Turntables

Sharp Optonica produce three types of turntable. The RP-5100 is a fully automatic, direct-drive type with stroboscopic indication, the RP-7100 is a quartz locked unit with an Auto Programme Locate Device (APLD) and the RP-9100 has all of these features plus remote control, digital speed display, etc. One may note that the RP-9100 employs some 40 integrated circuits, 40 transistors, 22 diodes, two Hall cells and two quartz crystals, so it is quite complex! The integrated circuits include a Z-80 microprocessor, an EPROM, 256 x 4-bit random access memories and a host of other logic devices.

The quartz locked motor systems of the models RP-7100 and RP-9100 are similar. A frequency generator comprising a 160-pole magnet and a multigap head having 80 pairs of pole teeth and coils is connected to the motor and generates a 44.44 Hz sine wave signal, when the motor is rotating at 33 $\frac{1}{3}$  rpm and a 60 Hz sine wave signal when the motor is rotating at 45 rpm.

The signal from the generator is fed to an operational amplifier and then to an astable circuit which produces a rectangular waveform of 50% duty cycle. This frequency is compared with a reference frequency generated from a crystal oscillator in the following way.

The crystal oscillator frequency of 9.3312 MHz is divided first by four and then by 972. The resulting frequency is

The Optonica RP-7100 turntable features a special 'Auto Programme Locating Device' (APLD).

then divided by either 27 (for 33 $\frac{1}{3}$  rpm) or by 20 (for 45 rpm) and finally by a factor of two to produce the reference frequency of either 44.44 Hz or 60 Hz.


The operation of the direct drive motor circuit with its Hall effect commutating devices is well illustrated in Figure 9. The outputs of each of the two Hall Effect cells (marked HE) are fed to the inputs of operational amplifiers. The output of each operational amplifier drives a pair of

complementary transistors which in turn control the current in the motor drive coils. The Hall cells detect the position of the rotor magnets and cause the currents in the motor drive coils to be phased accordingly. In addition, the voltage applied across the Hall cells is controlled by the servo phase control circuits and alters the switching times of the motor drive coil current so that the motor rotates at the desired speed.

The automatic programme locate

— to page 128. ▶



Figure 9. Basic circuit diagram of the Sharp Optonica motor drive system.

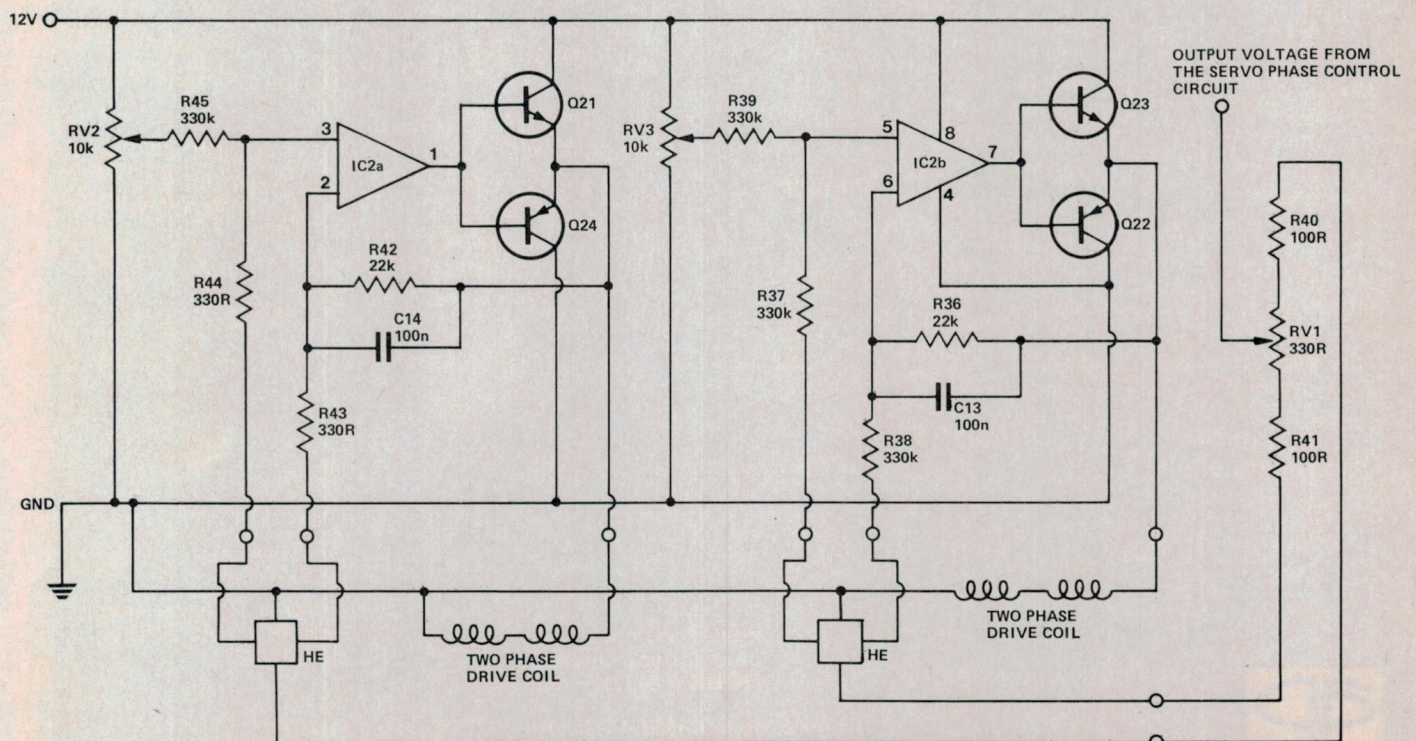


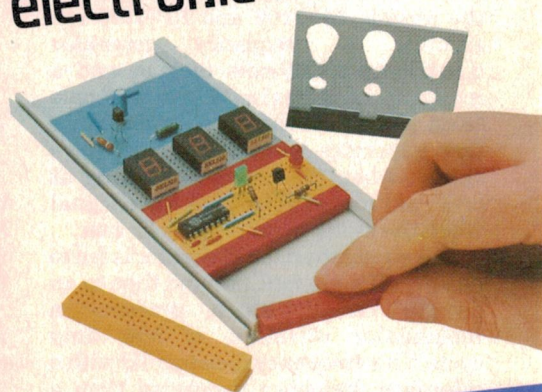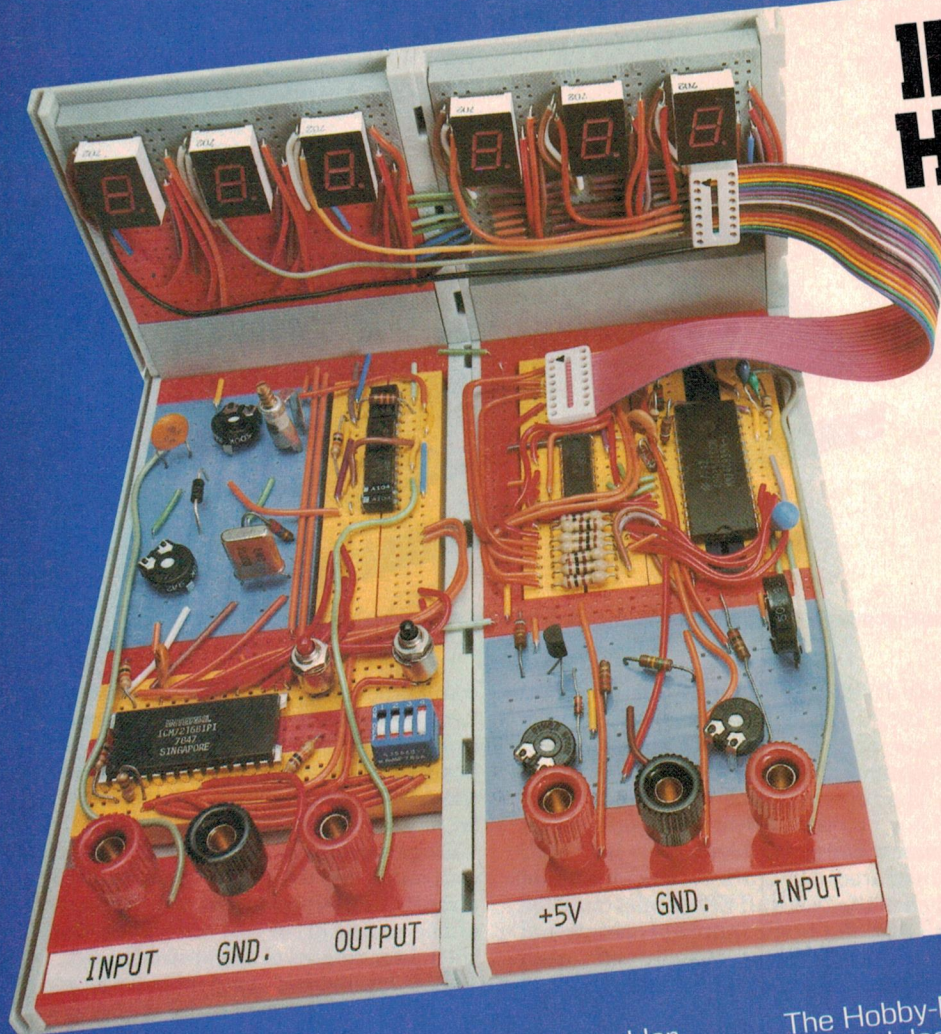
# INTRODUCING HOBBY-BLOX™

The new modular circuit building system designed especially for electronic hobbyists.



Until now, you had to buy "professional" solderless breadboards for your projects and pay "professional" prices. Now there's Hobby-Blox, a totally new circuit-building system that's not only economically priced but offers many more advantages to the hobbyist.

At the core of the system are two expandable starter packs, one for discrete component projects, the other for integrated circuit projects. Each comes with a number of Hobby-Blox modules that fit into a tray and an illustrated project booklet. In addition, the system includes 14 separate component packs you can purchase individually — terminal, distribution and bus strips, speaker panels, binding posts, etc.

The Hobby-Blox system is easy to use because the modules are color-keyed and letter/number indexed. It's time-saving, because they're solderless. It's compatible with DIP's of all sizes and a wide variety of discrete components. And you save money, because the parts can be reused again and again.

How far can you go with the Hobby-Blox system? Take a look at the example above. Then you'll know why we say, "your only limit is your own imagination!"

Patents Pending  
© A P PRODUCTS INCORPORATED 1980



A P PRODUCTS INCORPORATED  
1359 West Jackson Street  
Painesville, Ohio 44077  
(216) 354-2101

**For a free catalog,  
contact your local  
HOBBY-BLOX™ dealer:**

N.E.T. PTY. LTD.  
92 Woodfield Boulevard  
Caringbah, N.S.W. 2229  
TEL: 525-6090

RIFA PTY. LTD.  
P.O. Box 485  
Cross House, 2 Cross Street  
Hurstville, N.S.W. 2220  
TEL: 570-8122

RIFA PTY. LTD.  
P.O. Box 95  
202 Bell Street  
Preston, Victoria 3072  
TEL: (03) 480-1211




**Sansui**

Only hi-fi, everything hi-fi.



# Non-compromise computerized

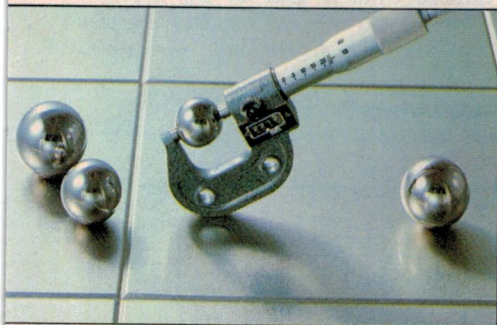

Fully computerized operations have many powerful advantages. Flawless decisions, meticulous monitoring, foolproof functions, record protection and the desirable convenience of random band selection are only a few.

But some audiophiles have had reservations about such systems and their reasons are not mysterious. Until now, you had to accept the one particular cartridge that came with the system.

From now, with Sansui's new XR-Q11, you can freely select whichever cartridge you like. This important

freedom is possible because Sansui engineers have perfected a dual sensor system which is independent of the cartridge.

Until now, the specs and performance of band selector turntables were usually not the very best. The XR-Q11 now changes the sound picture. Speed is better than 99.99% perfect! Wow and flutter is under 0.015%. And performance is peerless thanks to the direct-drive quartz-servo motor. Speed monitoring is exceptionally fast and accurate with Sansui's dual-heads that read the 960 magnetic "marks" coating the platter's inside rim.

Carefully examine the unique, straight D-O-B tonearm. Using basic principles of physics in a new configuration, this tonearm radically reduces all kinds of spurious vibrations, including feedback from the stylus. Combined with the BMC super-dense cabinet and PAT. PEND. floating sub-base, mechanical interferences of the most overt and subtle types have been virtually

eliminated for superb reproduction of even the most difficult dynamic musical qualities.

The facts are clear. The XR-Q11 is one of the world's finest turntables by any standard. And it is the only turntable in its class with the sophisticated convenience of computerized operation including Sansui's Computerized Track Sequence Selection (CTSS).

The new XR-Q11 CTSS turntable: when you want to approach the ultimate.

## **SANSUI** **XR-Q11**

**SANSUI ELECTRIC CO., LTD.**

14-1 Izumi 2-chome, Suginami-ku, Tokyo 168, Japan

**VANFI (AUST.) PTY. LTD.**



297, City Road, South Melbourne, Victoria 3205,

Australia Tel: 690-6200


283 Alfred Street, North Sydney, N.S.W. 2060,

Australia Tel: 929-0293



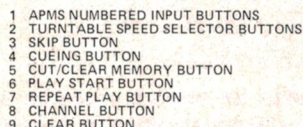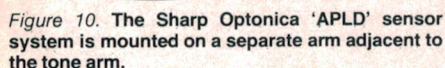

**Figure 12. Configuration and functions of the remote control unit for the Sharp Optonica RP-9100 turntable.**

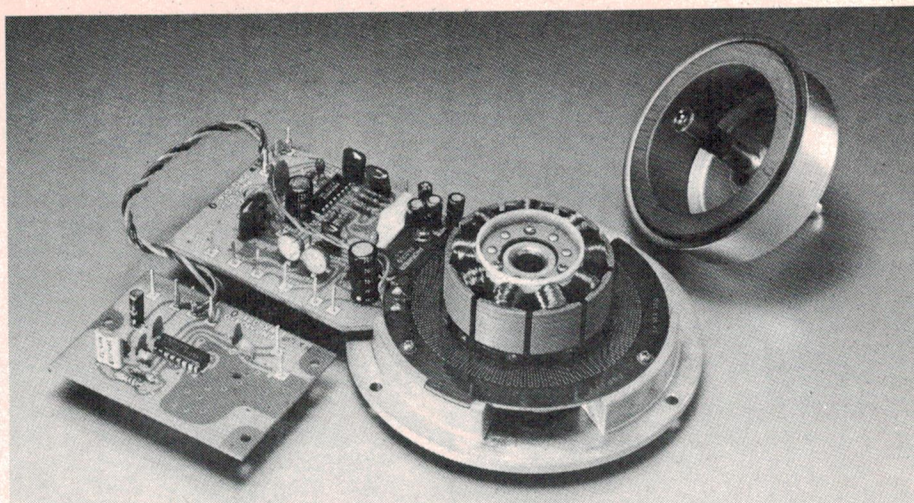

The Hall Effect dc drive motor and control electronics from Pioneer's model PL-560 turntable.


device (APLD) is carried on an arm separate from the tone arm, as shown in Figure 10, so that it does not alter the stylus force. This device utilises the difference in the reflection factor for infra-red radiation of sound modulated grooves and unmodulated grooves to detect the spaces between parts of the recorded material. When using the RP-7100, the user can push any APLD button, from one to seven, to select, for example, any song on a record. In the case of the RP-9100, the unit can be programmed to play up to 10 songs (with any specific songs repeated, if desired) in any order and to repeat the entire programme up to four times or indefinitely. A digital indicator displays the number of songs remaining.

The circuitry of the APLD sensor is shown in Figure 11. When the sensor reaches an unmodulated groove, positive-going pulses of some 20 to 40 mV in amplitude appear at the

collector of the sensor device. This is amplified to a level of 1 V to 3 V by the operational amplifier whose output is at B. The second amplifier shapes the pulses into square waves of 7 V amplitude at point C, after which they are differentiated by C221 and R264 to form sharp pulses which are used to trigger the monostable circuit of Q215 and Q216. The output pulses from this circuit are of constant amplitude and duration and are fed to the complex logic circuitry of this record player.

The remote control unit of the RP-9100 turntable is shown in Figure 12. The keys provide for the 10 song locations of the microprocessor controlled automatic programmable music selector to be entered into the turntable memory by means of infra-red radiation carrying the data from the remote control unit to the turntable itself. Speed selector buttons and other controls are also provided. — to page 130. ►

Figure 11. Basic circuitry of the Sharp Optonica APLD sensor system discussed here.

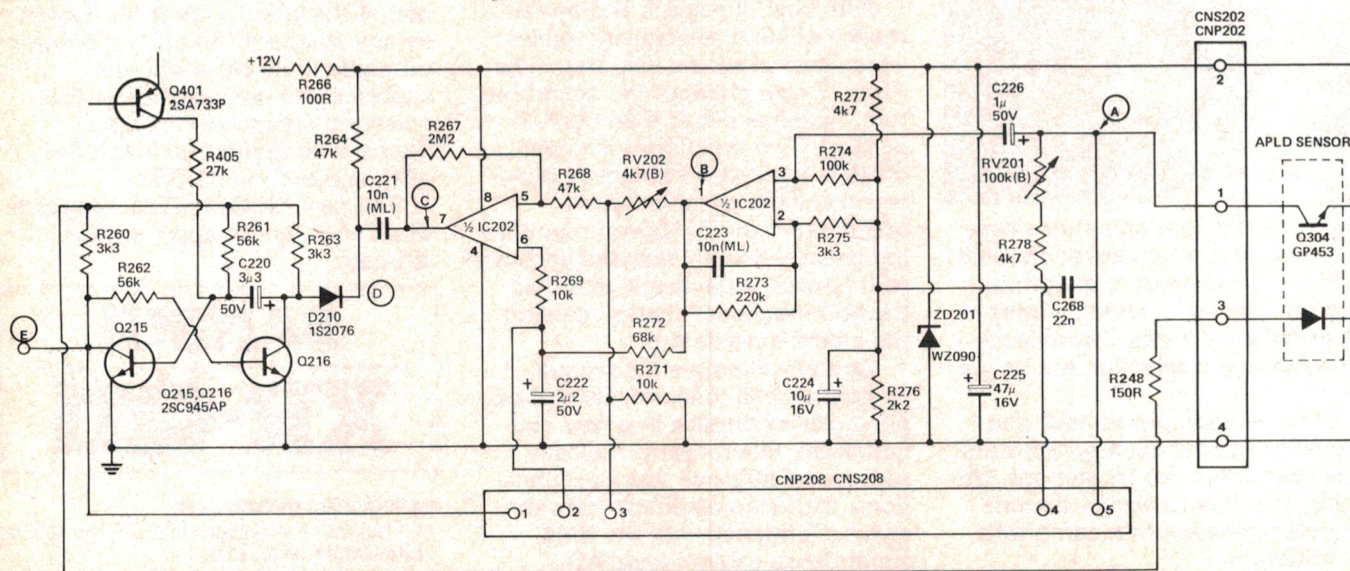




**Sansui**

Only hi-fi, everything hi-fi.



# The putative straight wire with gain.

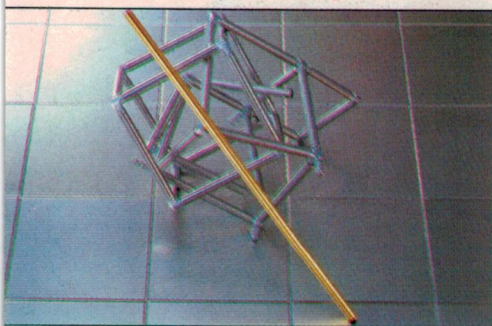

The design of all Sansui power amplifier sections mark a straight line toward that ideal of amplification: a straight wire with gain. And now, drawing on its priceless experience as a hi-fi specialist, Sansui presents its R-70 stereo receiver and A-80 integrated amplifier.

DC (direct coupling) circuitry is closest to our ideal of pure amplification. DC power amplifier stages are directly coupled and all capacitors

are eliminated. And Sansui's DC-Servo configuration prevents subsonic signals from reaching your speakers so the music you hear is purer and free from coloration.

Both power amplifier sections feature Sansui's original DC-Servo amplification. When you hear how accurately recorded music is reproduced, you may well wonder how Sansui achieved such an audible miracle.

Advanced technology includes the special microelectronic devices in the FM/AM tuner section of the R-70 and the OCL output of the A-80. Advanced features include LED peak power level displays for both units and a built-in MC pre-amplifier for the A-80.

But the real secret is that Sansui does not make a fetish of advanced technology. Instead, it is the application of that technology continuously

monitored by that sensitive instrument — the human ear — that receives the highest priority. Our dedication, in the final analysis, is to faithful reproduction of the actual musical performance.

#### **R-70 DC-Servo Receiver:**

65 RMS watts  $\times$  2. THD: 0.08%

#### **A-80 DC-Servo Integrated Amplifier:**

65 RMS watts  $\times$  2. THD: 0.05%

## SANSUI R-70/A-80

**SANSUI ELECTRIC CO., LTD.**

14-1 Izumi 2-chome, Suginami-ku, Tokyo 168, Japan

**VANFI (AUST.) PTY. LTD.**

297, City Road, South Melbourne, Victoria 3205,

Australia Tel: 690-6200

283 Alfred Street, North Sydney, N.S.W. 2060,

Australia Tel: 929-0293



## Technics turntables

Technics is an associate of the well-known Matsushita Electric Company of Japan. They produce a wide range of turntables from the SL-200 and SL-B2 semi-automatic servo types to the SL-Q2 fixed speed, quartz locked, the SL-5200 fixed speed with quartz lock or manually variable speed without quartz locking and the SL-150Mk2, the SL-1300Mk2, the SL-1400Mk2 and the SL-1500Mk2 which all offer  $\pm 9.9\%$  variation of speed with quartz locking and digital display of speed. Perhaps most remarkable is the SL10 which has tangential tracking and is extremely compact.

The SL10 has a record clamp built-in and the tracking force is applied by means of a fine spring, so this remarkable turntable can be used in any position, including on its side or even inverted! The arm runs along a pair of guide bars and is driven by a coreless electric motor. The motor is controlled by an optical system mounted in the shorter of the two arms near the tip of the stylus.

The SL10 will accept only the special moving coil cartridge with which it is supplied. The low output cartridge can be used with a step-up head amplifier which may be switched in and out of the circuit. However, this turntable is most remarkable for its portability.

## Revox turntables

The Revox Company (based in Switzerland) offer two turntables which both have the same type of tangential tracking system. The B790 has been available for over a year and incorporates a quartz controlled direct-drive system with a manual speed variation facility of  $\pm 7\%$  and digital indication of the speed to two decimal places by a four digit display. The B795 is a more economical turntable which has the same general performance, but without the speed variation facility and without the digital display. The stopping time of the platter is longer with the B795 than with the B790.

A servo-controlled motor is employed to achieve tracking together with a cord and pulley system which move a headset along horizontal parallel bars. The whole of the tracking system assembly is mounted in a rectangular shaped housing of substantial size on the right hand side of the turntable. This housing gives these turntables an unusual appearance and it can be swung forwards through  $90^\circ$  (or even through  $180^\circ$  to the right) when changing records. The shuttle carrying the cartridge moves in a straight line from the right hand edge of the record



Technics' SL-1500Mk2 turntable features direct drive, which the company pioneered, digital speed display and quartz-locked speed variation of nearly  $\pm 10\%$ .

towards the centre during the playing time. The shuttle is driven by two horizontal pulleys, one at each end of the parallel bars, and a nylon cord.


An infra-red sensor containing a diode emitter and a pair of photodiodes in a symmetrical circuit is used to detect any tracking error. Any displacement of the head from the tangential position causes a movement of the slot through which the infra-red beam passes and the photodiodes become unequally energised. This operates the control circuit and a small motor operates one of the pulleys so that the nylon cord moves

the shuttle just far enough to restore the symmetry of the circuit. The sensing circuit has an accuracy such that the lateral tracking error cannot exceed half a degree.

The shuttle has some free vertical movement to enable the cartridge to be raised and lowered. A solenoid-controlled lifting arm can hold the cartridge clear of the record or allow it to descend. The damping mechanism ensures that the stylus descends onto the record slowly and a muting circuit ensures that there is no audio output until the cartridge has been completely

— to page 132. ▶

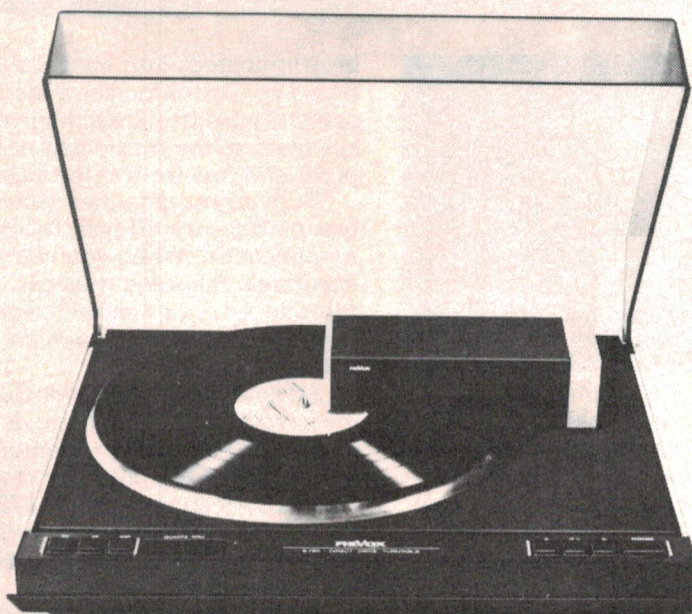The Revox B790 turntable is another tangential tracking unit, shown here with the tangential tracking assembly in the playing position.





**Sansui**

Only hi-fi, everything hi-fi.

# The significance of in-depth matching.



Nobody imagines you get smooth drinks by matching glass shapes. Or just quantities.

And it's not enough to match components that have the same design and exterior dimensions. Or merely match power levels. It's the quality of each component that counts. And the matching, the integration of subtle priorities that characterize a truly superior music system.

That's in-depth matching. That's SUPER COMPO. In-depth matching means, for example, exceptionally accurate dynamic response characteristics throughout the entire system.

Specifics of the SUPER COMPO system depicted include DC-Servo amplification and digitally quartz-locked tuning. Both developments by Sansui, the hi-fi specialist, maintain the purity of delicate nuances from the original source to your loudspeakers. The unique D-O-B tonearm assures resonant-free flawless tracking. And bright LED displays in both amplifier and tuner provide precise visual indications of how superbly your SUPER COMPO units are performing.

A wide variety of SUPER COMPO system are available to meet your budget and sonic demands.

Whichever system you select, in-depth matching is the exclusive Sansui stereo design concept that is built-in for superior sound.

#### **SUPERCOMPO 600**

- Computerized Full-Auto DD Turntable • Digitally Quartz-Locked Tuner • Integrated DC-Servo Amplifier (65 RMS watts x 2) • Stereo Cassette Deck
- Optional Sound Console and Audio Program Timer • Custom made Audio Cabinet • Matching Speaker System

## **SANSUI**

THE AUDIBLE EDGE

## **SUPERCOMPO**

**SANSUI ELECTRIC CO., LTD.**

14-1 Izumi 2-chome, Suginami-ku, Tokyo 168, Japan

**VANFI (AUST.) PTY. LTD.**

297, City Road, South Melbourne, Victoria 3205,

Australia Tel: 690-6200

283 Alfred Street, North Sydney, N.S.W. 2060,

Australia Tel: 929-0293



— from p. 130.

lowered onto the record. The amount of movement is limited so that it is impossible for the stylus to touch the rubber mat on the platter if there is no record on the turntable.

Three touch switches on the left hand side of the B790 set the speed to  $33\frac{1}{3}$  or 45 rpm or to the variable speed which is controlled by a small thumbwheel. Two of the buttons on the right hand side control the rapid movement of the shuttle inwards or outwards whilst the pick up is raised. When the third button on the right hand side is touched the cartridge will descend, whilst pressing this button again will raise the cartridge.

When a 300 mm diameter record is to be played, the cartridge will automatically position itself at the start of the record, but the position of the cartridge must be adjusted manually for playing records of a smaller diameter. The shuttle control buttons will move the stylus by about one groove when touched momentarily, but when a button is held down, the stylus takes some seconds to move from one end of the track to the other. At the end of a record, the widely spaced groove near the centre moves the stylus so that the optical system produces a signal which causes the stylus to be lifted off the record and the shuttle is returned to its rest position.

A particular advantage of these turntables is that it is almost impossible to damage the stylus, even if over-enthusiastic children operate the equipment. Any slight movement of the carriage immediately causes the stylus to be lifted off the record; for example, if the carriage is swung out whilst a record is playing, the mechanism will lift the stylus extremely rapidly.

Wow and flutter of both Revox decks are quoted as being better than 0.05% weighted. Speed accuracy is  $\pm 0.01\%$  — more than adequate, although lower than that quoted for many quartz controlled decks. The length of the tone arm is only 15 mm and this minimises any problems with resonances.

## Pioneer

The Pioneer Company of Japan's PL-L1000 turntable (reviewed Feb. '80 ETI) features tangential tracking using an ingenious linear motor to drive the arm. Two speeds are provided by a dc motor stabilised with a quartz oscillator, but no fine speed adjustment is possible. A small red lamp glows when the speed has become locked to the quartz frequency standard.

Perhaps the most unusual feature of the PL-L1000 is the use of a linear motor to drive the tone-arm. Although the principle of the linear motor is not

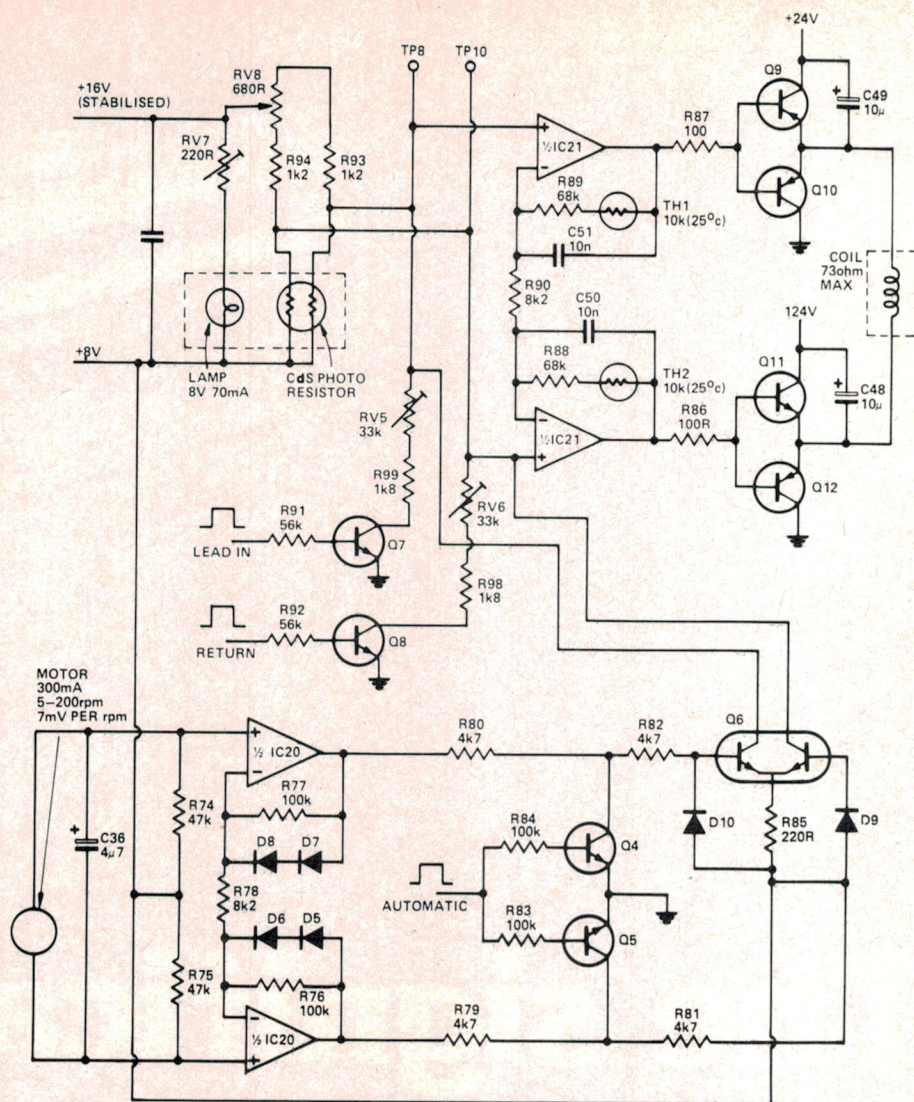


Figure 13. The Pioneer PL-L1000 turntable has a tangential tracking tone arm employing an optical tracking system. This is the optical sensor circuitry.

new, this is probably the first time a linear motor has been used in the hi-fi field. The uses of linear motors are few, although there is interest in their possible use for high speed rail transport; in the Pioneer deck the stylus must be transported along a rail. The coil of the motor is linear and magnets placed on either side of this coil move in a straight line under the influence of the magnetic fields.

The PL-L1000 employs an optical tracking sensor for its tangential tracking system which is sensitive to 0.2 degrees of deflection. See Figure 13. When the stylus is positioned exactly at right angles to the carrier, the beam from a miniature lamp illuminates both sections of a twin photoresistor which, together with R93, R94 and RV8, forms a Wheatstone bridge, RV8 being adjusted so that there is no potential difference between TP8 and TP10 when the stylus is accurately located at right angles to the stylus carrier.

If the stylus happens to move either to the right or to the left, the amount of light striking each section of the photoresistive cell will change so that the bridge becomes unbalanced and a potential difference appears between TP8 and TP10. This potential is amplified by the differential amplifier stage comprising the two parts of IC21 which drive the twin complementary output stages Q9 to Q12 inclusive. These output stages form a push-pull bridge circuit which can drive a current of up to 300 mA in either direction through the 73 ohm motor coil. The tracking motor moves to return the bridge back to the balanced state, whereupon the potential at TP8 becomes equal to that at TP10.

When a record is about to be played, a current is fed to the base of Q7; the collector of this transistor therefore takes a current through R99, RV5 and R93 and the potential drop across R93 causes the stylus carrier to move to the



left so that the stylus is above the record. The speed of movement is controlled by the setting of RV5. Similarly, after a record has been played, Q8 is made to conduct so that the potential difference between TP8 and TP10 causes the stylus carrier to return to its rest position on the right hand side at a rate determined by the setting of RV6.

During the automatic modes (lead-in, return or repeat), Q4 and Q5 are turned on and the resulting currents flowing through D9 and D10 turn Q6 off so that the groove locating function is inhibited. During manual operation, the differential amplifier IC20 is activated and this causes one side of Q6 to be turned on, the side being determined by the rotation direction of the dial. A voltage drop therefore occurs across R93 or R94 which, after amplification, causes a current to be passed through the coil to move the stylus carrier. This linear motor system has the advantages of being gearless and without mechanical linkages, the tone arm running on rails along the rear of the deck. The equipment will operate only if the turntable is accurately levelled and a spirit level is provided for this purpose; any tilting will probably result in the stylus carrier moving along its rails. The tone arm is 190 mm



The Pioneer PL-L1000 features a tangential tracking tone arm driven by a unique linear motor system. It employs an optical tracking sensor to maintain the arm position to within 0.2° of deflection.

long and (unlike most conventional decks) the equipment can accurately track records which are off-centred.

Pioneer's hanging rotor system (already mentioned) is employed. Wow and flutter figures of 0.025% and 0.013% WRMS (depending on the measurement technique) are quoted. Speed drift is less than 0.8 parts per million per hour and less than 0.3 parts

per million per centigrade degree at 33⅓ rpm.

### Conclusion

Modern electronic circuitry has enabled record decks to be made which offer a standard of performance and a level of automation which would have been out of the question just a few short years ago.

# The smart counters

## High resolution and easy operation for a low price

These new counters get it all together. The one-chip microcomputer design gives you high resolution and accuracy plus easy operation and compact construction... all for a low price.

The high resolution comes from the use of reciprocal frequency counting, which gives an intrinsically higher resolution without the traditional  $\pm 1$  cycle error. For example, a full 7-digit resolution is obtained in only one second. It therefore avoids the need for long gate times, period measurements or the limitations of phase-locked frequency multipliers.

Other big benefits that the micro-computer design brings are easy operation and minimal controls, since the built-in intelligence gives automatic triggering and range switching

Dimensions  
160 x 77 x 180 mm

PM 6667: 120 MHz



- ☐ Microcomputer control
- ☐ Self-diagnostic routine
- ☐ Reciprocal frequency counting

PM 6668: 1 GHz

- ☐ High-stability TCXO:  $10^{-7}$ /month
- ☐ Auto-triggering on all waveforms
- ☐ High-contrast liquid crystal display



Test & Measuring  
Instruments

# PHILIPS

For more details contact:  
**Philips Electronic Systems - Scientific & Industrial Equipment**  
P.O. Box 119, North Ryde,  
NSW 2113 or phone Sydney 888 8222  
Melbourne 699 0300 Adelaide 223 4022  
Perth 277 4199 Brisbane 44 0191  
Wellington NZ 859 859

AHEARN S110



# WHO SAID 'MEN

A woman with blonde hair is lying on a white wooden beach chair with pink cushions. She is wearing a white t-shirt and blue jeans. She is smiling and looking towards the camera, with her right hand behind her head. A magazine titled 'DREAM' is resting on her lap. The background is a blurred view of the ocean.

ST205L



# SMOKE DRUM'?

The natural  
satisfaction of  
full flavoured,  
imported Drum.

It's the most  
enjoyed ready—  
rubbed cigarette  
tobacco in  
Australia.








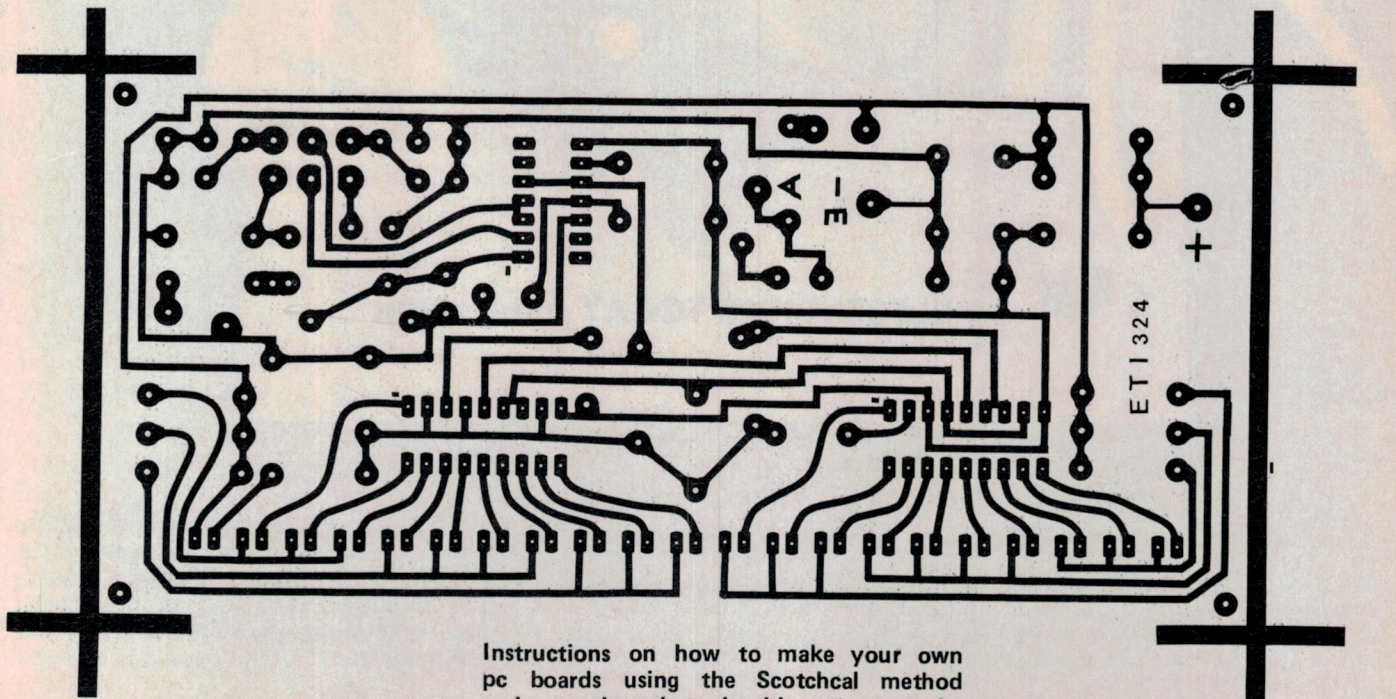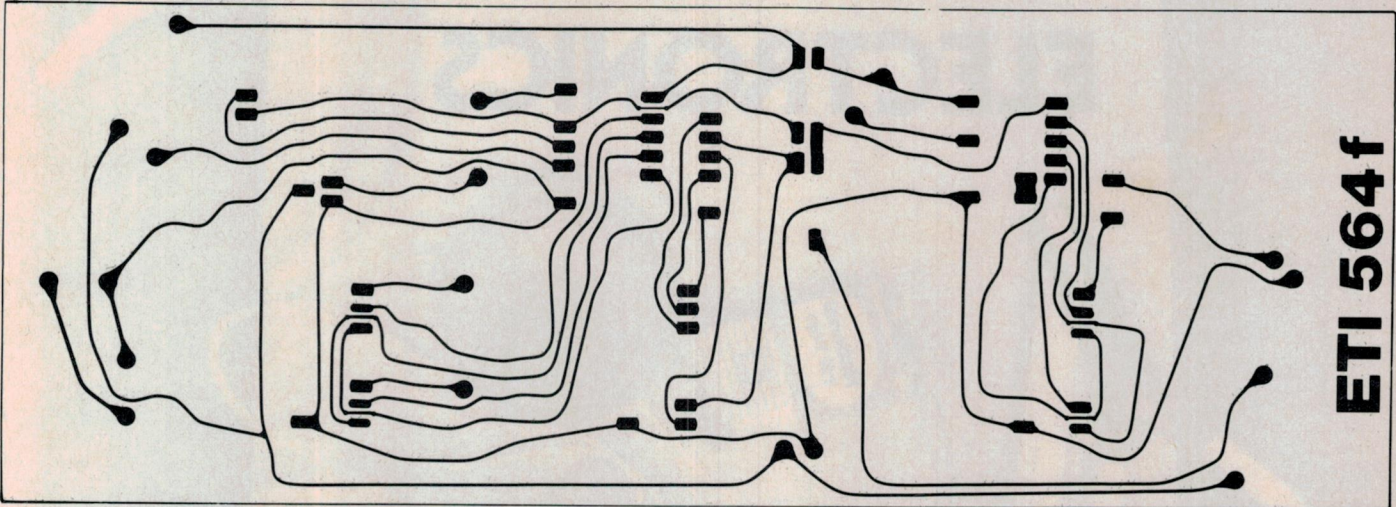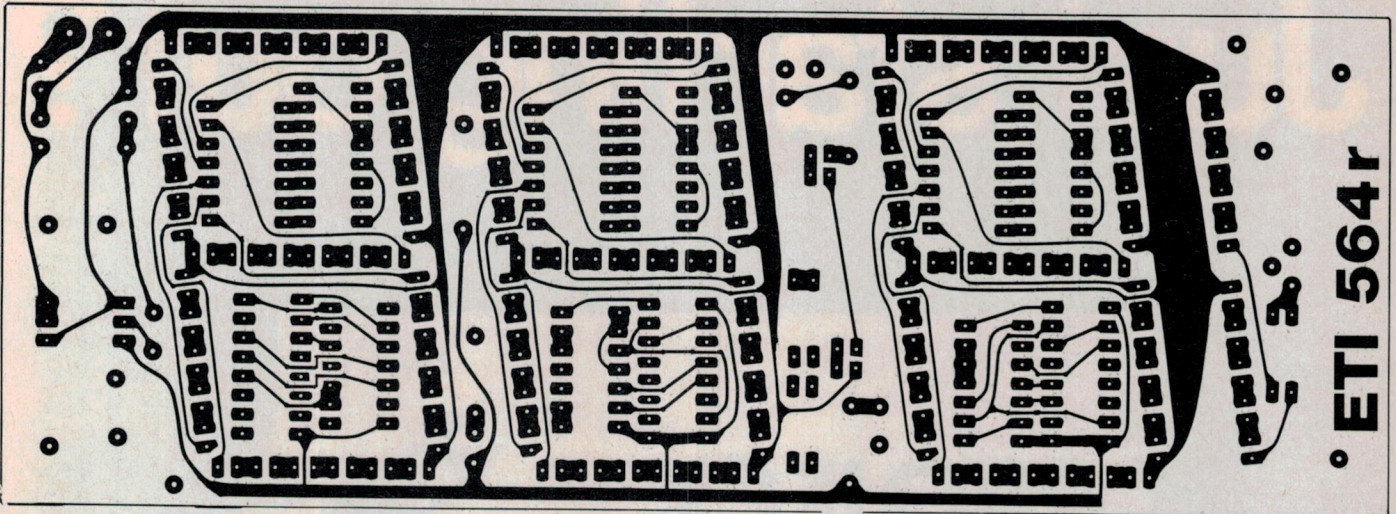**Sydney 439 3288 Melbourne 90 7444**

**N.S.W.** Sydney Dick Smith Stores 888 3200; George Brown & Co 519 5855; Radio Dispatch Service 211 0191. **Newcastle** D.G.E. Systems 69 1625; Elektron 2000 26 2644. **Wollongong** Hundell Engineering 74 0278; Macelec 29 1455; **A.C.T.** Canberra Electronic Components 80 4654.  
**QLD** Brisbane Audiotronics 44 7566; L.E. Boughen 36 1277; N.S. Electronics 36 5061. **VIC** Melbourne Browntronic 419 3986; Douglas Radio 211 1698; J.H. Magrath 663 3731; Radio Parts 329 7888; Tech Rentals 267 5877; G.B. Telepares 328 4301. **Geelong** Teleparts 21 7288. **S.A.** Adelaide K.D. Fisher & Co 269 2544; Gerard & Goodman 223 2222; Trio Electric 51 6718. **W.A.** Perth Hinc Engineering 381 4477; W.J. Montcrieff 325 5722; Rablec Engineering 381 2866. **TAS** Hobart Imbros Surpeth Systems 23 892. **Launceston** W & G Genders 31 2511.






Instructions on how to make your own pc boards using the Scotchcal method and exposing through this page may be found on page 113 of the March '80 issue.



# Just starting out?

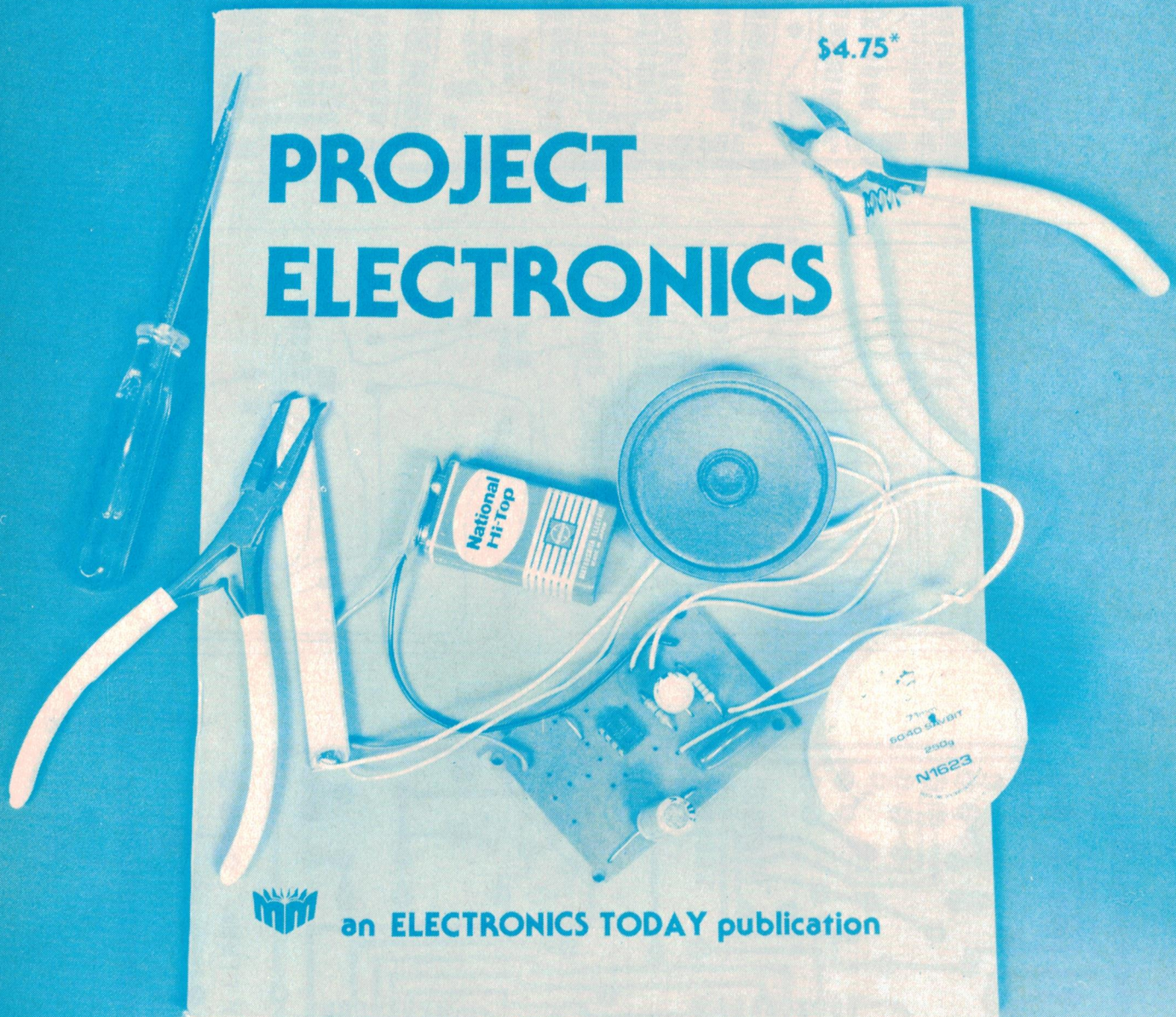

THIS BOOK has been specially designed and produced to meet the needs of newcomers to electronics. Students following the three-segment Industrial Arts syllabus at high school or embarking on the Electronics & Communications or a similar certificate course, will find the projects in this book an eminently practical introduction to the 'works' in electronics. Project Electronics has been a runaway success since it was first published. There are 26 projects included, many are readily available as inexpensive kits, and the book also provides advice on tools, identifying components, troubleshooting, how to solder etc. Available from specialist electronic suppliers or direct from the **ETI Subscription Department, 3rd Floor, 15 Boundary St, Rushcutters Bay NSW 2011** for \$4.75 plus 45 cents post and packing.



Ross and Sandra were feeling down. They wanted a good sound system but thought they couldn't afford one.




until they visited their nearest **DICK SMITH STORE**



& saw the fabulous **PLAYMASTER SPEAKERS**

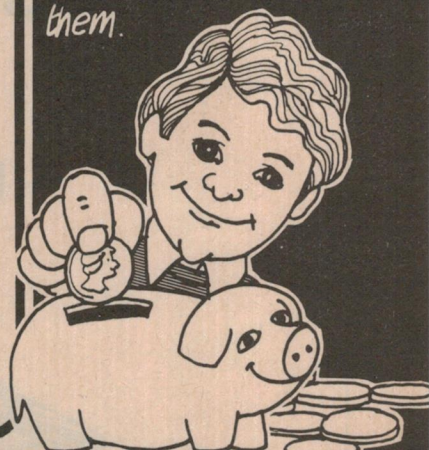Ross worked out how much they would save and decided Playmasters were for them.



next saturday morning they collected their **PLAYMASTERS**




assembly was a cinch.



Saturday evening, Sally & George called

Look at those speakers!

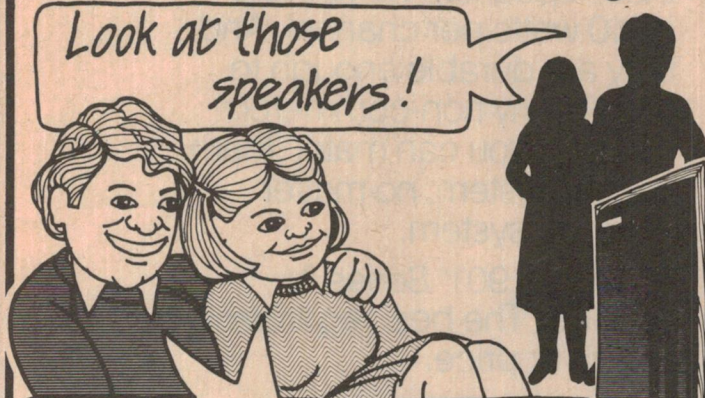

YES, we built them ourselves (with a little help from DICK SMITH)

**PLAYMASTERS ARE RIGHT FOR YOU!**

**8" SYSTEM**

26 litre infinite baffle system with 8 ohms impedance and 40 watts max. power handling.

**SAVE \$101\* \$159.50** pair

**10" SYSTEM**

53 litre infinite baffle system with 8 ohms impedance and 60 watts max. power handling.

**SAVE \$101\* \$248.00** pair

**12" SYSTEM**

75 litre infinite baffle system with 8 ohms impedance and 80 watts max. power handling. Also has mid-range and tweeter control networks.

**\$298.00** pair

\*Saving based on the same speakers in made up form (also available from Dick Smith).

**DICK SMITH ELECTRONICS**

SEE OUR OTHER ADVERTS IN THIS MAGAZINE FOR OUR STORE ADDRESSES AND RESELLERS



# The instant upgrade.


The new Bose® 901® IV  
Direct/Reflecting® speakers  
help your stereo sound better.



If you are thinking of upgrading your music system, Bose has the fastest way to do it.

The new Bose 901® Series IV speaker.

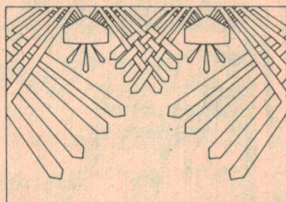Since the speaker has more to do with the sound you hear than any other part of your music system, you



can improve the quality of your sound by improving your speakers.

The new Bose 901® IV speakers

are the answer. You can drive these speakers with as little as 10 watts per channel. And they are durable enough to handle any non-commercial amp. So you can match them to your system, no matter what the system.

The Bose 901® Series IV speaker. The best regardless of size or price.

## **BOSE®**


BOSE AUSTRALIA INC., 11 MURIEL AVENUE, RYDALMERE, NSW. Tel: 684-1022, 684-1255.

**DEALERS AND DISTRIBUTORS:**

**HI FI HOUSE** Wollongong NSW, **D.M.E. HI FI** Sydney NSW, **APOLLO HI FI** Marrickville NSW, **HI FI COUNTRY** Engadine NSW, **NITRONICS** Coffs Harbour NSW, **BROWN AND JOLLIE** Lismore NSW, **HABERECHTS RADIO** Albury NSW, **DURATONE HI FI** Phillip ACT, **STEREO SUPPLIES** Brisbane QLD, **DENMAN AUDIO** St. Kilda VIC, **BELMONT STEREO SYSTEMS** Geelong VIC, **NORTHERN ELECTRONICS** Coburg VIC, **SOUND FACTORS** Dandenong VIC, **PROUDS AUDIO** Bendigo VIC, **TEAK HOUSE** Hobart TAS, **AUDIO WHOLESALERS** Burnie TAS, **BLACKWOOD SOUND** Blackwood SA, **THE AUDIO CENTRE** West Perth WA.

111689-9/78-11



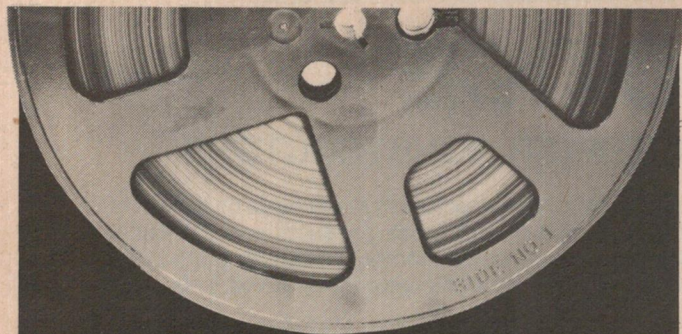

# Top AMPEX REEL to REEL TAPE $\frac{1}{3}$ normal price!

THE USA AMPEX CORPORATION has made available a substantial quantity of 'off-cut' tapes from their highest grade material. All tapes are 1800 ft (549 m) by  $\frac{1}{4}$ ", 1 mil ferric oxide on standard 7" reels.

There's a slight gamble involved — but one in which you either win a lot — or a hell of a lot!

Here's why:

The tapes offered are of differing types and you take pot luck on which you receive.

BUT, The lowest quality is Ampex' superb Ampex Plus series! The highest is Ampex' Grand Master series!

SO. If you draw the Ampex Plus you'll be paying about one-third the usual price. If you score the Grand Masters you'll be paying about a quarter usual price.

YOU CANNOT LOSE. If you are not totally and completely satisfied with your purchase, Dindy guarantee to return the full purchase price without question provided the tapes are returned within 14 days in the original packing.

Identical tapes to those offered are marketed in the USA by Ampex, using the trade name 'Shamrock'. This trade name is also used for those offered here.

*NOTE: This offer is made by Dindy Marketing (Aust.) Pty Ltd and this publication is acting as a clearing house only. Cheques should be made payable to 'Ampex Tape Offer', ETI Magazine, 15 Boundary Street, Rushcutters Bay NSW 2011. We will then process your order and pass it on to Dindy, who will send you the goods. Please allow up to four weeks for delivery.*

*Owing to the exceptionally low offer price the minimum ordering quantity is ten tapes (total \$39).*

## \$39 for 10 reels

AMPEX TAPE OFFER

Please supply .....tapes at \$39 for ten \$ .....

Plus post and packing, any quantity:— \$2.50

TOTAL \$ .....

Name .....

Address .....

.....

.....Post Code .....


# B&W 801

TO CREATE OUR  
SERIES 801  
WE BROKE THE RULES

With the B & W 801, the design brief was brief. In fact, the required performance was summarised in just four telling words; full professional monitor requirements.

To qualify as a monitor by B & W standards, a system must have linear free-field amplitude response from 30Hz to 20kHz, with minimal deviation horizontally and vertically. It must be free from distortion and colouration and have an audio-powered overload circuit to protect against accidental damage or overload.

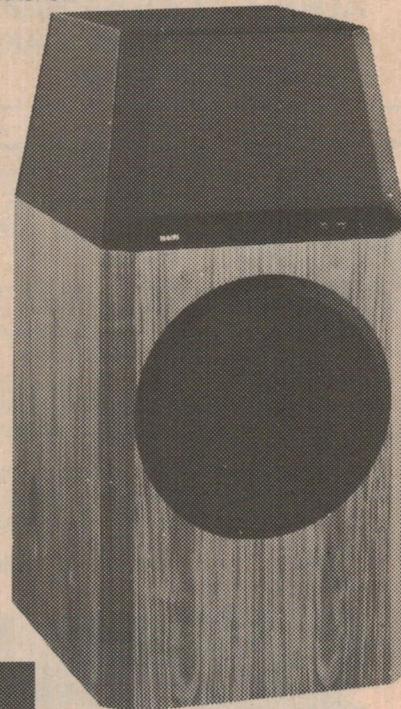This is the Series 80 concept in a nutshell.



**B&W**

**LOUDSPEAKERS**

For further information see your B & W dealer or contact  
Convoy International Pty Ltd  
4 Dowling Street  
Woolloomooloo NSW 2011  
Telephone (02) 3582088



# IMPORTANT NOTICE

## TO AUDIO ENTHUSIASTS AND LOUDSPEAKER CONSTRUCTORS

Since 1929 Audax Loudspeaker Drivers have been available to specialist constructors in many parts of the world. Today many of the best and most respected names in the Audio industry use Audax products and the Audax research department maintains contact with and aids both specialist constructors and organizations such as the B.B.C. The Audax High-Fidelity Loudspeaker Range is one of the best and most extensive in the world. This range is now available in Australia in the following ways.

1. Loudspeaker Systems. Either fully built by Audax or in well designed, easy to construct kit form. Laboratory designed to show off some of the better known Audax components these systems are available from selected specialist Hi Fi retailers.
2. For the specialist constructor (manufacturer) the superb Audax driver range is now available together with help and advice when required from our Australian and French offices. A cabinet factory has recently been established in Huntingdale Victoria. This factory will be able to construct speaker cabinets to top European standards. Manufacturers interested in this facility are invited to phone or write for more information.
3. For the Kit builder. Recently a number of designs have appeared in Wireless World, Practical Hi Fi and other magazines using one or more Audax drivers. We can supply parts (including crossover networks, felt panels etc in many cases) for these designs.

Please phone or write to Audax Loudspeaker for more information on any of the above services. For those people interested in listening to one of the excellent Audax Loudspeaker Systems call us for the name and address of your nearest dealer.

### AUDAX LOUDSPEAKERS

32 WILSON STREET, OAKLEIGH, VIC. 3166  
PHONE (03) 543-5266

# AUDAX

## LOUDSPEAKERS

**NEW  
SUPER  
RX**

### Introducing the NEW NO COMPROMISE JRC MODEL NRD-515 communications receiver.

This versatile high quality receiver covers 100KHz to 30MHz using a PLL and photo type rotary encoder to determine frequency setting.

With its continuous coverage and an optional 24 channel memory unit this receiver should meet the needs of professional and commercial services as well as sophisticated SWL, hams and others seeking excellence and quality.

This well made double super het has effective passband tuning, electronic switching and all solid state chassis. It features completely modular construction with all components mounted on plug in circuit boards for ease of servicing.

For further information write, phone or call in. Colour brochure and specifications available.



We also stock Australia's largest selection of scanning receivers! You can listen to aircraft, marine, police and other transmissions.

BEARCAT 210.  
BEARCAT 220FB.  
BEARCAT 250FB.  
BEARCAT POCKET  
SCANNERS.  
SX-100 etc.

Write for prices & specs.



### WRITE FOR OUR 36-PAGE FREE CATALOGUE CONTAINING:

Send 50c stamp

- RECEIVERS
- TRANSCEIVERS
- LINEAR AMPLIFIERS
- RTTY EQUIPMENT
- SSTV EQUIPMENT
- TV CAMERAS & MONITORS
- COMPUTERS
- ANTENNAS
- ROTATORS
- ACCESSORIES

### KENWOOD R-1000

Communications receiver of the year. Digital and analog dial, digital clock, automatic timer, three selectivity positions and many other features.



WRITE FOR  
SPECIFICATIONS



# emtronics

CITY & SHOWROOM: 649 George St, Sydney, NSW. (02) 211-0531.  
POSTAL: PO Box K21, Haymarket, NSW 2000. Cable: Emtron Sydney.



# SOUND PROFESSIONALS

## DP-1200

# DENON

- \* Direct Drive system \* Smooth AC Servo motor
- \* Record-end detection employs non-contact system — tonearm velocity is optically detected when it moves from sound groove to lead-out groove
  - \* Anti-vibration construction of lower portion of tonearm and turntable feet
- \* Magnetic Pulse Signal speed control system
- \* Oil-damped, automatic arm lifter
- \* Adjustable tonearm height
- \* Cueing and Stand-by switch
- \* Wow and flutter of 0.018% Wrms (as measured by Denon with magnetic pulse wheel)



### SPECIFICATIONS

#### Phono motor

Drive system ..... Direct drive by AC servo motor  
 Speed control ..... Frequency detection servo system  
 Speed ..... 33 1/3 rpm, 45 rpm  
 Speed adjustable range ..... over  $\pm 3\%$   
 S/N ratio ..... over 75 dB (DIN-B)  
 Starting time ..... less than 1.5 sec (33 1/3 rpm)  
 Turntable ..... Aluminum alloy diecast, 30 cm diam.

#### Tonearm

Type ..... Static balance type  
 (automatic arm lifter)

### Model DP-1200

Effective length ..... 244 mm  
 Overhang ..... 14 mm  
 Tracking error ..... less than  $2.5^\circ$   
 Stylus pressure adjustable range ..... 0 — 2.5 g  
 Acceptable weight of cartridge ..... 5 g — 11 g  
 Height adjustment range ..... 39 — 43 mm  
 Cueing ..... oil damped system

#### General

Power consumption ..... 17W  
 Dimensions ..... 485(W) x 163(H) x 396(D) mm  
 Weight ..... Aprox. 11 kg

# DENON

PROFESSIONAL AUDIO BRAND

For the location of your nearest Denon dealer, please contact

Canberra 80-5200	Melbourne 560 4533	Launceston 44 5155	Hobart 72 4366
Adelaide 272 2366	Perth 271 0888	Townsville 79 6155	Brisbane 44 1631

Hi-Fi Audio Equipment

**AMALGAMATED WIRELESS (AUSTRALASIA) LIMITED**  
 554 Parramatta Road, Ashfield, NSW 2131 Phone 797 5757





## Rotel RX1000 AM/FM receiver

"... a cleverly designed receiver. Whilst one might think from its price that performance would have suffered because of the innovatory design, this is not the case."

WHILST MANY of the receivers that we have reviewed in recent years have been bordering on the esoteric it is nice to be presented with a receiver where the features and construction tend to be at the other end of the spectrum. The Rotel RX1000 is a small and particularly neat receiver. The obvious underlying aim of the designers has been to achieve a unit offering the major features with a classical simplicity which is matched by the functional utility of the design. The nicest feature of the RX1000 is the front escutcheon. This features a painted, dark grey panel with white, silk screened lettering and neatly functional controls. As well as the name on the top line of lettering, the ubiquitous letters PLL and MPX, standing for phase locked loop and multiplex, stand out clearly.

### Description



The slide rule dial neatly shows station frequencies to a 1 MHz resolution on the FM band, and a lesser definition on the AM section. It also contains three other indicators in the form of a five level signal strength meter utilising bar-shaped light emitting diodes, a three-segment tuning "meter" with a red bar

either side of a central green bar to indicate correct station tuning and a single red bar to indicate that stereo FM has been selected. To the right of the slide rule dial is a modestly sized tuning knob.

The bottom row of controls feature, from left to right, a power switch, a standard tip-ring-and-sleeve headphone socket, two push buttons for selecting speaker system A and/or B. Next to these are three neatly shaped controls, two of which are for bass and treble. These each provide  $\pm 10$  dB of boost and cut at 50 Hz and 15 kHz respectively. The balance control which has a matching format provides better than  $\pm 10$  dB offset. These three controls each feature a neat taper waisted end which is both attractive and very functional. The volume control, which is centrally located and slightly larger than the bass, treble and balance controls, also features mechanical indents coupled to a normal pair of coaxial attenuator pots. To the right of the volume control there are four push buttons for loudness, on/off, a subsonic filter on/off, a stereo mono mode switch and FM muting on/off switch. The function switch provides for selection of AM,

FM, phono and auxiliary inputs whilst the final two switches on the front panel under the tuning control are for selection of tape recorders 1 and 2 which, when both switched, provide a facility for dubbing from tape recorder 1 through to tape recorder 2.

The rear of the receiver is functional but obviously not as attractive as the front! The first feature which catches one's eye is the ferrite loopstick antenna for AM reception. This consists of a space age type moulding featuring a ball socket connection on the back of the receiver. This allows for a wide range of adjustments without that unfinished look with dangling wires which have been a feature of most other similar loopstick antennas in the past. As well as a ground socket and a single pair of phono inputs for moving magnetic cartridge and auxiliary inputs, the tape connections have been simplified so that tape recorder 1 has normal coaxial input and output sockets whilst tape recorder 2 utilises a single DIN socket. The antenna connections are made by means of knurled terminals on an insulated escutcheon whilst the speaker connections are by neat but effective spring-loaded terminals into which one

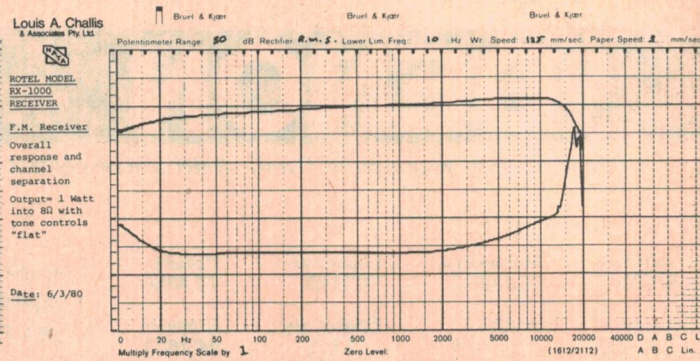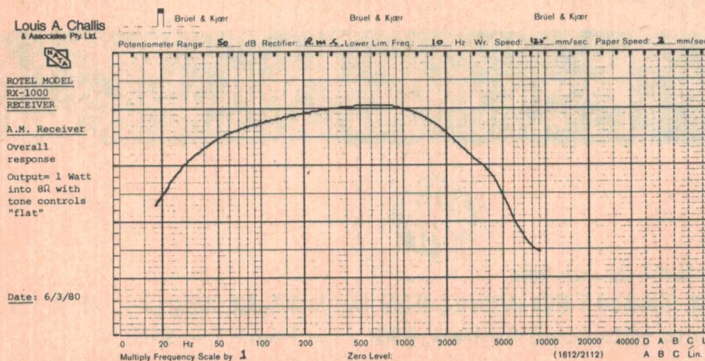





inserts the bared wire ends. The normal American style switched and unswitched power sockets which have been built into the unit have been carefully covered with aluminium plates. Unlike many competitive units available at the moment, the chassis features an all galvanised steel construction which is solidly made. This is matched by the slotted perforated steel top cover which features a practical plastic finished grey exterior. The inside of the unit is in some respects more interesting than the outside. Rotel have used what can only be described as an "avant garde" approach to simplify the constructional techniques and keep costs down. The first feature which caught our eye was the use of a single, centrally located heatsink with both the main power amplification stages incorporated in one large scale integrated circuit clamped on to it. The associated printed circuit card merely contains the power supply, mains fuses, rectifier and a voltage regulator. This is neat, and as our measurements showed, subsequently

quite effective. As a result of this simplification it has become possible to place the phono preamplifier stage right at the input terminals. This reduces hum pick up and a number of other possible problems. The largest printed circuit on the board, one of six, is the FM/AM tuner card. This has no RF stage for the AM but does have an RF stage for the FM. Whilst the phono preamplifier uses integrated circuit modules the tuner uses transistors plus two, dual integrated circuits both of which are in the FM, IF section.

The other three printed circuits are connected to the front panel. One is used for the speaker switching and head-phone amplifier; the second is a small satellite board to feed the light emitting diodes of the signal strength meter, tuning meter and FM stereo indication, whilst the third provides the circuitry for the bass, treble and volume control as well as interconnections for loudness, sub-sonic filter and mode switching. The internal wiring is conventional and the unit is designed for easy assembly



and repair should this prove necessary.

## On test

The objective testing of the unit showed it to offer excellent performance in most of the key regions. The frequency response extends from 4.5 Hz to 57 kHz  $\pm 3$  dB and the effect of the large scale integrated circuit power amplifier stage tends to show up in terms of a slight but inconsequential droop in the low frequency response of the amplifier. Harmonic distortion figures are slightly higher than claimed in the specification but are still quite acceptable with a maximum of 0.11% at 35 W output into 8 ohms.

The distortion figures at the lower power levels are somewhat better with a maximum of only 0.042%. The transient intermodulation distortion is very slightly higher than other top line amplifiers and receivers but at 0.19% is still very acceptable. By keeping the phono and auxiliary input preamplifiers at the input terminals the hum and noise levels in terms of both the un-

— to page 149. ▶

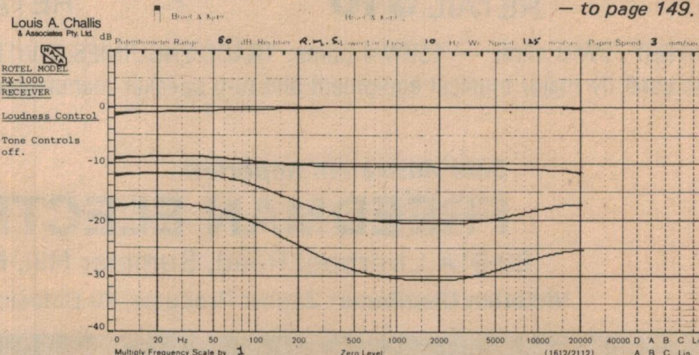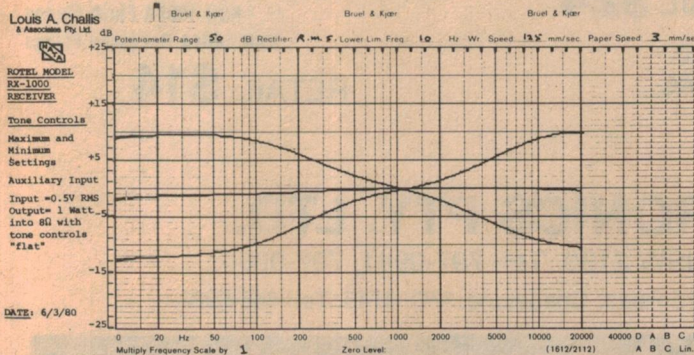



# SEVLEN

MANUFACTURERS OF LIGHTING CONTROL SYSTEMS  
Office: 4 Weldon St., Burwood. 2134 N.S.W.  
Tel. (02) 74 8905

# LIGHTING PTY. LTD.

**HERE NOW! Saturn 4 Chasers & Snakelights....**

The most portable, economical and adaptable low priced lighting system ever invented, a must for clubs, displays, windows and dance venues.


Connected to the "STARCHASER" controller, an amazing sequence is produced all within a tube.

Up to 300 metres of scintillating, pulsating chase.

No complicated connections, bend it, shape it, take it anywhere, anytime. (Each snakelight is 10 metres long). 12 different colours available.

**The price will amaze you.  
Find out more - now!**

DISTRIBUTOR AND TRADE ENQUIRIES WELCOME

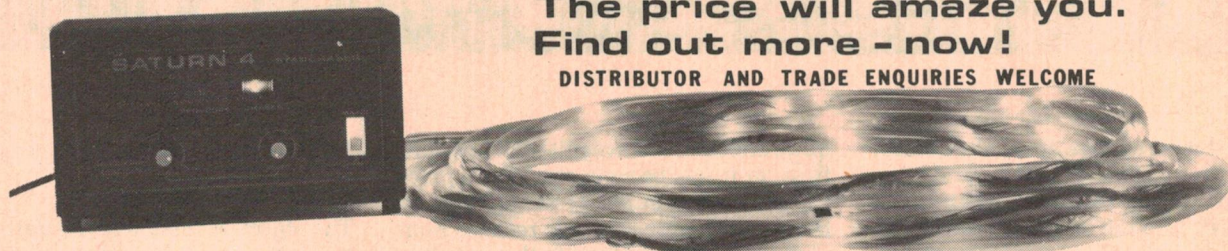

**DIRECT FROM U.S.A.**




## MOTOROLA PIEZO HORNS

RESPONSE 2K — 30K

RESPONSE 4K — 30K

RESPONSE 3.5K — 30K

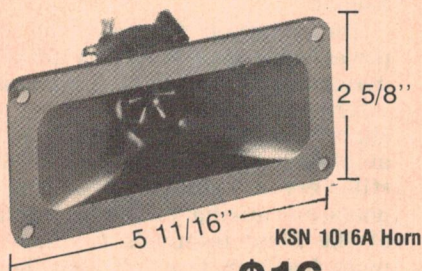


KSN 1016A Horn

RETAIL **\$16**



KSN 1025A Horn

RETAIL **\$24**

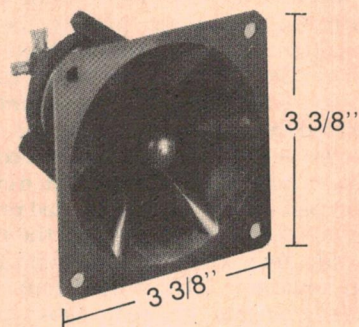

KSN 1005A Flush Flange

KSN 1001A Recessed Flange

RETAIL **\$14**

RATED 75W/8 ohms — 150W/4 ohms. TRADE ENQUIRIES INVITED.  
As used by major musical equipment and hi-fi speaker manufacturers.

*Sole Australian Importer:*

**FREEDMAN ELECTRONICS PTY. LTD.**


89-91A Liverpool Road, Summer Hill, NSW 2130. Tel: 797-9941, 797-0986.

Victorian Distributor: Zephyr Products, 70 Batesford Road, Chadstone, VIC. 3148. Tel: 568-2922.



# PROFESSIONAL AUDIO EQUIPMENT
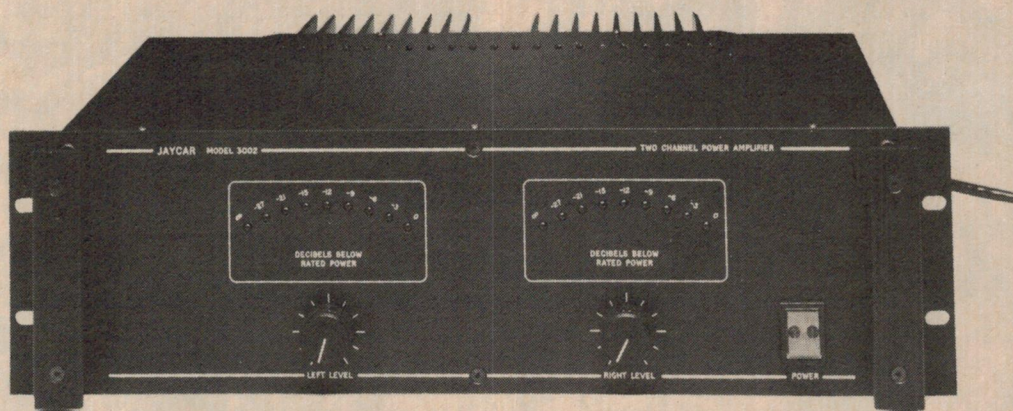
## MODEL 3002 — 2 CHANNEL POWER AMPLIFIER




### FEATURES

- 300 Watts per channel.
- Massive rear mounted heatsinks.
- Multiple speaker protection circuits.
- Peak output power meters.
- Constructed to withstand the tortures of 'On the road' use.
- Standard 19" rack mounting.
- Separate power supplies for each channel.
- Dual RCA input sockets to allow bridging to other amplifiers.
- Equally suited to Hi Fi use or P.A./Disco situations.
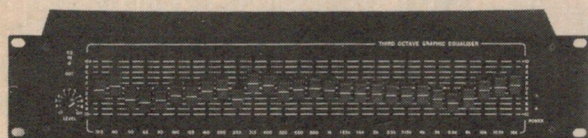
### BRIEF SPECIFICATIONS


Output Power — 300 watts/channel into 8 ohms.  
200 watts/channel into 4 ohms.  
Frequency Response — 20Hz to 20kHz  $\pm 0.5$ dB.  
Hum and Noise — 105dB below rated output.  
Harmonic Distortion — Less than 0.05% to 80 watts.  
Less than 0.15% at rated power.  
Input Sensitivity — 1.0 volts for rated output.  
Dimensions — 482mm x 133mm x 340mm.  
Weight — 20 kgs.


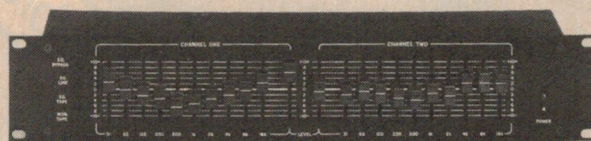
## MODEL 2801 — 1/3 OCTAVE EQUALISER

The 2801 is a single channel graphic equaliser that divides the audio spectrum into twenty-eight one third octave bands. Each frequency segment is controlled by a slider that provides up to  $\pm 10$  dB of adjustment in standard ISO steps.

The 2801 was designed primarily to compensate for any deficiencies in the linearity of speaker systems, acoustic peculiarities of the hall or listening room, and inadequacies of program source quality. In P.A. application the equaliser may be used to improve sound quality and increase intelligibility by attenuating problem frequencies that cause ringing, boominess, or other disruptive resonances that occur in acoustically difficult rooms. The 2801 allows sound systems to be "tuned" according to the special acoustics of a room, to maximise output and minimise feedback. As a creative tool in sound recording or re-recording the 2801 allows complete freedom in contouring response over the complete audio spectrum from 31.5 Hz to 16 KHz.



## MODEL 2021 — 2 CHANNEL EQUALISER

The 2021 is a two channel graphic equaliser featuring ten adjustable controls on octave centre frequencies (independent for each channel). Each control provides up to  $\pm 14$ dB of adjustment. Each channel is also equipped with a level match control giving an overall gain of adjustment of  $\pm 14$ dB.

The functional versatility of the 2021 equaliser is unsurpassed. Eight modes of operation are available from the push button switches on the front panel.

Included amongst these are the ability to equalise both recording and playback when dubbing tapes.

The 2021 has been designed to be compatible with all commercially available equipment and is ideal for use in a Hi Fi system or P.A. system.

***For further information, please send a 35c stamp  
for full specification sheets, or call at our showroom for a demonstration.***

**jaycar**  
PTY LTD

**380 SUSSEX STREET, SYDNEY, NSW  
P.O. BOX K39, HAYMARKET 2000  
TEL: (02) 211-5077**





# SONICS

the Australian  
magazine  
dedicated to  
the art and  
craft of sound

Available late June

Sonics is a magazine for **everyone** who has an interest or involvement in music or musical electronics. Published quarterly, in March, June, September and December, each issue contains features, equipment reviews, construction projects, distributor and brand index and much, much more.

**Sonics June 1980 line-up:**

**FEATURE** — Ibanez MC-500 guitar reviewed

**RIGS** — Fleetwood Mac: the sound of the band

**HOMEGROWN** — Jands: how a small lighting company became one of Australia's biggest PA system operators.

**SOUNDPROOF** — Mediasound studios: improving the style of a sound reputation

**HARDWARE** — Yamaha's CS-20M and Roland's Promars Compuphonic synthesizers reviewed



**PROFILE** — Charles Fisher of Trafalgar studio

**SHINE ON** — Latest products and news in the lighting game

**PLUS** — extra features, a B.I.Y. project or two, and all the news, views and happenings in music and electronics. Rendezvous with Sonics in June!

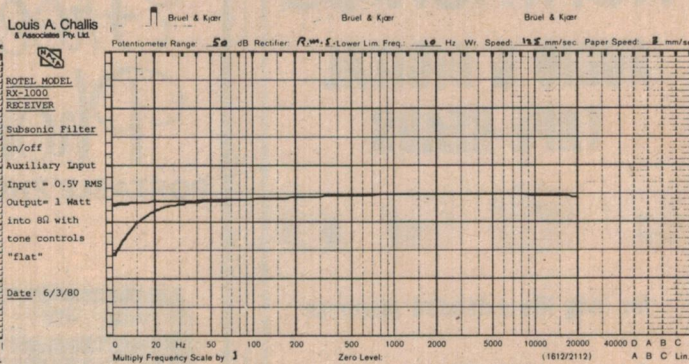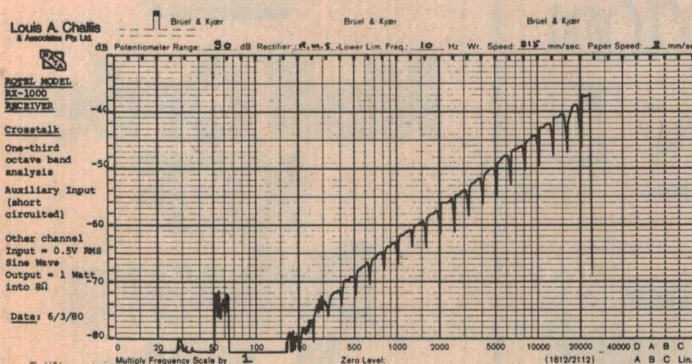Also available . . . . . Sonics 1980 Yearbook is Australia's first comprehensive directory of electronic musical equipment, featuring articles on keyboards, guitar pick-ups, amplifiers, speaker systems and microphones. The Yearbook is still available from most newsagents, or direct from Sonics, 4th Floor, 15 Boundary St, Rushcutters Bay, NSW 2011 — Price \$4.35 plus 75 cents post and packaging.





weighted and A-weighted levels are well controlled at -76 dB(A) for the auxiliary and -74 dB(A) for the phono input. The maximum power output at the clipping point is 52W and this provides a dynamic headroom of 1.8 dB.


It is interesting to note that this unit has been designed to comply with the American FCC Rule 15 and thus the power output claimed for the unit is quite modest compared with the peak power handling capacity of the amplifier's output stage.

The transient overload recovery test showed that the unit has quite stable performance and that the circuit designers have achieved a commendable performance.

The radio frequency stage of the

receiver is just as good as the audio stage and the FM receiver has a frequency response extending from 18 Hz to 17 kHz,  $\pm 3$  dB. The FM channel separation is a modest 25 dB from approximately 30 Hz to 2 kHz and this is only comparable with a modest phono cartridge. The FM distortion is commendably low and we were unable to fault the FM stage performance. The FM sensitivity is reasonably good being 2.3 microvolts for 6 dB signal-to-noise ratio on mono, and 7.8 microvolts on stereo. The 50 dB quieting sensitivity on mono is 5.7 microvolts and 58 microvolts on stereo.

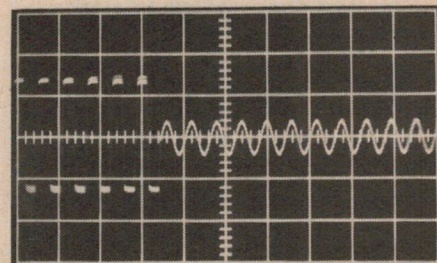The AM tuner stage exhibits the same desultory frequency bandwidth which we have come to expect from vir-



Transient overload recover test results for the RX1000. Overload of 10 dB re rated power into 8 ohm load, both channels driven. Overload duration: 20 ms; rep. rate: 512 ms.

tually all the receivers on the market, extending from 45 Hz to 2.4 kHz  $\pm 0.5$  dB, -6 dB. The AM tuner sensitivity is modest and only suitable for local reception.

— to page 151. ▶



Louis A Chellis and Associates Pty Ltd

**FREQUENCY RESPONSE:**  
(-3dB re 1 watt, 0.5V  
Input to Aux.)

**MEASURED PERFORMANCE OF**  
**ROTEL MODEL RX-1000 RECEIVER**  
**SERIAL NO. 21062**

**Tone Controls Centred**  
Left 4.5Hz to 57kHz  
Right 4.2Hz to 57kHz

**SENSITIVITY:**  
(for 1 watt in 8Ω)

	Left	Right
Aux.	24mV	24mV
Tuner	-	-
Tape	24mV	24mV
Phono M/M	400μV	410μV
Overload M/M	255mV	250mV

**INPUT IMPEDANCE:**  
(@ 1kHz)

	Left	Right
Aux.	47kΩ	47kΩ
Tuner	-	-
Tape	47kΩ	47kΩ
Phono	49kΩ	49kΩ

**OUTPUT IMPEDANCE:** ≈ 107 milliohms (@ 1kHz)

**TRANSIENT INTERMODULATION DISTORTION**  
(3.15kHz square wave and 15kHz sine  
wave mixed 4:1 @ 30w equivalent output)

0.19%

## HARMONIC DISTORTION:

(A) (At rated power of 35 watts  
into 8Ω = 16.7 volts)

	100Hz	1kHz	6.3kHz
2nd	-63.7	-62.5	-62.5dB
3rd	-64.2	-61.9	-63.4dB
4th	-	-87.9	-88.8dB
5th	-84.5	-82.1	-
THD	0.09	0.11	0.1 %

(B) (At 1 watt into 8Ω)

	100Hz	1kHz	6.3kHz
2nd	-69.2	-69.3	-68.8dB
3rd	-73.9	-72.8	- dB
4th	-90	-	- dB
5th	-87	-	- dB
THD	0.04	0.042	0.036 %

## NOISE & HUM LEVELS:

(re 1 watt into 8Ω)  
(with volume control set for  
1 watt output with:  
0.5V input (Aux.)  
5 mV input (Phono M/M)

AUX.	-69dB (Lin)	-76dB (A)
PHONO M/M	-66dB (Lin)	-74dB (A)

## MAXIMUM OUTPUT POWER AT CLIPPING POINT:

(1HF -A - 202)

(20ms burst repeated at 500ms  
intervals)

58 V P-P	
= 52.6 watts	
∴ Dynamic Headroom = 1.8 dB (re 35 watts)	





# NORTRONICS®

## AUDIO & DIGITAL TAPE HEADS



for long life extended response

- Replacement heads for cassette decks, reel to reel decks, cartridges and cassette recorders. Also professional recorders and duplicators.
- Will fit AMPEX, SCULLY, TEAC, ATC, GATES, PENTAGON, IFONICS and many more.
- Complete range of Alignment tapes for cassette, reel to reel and cartridge decks.
- REGULAR MAINTENANCE ENSURES CONTINUED OPTIMUM PERFORMANCE. Nortronics manufacturers a full range of audio care products.



MAGNETIC TAPE  
DEVELOPER



ALIGNMENT  
TAPES



BULK  
ERASER



TAPE  
HEAD  
CLEANER



TAPE  
SPLICER

- NORTRONICS audio care products are designed to care for and maintain your valuable recording equipment.
- SEND TWO 20c STAMPS FOR OUR FREE BROCHURE ON THE COMPLETE NORTRONICS RANGE.


**E.I. EMAC INDUSTRIES** Pty. Ltd.

2 Begal Crescent, Mount Waverley.  
Vic. 3149. Ph: (03) 277-9989.

# Royce

## Freedom Phone IV

PORTABLE PHONE SYSTEM

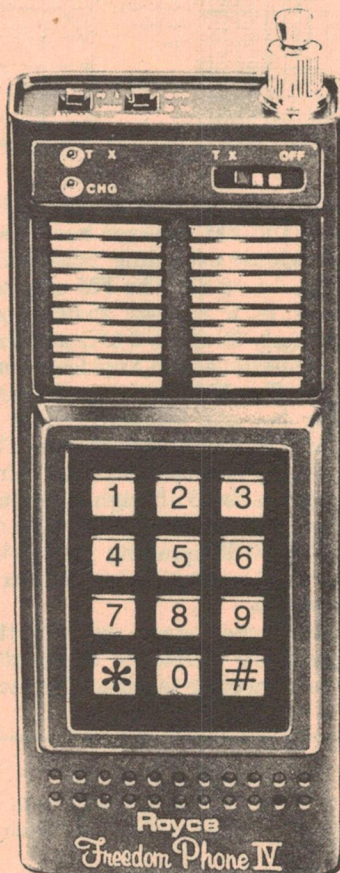

### THE HANDSET MODEL T-026 COMPLETELY PORTABLE CORDLESS PHONE SYSTEM

- Fully portable wireless telephone.
- Pocket sized — belt clip supplied.
- Rechargeable batteries included.
- 100 percent solid-state reliability.
- Make or answer calls anywhere inside or outside up to 600 feet.
- For home — office — factory — warehouse — farm.

This instrument is not a Telecom-approved apparatus and as such cannot legally be connected to Telecom equipment.

Available from:

**HOLDEN WASP  
INTERNATIONAL**

P.O. Box 532, Marrickville, 2204. 39  
Chalder St, Marrickville, NSW 2204  
Phone: (02) 560-3488




# Mail Order KEF Drivers & Kits

CERTIFIED MAIL  
DELIVERY THROUGHOUT  
AUSTRALIA  
& NEW ZEALAND  
Bankcard accepted
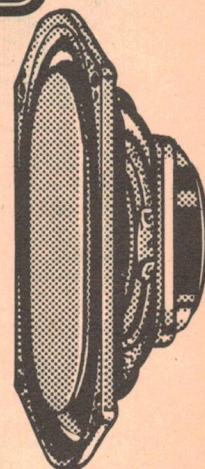
## KEF B139

Superb 30 x 21cm  
bass driver, with  
solid flat diaphragm  
of unique  
construction, acting  
as a perfect rigid  
piston, to give clean,  
distortion-free bass  
over the frequency  
range 20-1,000Hz.  
The KEF range also  
includes mid range  
and high frequency  
units, with dividing  
networks designed  
to link them into  
compatible systems.





*the no-compromise approach  
to uncoloured sound*

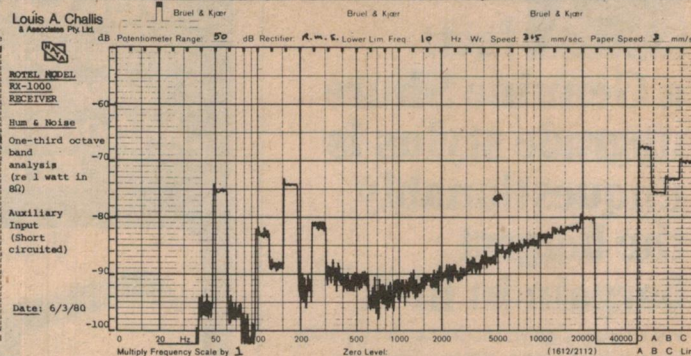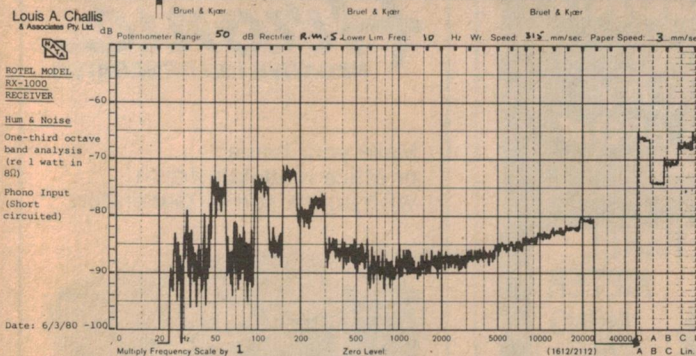For full information, write to:  
AUDIOKITS  
PO BOX 553  
BROOKVALE NSW 2100







## Subjectively

Our subjective impressions of the unit are generally quite favourable. The receiver quite happily picks up FM signals in the absence of any aerial and with an aerial can provide very clean reception with no trace of distortion. The AM section of the receiver also provides clean reception, but this does depend on the signal and presence of interference. The audio stage is a credit to the designers. Even though it is based on integrated circuits, which the purists will tell you do not lead to quality amplification, this particular receiver tends to belie that statement. With inputs

from a wide range of moving magnet cartridges the quality of sound is excellent and better than we would have expected.

## Summary

The RX1000 is a cleverly designed receiver. Whilst one might think from its price that performance would have suffered because of the innovatory design, but this is not the case. I think that the designers have achieved above average results without sacrificing performance and most important with an appearance which is both simple and attractive.

## ROTEL RX1000 AM/FM STEREO RECEIVER

Dimensions: 430 mm wide x 80 mm high x 290 mm deep

Net Weight: 7.7 kg Price: \$359 rrp.

Manufactured by The Rotel Company Limited, Tokyo, Japan

Absolute copyright in this review and accompanying measurements is owned by Electronics Today International. Under no circumstances may any review or part thereof be reprinted or incorporated in any reprint or used in any advertising or promotion without the express written agreement of the Managing Editor.

# ADVENT

now acclaimed in Australia



### Here's what some reviewers have said:

"... at least one order of magnitude better than the old Advent... produces... the cleanest... sound of any speaker in the under \$1000 bracket." Louis A. Challis. E.T.I. December, 1979.

"Bass response was quite remarkable... certainly the high frequency response was as clear as a mountain stream." David Cruse. Perth Sunday Independent. February, 1980.

"This is an impressive little loudspeaker. It is very true that Advent never brings out a product unless it considers it to be an advance on a previous model. The Advent/1 can only enhance the company's reputation." Stereo Buyers Guide — Manual 1980.

Australian Distributor:

**ADVENT LOUDSPEAKERS, 89 Carnarvon Street, Silverwater. NSW. 2141. Tel: (02) 647-1103.**

### ADVENT DEALERS:

**N.S.W.**  
**AUDIOCOM**, North Rocks, 872.3829. **AUDIOCOM**, Eastwood, 85.2726. **AUDIOCOM**, Birkenhead Point, 81.3132. **HI FI JUNCTION**, Bondi Junction, 389.4000. 27.4420. **HI FI SHOP**, Hurstville, 570.8163. **PARK HI FI**, Summer Hill, 799.2618. **NEWCASTLE HI FI**, Newcastle West, (049) 22400.

**A.C.T.**  
**DURATONE**, Phillip, 82.1388  
**VIC.**  
**NATSOUND**, Melbourne, 67.8158. **SOUND CRAFTSMAN**, Nth. Caulfield, 509.2444.  
**QLD.**  
**SOUND CENTRE**, Brisbane, 221.0821. **SOUND CENTRE**, Coolangatta, (075) 36.5443.






**DISCO & STEREO SUPPLIES**, Townsville. 72.3470.  
**S.A.**  
**GRENFELL PLAZA**, Adelaide, 51.5017. **SOUND CRAFTSMEN**, Hawthorn, 272.0341  
**W.A.**  
**THE SOUND CRAFTSMAN**, Subiaco, 381.5114.





**fact:**  
a Genuine Shure  
upgrade stylus is  
unquestionably  
the biggest  
bargain in hi-fi

We strongly urge you to check your stylus for wear at least once a year to protect your records and maintain the highest standards of listening pleasure. Regardless of when (or where) you purchased your Shure cartridge, there is a Genuine Shure replacement stylus available which will bring your cartridge right back to its original specifications. Even better, you may actually be able to improve its performance significantly over the original with a Genuine Shure upgrade stylus...at surprisingly low cost! For example:

IF YOU OWN:	UPGRADE WITH:
 <b>V15 Type III SERIES</b>	 <b>VN35HE</b> Hyperelliptical stylus
 <b>M95 SERIES</b>	 <b>N95HE*</b> Hyperelliptical stylus
 <b>M70 SERIES</b>	 <b>N72EJ</b> Biradial (Elliptical) stylus <b>N72B</b> Spherical stylus
<b>ANY M91, M92, M93</b>	<b>N91ED*</b> stylus
<b>ANY M71, M73, M75</b>	<b>N75 TYPE 2*</b> Series styli
<b>ANY M44 Series</b>	<b>N55E</b> stylus
<b>M3D, M7D</b>	<b>N21D*</b> stylus

\*Before purchasing any replacement stylus be certain your turntable is compatible with the tracking force of the stylus you select.

**Always insist on a Genuine Shure replacement stylus. Look for the name "Shure" on the stylus grip.**

**SHURE**  
AUDIO ENGINEERS PTY LTD  
342 Kent Street,  
Sydney, 2000 NSW

HAWKAE147/TP


— PTY. LTD —  
**DELSOUND**  
BRISBANE  
NEW QUALITY  
PRODUCTS FROM  
CLIFF

**V.U. PANEL**



**METER**

MONO  
\$28zea.  
STEREO  
\$49 ea.

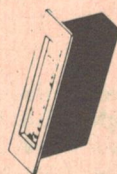

**BARGRAPH**

MONO  
\$49 ea.

**TO 3 INSULATOR PADS**

20c ea. \$15/100

**JACK SOCKETS**

**INSULATED**



MONO  
\$40/100  
S1-SS

COLOURS: RED,  
BLACK, WHITE,  
GREY



**JACK PLUGS**

MONO \$70/100 P2

COLOURS:  
RED, YELLOW,  
BLACK, GREEN,  
WHITE, GREY



**PLASTIC FEET**


\$30/100 PFI

For further information, local agents and wholesale prices, write to the Australian Importers:

**DELSOUND PTY. LTD.**  
1 Wickham Tce. (Cnr. Wharf St.)  
Brisbane. Phone 229-6155.  
Wholesale and Retail suppliers of  
Electronic Hardware and  
Components.

**Aironic**  
NEGATIVE ION GENERATOR

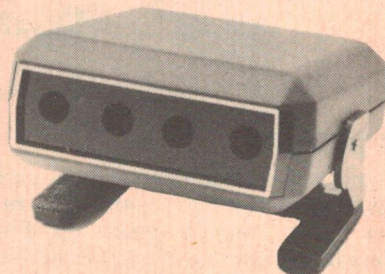Make your home  
or office mountain fresh  
with an "Aironic" Generator.



**NEGATIVE IONS:**

Medical reports indicate that negative ions can help to clear cigarette smoke — reduce fatigue and increase alertness — increase resistance to colds and flu — reduce up to 75 percent airborne bacteria — alleviate sensitivity to weather — minimise travel sickness — speed up the healing process and reduce post-operative pain.

**TWO MODELS AVAILABLE:**

Home and Office model,  
\$85.00 plus \$2.00 P&P

DE "LUXE" WOOD Casing  
model,  
\$95.00 plus \$2.00 P&P

**BOOK AVAILABLE:**

The Ion Effect by Fred Soyka,  
\$3.25 inc. post.



Bankcard Mail Orders Welcome

Expiry Date .....

Signature .....



**BELLE LUMIERE  
ELECTRONICS P/L**

P.O. Box 216, Lane Cove, NSW 2066.  
Telephone (02) 428-1334.

5/47 Fitzroy Street, St. Kilda, VIC 3182.  
Tel (03) 534-7493 A.H. (03) 211- 6549.  
P.O. Box 184, Toowoomba, QLD 4066.  
Telephone (07) 371-3645.


Pamphlet available free — send SAE.


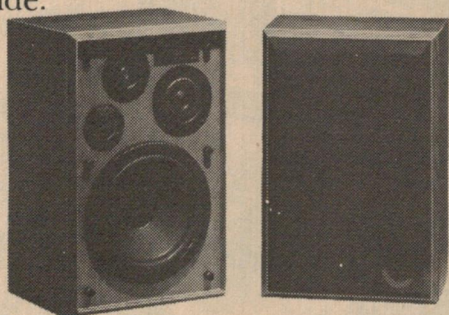
# The best is worth the little extra.



Forty years experience has produced a range of speaker components unmatched in sensitivity and long-term acoustic output, offering a robustness that is hard to equal. Altec Lansing is the choice of professionals world-wide.



## THORENS

Every Thorens Transcription turntable is a technical masterpiece designed to reproduce the most sensitive sound performances. Rumble figures are among the best in the world, some say the best. Thorens has achieved an effective tone arm mass of 7.5 g which is comparable to the best available.



*Cecil & Watts Ltd*


## The Dust Bug®



The original Dust Bug collects particles of destructive dust, discharges residual static leaving a perfectly clean recording groove for the stylus to trace. Reproduction improves, records last longer.


Wharfedale 'E' Series Hi-Fi speakers will amplify your amplifier. Make 20 watts sound like 200.

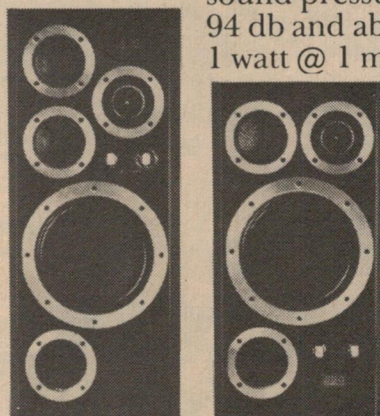That's because their generous performance characteristics give you power-plus, when the sound pressure level is 94 db and above (SPL @ 1 watt @ 1 metre).


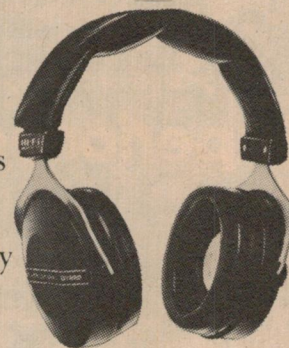
## BEYER DYNAMIC

The lightweight padded headband offers the best possible wearing comfort. The inbuilt wideband transducer system supplies impulse fidelity and true sound reproduction even at the highest levels. A truly professional product.



Distributed by

**RANK AUSTRALIA**

Sydney 406 5666, Melbourne 541 8441, Brisbane 44 2851, Adelaide 294 6555, Perth 328 3933, Newcastle 26 2466, Townsville 72 2547.

Rank Australia P/L, 12 Barcoo St., E. Roseville 2069.

Please send me more information on Altec ☐

Wharfedale ☐ Thorens ☐ Watts ☐ Beyer ☐

Name


Address

Postcode

CU416/79


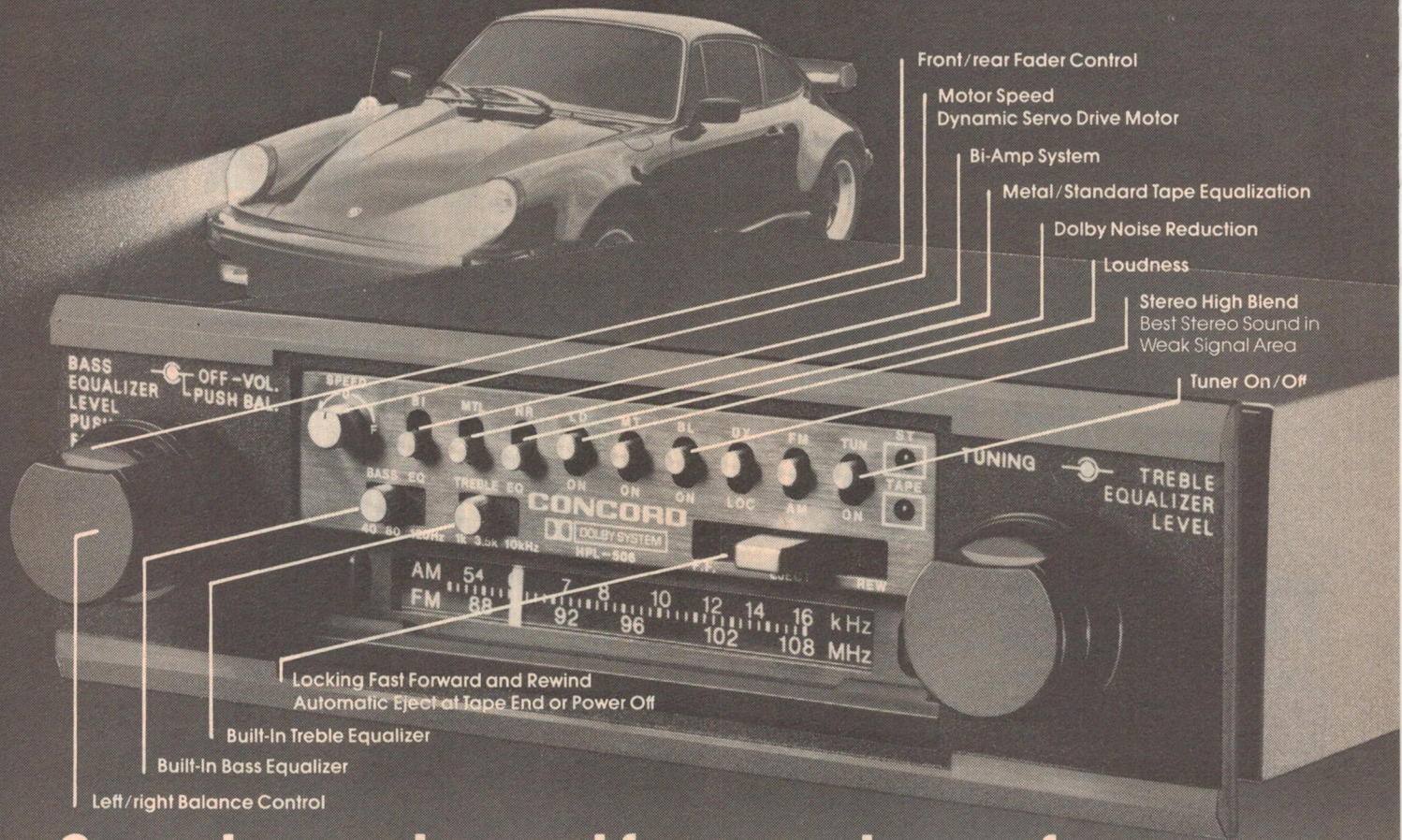
# CONCORD<sup>®</sup> drives auto high fidelity to new limits.



## Superior equipment for superior performance.

Concord Hi-Fi Series is the choice of the dedicated "sound buff" who demands superior performance—

- Dolby Noise Reduction ● Sendust Alloy Head ● Metal Tape compatibility
- Hi-Fidelity Power ● Fader Control ● Din Size (dashboard installation) ● Bi-Amp Facility ● Superior FM Sensitivity ● Low Wow, Flutter ● Separate Bass and Treble Control.


The Concord range of auto high fidelity equipment includes hi-fi car stereo amplifier, 5-band graphic equaliser and a range of speakers.
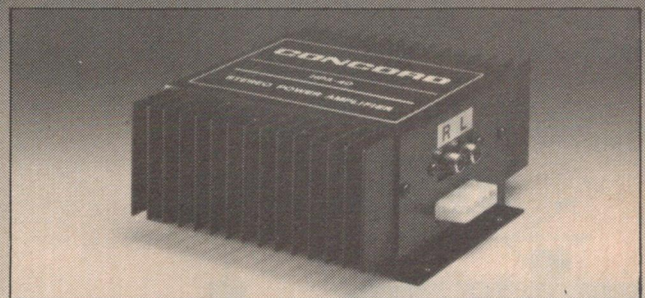
# CONCORD<sup>®</sup>



CONCORD is distributed and serviced in Australia by the PHODIS GROUP OF COMPANIES.

**CONCORD DEALERS:** N.S.W. Chatswood Car Radio 419 8229/419 2288 ● Kent Hi Fi, City 29 7406 ● Cronulla Radio 523 9884 ● Auto Acoustics, Kings Cross 357 1810/357 3470 ● Miranda Hi Fi, Roselands 750 7311 ● Paul Barden Car Radio, St. Leonards 439 3318 ● Sprint Electronics Taren Point 525 0902 ● D.M.E. Hi Fi Sydney 02. 61 3189 ● Northern Auto Sound Newcastle 049. 61 3260 ● Galaxy Sound - Newcastle 049. 29 1712 A.C.T. ● Polymedia Car Stereo Phillip 062. 81 1966 ● Radio World Fyshwick 062. 80 6550 VIC. ● Sound City, Melbourne (03) 67 6771. TAS. ● 9 Wilson Street Hi Fi Burnie 004. 31 5633 QLD. ● Stereo Supplies, Brisbane (07) 221 3623 ● Sound Centre, Brisbane (07) 221 0821 S.A. ● Blackwood Sound Blackwood 08. 278 6888 ● Blackwood Sound North Adelaide 08. 267 4220 W.A. ● Alberts Hi Fi, Perth, Victoria Park, Balga, Fremantle (09) 361 5422 ● Alpine Hi Fi, Bunbury (097) 21 6133



### SPECIFICATIONS

- High fidelity power: 25 watts RMS per channel into 2 ohms (18 watts into 4 ohms) both channels driven 20-20000 Hz at less than 0.3% T.H.D. ● Tape signal-to-noise ratio (Dolby on) 56 dB ● Tape frequency response—standard tape 30-15000 Hz ± 2 dB—metal tape 30-20000 Hz ± 2 dB ● Tape Wow and Flutter—0.08% WRMS ● FM tuner sensitivity at 30 dB S/N—1.0 Microvolt (11.2 dBf) ● FM S/N ratio—68 dB ● AM tuner sensitivity—11 microvolts ● AM S/N ratio—50 dB

For further information write to PHODIS PTY. LTD.  
5 Campbell Street, ARTARMON 2064. (02) 439 8900.

Dolby is registered Trade Mark of Dolby Laboratories



# BOOKS

Just some of the books from the biggest range of radio and electronics books in Australia. If the book you require is not listed below, it can be ordered from us.

**NEW - NEW - NEW** Latest editions of some of the most popular books on the subject:

How to Design and Build Audio Amplifiers (Mannie Horowitz)	\$12.50
The Master IC Cookbook (Clayton L. Hallmark)	\$12.50
IC Array Cookbook (Walter G. Jung)	\$10.00
Amateur Operator's Handbook (Revised Dec. 78) (Postal & Telecommunications Dept.)	\$3.00
Radio Amateur Callbook — US Listings 1980	\$23.00
Foreign Radio Amateur Callbook — DX Listings 1980	\$21.60
ARRL Handbook 1980	\$14.95
World Radio and TV Handbook (now available 1980 edition)	\$16.95
R.S.G.B. Handbook — Volume 1	\$21.95
R.S.G.B. Handbook — Volume 2	\$18.90
The World in My Ears (Cushen)	\$13.35
Radio Handbook — 21st Edition (New edition) (William Orr)	\$27.75

## ADAM OSBORNE BOOKS:

An Introduction to Microcomputers — Volume 0 — The Beginner's Book	\$11.50
An Introduction to Microcomputers — Volume 1 — Basic Concepts	\$13.50
An Introduction to Microcomputers — Volume 2 — Some Real Microprocessors	\$29.00
An Introduction to Microcomputers — Volume 3 — Some Real Support Devices	\$19.00
Some Common Basic Programs	\$16.20
Accounts Payable and Accounts Receivable	\$18.60
Payroll with Cost Accounting in Basic	\$18.60
General Ledger	\$24.50
Z80 Assembly Language Programming	\$16.20
Z80 Programming for Logic Design	\$13.50
8080A/8085 Assembly Language Programming	\$16.20
6800 Programming for Logic Design	\$13.50
6800 Assembly Language Programming	\$13.50
8080 Programming for Logic Design	\$13.50
6502 Assembly Language Programming	\$16.20

## AMERICAN RADIO RELAY LEAGUE PUBLICATIONS:

All New A.R.R.L. Code Kit	\$14.50
Hints and Kinks for the Radio Amateur	\$7.20
The Radio Amateur's VHF Manual	\$7.20
Understanding Amateur Radio	\$8.80
The Radio Amateur's License Manual	\$7.20
A Course in Radio Fundamentals	\$7.20
Specialized Communications Techniques for the Radio Amateur	\$7.20
FM & Repeaters for the Radio Amateur	\$8.80
Single Sideband for the Radio Amateur	\$7.20
Ham Radio Operating Guide	\$7.20
Electronics Data Book	\$7.20
Solid State Design for the Radio Amateur	\$12.80

## MICROCOMPUTERS/MICROPROCESSORS BOOKS:

6502 Software Gourmet Guide & Cookbook (Scelbi)	\$16.80
Z80 Software Gourmet Guide & Cookbook (Scelbi)	\$20.60
How to Build Your Own Working Robot Pet (Frank DaCosta)	\$8.50
The Complete Handbook of Robotics (Edward L. Safford, Jr.)	\$9.95
Programming Microprocessors (M.W. McMullan)	\$9.25
Microcomputer Primer (Waite & Pardee)	\$10.75
How to Buy and Use Minicomputers and Microcomputers (W. Barden, Jr.)	\$13.50
Programming the 6502 (Zaks)	\$17.00
Z80 Microcomputer Handbook (Barden)	\$11.95
Microcomputers for Business Applications (Barden)	\$11.95
Getting Acquainted with Microcomputers (Lou Frenzel)	\$11.95
The S-100 Bus Handbook (Bursky)	\$16.50
Understanding Microcomputers and Small Computer Systems (Scelbi)	\$15.40
Scelbi "8080" Software Gourmet Guide and Cookbook	
Reduced from \$10.00 to	\$4.99

## OTHER TITLES:

300 Circuits for the Home Constructor (Elektror)	\$10.10
Understanding Electronics (R.H. Warring)	\$6.50
Master Handbook of 1001 More Practical Electronic Circuits (Michael L. Fair)	\$15.95
Master Handbook of 1001 Practical Electronic Circuits (Ed. Kendall Webster Sessions)	\$15.95
The Complete Handbook of Public Address Sound Systems (F. Alton Everest)	\$9.95
Getting Acquainted with the IC (Rufus P. Turner)	\$6.75
111 Digital and Linear IC Projects (Don Tuite)	\$7.50
Practical Antennas for the Radio Amateur (Scelbi)	\$15.40
IC OP-AMP Cookbook (Walter Jung)	\$17.50
TTL Cookbook (Lancaster)	\$12.95
TV Typewriter Cookbook (Lancaster)	\$13.50
CMOS Cookbook (Lancaster) 1st Edition 1977	\$14.25
Active Filter Cookbook (Lancaster)	\$19.95
IC Timer Cookbook (Jung)	\$13.50
The Cheap Video Cookbook (Lancaster)	\$7.95
Electronics Pocket Book — 3rd Edition (P.J. McGoldrick)	\$10.50
Microcomputer Interfacing with the 8255 PPI Chip (Paul F. Goldsbrough)	\$11.95
Computers in Action — How Computers Work 2nd Edition (Donald D. Spencer)	\$8.00

For mail orders please add: \$1.40 Local \$1.75 Interstate

**McGILL'S AUTHORISED NEWSAGENCY PTY. LTD.**

187 Elizabeth Street, Melbourne. Phone: 60-1475-6-7

Prices Subject to Alteration

# B&W DM12

## THE UNOBTRUSIVE REVOLUTIONARY

We could have built something smaller, but we were determined to build a miniature speaker that rises way above the limitations hitherto imposed by a small enclosure. In particular, we wanted to achieve wider response and more realistic sound levels in the low frequency range. We also wanted safe power-handling capacity. Thanks to our unique resources in computer and laser technology and the sheer creativity of our design team, DM12 achieves all this and more.



## B&W LOUDSPEAKERS



### It's certainly small.

Just 355mm (14 in) high x 220mm (8¾ in) wide x 270mm (10½ in) deep.

### 106dB.

That's the surprising peak sound pressure level DM12 produces from its 12 litre enclosure.

### Monitor standard.

Frequency linearity + 2 dB 85 Hz to 20kHz.

### APOC-protected.

B & W's exclusive audio-powered overload circuit protects against accidental damage or overload.

For further information see your B & W dealer or contact  
Convoy International Pty Ltd  
4 Dowling Street Woolloomooloo NSW 2011  
Telephone (02) 3582088



## Dick Smith model A2375 mini speakers

When space is limited, these compact little units could be just what you need. Louis Challis discusses their merits and deficiencies.

WHEN CAR STEREO started to become a big market in the U.S.A. a number of speaker manufacturers created a new concept. They confounded the theoreticians (who said it couldn't be done) and achieved a reasonable bass response from 'mini' speaker systems that were almost 'pocket-size'.

The most successful of these minis achieved an almost flat frequency response from 80 Hz to 15 kHz and were a talking point for anyone who heard them. It didn't take long for imitators to realise that the automobile isn't the only place where a mini speaker system has tremendous market potential. The average apartment in New York or Tokyo suffers from exactly the same space limitations.

Today, some ten years later, there must be close to 500 different descendants of that first generation of mini speakers. Like the originals, virtually all of these are designed around a die-cast cabinet. Many have an integral back and separate front panel containing a complement of mini woofer and

domed tweeter. Perforated steel grilles have also been religiously adopted by each new manufacturer.

The Dick Smith compact speaker system is a typical example of this speaker concept. Each unit has a 75 mm diameter flexible surround woofer and a 25 mm domed tweeter in a cabinet which is almost as small as any manufacturer could reasonably hope to achieve. Each speaker is protected by a strong and durable perforated steel grille set back into an aluminium coloured plastic trim which surrounds the front edge of the cabinet. The back of the cabinet is a separate panel glued into the sides. The woofer features a lightweight steel supporting frame for the ferrite magnet assembly whilst the tweeter has an integral back, which avoids the need for separate enclosure.




Electrical connections are simple — two screw terminals accept the bared ends of the speaker leads. The makers provide a pair of universal support brackets to facilitate hanging the units on a wall or bulkhead.

### Evaluation

The objective testing of these units showed that they have been designed to achieve a pronounced presence in the 500 Hz to 7 kHz region. The fundamental resonance of the woofer occurs at 130 Hz and the non-vented enclosure volume of 1.3 litres provides a small peak in the response at 180 Hz.

The on-axis response measured in an anechoic chamber is generally acceptable, although it is not nearly as flat as that of the original 'minis'. Crossover between the woofer and tweeter is undetectable and the high frequency output of the tweeters extends all the way to 20 kHz.

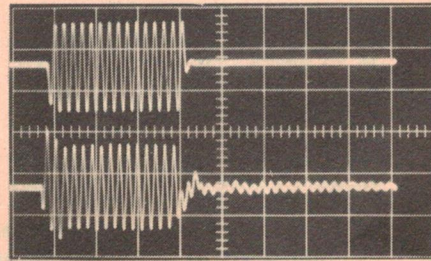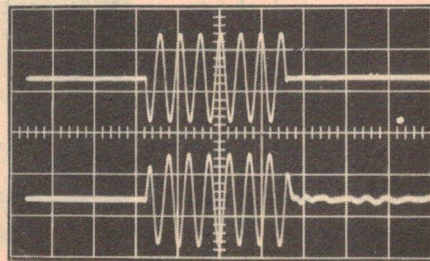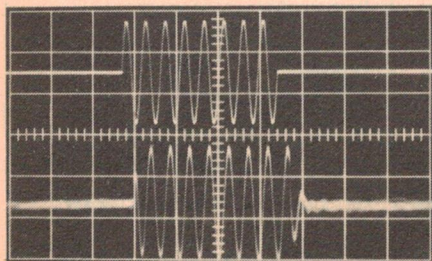The impedance curve is particularly flat, but as it dips below 8 ohms over the most significant portion of the frequency range it is apparent that the intending user would have to be careful when paralleling these units with other speakers also having low input impedance. The phase response is reasonably smooth and tends to indicate that the crossover frequency is in the



Tone burst response oscillographs of the Model A-2375 loudspeakers, measured with respect to 90 db steady-state spl at 2m on axis. LEFT: at 100 Hz, (20 ms/div, 80 dB spl). CENTRE: at 1 kHz (2 ms/div) and RIGHT: at 6.3 kHz (0.7 ms/div).





3-4 kHz region. The relative positions of the woofer and tweeter achieve a more than acceptable phase balance, which does enhance the quality of reproduction as subsequent subjective testing showed.



Tone burst testing revealed that at frequencies above 100 Hz the speaker

performs moderately well, although at 6.3kHz and 100 Hz the quality fell short of what we would have liked. The distortion characteristics of the speaker are generally adequate at high frequency but not at 100 Hz. At this frequency the system can't cope with our standard test of 90 dB at two metres and even with

80 dB output it produced a hefty 5.6% distortion.

The sensitivity of 6.8 W input to achieve 90 dB on axis at 2m is reasonably good and only a small amplifier with a 20-30 W rating would be needed to produce a healthy output in a small or medium sized room.

— to page 161.►

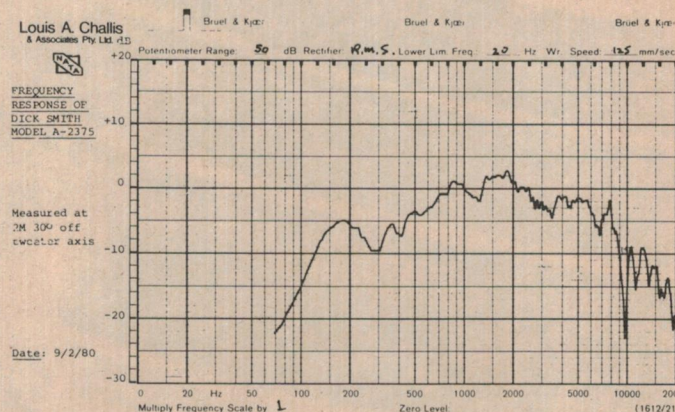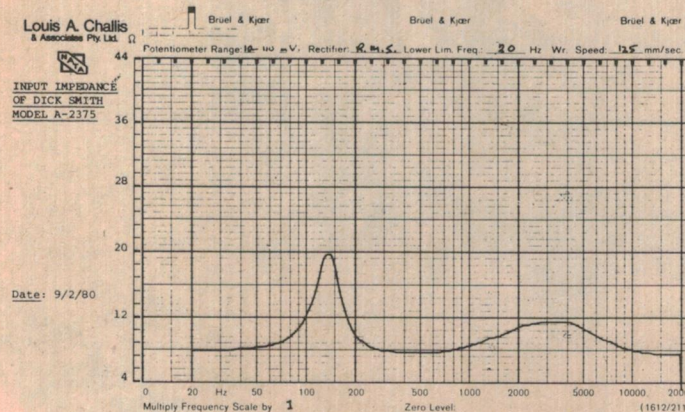



# Professional Sound Systems Start With The Stanton 881S

Stanton Magnetics presents the new 881S Professional Calibration Standard Cartridge. It's the cartridge preferred by recording engineers worldwide and it assures a new standard for home audiophiles desiring the very best in recorded sound. Its patented, low mass Stereohedron™ stylus

tip makes possible the flawless reproduction of high velocity modulations present on today's finest recordings. The Stanton 881S... where great sound begins.



## STANTON

THE CHOICE OF THE PROFESSIONALS™

Sole Australian Distributors:  
**LEROYA INDUSTRIES** PTY LTD

**Head Office:** 156 Railway Pde, Leederville, Western Australia, 6007. Phone 81 2930  
**NSW Office:** 7 Jordan Rd., Wahroonga, 2076. Phone 487-2543

*Available at quality conscious Hi-Fi dealers throughout Australia!*







# STAGE & EFFECTS LIGHTING

## ALL YOUR REQUIREMENTS AUSTRALIA WIDE

### LANTERNS
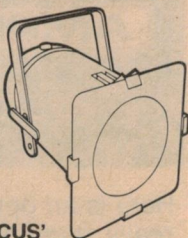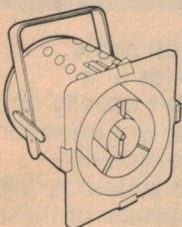
#### PAR 56 'POLE FOCUS'

300 watt, 240 volt sealed beam lamp. Available in either narrow or medium flood lamps with a remarkable 2,000 hours lamp life. APPLICATIONS: Stage lighting from overhead or sides; stage lighting from front of house using optional barn doors. Colour Wheel available.





#### ROCKBEAM 'POLE FOCUS'

1000 watt, 240 volt beamlight. Projects narrow, intense beam suitable for long throws of up to 30 metres. Standard T11 tungsten halogen lamp is used, giving 800 hours lamp life. APPLICATIONS: Long throw stage lighting; "Specials" lighting and pin spotting.
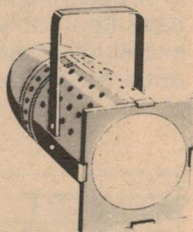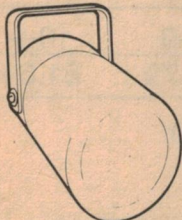
#### PAR 64 'POLE FOCUS'

1000 watt sealed beam lamp, available in narrow spot or medium flood. The Par 64 is an American 120 volt lamp and the lanterns are operated in pairs, giving series operation to 240 volts. 2,000 hours lamp life. APPLICATIONS: Stage lighting from any position; optional barn doors offer beam shaping facilities.



#### HOTSPOTS, RAINLIGHTS & SOLOS

The compact pencil beam light used by disco's and bands around Australia. Tiny Par 36 lamp gives punchy, intense shaft of light. Several versions are available for either single use or large installations. APPLICATIONS: Special effects lighting; mirror ball lighting for disco's, bands, etc. Colour Wheel available.

### SUPPORT SYSTEMS

We distribute a complete range of stands and support systems including the following.

**WINCHUP STANDS** — wind up from less than 2 metres to either 4 metres or 6 metres maximum height. Load up to 100 kg. T-Bar accepts 8 lanterns or frames.

**TRUSS SYSTEMS** — 2 metre box sections bolt together to form a rigging gantry across the stage. A truss of up to 10 metres can be used on two winchup stands or flown with lines. Maximum capacity (10 metre truss) is 100 kilos.


**T-STANDS** — collapsible, portable telescopic stands to take up to 4 lanterns. Extends to 3 metres.

**SPOT STANDS** — stands for every occasion! We manufacture stands to suit all lanterns.

**HOOKS and ACCESSORIES** — all rigging accessories, the whole range.
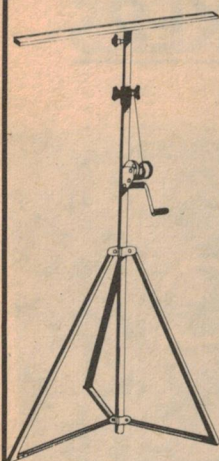
### LAMPS

We sell theatrical and effects lamps plus those hard-to-get items.



### CONTROL SYSTEMS

There are dimmers and there are control systems — only your Barratt Lighting agent can offer you this range:

**STRAND** • 12 channel SMC desk, 2 preset • 24 channel DMC desk, 2 preset, A&B masters • 12 channel mini pack dimmer rack, 12 x 2000W dimmers • 24 channel desk, 8 scene masters on matrix and chaser. **JANDS** • 36 channel desk, 12 scene masters on matrix and chaser • 24 channel desk, A&B masters, flash buttons • 36 channel desk, A&B masters, flash buttons. **ACCESS** • 12 channel remote switching system, zero switching • 4 preset switch desk and chaser, flash buttons. **SMALL DIMMERS** • Strand Model 3 — 3 x 1000W dimmers • Strand Model 1 — 1 x 2000W dimmer. **ARLEC DISCOLITE**: 1 x 500W dimmer and effects. **CEITEX COLOURGRAM 4**: 4 x 1000W dimmers and master, chaser plus colourgan. **ACCESSORIES**: Multicores, 3-Phase plugs, Sockets, Leads & Tails.

### EFFECTS EQUIPMENT

Ceutex and Rock Industries manufacture the largest range available.

**ZERO CHASER**: 3 channel, 1000W per channel, shadow function. **AUDIO CHASERS**: 3 channel, 100W per channel, normal or audio chase. • 4 channel, 10A max. load, normal or audio chase (heavy duty audio chasers are available). **COLOURGAN**: 3 channel, sound to light, 10A max. load, built-in mic. **CHASER FOUR**: 4 channel, combination audio chaser and colourgan, 10A max. load. **MEMORY CHASER**: 8 channel multi-function controller, 20A max. load, slave output for additional 20A slave chasers. **COLOURGRAM 4**: 4 channel dimmer, chaser, colourgan — multifunction! **STROBES**: Super Strobe, high output, can be slaved or run from strobe pulser. Best strobe available: **STROBE PULSER**: 4 channel strobe chaser/controller, variable speed with built-in mic for audio chase. For up to 32 strobes. **MIRRORBALLS**: 16" (400mm), 18" (460mm), 22" (560mm), 36" (920mm), and motor drives available. **BEACONS**: Police, Fire, Ambulance, plus power supplies — complete! **SNAKELITE**: Clear, flexible tubing with multicoloured lamps, run by 24V chasers. **FLOWBOX**: Low cost Snakelite/Tubelite chaser. **SNAKE CHASER**: Audio chaser for up to 20M of Snakelite or Tubelite. **TUBELITE**: Clear, hi-impact square tubes of lamps, for floors, roofs, etc. **LASERS**: Disco scanning lasers, 1mW, 2mW, 4mW, 5mW, Helium Neon, Ruby Beam, speaker level drive. **SPACE BEACONS**: 4, 8 or 16 spinning pencil beams — stunning! **SCANNERS**: Single oscillating pencil beams. **DRY ICE FOG MACHINES**: For use with dry ice pellets for a low-lying fog effect. **B.V.I. FOGGERS**: Electric fog generators for use with Genie Fog Oil. **COLOURWHEELS**: Rotating colour wheels to suit Patt 23, Hotspots, Rainlights, Par 56, Patt 123, etc.

**MISCELLANEOUS**: All those things you have trouble finding. **COLOUR FILTERS**: Lee Filter, Roscolene & Cinemoid. • Cables • Plugs • Sockets • Leads • Accessories.

#### WHY WASTE TIME?

Contact the professionals for hire and sales.

**NOTE**: Not all Barratt Lighting agents stock our complete range at any one time — please phone first to check stock and availability.

**SYDNEY**: Ceitex 2/33 College St, Gladesville (02) 896-2900  
**WOLLONGONG**: Trilogy Electronics 40 Princes Hwy, Fairy Meadow (042) 83-1219

**NEWCASTLE**: Your Move Lighting 37a Beaumont St, Hamilton (043) 69-3560

**BRISBANE**: Harvey Theatrical Lighting 21 Crosby Rd, Albion (07) 262-4622

**BRISBANE**: Mothers Lightworks 624 Brunswick St, New Farm (07) 358-2210

**GOLD COAST**: Rave Audio Visual 2388 Gold Coast Hwy, Mermaid Beach (075) 38-3331

**MELBOURNE**: Clearlight Shows 17 Alex Ave, Moorabbin (03) 553-1446

**MELBOURNE**: Lighting Corporation 131 Brighton St, Richmond (03) 429-5122

**ADELAIDE**: Hiwatt Lighting 37 Angus St, Nth Adelaide 5006 (08) 212-2033

**ADELAIDE**: Optical Acoustics 22 Finnis St, Nth Adelaide 5006 (08) 267-2049

**ACT**: Topstage Productions 12/4 Ipswich St, Fyshwick ACT 2609 (082) 80-6940

**PERTH**: Stagecraft 1142 Hay St, West Perth 6005 (09) 321-9363.

**PERTH**: Kosmic Sound 1074 Albany Hwy, Bentley (09) 361-8981

**HOBART**: Good Oil Sound 310 Liverpool St, Hobart (002) 23-5151

Also available Australia-wide at Strand Rank Electronic outlets.

New Brisbane outlet: **RAVE LIGHT & SOUND** 95 Bridge Rd, Fortitude Valley. Phone (07) 52-3310.

Distributed nationally by

Telex AA25298

**BARRATT LIGHTING PTY. LTD.**

140 Myrtle Street, Chippendale, NSW 2008.

NOW OPEN: New One-Stop Lighting Shop Showroom. All products ex-stock.

New Phone No. (02) 698-8499



## 2 SPECIAL OFFERS ON AMPEX C90 CASSETTES

**AMPEX**

*Grand Master I™*



If you have been using a UD type tape, we now offer you the opportunity to try a really top-end tape at a similar price. Such a tape can generally be recognized by its superior shell design and by its exceptionally smooth high-gloss surface. You would expect to pay six to seven dollars for such a tape. To introduce you to Grand Master I we are offering a limited quantity at

**UNDER \$4**

QUANTITY:	1-4	5-9	10+
PRICE EACH:	\$3.95	\$3.75	\$3.60

**AMPEX**

**360**

**PROFESSIONAL**

Here is an opportunity to stock up on some really good general purpose cassettes at a never-to-be-repeated price. You don't usually find these cassettes in retail outlets; they are intended for professional users, such as government, broadcasting and educational establishments. We have been able to secure a few thousand of these excellent cassettes, which we offer to you at a once-only price of

**UNDER \$2**

QUANTITY:	1-4	5-9	10+
PRICE EACH:	\$1.99	\$1.79	\$1.69

MAIL ORDER CHARGES: 1-20:\$2.75, 20-50:\$3.50, over 50:\$5.00



## PHILIPS LOUDSPEAKERS

### PROFESSIONALLY DESIGNED SPEAKER KITS

If you are in the market for a \$2000 set of speakers with only a few hundred dollars in your pocket, we could have just what you want. The ETI 4000 Series Speakers — using Philips Drivers — compare very favourably with speakers costing twice to three times as much. If you are on a really tight budget you could consider the Philips AD12K12 kit — a 70 watts r.m.s. per channel 12" 3-way system — which you assemble completely in about 2 hours. A steal at under \$300 per pair. You can buy all components with or without boxes, any way you like. We have both the ETI 4000-I and II on display, as well as other Philips Kits. Come in for an audition, or write for further information.





**northpoint hi-fi**

**WAGNER** ELECTRONICS  
SALES & SERVICE

100 Miller St, North Sydney.  
Ph 922-7780.

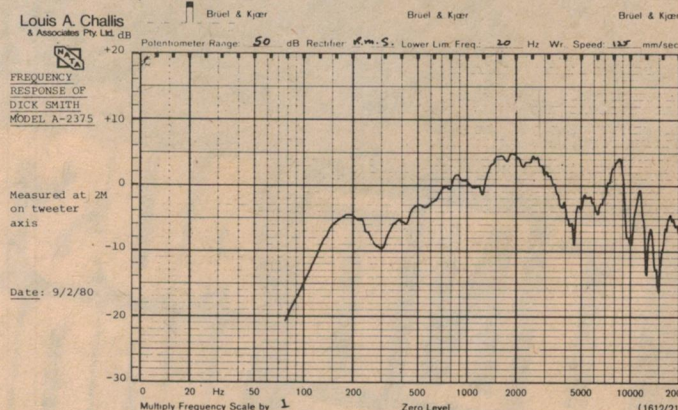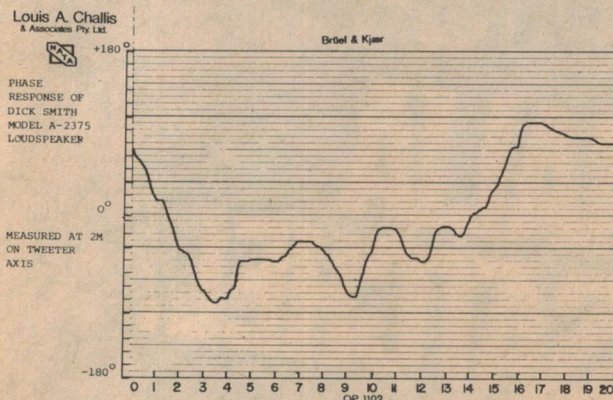305 Liverpool Rd, Ashfield.  
Ph 798-9147.





## Subjectively

The subjective testing of these speakers highlighted a number of features which the objective testing did not. The first of these was the pronounced presence that they possessed. This presence colours speech and provides a most unnatural sound. The second feature was the irremediably poor response at low frequencies.

Soft rock, drums, vibes or even guitar sounds are not reproduced in such a way as to maintain a natural or acceptable sound. While guitars in general may sound reasonable, violins acceptable and a piano almost normal, speech and vocals have a quality and timbre which disturbed me and would disturb most musicians.

I took the opportunity to try out a number of records especially designed for speaker testing but because these speakers have such a very small volume I mainly chose passages which didn't call for a high quality bass response. Nevertheless I found that the test records tended to highlight the lack of bass response, although the system did perform adequately on some passages.

## Summary

Mini speakers have their problems. Although they can sometimes reproduce with surprising fidelity, their small enclosures impose severe limitations at the lowest frequencies. The Dick Smith A2375 speakers provide a passable performance for such a petite envelope and may well be suitable for a first speaker system. But they will not satisfy young people looking for a reasonable bass response, nor the majority of 'oldies' who aspire to a sound of better quality than a shoe box system.

## THE DICK SMITH MODEL A2375 MINI SPEAKER SYSTEM


Dimensions: 190 mm H x 120 mm W x 120 mm D

Weight: Approx 3 kg.

Price: \$99.50 a pair

Manufactured in Taiwan

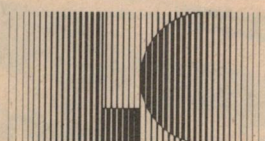Absolute copyright in this review and accompanying measurements is owned by Electronics Today International. Under no circumstances may any review or part thereof be reprinted or incorporated in any reprint or used in any advertising or promotion without the express written agreement of the Managing Editor.



Louis A. Challis and Associates Pty Ltd

### MEASURED PERFORMANCE OF

### DICK SMITH LOUSPEAKER MODEL A-2375

#### FREQUENCY RESPONSE:

100Hz to 12kHz  $\pm$  10dB

#### CROSSOVER FREQUENCIES:

Not detectable

#### SENSITIVITY:

(for 90dB average at 2m)

7.4 VRMS = 6.8 Watts (nominal into 8 $\Omega$ )

#### HARMONIC DISTORTION:

(for 90dB at 2m)

(except at 100Hz which was measured at 80dB)

	100Hz	1kHz	6.3kHz
2nd	-26	-40.5	-36.8 dB
3rd	-33.3	-50.5	-45.8 dB
4th	-45.4	-56.9	-55.2 dB
5th	-39	-61.7	-
THD	5.6%	1.1%	1.5%

#### INPUT IMPEDANCE:


100Hz	12 $\Omega$
1kHz	8.5 $\Omega$
6.3kHz	9 $\Omega$
Minimum at 20kHz	7.5 $\Omega$



**TNT**  
COURIER

# AUSTRALIA WIDE SATCHEL.

**URGENT!**

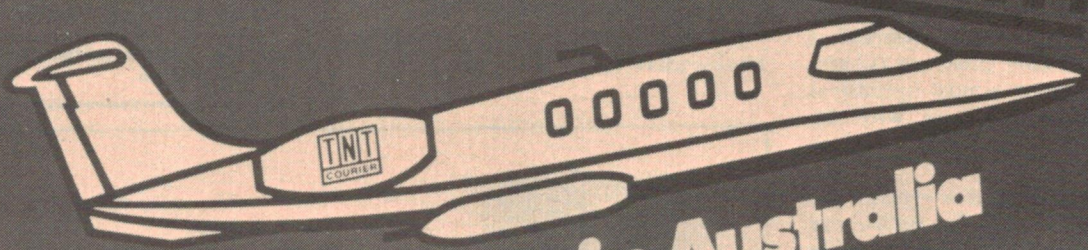

**\*anywhere in Australia  
overnight.**

*\*Anything which fits inside this satchel may be sent almost anywhere in Australia, overnight.*



## Now your newsagent can solve your urgent parcel problems.

This TNT Courier Overnight Satchel has just turned your friendly newsagent into an air freight depot. For \$8.75 you can send anything that fits inside to almost anywhere in Australia. Overnight. You don't have to wrap a thing. The bag is tough, waterproof and tear resistant.

You can buy TNT Satchels at most newsagents throughout Australia. (At present in N.S.W., they are

available only in Sydney, Newcastle, Wollongong, Gosford and A.C.T.). Just address the satchel and leave it with your newsagent. TNT Courier collect it, air freight it overnight and deliver the next morning.

The TNT Courier Suburban Satchel is for overnight local deliveries in all mainland capitals (and soon Hobart) for just \$5.00.

**TNT Courier Overnight Satchels. Anything, anywhere, overnight.**

A Speedy Communications product. \*Anything which fits inside the satchel may be sent almost anywhere in Australia, overnight.





# JBL's 4311 STUDIO MONITOR.

**NOW IT'S  
NOT FOR  
STUDIOS  
ONLY.**



**FIRST  
WITH THE  
PROS.**

JBL, is making its most popular studio monitor available to everyone.

It's a 3-way, high-efficiency system that gives you wide range response. And, because it's compact for use in small studios, and is finished in hand-rubbed walnut, it's perfect for your living room or den. The JBL 4311 compact studio monitor.

For details and demonstrations visit us  
**THE PROFESSIONALS IN JBL**

## insound

PTY. LTD.

108 WEST ST., CROWS NEST  
929 2714 92 1498

SPECIALISTS IN HOME INSTALLATIONS  
AND BUILT-IN SOUND SYSTEMS.

# WHEN IT COMES TO SOUND . . .

*We've been hiring, for the last 5 years, sound systems to many local, interstate & international groups & artists. Now our expertise in equipment knowledge goes into selling the right sound equipment to you! Talk to us first, we'll get your act together!*

**RIGHT FROM THE:**  
MICROPHONES (BEYER/SHURE)  
STANDS/CABLES  
MIXERS (JANDS)  
MXR GRAPHIC EQUALIZERS  
DBX COMPRESSOR/LIMITERS  
CROSSOVER (JANDS)  
POWER AMPS (JANDS)  
JBL SPEAKERS  
'W' BINS  
MID CABINETS  
JBL HORNS  
JBL TWEETERS

**MISCELLANEOUS:—**  
CANNONS  
PIEZOS  
GAFF  
DI BOXES  
SESSIONS  
CATCHES/CORNERS  
MUFFIN FANS  
MODIFICATIONS  
RACK/ROAD CASES  
ETC. ETC.

**SALES & HIRE  
DROP IN OR GIVE US A CALL!**

**DSA CONCERT SYSTEMS**  
156 GIVEN TCE. PADDINGTON 4064  
PHONE (07) 36 6367

# CHEAP TAPES!

**BULK TAPES DISCOUNTED**

## MAXELL

		\$
LN C60	ULTRA LOW NOISE	Box of 12 18.00
LN C90	ULTRA LOW NOISE	Box of 12 25.00
LN C120	ULTRA LOW NOISE	Box of 12 37.00
UD C60	ULTRA DYNAMIC	Box of 12 29.00
UD C90	ULTRA DYNAMIC	Box of 12 35.00
UDXLI C60	EPITAXIAL	Box of 12 38.00
UDXLI C90	EPITAXIAL	Box of 12 48.00
UDXL II C60	EPITAXIAL	Box of 12 40.00
UDXL II C90	EPITAXIAL	Box of 12 50.00

## TDK

		\$
D-C60	DYNAMIC	Box of 10 18.00
D-C90	DYNAMIC	Box of 10 23.00
AD-C60	ACOUSTIC DYNAMIC	Box of 10 28.00
AD-C90	ACOUSTIC DYNAMIC	Box of 10 33.00
SA-C60	SUPER AVILYN	Box of 10 34.00
SA-C90	SUPER AVILYN	Box of 10 43.00
MAR-C60	METAL (METAL CASE)	Each 14.00
MA-C60	METAL	Each 11.00

## SONY

		\$
CHF C60	ORANGE CASE	Box of 10 18.00
CHF C90	ORANGE CASE	Box of 10 24.00
BHF C60	GREEN CASE	Box of 10 24.00
BHF C90	GREEN CASE	Box of 10 28.00
AHF C60	BLUE CASE	Box of 10 29.00
AHF C90	BLUE CASE	Box of 10 39.00

## FUJI

		\$
FL C60	SUPER LOW NOISE	Box of 10 17.00
FL C90	SUPER LOW NOISE	Box of 10 23.00
FXI C60	PURE FERRIX	Box of 10 26.00
FXI C90	PURE FERRIX	Box of 10 31.00
FXII C60	BERIDOX	Box of 10 32.00
FXII C90	BERIDOX	Box of 10 41.00
MC 60	METAL	Each 11.00
MC 90	METAL	Each 14.50

## OPUS

		\$
UD C90	EXT. RESPONSE	Box of 12 25.00
G-C90	G-TAPE LOW NOISE	Box of 20 19.00

### FURTHER DISCOUNTS AVAILABLE ON PURCHASE OF 10 BOXES OR MORE

ADD: PACK & POST —

	VIC.	TAS/SA/NSW	WA/NT/QLD
1 - 2 Boxes	\$1.00	\$2.00	\$3.00
3 - 4 Boxes	\$1.50	\$3.00	\$3.50
5+ Boxes	\$2.00	\$4.00	\$5.00

STOCK AT PRICES SHOWN AVAILABLE  
AT TIME OF GOING TO PRESS

**TO:  
MAIL ORDER CENTRE  
A.M.S. SYSTEMS,  
135 Hawthorn Road,  
CAULFIELD. VIC. 3162.  
PHONE (03) 523-7145.**



# MINI-MART

## Where readers can advertise — For Sale/Wanted/Swap/Join.

• We'll publish up to 24 words (maximum) totally free of charge for you, your club or your association. Copy must be with us by the 1st of the month preceding the month of issue. Please — **please** — print or type adverts clearly, otherwise it may not turn out as you intended! Every effort will be made to publish all adverts received however, no responsibility for so doing is accepted or implied. Private adverts only will be accepted. We reserve the right to refuse adverts considered unsuitable.

• **Conditions:** Name and address plus phone number (if required) must be included within the 24 words. Reasonable abbreviations, such as 25 W RMS or 240 Vac, count as one word. Adverts must relate to electronics, audio, communications, computing etc — general adverts cannot be accepted. Send your advert to:  
**ETI Mini-Mart, Modern Magazines**  
15 Boundary St,  
Rushcutters Bay NSW 2011

### AUDIO

**SELL:** Six hundred LPs, mostly baroque, classical and early romantic. Reason for sale — taping the lot. Enquiries to Henry Smith, P.O. Box 21, Latrobe, Tasmania 7307.

**SELL:** Tonearms; JH Formula 4 \$80, Lustre \$40. JH turntable \$40. DC Pre-amplifier suit DYNA-VECTOR 20B/mk1 \$100. Shure M91ED \$25. Upgrade is only reason for sale. Write to Ray White, P.O. Box 117, Adamstown, NSW 2289. Phone (049) 52-2638 a.h.

Enthusiast seeking Ortofon mono cartridges, long Ortofon arm for above, Micro 202 arm, parts from any — also DA 100 triodes, 5933 pentodes. L. Nelson 307 Bambra Rd, Sth Caulfield, Vic 3162. Phone 689-4411 b.h., 578-1582 a.h.

**HARMON KARDON 500** Integrated valve amplifier, 35 watts/ch original condition, complete with extra set of output tubes and circuit. \$200 o.n.o. Phone (02) 46-5451.

**SELL:** Auditec power amp 110W RMS per channel, short circuit and overload protected. \$500. Phone Louis Ziras (03) 481-1209 at 10 a.m.

**SELL:** Playmaster 25W RMS per channel stereo amplifier and graphic equaliser in perfect condition. \$95 each. Phone Iain Burry (02) 798-5656 (8 a.m. - 4.30 p.m.).

**SELL:** ETI 4600 Synthesizer 85% completed in cabinet, works 100%, \$750 o.n.o. 4/9 Finchaven St, Herne Hill, Geelong, Vic 3218.

**BOSE 901 speakers series IV** unused still in cartons, only \$1090, o.n.o. Philips Motional Feedback Speakers 60w rms unused, \$690. o.n.o. Phone (02) 46-5451 a.h.

### COMMUNICATIONS

**SELL:** Yaesu FT200 TXCVR in excellent condition. Also IC 22A 2m FM TXCVR. Camberwell Grammar School, P.O. Box 151, Balwyn, Vic 3103. Phone (03) 836-6266 ext. 237.

**DX160 receiver 150 kHz to 30 MHz** works like new but no speaker, scungy exterior, \$80. Also three morse cassettes \$10. Phone John (02) 502-4863 after 4 p.m.

**YAESU FT901DM SSB transceiver** with CW and AM filters factory installed, Yaesu microphone, FV901DM external scanning 40 memory VFO, equipment brand new in unopened boxes, surplus to my requirements \$1450.00. James VK2JO, Phone (02) 799-5566 or (02) 36-7756, G.P.O. Box 5076, Sydney, NSW 2001.

**CB RADIO** — Bengal SSB/AM base station with 18ft ringo, separate SWR meter, and approx 30ft coax with plugs. \$250. Write to H. Saharinen, 5 Bartoman St, Batlow, NSW 2730.

**AUSTRALIAN Radio Dx Club** for shortwave, mediumwave Dxers, for a sample copy send one 22c stamp to P.O. Box 79, Narrabeen, NSW 2101 mentioning this ad.

**SELL:** Communications receiver TRIO model 9R59DS in spotless condition, and very little use. Will sell for \$120, P. Theodore, 26 Waratah St, Canterbury, NSW 2193.

**SELL:** Teletype Model 19. Good condition \$60 o.n.o. Write to R. Antaw, P.O. Box 333, Coonababran, NSW 2857. Phone (068) 42-1470 a.h.

### COMPUTERS

**HORIZON II** system dual SSDD disk 32K matrix alphanumeric and graphics boards. ASR33 and monitor. Software Basic, Pascal, 2D and 3D graphics. Details D. Cowie, 21 Dublin St, Clayfield, Qld 4011. (07) 262-3957.

**WANTED:** Mini scamp computer, complete or kit set. Details and price to Box 177, Woden, ACT 2606.

**P.E.T. CBM Minicomputer** as new. Ample software including assembler/editor/disassembler. Full documentation — manuals, circuit diagrams, memory maps, diagnostics — worth \$2000 new, \$1250 ono. Phone Chris (02) 419-4424.

**SORCERER Computer**, 16k RAM and cassette recorder, \$950. Also Development pac \$99; 50bd teletype, \$50. Glen Grigg, 2/22 Hill St, Campsie, NSW 2194. (02) 787-1096 a.h.

**BLACK BOX printer 10 CPS 80 column tractor feed**, including harnesses and power supply for TRS 80 operation with or without expansion interface \$475. Lew Nyeholt (09) 364-7385.

**COPYRIGHT:** The contents of Electronics Today International and associated publications is fully protected by the Commonwealth Copyright Act (1968).

Copyright extends to all written material, photographs, drawings, circuit diagrams and printed circuit boards. Although any form of reproduction is a breach of copyright, we are not concerned about individuals constructing projects for their own private use, nor by pop groups (for example) constructing one or more items for use in connection with their performances.

Commercial organisations should note that no project or part project described in Electronics Today International or associated publications may be offered for sale, or sold, in substantially or fully assembled form, unless a licence has been specifically obtained so to do from the publishers, Modern Magazines (Holdings) Ltd or from the copyright holders.

**LIABILITY:** Comments and test results on equipment reviewed refer to the particular item submitted for review and may not necessarily pertain to other units of the same make or model number. Whilst every effort has been made to ensure that all constructional projects referred to in this edition will operate as indicated efficiently and properly and that all necessary components to manufacture the same will be available no responsibility whatsoever is accepted in respect of the failure for any reason at all of the project to operate effectively or at all whether due to any fault in design or otherwise and no responsibility is accepted for the failure to obtain any components parts in respect of any such project. Further, no responsibility is accepted in respect of any injury or damage caused by any fault in the design of any such project as aforesaid.

**SELL:** 2708 EPROM programmer board with software driver and full details, \$100. 1200 baud cassette interface with connection and operating details, \$100. W. Geary, Koolan Island, WA 6733.

**SELL:** Ithica Audio 4 MHz Z80 Processor, three 8k 250 ns. RAM cards DG 640 VDU card. \$130 ea. \$600 the lot. 18 slot mother board 10 connectors \$80. Keith Dick (02) 359-2384 b.h., (02) 665-2044 a.h.

**SELL:** "DREAM 6800" ICs 2x2708 programmed chips \$11 each, 1xMC6800L \$9, 1x6820 \$5, all working, will separate. C. Rogers, 8 Buchanan Rd, Berwick, Vic 3806.

**WANTED:** Plans for computer for beginner (photocopies, etc). D. Howe, 7 Royston Place, Gladstone Park, Vic 3043. (03) 338-6010.

2650 mini computer, VDU, 4k RAM, x-tal CLK, keyboard, cassette interface, BASIC, lots software, manuals etc. \$400 o.n.o. Phone Paul (VK3YRS) (03) 336-7471.

**SELL:** DREAM 6802, with power supply in cabinet, plus programs, no bugs. \$170. R. Patterson (08) 258-8647. 20 Donegal St, Salisbury Downs, 5108.

**S2650 PIPBUG** — compatible machine language programs. Program relocater, clock & day calculator, noughts and crosses. Listings and instructions. \$4 each. Phone Chris (02) 411-3618 after 6 p.m.

**SELL:** 57 key ASCII keyboard. As new — unused \$90 o.n.o. D. Stuart-Smith, 98 Grasmere Rd, Cremorne, NSW 2090. (02) 90-1473.

Baby 2650 unopened (still sealed) chassis, 3 books and keyboard. Also partly built encoder ETI April '77, including 10 ICs. J. Crooks, (02) 95-1683.

**TRS-80 "Keyboard Music"** program lets you play music directly using your TRS-80 keyboard. Send \$12 (inc P&P) to J. Zelnik, 14/446 Pacific Highway, Artamon, NSW 2066. (02) 427-5982 after 7 p.m.

**SELL:** Centronics Microprinter P.1. As new, print 20, 40 or 80 characters per line. Parallel interface \$350. Peter Wearne, Eilerslie, Vic 3265. (055) 99-6222.

**WANTED:** To buy or borrow — users manual for Percom LFD400 diskette system. Geoff Drury, 27 Creslin Tce, Camden Park, 5038. (08) 295-2778.

**CHESS COMPUTER**, Chess Challenger level-10 \$299. DG-640 VDU card with manual \$100. ASCII encoded keyboard \$70. All brand new, unused! 55 Ryan Place, Beacon Hill, NSW2100. (02) 938-5432.

**WOLLONGONG Computer Club** requires members. Phone Paul (042) 61-5451.

**OSI SUPERBOARD II** or Challenger 1P users in Adelaide, I would like some information please. Phone Mark 298-2549.

6800-9 SS50 BUS computer user would like to contact other users to exchange information ideas programs etc. Ray Evans (066) 46-6173, or P.O. Box 36, Iluka, NSW 2460.



**SELL:** EME-1, brand new, plus resistors, sockets, etc, plans, conversion tables and wires included. Will sell all from \$25. Benjamin, 48a Malton Rd, Beecroft. (02) 848-8141.

**SELL:** Challenger 1P, 4K RAM \$359. 4K expansion RAM \$50. 610 expansion board for Challenger 1P \$200. 21 Beltana St, Ryde. (02) 807-3951.

**SELL:** One only KTM2 VDU normally \$400 will accept \$350 o.n.o., or swap for Superboard II. Phone G. Dicker (08) 332-2389 b.h., (08) 278-7147 a.h.

**JOIN** the Ohio Superboard User Group. Send S.A.E. to "Ohio Superboard User Group", 146 York St, Nundah, Qld 4012 for full details and a free graphics chart.

**SELL:** Video terminal, has 63-key keyboard. Accepts serial or parallel data. Use with almost any micro. \$250 o.n.o. (042) 55-8087.

**MICROPOLIS** Dual Drives Quad Density 630K Model 1053 as new with manuals/software 30 day warranty, suit Sorcerer or other \$100 \$1500 (02) 450-1716.

**SELL:** Data Entry Terminal Olivetti Model DE521, v.good condition, \$800 o.n.o. Keith Dick (02) 359-2384 b.h., (02) 665-2044 a.h.

**SELL:** SYM-1, 8K RAM and 8K BASIC \$380. KTM-2 keyboard/terminal \$300. Power supply +5V@10A/+/-12V@1A \$50. Dick Smith Video Monitor \$125. B. Williamson, 216 Wirruna Av, Woomera, SA 5720.

**SELL:** TRS-80 16K memory. Level II BASIC computer includes video monitor, cassette recorder, keyboard, all original Tandy equipment, no cheapie upgrade. Included extensive range of software value \$750. The lot \$825. O. Fleming (075) 32-4810.

**OLIVETTI** TE300 Computer Terminal, 150 Baud, R5232, 120 character thirteen inch tractor feed paper, ASCII keyboard and numeric keypad, solid unit, \$350. (03) 418-6337 b.h., (03) 288-2191 a.h.

**TRS-80** Level II, 16K RAM recorder, monitor, keyboard software, as new \$850. (03) 873-3820.

**TRS-80** Level II inc. power supply manuals & cables \$850, monitor \$100, cassette recorder \$30. (02) 939-1576.

**NORTHSIDE** computer owners and users. Our club meets on the 2nd Monday of the month at Manly Youth Centre, Kangaroo St, Manly, NSW.

**WOLLONGONG** Computer Club, wishes to exchange software etc with other individuals and clubs, CPUs involved 6502, 6800, Z80, 8085, etc. (042) 61-5451.

### MISCELLANEOUS

**SELL:** Philips Video Recorder N1500 VHF play-back \$250 o.n.o. K. Dick 359-2384 b.h., 665-2044 a.h.

Valve and circuit tester Model University TST/2 complete with instruction manual and circuit. Phone (02) 46-5451.

**WANTED:** Unbuilt ETI-140 IGHZ frequency meter — timer kit. Phone 7.30 - 9.30 p.m. 870-4017 or write Mark Barber, 8 Hilldale Close, Ringwood, Vic 3134.

**TRANSFORMERS:** 240 to 24 volts, 1 kva. In mounting boxes with circuit protection. Very cheap (02) 827-3778 (preferably mornings or late nights).

**WANTED:** Valves, new or s/h, 6M5 6A8. F. King, 161 Longueville Rd, Lane Cove, NSW 2066. (02) 427-2626.

**WANTED:** IC Chip AY-3-8760 for TV cycle game. Barry Moon, 26 Beaufort St, Mitcham, Vic 3132. (03) 874-3463.

**Alternative Technology Co-operative.** People interested and involved in the use of alternative technology and energy sources. Details A.T.Co-op, 366 Smith St, Collingwood, Vic 3066, enclose 30c stamp.

**WANTED:** Practical Wireless Jan 80 for collection. Will pay \$2 and postage. Write B. McDonald, 46 Aberdare St, Kitchener, NSW 2325.

**WANTED:** Circuit diagram etc for Yunker Electronics Universal Counter Mod 185U. Will pay copying costs etc. J. Brown-Sarre, Box 82, Red Cliffs, Vic 3496.

# What oil shortage?

Australia is about to try and ring more drops of oil from the same old wells. And new oil from several new sources. If we succeed, by 1990 we may only have to import 12% of our needs.

## The drought of 1981.

Some rains have come, but this year's drought's long term effects will last for years.


## Making a buck out of the bush.

Overlander tells you how and where.

August Overlander.  
Because there's an  
Australia outside  
the city.



# overlander

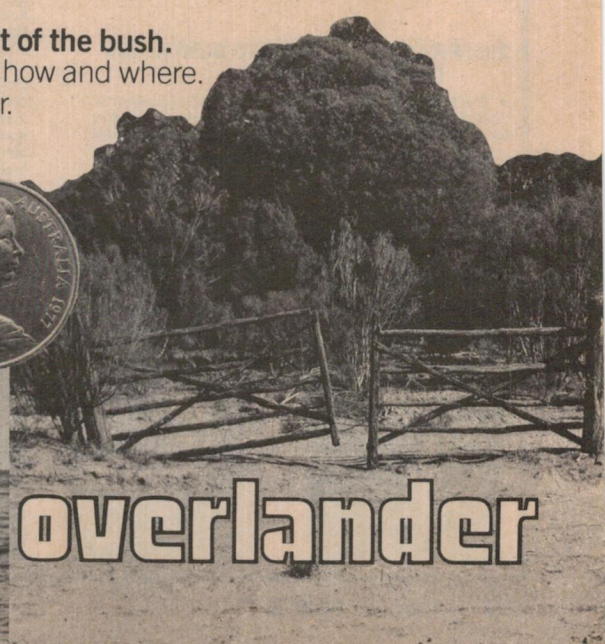



# Radio & Electronics Books

**BERNARD BABANI (publishing) LTD**

**160: COIL DESIGN & CONSTRUCTION MANUAL**  
B.B. Babani

- Complete book on how to design and make RF, IF, audio and power coils, chokes and transformers. Every type is discussed and calculations given. Covers AM and FM radio and TV.

96 pages

Price \$2.25

**202: HANDBOOK OF ICs EQUIVALENTS AND SUBSTITUTES.**  
B.B. Babani

- One of the most complete IC equivalent and substitute guides yet published. Full data on over 9500 ICs. Covers digital and linears of all types from UK, USA, Japan, Germany, France, Czechoslovakia etc.

128 pages

Price \$3.00

**221: 28 TESTED TRANSISTOR PROJECTS**  
R. Torrens

- Some circuits are completely new — others are more familiar designs. The projects can be split into simple building blocks to enable readers to combine circuits for specialised needs.

96 pages

Price \$3.75

**224: 50 CMOS IC PROJECTS**  
R.A. Penfold

- CMOS ICs are suitable for an extraordinarily wide range of applications, are cheap and easy to obtain. Here are a number of interesting and useful projects in four general categories: (1) Multivibrators, (2) Amplifiers and oscillators, (3) Trigger devices, (4) Special devices.

112 pages

Price \$2.85

**225: PRACTICAL INTRO TO DIGITAL ICs**  
D.W. Easterling

- This book introduces the reader to digital ICs (mainly TTL 7400 series). Besides a number of simple projects, contents include details of a Logic Test Set which enables constructors to identify and test digital ICs. Also includes digital counter-timer.

80 pages

Price \$2.85

**227: BEGINNERS GUIDE TO BUILDING ELECTRONIC PROJECTS**  
R.A. Penfold

- Enables total beginners to tackle practical electronic so he or she can confidently build electronics projects such as published in ETI and other magazines and books. Subjects include component identification, tools, soldering, various building methods, cases, legends etc. Practical basic projects are also included.

112 pages

Price \$3.75

**BP1: 1ST BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES**  
B.B. Babani

- Complete transistor equivalents guide. More than 25 000 transistors with alternatives and equivalents. Covers devices made in UK, USA, Japan, Germany, France, Europe, Hong Kong etc. See also BP 14 (below).

80 pages

Price \$2.25

**BP 14: 2ND BOOK OF TRANSISTOR EQUIVALENTS AND SUBSTITUTES**  
B.B. Babani

- The second book contains data on devices not included in the first. This book supplements BP1, no data is duplicated.

208 pages

Price \$3.50

**BP 24: 52 PROJECTS USING IC 741**  
Rudi & Uwe Redmer

- Originally published in German, this book achieved huge European sales. Now translated into English with copious notes, data and circuits, this book is a must for those interested in any way in this inexpensive and most versatile IC.

80 pages

Price: \$2.85

**BP 33: ELECTRONIC CALCULATOR USERS HANDBOOK**  
M.H. Babani

- An invaluable book for all calculator users. Presents formulae, data, methods of calculation, conversion factors etc, often with examples. Includes way to use simple four-function calculator for Trig functions (sin, cos, tan); Hyperbolic functions (sinh, cosh, tanh), Logs, Square Roots & Powers.

Comprehensive conversion factors incorporated, including length, area, volume & weight through specialised conversions such as viscosity, illumination, cargo shipping measures etc. Also formulae for discounts and mark-up, currency conversions, interest, solutions of equations, binary and octal numbers, areas and volumes, stats and maths etc.

208 pages

Price \$2.85

**BP 36: 50 CIRCUITS USING GERMANIUM, SILICON, ZENER DIODES**  
R.N. Soar

- Contains 50 interesting and useful circuits and applications in many different branches of electronics.

64 pages

Price \$2.25

**BP 37: 50 PROJECTS USING RELAYS, SCRs & TRIACS**  
F.G. Rayer

- Relays, SCRs and Triacs have a wide range of applications — from motor speed control, dimming, heating, timers, light-sensitive circuits, warning devices, light modulators, priority indicators, circuit breakers etc. Book gives tried and proven circuits which will tolerate wide latitude of components and values allowing easy modification to suit special needs.

112 Pages

Price \$3.75

**BP 39: 50 (FET) FIELD EFFECT TRANSISTOR PROJECTS**  
F.G. Rayer

- Field effect transistors are used in many circuits. The projects here include amplifiers and converters, test equipment and receiver aids, tuners, receivers, mixers and tone controls, plus miscellaneous devices. The FET used is not critical and many other types will work as well. This book will be of interest to all enthusiasts, shortwave listener, radio amateur, hi-fi buff or general electronics experimenter.

112 pages




Price \$3.75

**BP 40: DIGITAL ICs AND PIN CONNECTIONS**  
Adrian Michaels

- Equivalents and pin connections of a popular user-orientated selection of digital ICs. Shows details of packaging, families, functions, manufacturer and country of origin. Includes devices by Fairchild, Ferranti, Harris, ITT, Motorola, National, Philips, RCA, Signetics, Sescocem, SGS-Ates, Siemens, SSSI, Stewart Warner, AEG-Telefunken, Texas, Teledyne. Companion volume to BP 41 — Linear ICs.

320 pages

Price \$7.50

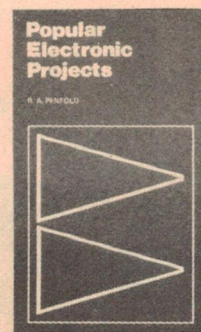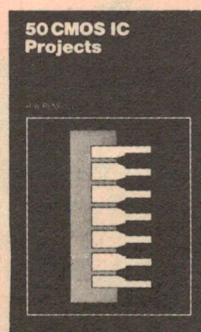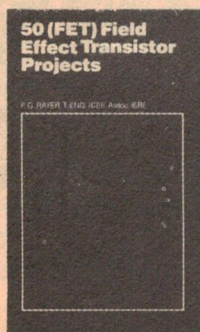



**BP 41: LINEAR IC EQUIVALENTS  
AND PIN CONNECTIONS**  
Adrian Michaels

• Essentially similar in concept to above but deals with linear integrated circuits.  
**320 pages** **Price \$8.25**

**BP 42: 50 SIMPLE LED CIRCUITS**  
R.N.Soar

• 50 interesting and useful circuits and applications using LEDs. A useful book for beginner and advanced enthusiast alike.  
**64 pages** **Price \$2.25**

**BP 44: IC 555 PROJECTS**  
E.A.Parr

• Every so often a device is made that is so useful one wonders how life went on before it! The 555 IC is one such. First made by Signetics it is now manufactured by almost everyone in the business. It is very cheap and readily obtainable.  
Included in this book are basic and general circuits, motor car and model railway circuits, alarms and noise makers plus a section on the subsequent 556, 558 and 559 devices.  
**160 pages** **Price \$5.25**

**BP 45: PROJECTS IN  
OPTO-ELECTRONICS**  
R.A.Penfold

• Opto-electronic projects of interest to all electronics enthusiasts. Included are simple circuits using ordinary LEDs as well as more sophisticated designs such as infra-red transmitters and receivers, modulated light transmission and photographic projects.  
**112 pages** **Price \$3.75**

**BP 47: MOBILE DISCO HANDBOOK**  
Colin Carson

• Most people who start mobile discos know little about equipment or what to buy. This book assumes no preliminary knowledge and gives enough info to enable you to have a reasonable understanding of disco gear.  
**128 pages** **Price \$4.15**

**BP 48: ELECTRONIC PROJECTS FOR  
BEGINNERS**  
F.G.Rayer

• This book gives the newcomer to electronics a wide range of easily built projects. Actual component and wiring layouts aid the beginner. Some of the projects may be built without using soldering techniques.  
**128 pages** **Price \$4.15**

**BP 49: POPULAR ELECTRONIC  
PROJECTS**  
R.A.Penfold

• A collection of the most popular types of circuits and projects covering radio, audio, household and test equipment.  
**144 pages** **Price \$4.35**

**BP 51: ELECTRONIC MUSIC AND  
CREATIVE TAPE RECORDING**  
M.K.Berry

• This book shows how electronic music can be made at home with simple and inexpensive equipment. It describes how sounds are created and recorded to build up a final composition. It shows how to build a small studio including mixer and various sound effects units.  
**96 pages** **Price \$3.75**

**BP 53: PRACTICAL ELECTRONIC  
CALCULATIONS AND FORMULAE**  
F.A.Wilson

• This book is for the practical person's workshop bench. It bridges the gap between technical theory and cut-and-ried methods which may work but leave the experimenter unfulfilled. There's a strong practical bias. Tedious and higher maths has been avoided where possible. Many tables are included. This one's a beauty!  
**256 pages** **Price \$6.75**

**BP 56: ELECTRONIC SECURITY  
DEVICES**  
R.A.Penfold

• Simple and more sophisticated burglar alarms using light, infra-red and ultrasonics; also other types of alarm such as gas and smoke detectors, flood alarms, doorphone and baby alarms etc.  
**112 pages** **Price \$4.35**

**ELEMENTS OF ELECTRONICS**  
F.A.Wilaon

**BP 62 — Book 1**

**BP 63 — Book 2**

**BP 64 — Book 3**

• This series provides an inexpensive intro to modern electronics. Although written for readers with no more than basic arithmetic skills, the use of maths is not avoided — all the maths is taught as the reader progresses.  
The course concentrates on the understanding of concepts central to electronics rather than continually digressing over the whole field — on the basis that once the fundamentals are mastered, the workings of most other things are soon revealed. The author anticipates where the difficulties lie and guides the reader through them.

Book 1 . . . All the fundamental theory necessary to a full understanding of simple electronic circuits and main components.

Book 2 . . . Alternating current theory.

Book 3 . . . Semiconductor technology leading to transistors and ICs.

These three books constitute a complete, inexpensive electronics theory course of inestimable value in either hobby or career.

**224 pages** **Price \$6.75 (each volume)**

**BP 65: SINGLE IC PROJECTS**  
R.A.Penfold

• All projects in this book are simple to build and are based on a single IC. A few projects use one or two transistors in addition. A strip board layout is provided for each project together with special constructional points and setting up info. The five chapters are: Low level audio, Audio power amps, Timers, Op-amps, Miscellaneous circuits.  
**128 pages** **Price \$4.50**

**BP 66: BEGINNERS GUIDE TO  
MICROPROCESSORS AND  
COMPUTING**  
E.F.Scott

• An introduction to basic theory and concepts of binary arithmetic, microprocessor operation and machine language programming. The only prior knowledge assumed is very basic arithmetic and an understanding of indices.  
**128 pages** **Price \$5.25**

**BABANI BOOKS — MAIL ORDER, DIRECT FROM ETI !**

Please send me:

Book	Qty.	
160	...	BP41
202	...	BP42
221	...	BP44
224	...	BP45
225	...	BP47
227	...	BP48
BP1	...	BP49
BP14	...	BP51
BP24	...	BP53
BP33	...	BP56
BP36	...	BP62
BP37	...	BP63
BP39	...	BP64
BP40	...	BP65
		BP66

Post & handling:

1 - 4 books:	\$1.10
5 - 10 books:	\$2.70
11 - 20 books:	\$3.50
over 20 books:	\$5.00

I enclose \$ . . . . . (inc. p & h.)

Name . . . . .

Address . . . . .

. . . . . postcode . . . . .

Send to: ETI 'Book Sales', 3rd Floor,  
15 Boundary St, Rushcutters Bay NSW 2011.  
Please allow 4 - 5 weeks for delivery.



# KITS for projects

WE GET MANY enquiries from readers wanting to know where they can get kits for the projects we publish. This list is a guide to suppliers of kits and components for ETI projects.

We have listed here most of the projects published over the last few years which are either available as kits or can still be made up by shopping around for components. Suppliers listed against a particular project will either stock it as a kit or stock the pc board plus the other components.

## Printed circuit boards

Those suppliers listed against specific projects here are able to supply pc boards for those projects. Printed circuit boards for every project ever published in ETI are available through the following companies (to the best of our knowledge):

RCS Radio Radio Despatch Service  
651 Forest Rd 869 George St  
Bexley NSW Sydney NSW 2000

For current projects and a more comprehensive list of pc board suppliers refer to the Shoparound page in this and previous issues. This list will be updated roughly every four months.

## Key to Companies

- A Applied Technology Pty Ltd, 1A Pattison Avenue, Waitara, NSW 2077. Ph. (02) 487-2711.
- B Bill Edge Electronic Agencies, 115 Parramatta Road, Concord (PO Box 1005, Burwood North 2134). Ph. (02) 747-6472.
- C J.R. Components, PO Box 128, Eastwood, NSW 2122. \*Ph. (02) 85-3976.
- D Dick Smith Electronics P/L, Cnr Waterloo & Lane Cove Roads, North Ryde, 2113. Ph. (02) 888-3200.
- E All Electronic Components, 118 Lonsdale Street, Melbourne, Vic 3000. Ph. (03) 662-3506.
- F Tasman Electronics, 12 Victoria Street, Coburg, Vic 3058. Ph. (03) 354-5062.
- J Jaycar Pty Ltd, PO Box K39, Haymarket, NSW 2000. Ph. (02) 211-5077.
- K S M Electronics, 10 Stafford Court, Doncaster East, Vic 3109. Ph. (03) 842-3950.
- L Ellistronics, 289 Latrobe Street, Melbourne, Vic 3000. Ph. (03) 602-3282.
- M Mode Electronics, PO Box 365, Mascot, NSW 2020. Ph. (02) 666-6324.
- N Nebula Electronics Pty Ltd, 15 Boundary Street, Rushcutters Bay, NSW 2011. Ph. (02) 33-5850.
- O Orbit Electronics, PO Box 7176, Auckland, New Zealand.
- P Pre-Pak Electronics, 1A West St, Lewisham, NSW. Ph. (02) 569-9797.
- R Rod Irving, PO Box 135, Northcote, Vic 3070. Ph. (03) 489-8131.
- V Silicon Valley, 23 Chandos Street, St. Leonards, NSW 2065. Ph. (02) 439-4655.
- W Willis Electronics, 993 Hay Street, Perth, WA 6000. Ph. (09) 321-7609.
- Y Trilogy, 40 Princes Highway, Fairy Meadow, NSW 2519.

## Project Electronics

- 041 Continuity Tester ..... W,R,D,B,Y,L
- 042 Soil Moisture Indicator ..... R,B
- 043 Heads or Tails Circuit (Oct 76) ..... W,R,D,E,A,F,B,Y,L
- 044 Two Tone Door Bell (Oct 76) ..... W,R,D,E,O,A,F,B,Y,L
- 045 500 Second Timer ..... W,D,E,A,B,Y,L
- 047 Morse Practice Set ..... W,D,O,A,B,Y,L
- 048 Buzz Board ..... W,D,A,B,Y,L
- 061 Simple Amplifier (Oct 76) ..... W,R,D,E,A,B,Y,L
- 062 Simple AM Tuner (Mar 77) ..... W,D,E,B,Y
- 063 Electronic Bongos ..... R,D,A,B,Y,L
- 064 Simple Intercom (Nov 76) ..... W,A
- 065 Electronic Siren ..... W,R,D,E,O,A,B,Y,L
- 066 Temperature Alarm (Dec 76) ..... W,D,E,A,B,Y,L
- 067 Singing Moisture Meter ..... D,B,Y
- 068 LED Dice Circuit (Oct 76) ..... Y,W,R,D,E,A,B,L
- 070 Electronic Tie Breaker (Jan 77) ..... R,E,F
- 071 Tape Noise Limiter (Jun 78) ..... W,D,B,Y
- 072 Two-Octave Organ (Jun 78) ..... W,D,B,Y
- 081 Tachometer (Mar 77) ..... W,E,O
- 082/
- 528 Intruder Alarm ..... W,R,E,A
- 083 Train Controller ..... Y,W,R,E,L
- 084 Car Alarm ..... W,R,D,E,A,B,Y,L
- 085 Over-rev Alarm ..... W
- 086 FM Antenna ..... W
- 087 Over-LED ..... Y,W,E
- 088 Hi-Fi Speaker ..... W

## Test Equipment

- 132 Experimenter's Power Supply (Feb 77) ..... E,O
- 133 Phase Meter (Apr 77) ..... E
- 134 True RMS Voltmeter (Aug 77) ..... E
- 135 Digital Panel Meter (Oct 77) ..... E
- 136 Linear Scale Capacitance Meter (Mar 78) ..... W,D,E
- 137 Audio Oscillator (May 78) ..... E,B
- 138 Audio Wattmeter (Nov 78) ..... E,B
- 139 SWR/Power Meter (May 78) ..... C
- 140 1GHz Frequency Meter-timer (Mar 78) ..... C
- 141 Logic Trigger (Jan 79) ..... E
- 142 High Current Power Supply (Feb 79) ..... W,E
- 143 Curve Tracer (Jan 79) ..... W
- 144 Expanded-scale RMS Voltmeter (Jun 79) ..... E
- 148 Versatile Logic Test Probe (Jul 79) ..... E,L

## Simple Projects

- 243 Bip Beacon (Apr 77) ..... F
- 244 Alarm Alarm (Feb 77) ..... F
- 245 White Line Follower (Nov 77) ..... F
- 246 Rain Alarm (Apr 78) ..... F
- 248 Simple 12V to 22V Converter (Jul 78) ..... W
- 249 Electronic Combination Lock (Apr 79) ..... E
- 252 The Passionmeter (Aug 79) ..... Y,W
- 253 Electronic Grenade (Hot Potato) (May 79) ..... Y,W
- 254 Egg Timer (Jun 79) ..... Y,W

## Motorists' Projects

- 316 Transistor Assisted Ignition (May 77) ..... W,E,O,K
- 317 Rev. Monitor Counter (Jul 77) ..... W,E,K
- 318 Digital Car Tacho (Jul 78) ..... W,E,K
- 319 Variwiper MK II (Sep 78) ..... W,E,O
- 320 Battery Condition Indicator (Apr 79) ..... Y,E,L

## Audio Projects

- 448 Disco Mixer (Nov 76) ..... W
- 449 Balanced Microphone Amp (Nov 76) ..... W,D,E,J,F,Y
- 450 Bucket Brigade Audio Delay Line (Dec 77) ..... W,E
- 451 Hum Filter (Jul 79) ..... D,E,F
- 455 Class A Headphone Amp (Nov 78) ..... Y,W,R,E,F,B,P,L,A,V
- 470 60 W Amp Module (May 79) ..... W,R,E,F,B,P,A,V,L
- 471 High Performance Stereo Preamplifier Control Unit (Jun 79) ..... W,R,E,F,B,P,A,V,L
- 472 Power Supply — the Series 4000 Stereo Amp (Jul 79) ..... W,R,E,F,B,V,L
- 473 Series 4000 Moving-coil Cartridge Preamplifier ..... F,J
- 480 50-100 Watt Amp Modules (Dec 76) ..... W,R,D,E,J,O,Y,L
- 481 12V 100 Watt Audio Amp (May 77) ..... R,E
- 482 High Power PA/Guitar Amp (Jun 77) ..... W
- 482 Stereo Amp (Jan 77) ..... O,E
- 482 Stereo Amp Part 2 (Feb 77) ..... O,E
- 483 Sound Level Meter (Feb 78) ..... E
- 484 Simple Compressor Expander (Jul 77) ..... Y,W,E,J,O
- 485 Graphic Equaliser (Jun 77) ..... J
- 486 Howl-round Stabiliser (Nov 77) ..... E
- 487 Audio Spectrum Analyser (Feb 78) ..... E,J
- 489 Audio Spectrum Analyser 2 (Apr 78) ..... E,J
- 490 Audio Compressor (Dec 78) ..... W,E
- 491 Simple Graphic Equaliser (Mar 79) ..... W,E
- 495 Transmission Line Speakers (Aug 77) ..... W,E

## Miscellaneous

- 546 GSR Monitor (Mar 77) ..... W,E
- 547 Telephone Bell Extender (Jun 77) ..... E
- 548 Photographic Strobe (May 77) ..... W,E
- 549 Induction Balance Metal Detector (May 77) ..... Y,W,D,E,L
- 550 Digital Dial (Aug 78) ..... E,O
- 551 Light Chaser (Sep 78) ..... W,E,O
- 552 LED Pendant (Sep 78) ..... E
- 553 Tape/Slide Synchroniser (Oct 78) ..... E
- 556 Wind Speed/Direction Indicator (Dec 78) ..... E
- 557 Reaction Timer (Feb 79) ..... E
- 558 Mast-head Strobe (Feb 79) ..... E
- 559 Cable Tester (Mar 79) ..... W
- 575 Portable Fluorescent Light Wand for Car, Camping (Aug 79) ..... J
- 577 General Purpose Power Supply ..... W,E,Y
- 581 Dual Power Supply (Jan 77) ..... W,E,O,A
- 582 House Alarm (Jul 77) ..... W
- 583 Installation Instructions (Aug 77) ..... D,E,M
- 583 Marine Gas Alarm (Aug 77) ..... R,D,E,O,F
- 585 Ultrasonic Switch (Sep 77) ..... E
- 586 Shutter Speed Timer (Oct 77) ..... N
- 587 UFO Detector (May 78) ..... E
- 588 Theatrical Lighting Controller (Nov & Dec 77 Jan & Mar 78) ..... N
- 589 Digital Temperature Meter (PCB135) (Dec 77) ..... E
- 590 LCD Stopwatch (Oct 78) ..... O,N
- 591 Up/Down Presettable Counter (Jul 78) ..... D,E
- 592 Light Show Controller (Aug 78) ..... E
- 593 Colour Sequencer (Dec 78) ..... E
- 594 Development Timer (Apr 79) ..... E
- 595 Aquarium Lamp Controller (May 79) ..... E

## Electronic Music

- 602 Mini Organ (Aug 76) ..... W,D,E,Y
- 603 Sequencer (Aug 77) ..... W
- 604 Accentuated Beat Metronome (Sep 77) ..... E
- 605 Temp Stabilized Log-exponential Converter (Sep 78) ..... E

## Computer Projects

- 630 Hex Display (Dec 76) ..... E,A
- 631 ASCII Keyboard (Dec 76) ..... W,E,O,A
- 631 Keyboard Encoder (Apr 77) ..... W,E,O,A
- 632 Video Display Unit (Jan 77) ..... E,O
- 633 TV Sync Generator (Jan 77) ..... E
- 634 8080 Educational/Prototyping Interface (Jul, Aug 78) ..... O
- 635 Microcomputer Power Supply (Sep 77) ..... V,E,A
- 637 Cuts Cassette Interface (Jun 78) ..... W,E
- 638 Eprom Programmer (Jul 78) ..... A
- 639 Computerised Musical Doorbell (Mar 78) ..... W,O,A,V
- 640 S100 VDU (Apr, May, Jun 78) ..... O
- 641 S100 Printer (Sep 78) ..... K
- 642 16k S100 RAM Card (Feb 79) ..... E,L
- 650 STAC Timer (Nov 78) ..... E
- 651 Binary to Hex Number Converter (Jun 79) ..... E
- 680 Z-80 based CPU (Nov, 79) ..... A

## Radio Projects

- 712 CB Power Supply (Jun 77) ..... W,E
- 713 Add-on FM Tuner (Sep 77) ..... W,D,E,A,Y
- 714 VHF-Log-Periodic Antenna (Feb, Mar 78) ..... E
- 715 VHF Power Amplifiers (Nov 77) ..... W,D,E,A,Y
- 716 VHF Power Amplifiers (Jan, Feb 78) ..... E
- 717 Crosshatch Generator (May 78) ..... W,D,E,A,Y
- 718 SW Radio (Oct 78) ..... E
- 719 RF Field Strength Indicator (Nov 78) ..... W,E
- 720 2m VMOs Power Amp (Jan 79) ..... W,E
- 721 Aircraft Band Converter (Mar 79) ..... E
- 722 Antenna for Aircraft Band Converter (May 79) ..... D,E,B
- 724 Microwave Oven Leak Detector (Jul 79) ..... E,L
- 725 Simple SSB Generator employs Polyphase Network using Standard Components (Aug 79) ..... E,L
- 730 Get Going on Radioteletype (Aug 79) ..... E,L

## Electronic Games

- 804 Selectagame (Nov 76) ..... O
- 804 Selectagame (Rifle Project) (Mar 77) ..... O
- 805 Puzzle of the Drunken Sailor (Oct 77) ..... O
- 806 Skeet (Jan 78) ..... O
- 810 Stunt Cycle TV Game (Jun 78) ..... D,O
- 811 TV Tank Game (Oct 78) ..... O
- 812 Wheel of Fortune (Dec 78) ..... O
- 813 Race Track Game (Jan 79) ..... O
- 814 The 'Dinky-Die' (Aug 79) ..... O



# eti

Editor

**Roger Harrison VK2ZTB**

Technical Editor

**David Tilbrook VK2YMI**

Project Manager

**Phil Wait VK2DKN**

Editorial Staff

**William Fisher B.Sc. (Hons)**

**John Pollard M.A., Ph.D.**

**Jonathan Scott B.Sc. (Hons)**

**Jan Vernon B.A.**

Art Direction and  
technical photography

**Ivy Hansen**

Layout

**Bill Crump**

Reader Services

**Jan Collins**

Managing Editor

**Collyn Rivers**

Acoustical Consultants

**Louis Challis & Associates**

Editorial and Sales Office  
**4th Floor, 15 Boundary St  
Rushcutters Bay NSW 2011  
Ph: 33-4282; Tlx: 27243**

Sales Manager: **Bob Taylor**  
Sales Admin: **Jan Collins**  
(address as above)

#### Melbourne

Tom Bray  
150 Lonsdale St  
Melbourne Vic 3000  
Ph: 662-1222; Tlx AA34543

#### Adelaide

Admedia Group  
24 Kensington Rd  
Rose Park SA 5067  
Ph: 332-8144; Tlx AA82182

#### Brisbane

Geoff Horne Agencies  
60 Montanus Drive  
Bellbowrie QLD 4070  
Ph: 202-6229

#### Hobart

H.W. Lincolne  
23 Lord St  
Sandy Bay Tas 7005  
Ph: 34-2630

#### Perth

Aubrey Barker  
133 St Georges Terrace  
Perth WA 6000  
Ph: 322-3184; Tlx: AA93810

#### New Zealand

Geoff Collins  
P.O. Box 39163  
Tel: (9)760-150  
Auckland NZ

#### United Kingdom

Australian Consolidated Press  
Ludgate House  
107 Fleet St  
London EC4A 2AL  
Ph: 353-1040; Tlx: 267163

#### Japan

Genzo Uchida  
Banco Media Services  
15 Sanyocho  
Shinjuku-Ku  
Tokyo 160  
Ph: 359-8866  
Cable: Elbanchorito

#### USA

George McGann  
Australian Consolidated Press  
444 Madison Avenue  
New York NY 10022  
Ph: 751-3383; Tlx: 620892

Electronics Today International is published by Modern Magazines (Holdings) Ltd, 15 Boundary St, Rushcutters Bay, NSW 2011. It is printed (in 1980) by Wilke & Co, Browns Rd, Clayton, Victoria and distributed by Gordon and Gotch. Recommended retail price only.

## Reader Enquiries

**By Mail:** There is no charge for replies but a foolscap-size stamped addressed envelope **must** be enclosed. Queries relating to projects can **only** be answered if related to the item as published. We cannot advise on modifications to projects, other than errata or addenda, nor if a project has been modified or if components are otherwise than specified. We try to answer letters as soon as possible. Difficult questions may take time to answer.

**By phone:** We can only answer readers' technical enquiries by telephone **after 4.30 pm**. In enquiring by telephone about back issues or photostats, please ask for the "Subscriptions Department".

33-4282

## ORDER FORM

I enclose \$..... for (tick appropriate box/es):

NAME .....

ADDRESS .....

POSTCODE .....

- ☐ Subscriptions \$21.50 per year within Australia \$...  
\$27.00 overseas (surface mail) \$...  
Airmail rates on application.  
☐ Back issues (\$2.50 from April 1977 on)  
☐ or photocopies (\$2.50 per article per issue)

Project No. .... Month ..... Year .....  
Project No. .... Month ..... Year .....  
Project No. .... Month ..... Year .....  
Project No. .... Month ..... Year .....

\* Please attach a list if more than four required.


- ☐ Binders No. .... @ \$6.10 each in NSW  
No. ... @ \$7.50 each other state

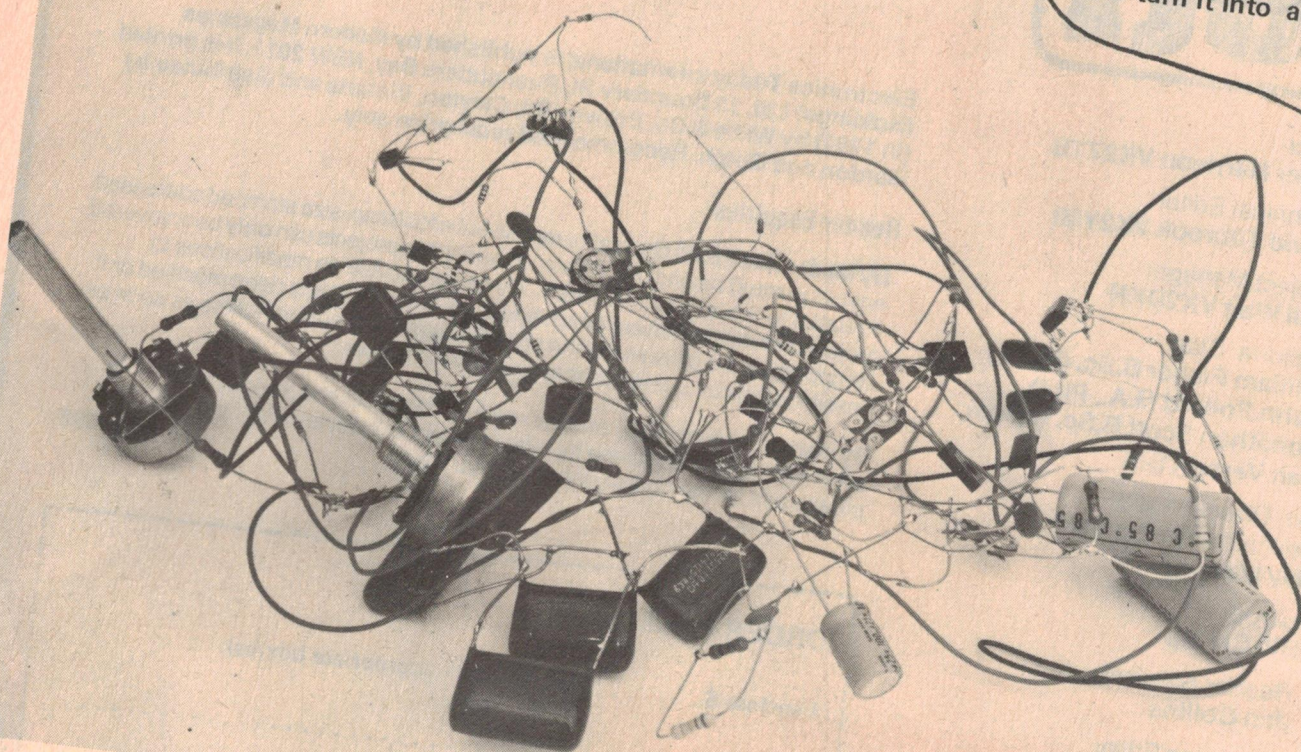**ALL PRICES INCLUDE POSTAGE**

Send orders to: **ETI, 4th Floor, 15 Boundary St,  
RUSHCUTTERS BAY NSW 2011**



Very good, David . . .  
now turn it into a project!



R ELECTRONICS projects are  
ays popular. In a secret laboratory  
advanced R & D team is working  
he ultimate in this line. Provisionally  
ed the Electronic Back Seat Driver,  
new device is aimed at overcoming  
problem of drowsiness on long  
y car journeys.

EBSD uses the latest advances  
technology to provide inter-  
t and unpredictable stimulation.  
icroprocessor brain receives in-  
from a tachometer, fuel line  
eter, pressure sensors in the  
seat and a random pulse  
or (to mention only a few) and  
s a speech synthesis chip to  
n appropriate sentence from a  
ertoire.

ms are being developed to  
EBSD to say such things as  
own, you're using too much  
or "Sit up straight — no  
ou've got a bad back." The  
pulse generator will trigger  
like "What's that funny  
"Did you lock the back



door?" We guarantee the EBSD's  
comments will be so irritating or alarm-  
ing that no driver will fall asleep. In fact  
the designers have had to incorporate  
a special cutout that turns the device  
off and plays soothing music whenever  
the driver becomes so uptight that his  
or her competence is impaired.

The cutout makes use of the fact  
that people's skin resistivity alters when  
they are angry or upset. Two metal  
strips are inlaid into the rim of the  
steering wheel and the current flowing  
between them across the driver's  
palms is used to operate a transistor  
switch.

Wonder if it will sell?

## PANIC

To pay for our skiing holidays, Dregs is  
planning go into the mail order busi-  
ness. We've noticed that some people  
will buy anything if it's described in the  
right way, so we'll shortly be advertising  
our Positional Analog Numerical Indi-  
cator and Calculator — the computing  
machine you can use anywhere.

The ad will stress PANIC's complete  
independence of any battery or mains  
supply and its outstanding stability in  
extremes of temperature and humidity.  
It will even work underwater, a feature  
we're sure none of our competitors can  
match. PANIC is rugged too — you can  
drop it onto concrete from a height of  
several metres without damaging the  
working parts. And instead of the  
boring old plastic that most calculators  
are housed in, we'll be offering PANIC  
in a real cedar wood case.

Gullible readers who send us the  
necessary fifty dollars will receive an  
old cigar box, a ball of string, several  
dozen plastic beads and instructions  
on how to assemble an abacus.



# REAL HI-FI

## AND IT'S ALL IN OUR COLOUR CATALOGUE

The truth is, JVC have always produced real hi-fi components and we believe this current range represents JVC's finest range ever. Here are some real innovations and performance features to whet your appetite:— Quartz locked turntables with uncanny accuracy; Receivers/Amplifiers, some with built-in SEA Graphic Equaliser and DC, class A/B amplification; Cassette deck with JVC automatic computerised tape tuning; Computer designed

speaker systems; Separate but matching JVC components designed to compliment one another, perfectly. And all this real hi-fi know-how is yours ...merely for the asking.



**If you think they look different,  
wait till you've heard them!**

### FREE OFFER COLOUR HI-FI CATALOGUE

Just fill out this coupon and we'll fill you in on what's available and new in terms of JVC hi-fi entertainment...and it's all FREE!

Name \_\_\_\_\_

Address \_\_\_\_\_

Postcode \_\_\_\_\_

WT1323/ETI/79

I am especially interested in...

- ☐ Cassette Decks
- ☐ Matching Systems ☐ Amplifiers
- ☐ Speakers
- ☐ Turntables
- ☐ Receivers

Just address your envelope to...  
JVC Hi-Fi Advisory  
Service,  
Post Office Box 307,  
North Ryde,  
N.S.W. 2113

# JVC

**the right choice**



# Technics SL-10

**Sounds  
Alive**

Quartz-Phase-Locked  
Control Direct-Drive  
Turntable with Linear Tracking  
Tonearm



## Marking the 10th anniversary of the direct-drive turntable.

It has been 10 years since Technics introduced the world's first direct-drive turntable, the SP-10. When it was introduced this turntable had less wow and flutter and better speed accuracy than the cutting lathes used to make records. And because the drive system did not use rubber parts like belts and idler wheels, it insured that its excellent specifications would be retained for a long time.

Six years after the introduction of the SP-10, Technics brought out an improved version, with higher torque and quartz control. Today, more than 1500 of these SP-10MKII's are used by broadcasters in 27 countries around the world. In the past two years, Technics has added quartz synthesizer control to various models, permitting the precision of quartz to be retained in speeds above and below the standard 33-1/3, 45 and 78 rpm.

More significant to the consumer, Technics has also developed direct-drive turntables which have a very high degree of precision, yet cost much less than the professional grade models. It is possible to get numerous Technics direct-drive turntables in the popular price range, yet with specifications that were obtainable only in very expensive equipment a few years ago. With the SL-10, Technics continues to lead the industry in turntable innovation. This new turntable represents as radical a departure from conventional design as did the SP-10 ten years ago.

It has the same width and depth dimensions as an LP record jacket, yet within the compact package are an amazingly precise drive system, a gimbal suspended linear-tracking tonearm, a high-grade moving coil cartridge, plus extensive control systems which permit even a complete hi-fi novice to use the SL-10 without any problem. Nearly every operation is automated, with the upper and lower halves of the cabinet closed during record play. And the tonearm is designed so that the system can be stood vertically without any sacrifice in tracking accuracy. The SL-10 marks as great a step forward in convenience as did the development of cassette tapes versus the open-reel format. Yet there is absolutely no loss in reproduction quality. On the contrary, numerous factors in the SL-10's design will significantly enhance the sound from records.

**Technics changes the face of turntable technology . . . again.**



# Technics

For further information contact The Technics  
Advisory Service,  
P.O. Box 319, North Ryde 2113

TT2.80